

--	--	--	--	--	--	--	--	--	--

Fifth Semester B.E. Degree Examination, June/July 2017
Fundamentals of CMOS VLSI

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1
 - a. Describe in detail the step-by-step procedure involved in the fabrication of nMOS. (08 Marks)
 - b. Calculate the threshold voltage with $\epsilon_{si} = 11.7\epsilon_0$, $\epsilon_{ox} = 3.9\epsilon_0$ for an nMOS transistor with $Q_{fc} = 0$, $N_i = 1.45 \times 10^{10}/\text{cm}^3$, $N_A = 5 \times 10^{17}/\text{cm}^3$, $t_{ox} = 150 \text{ \AA}$ and $\phi_{ms} = -0.9V$ using the equation $V_t = V_{tmos} + V_{fb}$. Plot the graph of ' V_t ' versus ' t_{ox} ' for t_{ox} ranging from 50 \AA to 300 \AA and interpret the graph. (06 Marks)
 - c. With the truth table, draw the schematic for 2:1 MUX and 2-input XOR gate using transmission gate. (06 Marks)
- 2
 - a. List the colour, stick encoding, mask layout encoding for n-diffusion, p-diffusion, polysilicon metal 1 and metal 2. (07 Marks)
 - b. Draw the circuit and stick diagram for one-bit CMOS shift register. (06 Marks)
 - c. Draw the optimum layout of CMOS inverter whose $\left(\frac{W_p}{W_n}\right) = \frac{4}{2}$ by stitching the source and drain regions of 2:1 inverter with the contacts and metal. Discuss the merits of such design. Given $L_p = L_n = 1$. [Hint : Placing the transistor back to back]. (07 Marks)
- 3
 - a. Write the voltage-current equations for nMOS and pMOS transistor, with V-I characteristics discuss channel length modulation. (08 Marks)
 - b. Realize the boolean equation using CMOS and C²MOS logic $Z = \overline{A(B+C)} + DE$ (06 Marks)
 - c. Discuss BiCOMS logic and CMOS domino logic with relevant schematic. (06 Marks)
- 4
 - a. Discuss the limits of scaling
 - i) Substrate doping
 - ii) Limits on miniaturization
 - iii) Limits on interconnect and contact resistance. (06 Marks)
 - b. Describe the possible effect of propagation delay in cascaded pass transistors and long polysilicon wires. (06 Marks)
 - c. Calculate the area capacitance of a multilayer structure shown in Fig Q4(a), if feature size = $5 \mu\text{m}$ and relative value of metal to substrate = 0.075, polysilicon = 0.1, diffusion = 0.25. (08 Marks)

 


Fig 4(c)

PART – B

- 5 a. Discuss the architectural issues to be followed in the design of a VLSI subsystem. (08 Marks)
 b. Show an arrangement to generate any logic function of two variable (A, B) by programming the inputs $I_0 - I_3$ appropriately with 0's and 1's using 4-way multiplexer. (08 Marks)
 c. Define Metastability. Find the MTBU (t_f) of a system given $f_c = 50\text{MHz}$, $f_d = 100\text{KHz}$, $t_f = 10\text{ns}$, $T_0 = 0.1\text{s}$, $\tau_r = 0.2\text{ns}$ using the equation $\text{MTBU}(t_f) = \frac{1}{f_c f_d T_0 e^{-\frac{t_f}{\tau_r}}}$. (04 Marks)
- 6 a. Design a 4-bit serial-parallel multiplier. (10 Marks)
 b. Derive carry look – ahead adder equations and design a 4-bit CLA adder with a combination of ripple-through, given the following equation for carry and sum is

$$C_k = A_k \cdot B_k + (A_k + B_k)C_{k-1}$$

$$S_k = A_k \cdot B_k + B_k \cdot C_k + C_k \cdot A_k$$
 Where A, B, C are input variables and $K = \{0, 1, 2, \dots, n-1\}$. (10 Marks)
- 7 a. Discuss the various system timing considerations. (06 Marks)
 b. Describe the working of CMOS pseudo static RAM cell. Determine the area requirement, estimated dissipation per bit stored and volatility of the same. (08 Marks)
 c. Draw the schematic of 6-transistor SRAM cell. Discuss read '0' and write '0' operations with appropriate schematic diagrams. (06 Marks)
- 8 a. Mention the types of I/O pads and discuss their functionalities. (08 Marks)
 b. Discuss noise margin in CMOS technology for a cascaded inverters (set of 2). Draw the noise margin graphs indicating NM_H , NM_L , V_{OH} , V_{IL} , V_{OL} and V_{IH} (08 Marks)
 c. From the Figure Q 8(c) shown below, identify appropriate widths for nMOS and pMOS transistors to obtain optimum delay and area. (04 Marks)

 


Fig Q8(c)
