

--	--	--	--	--	--	--	--	--	--

**Fifth Semester B.E. Degree Examination, June/July 2017**

**Transmission Lines and Waveguides**

Time: 3 hrs.

Max. Marks:100

*Note: Answer FIVE full questions, selecting at least TWO questions from each part.*

**PART – A**

- 1
  - a. Starting from the fundamental, derive the expression for the voltage and current at any point on the transmission line. (10 Marks)
  - b. Derive the expression for attenuation constant phase constant and velocity of propagation for an ordinary telephone cable. (04 Marks)
  - c. The primary constant of a  $\mu$ W transmission lines are :  $R = 1.5 \Omega/m$ ,  $G = 0.2 \text{ m}\Omega /m$ ,  $L = 2.5\text{nH/m}$  and  $C = 0.1\text{pF/m}$ . The transmission line is terminated in a  $400\Omega$  pure resistance and operated at a frequency of 1.5GHZ. If the length of the line is 20m, Find :
    - i) Characteristic impedance    ii) Propagation constant    iii) Attenuation constant
    - iv) Phase constant    v) Wavelength and    vi) Phase velocity. (06 Marks)
- 2
  - a. Design a constant K-LPF having  $f_c = 2000\text{Hz}$  and nominal characteristic impedance =  $600\Omega$ . Also find the frequency at which the filter offers attenuation of 19.1dB. (08 Marks)
  - b. A load impedance of  $z_l = 60 - j80\Omega$  is required to be matched to a  $50\Omega$  coaxial line by using a short circuit stub of length ' $l$ ' and placed at a distance ' $d$ ' from the load. The wavelength of operation is 1m. Using smith chart find ' $l$ ' and ' $d$ ' write the suitable steps of construction. (08 Marks)
  - c. Discuss the application of smith chart. (04 Marks)
- 3
  - a. Derive the expression for input impedance of an open circuit and short circuit line. (06 Marks)
  - b. Derive the relation between SWR and reflection coefficient. (08 Marks)
  - c. Illustrate the SWR of a lossless line. (06 Marks)
- 4
  - a. Explain the S – matrix for a multipart network. (06 Marks)
  - b. Deduce the symmetrical property of S-matrix. (06 Marks)
  - c. Discuss the different losses in a microwave network. (08 Marks)

**PART – B**

- 5
  - a. With a neat diagram, explain the working of 2 hole directional coupler. (10 Marks)
  - b. With a neat diagram explain the operation of Faraday rotation isolator. (10 Marks)
- 6
  - a. What is GUNN effect? With a neat diagram explain the construction details of a Gunn diode. (10 Marks)
  - b. With a neat sketch explain the operation of IMPATT diode and draw the negative resistance curve. (10 Marks)

- 7 a. Explain the parametric amplifier with equivalent circuit. (10 Marks)
- b. An IMPATT diode has the following parameters :
- Carrier drift velocity  $V_d = 2 \times 10^7 \mu\text{m/s}$
  - Drift region length  $L = 6\mu\text{m}$
  - Maximum operating voltage = 100V
  - Maximum operating current = 200mA
  - Efficiency  $\eta = 15\%$
- Break down voltage  $V_{th} = 90\text{V}$ . Compute
- i) Maximum output power and
  - ii) Resonant frequency. (05 Marks)
- c. A typical Si-BARITT diode has the following parameters :
- Relative dielectric constant  $C_r = 12.5$
  - Carrier concentration  $N = 3.2 \times 10^{22}/\text{m}^3$
  - $E_0 = 8.854 \times 10^{-12}$
  - Drift length  $L = 8\mu\text{m}$ . Calculate :
  - i) Critical voltage
  - ii) Break down voltage
  - iii) Break down electric field. (05 Marks)
- 8 Write short notes on :
- a. TE, TEM, Modes in parallel lines
  - b. BARITT diode
  - c. PIN diode
  - d. Properties of S-matrix. (20 Marks)

\* \* \* \* \*