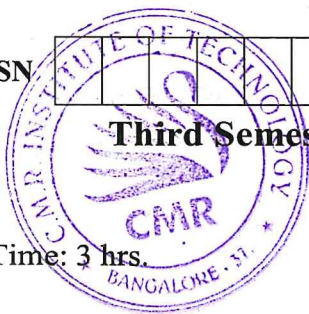


# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC35



**Third Semester B.E. Degree Examination, July/August 2021**

## Network Analysis

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions.*

- 1 a. Using source transformation techniques, find 'v' for the circuit in Fig.Q1(a).

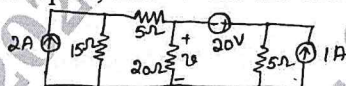


Fig.Q1(a)

(07 Marks)

- b. Obtain equivalent resistance  $R_{ab}$  for the circuit in Fig.Q1(b) and hence find 'i'.

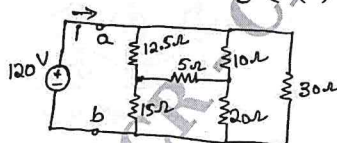


Fig.Q1(b)

(07 Marks)

- c. Explain ideal and practical current sources.

(06 Marks)

- 2 a. Determine the current  $I_0$  in the circuit of Fig.Q2(a) using Mesh analysis.

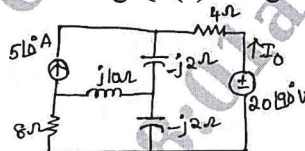


Fig.Q2(a)

(08 Marks)

- b. Use nodal analysis to find  $v_0$  in the network of Fig.Q2(b).

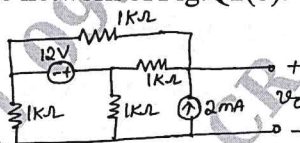


Fig.Q2(b)

(08 Marks)

- c. Explain the concept of super node with an illustration.

(04 Marks)

- 3 a. State and prove Reciprocity theorem.

(06 Marks)

- b. Use superposition theorem to find  $i_0$  in the circuit shown in Fig.Q3(b).

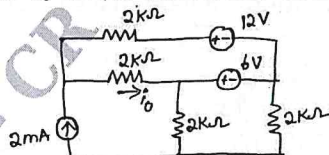


Fig.Q3(b)

(06 Marks)

- c. Find Thevenin's equivalent circuit across the terminals a – b for the circuit shown in Fig.Q3(c).

(08 Marks)

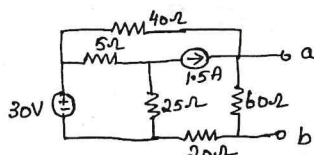


Fig.Q3(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 4 a. State and prove maximum power transfer theorem for the case of AC source, hence show

that 
$$P_{\max} = \frac{|V_{TH}|^2}{8R_L}$$
 (08 Marks)

- b. Find the current through  $16 \Omega$  resistor using Norton's theorem in Fig.Q4(b).

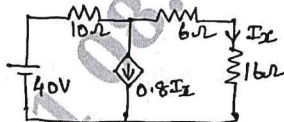


Fig.Q4(b)

(08 Marks)

- c. Find the current through  $(10 - 3j)\Omega$  using Millman's theorem in Fig.Q4(c).

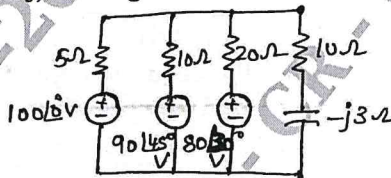


Fig.Q4(c)

(04 Marks)

- 5 a. The switch 'K' is changed from position 1 to position 2 at  $t = 0$ . Steady state condition having been reached at position 1. Find the values of  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ .

[Refer Fig.Q5(a)]

(06 Marks)

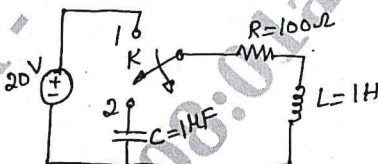


Fig.Q5(a)

- b. In the network shown in Fig.Q5(b),  $V_1(t) = e^{-t}$  for  $t \geq 0$  and is zero for all  $t < 0$ . If the capacitor is initially uncharged. Determine the value of  $\frac{d^2V_2}{dt^2}$  and  $\frac{d^3V_2}{dt^3}$  at  $t = 0^+$ .

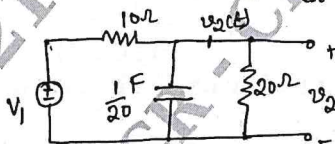


Fig.Q5(b)

(08 Marks)

- c. Explain initial and final conditions in case of a capacitor.

(06 Marks)

- 6 a. For the circuit shown in Fig.Q6(a),  
 (i) Find the differential equation for  $i_L(t)$   
 (ii) Find Laplace transform of  $i_L(t)$   
 (iii) Solve for  $i_L(t)$

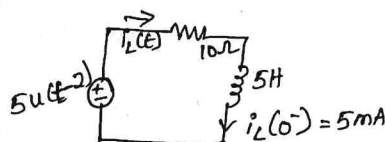


Fig.Q6(a)

(08 Marks)

CMRIT LIBRARY  
 BANGALORE - 560 037

- b. For the circuit shown in Fig.Q6(b), (i) Find the differential equation for  $i_L(t)$ , (ii) Find Laplace transform of  $i_c(t)$ , (iii) Solve for  $i_L(t)$ . (08 Marks)

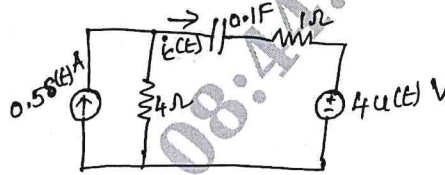


Fig.Q6(b)

- c. Obtain Laplace transform for a decaying exponential signal. (04 Marks)

- 7 a. Prove that the resonant frequency is the geometric mean of the two half power frequencies i.e., Show that  $\omega_0 = \sqrt{\omega_1\omega_2}$  (08 Marks)  
 b. Obtain an expression for quality factor of an capacitor. (07 Marks)  
 c. In a series circuit,  $R = 6 \Omega$ ,  $\omega_0 = 4.1 \times 10^6$  rad/sec, bandwidth =  $10^5$  rad/sec. Compute L, C half power frequencies and Q. (05 Marks)

- 8 a. Obtain an expression for the resonant frequency in a parallel resonant circuit. (08 Marks)  
 b. Show that a two branch parallel resonant circuit is resonant at all frequencies when

$$R_L = R_C = \sqrt{\frac{L}{C}}$$

(07 Marks)

- c. Find the value of  $R_L$  for which the circuit is at resonance, as shown in Fig.Q8(c). (05 Marks)

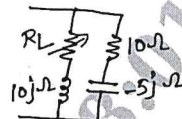


Fig.Q8(c)

- 9 a. Obtain an expression for h-parameters in terms of Z-parameters. (08 Marks)  
 b. Find Z and Y parameters for the network shown in Fig.Q9(b). (08 Marks)

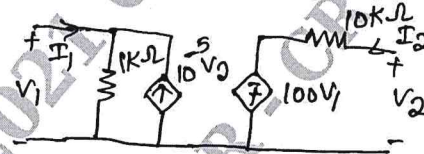


Fig.Q9(b)

- c. Explain ABCD parameters. (04 Marks)

- 10 a. Obtain an expression for Y-parameters in terms of ABCD parameters. (08 Marks)  
 b. Find ABCD parameters for the network shown in Fig.Q10(b).

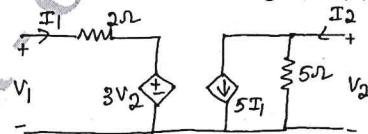


Fig.Q10(b)

(08 Marks)

- c. State reciprocity condition for  
 (i) Z – parameters  
 (ii) Y – parameters  
 (iii) h – parameters  
 (iv) ABCD – parameters

CMRIT LIBRARY  
 BANGALORE - 560 037

(04 Marks)

\*\*\*\*\*

