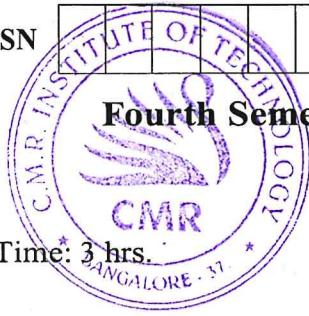


USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

10EC46



**Fourth Semester B.E. Degree Examination, July/August 2021**

**Linear IC's and Applications**

Time: 3 hrs.

Max. Marks:100

*Note: Answer any FIVE full questions.*

- 1 a. Write an ideal characteristics of an op-amp. (04 Marks)
- b. Define the following op-amp parameters:
  - (i) CMRR
  - (ii) PSRR
  - (iii) Slew rate
  - (iv)  $V_o$  (offset) (04 Marks)
- c. Explain how the op-amp can be used as a direct coupled:
  - (i) Inverting
  - (ii) Non-inverting
  - (iii) Summing
  - (iv) Difference amplifier (12 Marks)
- 2 a. Draw the circuit diagram and derive the design equations of a capacitor-coupled voltage follower. (10 Marks)
- b. Design the basic capacitor-coupled inverting amplifier with  $A_v = 50$ ,  $V_o = 2.5$ ,  $R_L = 250 \Omega$  and signal frequency ( $f_s$ ) = 10 Hz to 1 kHz. (10 Marks)
- 3 a. With suitable circuit and graph, how phase-lead and phase-lag compensation is used to stabilize op-amp circuit. (10 Marks)
- b. With a neat circuit diagram, explain  $Z_{in}$  mod technique for frequency compensation of op-amp circuit. (10 Marks)
- 4 a. Explain the operation of an instrumentation amplifier using three op-amps. (10 Marks)
- b. Draw and design a precision full-wave rectifier to produce 2V peak output from a sine wave input with a peak value of 0.5 V and frequency of 1 MHz, with supply voltage of  $\pm 15V$ . Select  $I_1 = 500 \mu A$ . (10 Marks)
- 5 a. Show how the current-to-voltage converter is realized using op-amp. (04 Marks)
- b. Realize logarithmic amplifier using op-amp and transistor. Derive the expression for output voltage. (08 Marks)
- c. Draw and design a phase-shift oscillator using op-amp to generate a sine wave of 100 Hz. Select  $C = 0.1 \mu F$ . (08 Marks)
- 6 a. Explain how the op-amp can be used as a zero-crossing detector. (04 Marks)
- b. Explain the working of an inverting Schmitt trigger. Draw input, output waveforms and transfer curve. (08 Marks)
- c. Using 741 op-amp, design and draw second order LPF with  $f_c = 5$  kHz. (08 Marks)
- 7 a. Give the classification of voltage regulators. Explain current fold back and current boosting techniques in voltage regulators. (08 Marks)
- b. Explain using op-amp, operation of switching voltage regulator. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

- c. Calculate the output voltage of the adjustable regulator shown in Fig.Q7(c), if  $R_2$  is varied from  $1\text{ K}\Omega$  to  $10\text{ K}\Omega$ , find the range of output voltage.

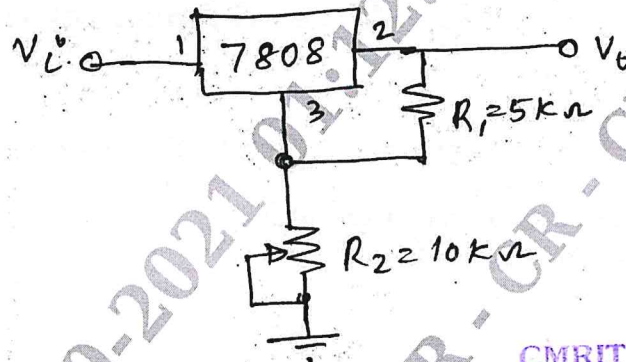


Fig.Q7(c)

CMRIT LIBRARY  
BANGALORE - 560 037

(06 Marks)

- 8 a. With a neat block schematic, explain the operation of each component in PLL. (08 Marks)
- b. Draw the circuit diagram of Astable multivibrator using 555 Timer and derive the expression for output signal frequency. (06 Marks)
- c. Draw the circuit diagram and explain the operation of 3-bit R-2R D/A converter using op-amp. (06 Marks)

\*\*\*\*\*