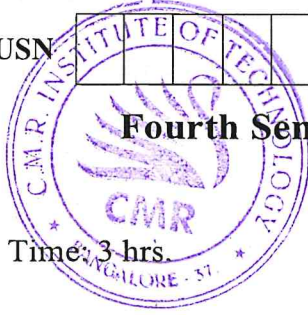


# CBCS SCHEME

18EC42

USN 

--	--	--	--	--	--	--	--	--	--



**Fourth Semester B.E. Degree Examination, July/August 2021**

## Analog Circuits

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions.*

- 1 a. Explain the voltage divider biasing for BJTs using single power supply. How does  $R_E$  provides a negative feedback action to stabilize the bias current with necessary supporting mathematical equations. (08 Marks)
- b. For the circuit shown in Fig.Q1(b), derive the expression of voltage gain.

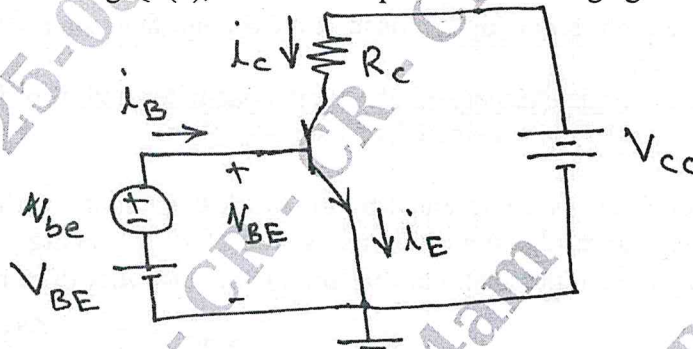


Fig.Q1(b)

(06 Marks)

- c. A BJT having  $\beta = 100$  is biased at a dc collector current of 1 mA. Find the value of  $g_m$ ,  $r_e$  and  $r_\pi$  at the bias point. Assume  $V_T = \frac{1}{40} V$ . (06 Marks)

- 2 a. For the circuit shown in Fig.Q2(a), find the required value of  $V_{GS}$  to establish a dc bias current  $I_D = 0.5$  mA. Device parameters are  $V_t = 1$  V,  $K'_n \frac{W}{L} = 1$  mA/V<sup>2</sup> and  $\lambda = 0$ . What is the percentage change in  $I_D$  obtained when the transistor is replaced with another having  $V_t = 1.5$  V.

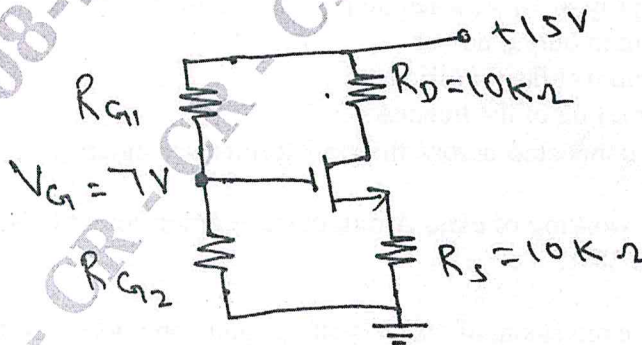


Fig.Q2(a)

(08 Marks)

- b. What is trans-conductance of a MOSFET and mention the three different expression used to calculate the trans-conductance. (06 Marks)
- c. Explain biasing of MOSFET by fixing  $V_{GS}$ . (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 3 a. For the circuit shown in Fig.Q3(a), derive the expression of  $R_{in}$ ,  $R_o$ ,  $A_v$  and  $A_v$  using T-model.

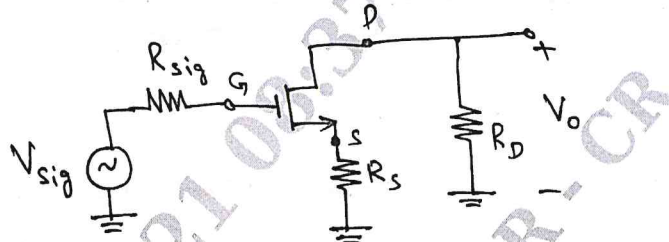


Fig.Q3(a)

(10 Marks)

- b. With mathematical equations, explain the different internal capacitances in the MOSFET.

(10 Marks)

- 4 a. Explain the high frequency response of a CS amplifier using MOSFET and derive its upper cutoff frequency. (10 Marks)
- b. Explain the working principles of Colpitts oscillator and also discuss the drawback of this oscillator are over come using Clapp oscillator. (10 Marks)

- 5 a. In a particular circuit represented by the block diagram shown in Fig.Q5(a), a signal of 1V from the source results in a difference signal of 10 mV being provided to the amplifier (A) and 10V applied to the load. For this arrangement identify the value of A and  $\beta$  that apply.

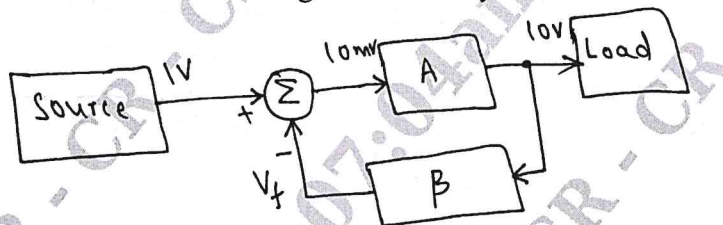


Fig.Q5(a)

(06 Marks)

- b. Draw the general feedback structure and explain with necessary expressions. (06 Marks)
- c. What are the properties of negative feedback and explain it. (08 Marks)

- 6 a. What is output stage and discuss the classification of output stages based on the collector current? (06 Marks)
- b. A transformer coupled class A power amplifier drawn a current of 200 mA from the collector supply of 10 V, when no signal is applied it. Determine:
- Maximum output power
  - Maximum collector efficiency
  - Power rating of the transistor

If the load connected across the transformer secondary is  $2 \Omega$  and transformer turn ratio is 5:1. (06 Marks)

- c. Explain the working of class A output stage amplifier and also prove that power conversion efficiency is 25%. (08 Marks)

- 7 a. Derive the expression of exact voltage gain and ideal voltage gain of a voltage shunt feedback amplifier using OP-AMP. (08 Marks)
- b. The 741 OP-AMP having the following parameter is connected as a non-inverting amplifier with  $R_1 = 1 \text{ K}\Omega$  and  $R_F = 10 \text{ K}\Omega$ . Given  $A = 200000$ ,  $R_i = 2 \text{ M}\Omega$ ,  $R_o = 75 \Omega$ ,  $f_0 = 5 \text{ Hz}$  and supply voltage =  $\pm 15 \text{ V}$ . Compute the value of  $A_F$ ,  $R_{iF}$ ,  $R_{oF}$  and  $f_F$ . (06 Marks)
- c. With the circuit and waveforms, explain the working of non-inverting comparator. (06 Marks)

- 8 a. Explain the working of instrumentation amplifier using transducer bridge and derive the expression of output voltage. (10 Marks)
- b. Explain the operation of an inverting Schmitt Trigger. (06 Marks)
- c. The circuit shown in Fig.Q8(c) is to be used as an averaging amplifier with the following specifications:  $V_a = V_b = 1.5\text{ V}$ ,  $V_c = 3\text{ V}$ ,  $R_1 = R = 1.5\text{ K}$  and  $V_0 = 5.2\text{ V}$ . Determine the required value of  $R_F$ .

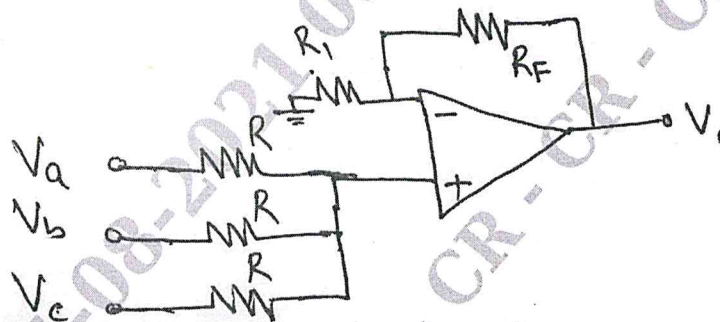


Fig.Q8(c)

(04 Marks)

- 9 a. Derive the expression of output voltage of a binary weighted resistor type DAC. (08 Marks)
- b. For the DAC using an R-2R network with  $R = 10\text{ K}\Omega$ ,  $R_F = 27\text{ K}\Omega$  and  $V_R = 5\text{ V}$ .
- (i) Determine the size of each step
- (ii) Calculate the output voltage when  $b_0 = b_1 = b_2 = b_3 = 5\text{ V}$ . (06 Marks)
- c. Explain the working of a first order active low pass filter with circuit and frequency response. (06 Marks)
- 10 a. Explain the operation of a successive approximation DAC and mention its advantages. (08 Marks)
- b. Mention the applications of 555 IC Timer. (04 Marks)
- c. Design an Astable Multivibrator using 555 IC Timer with
- (i)  $f_0 = 1\text{ kHz}$  and  $D = 40\%$
- (ii)  $f_0 = 2\text{ kHz}$  and  $D = 50\%$
- (iii)  $f_0 = 1\text{ kHz}$  and  $D = 70\%$
- Assume  $c = 0.01\text{ }\mu\text{F}$  for all cases. (08 Marks)

\*\*\*\*\*

