

Fifth Semester B.E. Degree Examination, July/August 2021
Fundamentals of CMOS VLSI

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions.

- 1 a. Explain the Fabrication steps of CMOS-P-Well process with neat diagram, write the mask sequence. (10 Marks)
- b. Explain second order effects with respect to a MOS device. (10 Marks)
- 2 a. With neat circuit diagram and relevant mathematical equations explain differential inverter. (10 Marks)
- b. Draw the circuit schematic, stick diagram and layout diagram of nMOS, 2 I/P Nand Gate. (10 Marks)
- 3 a. Describe the following logic structures:
 - i) Complementary CMOS logic
 - ii) Pseudo nMOS logic. (10 Marks)
- b. Explain the operation of CMOS dynamic logic. Also discuss the cascading problems of dynamic CMOS logic. (10 Marks)
- 4 a. Calculate the capacitance of the structure given below.

 


Fig.Q.4(a)

Relative area capacitance values

Metal 1 to substrate = 0.075

Polysilicon to substrate = 0.1

Gate to channel = 1.0

(10 Marks)

- b. Obtain the scaling factors for the following device parameters.
 - i) Gate capacitance per unit area (C_o)
 - ii) Channel resistance (R_{on})
 - iii) Gate Delay (T_D)
 - iv) Saturation current (I_{dss})
 - v) Power dissipation / Gate P_g . (10 Marks)

- 5 a. Discuss the architectural issues related to subsystem design. (10 Marks)
b. Explain dynamic register element and 4 bit shift register using nMOS and CMOS logic. (10 Marks)
- 6 a. Design 4×4 barrel shifter. (10 Marks)
b. With the neat diagram, explain parity generator structured design. (10 Marks)
- 7 a. Explain three transistor dynamic RAM cell. (10 Marks)
b. Explain CMOS pseudo static memory cell. (10 Marks)
- 8 a. Explain scan design techniques. (10 Marks)
b. Write short notes on:
i) Noise Margin
ii) I/O pads
iii) Silicides. (10 Marks)

CMRIT LIBRARY
BANGALORE - 560 037
