

Internal Assessment Test - II

Sub:	Analog Circuits	Code:	18EC42
Date:	22/ 06 / 2021	Duration:	90 mins
		Max Marks:	50
		Sem:	4 th
		Branch:	ECE

Answer Any FIVE FULL Questions


		Marks	OBE	
			CO	RBT
1.	Draw and explain the complete frequency response of a common source amplifier. Derive the expression for its lower cut-off frequency.	[10]	CO2	L3
2.	With the help of neat circuit diagram and small signal equivalent model explain the working of FET based RC Phase shift Oscillator. Also explain how three RC pair can be used to in the feedback to achieve 180 degree phase shift.	[10]	CO3	L3
3.	a) With a neat circuit diagram and ac equivalent circuit derive the expressions for R_{in} , A_{vo} , A_v for common source amplifier with source resistance.	[06]	CO2	L3
	b) Find the midband gain A_M , and the upper 3-dB frequency f_H of a CS amplifier fed with a signal source having an internal resistance $R_{sig} = 100 \text{ k}\Omega$. The amplifier has $R_G = 4.7 \text{ M}\Omega$, $R_D = R_L = 15 \text{ k}\Omega$, $g_m = 1 \text{ mA/V}$, $r_o = 150 \text{ k}\Omega$, $C_{gs} = 1 \text{ pF}$ and $C_{gd} = 0.4 \text{ pF}$	[04]	CO2	L3
4.	Explain the internal capacitances of a MOSFET. For the n-channel MOSFET in saturation with $t_{ox} = 10 \text{ nm}$, $L = 1 \mu\text{m}$, $W = 10 \mu\text{m}$, $L_{OV} = 0.05 \mu\text{m}$, $C_{sbo} = C_{dbo} = 10 \text{ fF}$, $V_{O} = 0.6 \text{ V}$, $V_{SB} = 1 \text{ V}$ and $V_{DS} = 2 \text{ V}$. Given dielectric used is SiO_2 . Calculate i) C_{OX} ii) C_{OV} iii) C_{gs} iv) C_{gd} v) C_{sb} vi) C_{db}	[10]	CO2	L3
5.	Show how noise reduction and bandwidth increment occurs with the application of negative feedback.	[10]	CO2	L3
6.	a) Draw the four basic negative-feedback topologies.	[04]	CO2	L2
	b) Draw and explain Series-Series feedback amplifier ideal structure. Also, derive R_{if} and R_{of} .	[06]	CO2	L2
7.	With a neat diagram explain working of a crystal oscillator. Explain series and parallel resonance action with equivalent circuits and relevant expressions. A crystal has $L = 0.334 \text{ H}$, $C_s = 0.065 \text{ pF}$, $C_p = 1 \text{ pF}$. Calculate its series and parallel resonant frequency.	[10]	CO3	L3
8.	With a neat circuit diagram and ac equivalent circuit derive the expressions for R_{in} , A_{vo} , A_v , R_o and G_v for a source follower.	[10]	CO2	L3

①

Internal Assessment - II

Solution and Scheme of 18EC42 Analog circuits

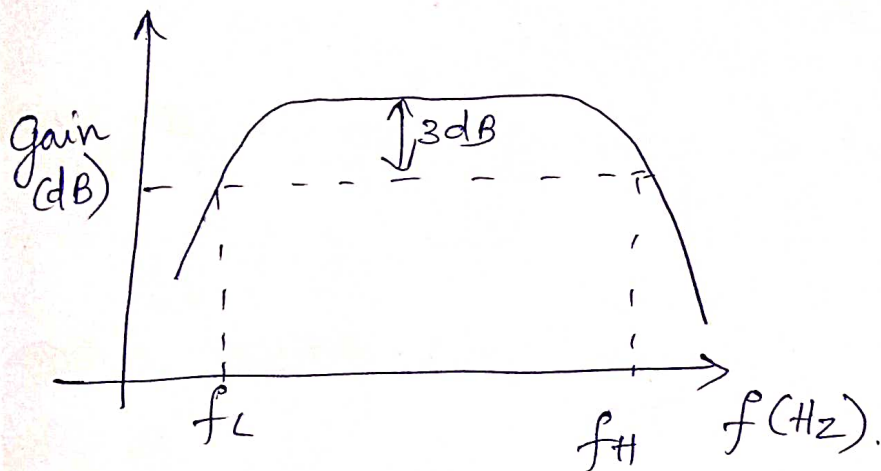1. Frequency response of common source amplifier



Graph + explanation \rightarrow 5M

Expression for lower cutoff freq.

Derivation + explanation \rightarrow 5M

$$\frac{V_o}{V_{sig}} = - \left[\frac{R_o}{R_o + R_{sig}} \right] g_m R_D // R_L \left(\frac{s}{s + \omega_{p1}} \right) \left(\frac{s}{s + \omega_{p2}} \right) \left(\frac{s}{s + \omega_{p3}} \right)$$

2. FET based RC phase shift oscillator (10M)

circuit diagram (2M), equivalent model (2M)

explanation (2M)

3 RC pair in the feedback providing 180° phase shift (4M)

(2)

(3)

(a)

$$R_{in} = R_i = R_G$$

$$A_{v_0} = \frac{-g_m R_D}{1 + g_m R_S}$$

$$A_V = \frac{V_o}{V_i} = \frac{-g_m (R_D // R_L)}{1 + g_m R_S}$$

expression $1+1+1$
 $= 3M$

6M

Circuit diagram and eq. circuit 3M

(3)

(b)

$$R_{sig} = 100k, R_G = 4.7M, R_D = R_L = 15k$$

$$g_m = 1mA/V, r_o = 150k, C_{gs} = 1pF, C_{gd} = 0.4pF$$

$$A_m = \frac{-R_G}{R_G + R_{sig}} g_m R_L' = -7V/V \quad (2M)$$

$$f_H = \frac{1}{2\pi C_{in} (R_{sig} // R_G)} = 382kHz \quad (2M)$$

$\frac{4M}{4M}$

(4)

Internal capacitance of MOSFET

$C_{gs}, C_{gd}, C_{gb}, C_{sb}, C_{db} \rightarrow$ All capacitors
explanation with diagram (5M)

$$C_{ox} = 3.45fF/\mu m^2, C_{ov} = 1.72fF, C_{gs} = 24.7fF$$

$$C_{gd} = 1.72fF, C_{sb} = 6.1fF, C_{db} = 4.1fF \quad (5M)$$

(3)

(5) Noise reduction

(Block diagram) — 2M.

$$V_o = V_s \frac{A_1 A_2}{1 + A_1 A_2 \beta} + V_n \frac{A_1}{1 + A_1 A_2 \beta}$$

} explanation
+
equation (3M)

$$\frac{S}{N} = \frac{V_s}{V_n} A_2$$

BW extension

(5M)

$$A_f(s) = \frac{A_m}{1 + A_m \beta} = \frac{A_m f}{1 + \frac{s}{\omega_H (1 + A_m \beta)}} = \frac{A_m f}{1 + \frac{s}{\omega_{Hf}}}$$

(6)(a) Four basic topology (block diagram) 4M.

(b) Series-series feedback explanation and gain (2M)

Rif (2M)

Rof (2M)

} 6M.

⑦ - Crystal Oscillator - structure, equivalent circuit (2M).

Explanation - Series and parallel Resonance action + expressions (3M)

Numerical problem - 5M.

⑧

$R_{in} = R_G$

$A_V = \frac{R_L // r_o}{R_L // r_o + \frac{1}{g_m}} \approx \frac{R_L}{R_L + \frac{1}{g_m}}$ when $r_o \gg R_L$

$A_{V_0} = \frac{r_o}{r_o + \frac{1}{g_m}} \approx 1$

$G_v = \frac{R_a}{R_a + R_{sig}} \cdot \frac{R_L // r_o}{(R_L // r_o) + \frac{1}{g_m}}$

} 7M.

$R_{out} = \frac{1}{g_m} // r_o \approx \frac{1}{g_m}$

circuit diagram and equivalent circuit 3M - 10M.