

Internal Assessment Test - III

Sub:	Analog Circuits	Code:	18EC42
Date:	29/ 07/ 2021	Duration:	90 mins
		Max Marks:	50
		Sem:	4 <sup>th</sup>
		Branch:	ECE

Answer Any FIVE FULL Questions

		Marks	OBE	
			CO	RBT
1.	Explain a Class B Output stage. Prove that the maximum conversion efficiency of a Class B transformer coupled amplifier is 78.5%.	[10]	CO3	L3
2.	Explain with a neat diagram and relevant expressions, an opamp voltage series feedback amplifier	[10]	CO4	L3
3.	(a) Explain the basic comparator circuit using an opamp. How can this circuit be used in an application as a zero crossing detector?	[06]	CO4	L3
	(b) What is cross over distortion?	[04]	CO3	L3
4.	Explain an Instrumentation amplifier using transducer bridge with relevant equation.	[10]	CO4	L3
5.	Explain the operation of a Successive –approximation ADC with neat circuit diagram.	[10]	CO5	L3
6.	Explain the operation of 4-bit R-2R DAC with neat circuit. For the R-2R DAC, with $R=10k\Omega$ and $R_F=20k\Omega$ and $V_{REF}=5V$ , determine the output voltage when the inputs $b_0=b_1=5V$ and $b_2=b_3=0V$	[10]	CO5	L3
7.	Discuss about summing, scaling and averaging amplifier for inverting configuration	[10]	CO4	L3
8.	For an opamp non-inverting amplifier using 741 IC with $R_L=1 K\Omega$ and $R_F=10K\Omega$ , $A= 200,000$ ; $R_i =2M\Omega$ , $R_o = 75\Omega$ , $f_o =5 Hz$ ; supply voltages $\pm 15V$ , output voltage swing = $\pm 13V$ , Compute $A_F$ , $R_{if}$ , $R_{of}$ , $f_F$ .	[10]	CO4	L3

# **Analog Circuits (18EC42)\_IAT-3**

## **Marking Scheme-4<sup>th</sup> Sem**

**Exam Date: 29, July\_2021**

**Q-1 Class B explanation -5 marks**

**Efficiency calculation- 5 marks**

**Q-2 Diagram-2 marks**

**Explanation-8 marks**

**Q-3 (a)Explanation-3 marks**

**Application- 3 marks**

**(b) Expalnation-4 marks**

**Q-4 Circuit- 2 marks**

**Explanation-6 marks**

**Equations-32 marks**

**Q-5 Circuit-4 marks**

**Explanation-6 marks**

**Q-6 Explanation-6 marks**

**Numericals- 4 marks**

**Q-7 Summing-4 marks, Scaling-3 marks, Averaging-3 marks**

**Q-8 Diagram-2 marks, Af, Rif, Rof, Ff (2 mark each)**

29-07-21

ANALOG CIRCUITS - 18EC42

IAT-3

Ans 8

$R_L = 1k\Omega$  and  $R_F = 10k\Omega$

$A = 200,000$ ,  $R_i = 2M\Omega$ ,  $R_o = 75\Omega$ ,  $f_o = 5Hz$

supply voltages =  $\pm 15V$

output voltage swing =  $\pm 13V$

to find B:  $B = \frac{R_L}{R_L + R_F} = \frac{1k\Omega}{1k\Omega + 10k\Omega} = \frac{1}{11}k\Omega$

$1 + AB = 1 + \frac{200000}{11} = 1 + 18181.818 = 18182.8$

i) To find  $A_F$ :  $A_F = \frac{A}{1 + AB} = \frac{200000}{18182.8} = 10.9994$

$\therefore A_F = 10.999$

ii) To find  $R_{iF}$ :  $R_{iF} = R_i (1 + AB) = 2M\Omega (18182.8) = 2 \times 10^6 (18182.8) = 3.6365 \times 10^{10}$

$\therefore R_{iF} = 3.637 \times 10^{10} \Omega$

iii) To find  $R_{oF}$ :  $\frac{R_o}{1 + AB} = R_{oF} \Rightarrow R_{oF} = \frac{75}{18182.8} = 4.1247 \times 10^{-3} \Omega$

$\therefore R_{oF} = 4.124 m\Omega$

iv) To find  $f_F$ :

$f_F = f_o \times (1 + AB)$

$= 5 \times (18182.8) = 90914 Hz$


$= 90.914 kHz$

$\therefore f_F = 90.914 kHz$

Ans 5

SUCCESSIVE-APPROXIMATION ADC: It converts an analog voltage to digital output that best represents the input. They are also specified as 8, 10, 12, 16, etc bit.

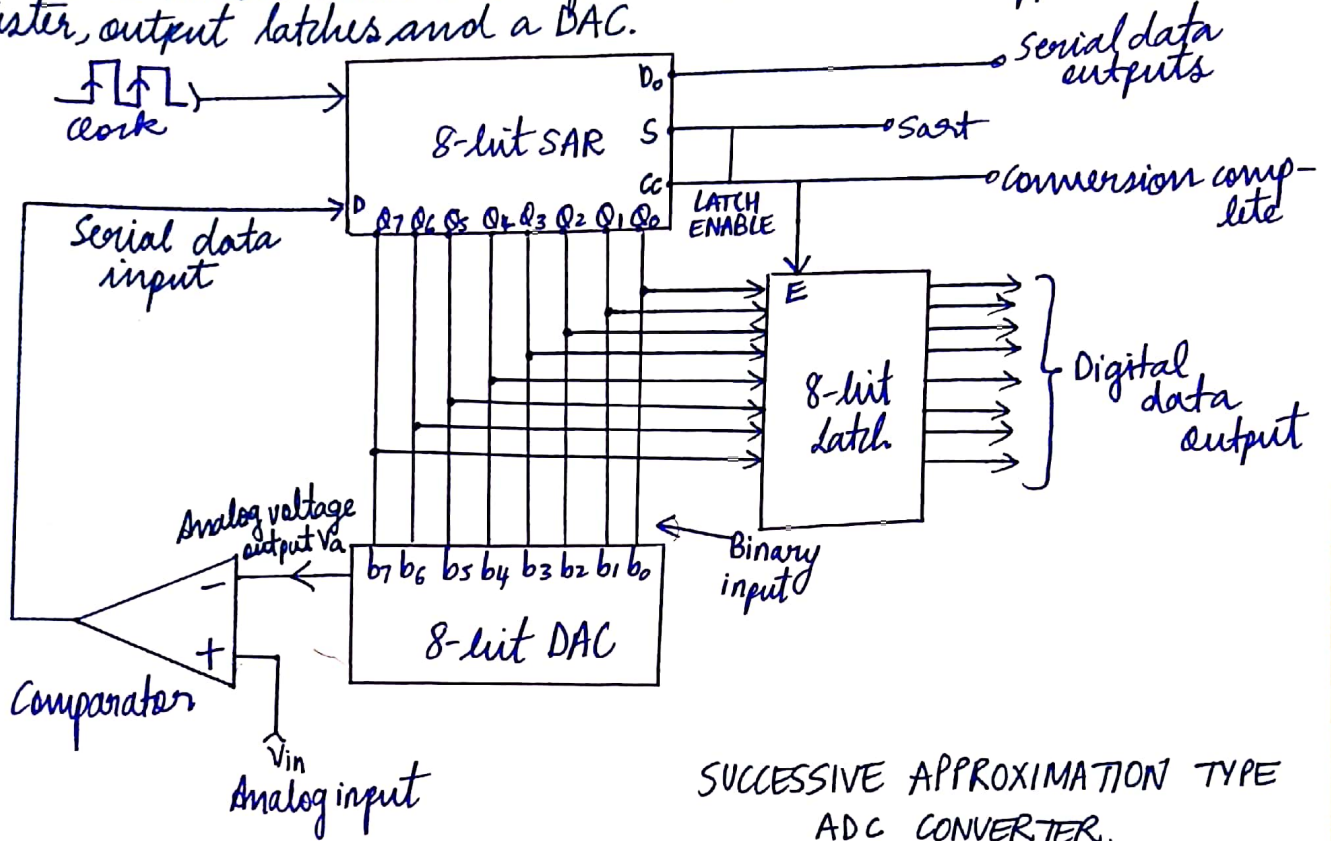The circuit below uses a comparator, a successive approximation register, output latches and a DAC.




### WORKING:

- At the start of a conversion cycle, the SAR is reset by holding the start (S) signal high.
- On the LOW to HIGH transition, the most significant output bit  $Q_7$  of the SAR is set.
- The DA converter then generates an analog equivalent to the  $Q_7$  bit, which is compared with  $V_{in}$ .
- If the comparator output is low, that means DAC output  $> V_{in}$  and the SAR will clear its MSB  $Q_7$ . On the other hand, if comparator output is high, which means DAC output  $< V_{in}$ , the SAR will keep MSB  $Q_7$  set.
- Similarly depending on the comparator output, the SAR will then either keep or reset bit  $Q_6$ , on the next clock pulse LOW to HIGH.
- This process is continued until the SAR tries all the bits (i.e.  $Q_5$ ,



- $Q_4, Q_3, Q_2, Q_1, Q_0$ )
- As soon as LSB  $Q_0$  is tried, the SAR forces the conversion complete (CC) signal HIGH to indicate that the parallel output lines contains valid data.
  - The CC signal in turn enables the latch and digital data appears at the output of the latch, which gives the digital representation of the analog voltage  $V_{in}$ .
  - For 8 bit SAR type ADC eight clock pulse is required, for 12 bit, 12 clock pulse is required and so on.
  - The advantages are that it has high speed and a very good resolution.

### Ans 7: INVERTING CONFIGURATION:

 

FIGURE

$R_{om}$  is the offset minimizing resistor

Apply KCL at node  $V_2$  :  $I_a + I_b + I_c = I_B + I_F$

$I_B = 0$  for ideal OP-AMP.

$$\therefore I_a + I_b + I_c = I_F$$

$$\Rightarrow \frac{V_a - V_2}{R_a} + \frac{V_b - V_2}{R_b} + \frac{V_c - V_2}{R_c} = \frac{V_2 - V_o}{R_f}$$

( $V_1 = V_2$  for ideal op-amp)

$$\therefore \frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} = -\frac{V_o}{R_f}$$

$$\therefore V_o = -\left(\frac{R_F}{R_a} V_a + \frac{R_F}{R_b} V_b + \frac{R_F}{R_c} V_c\right) \quad \text{--- ①}$$

SUMMING AMPLIFIER: In the figure, if  $R_a = R_b = R_c = R$ , then Eq. ① can be written as  $V_o = -\frac{R_F}{R}(V_a + V_b + V_c)$  and if  $R$  is chosen such that  $R = R_F$

$$V_o = -(V_a + V_b + V_c)$$

It is clear that output voltage is equal to the negative sum of all input voltages.

SCALING OR WEIGHTED AMPLIFIER: If each input voltage is amplified by different factor, it is known as scaling amplifier. This condition can be accomplished if  $R_a$ ,  $R_b$  and  $R_c$  are different in values.

$$\therefore V_o = -\left(\frac{R_F}{R_a} V_a + \frac{R_F}{R_b} V_b + \frac{R_F}{R_c} V_c\right)$$

$$\text{where } \frac{R_F}{R_a} \neq \frac{R_F}{R_b} \neq \frac{R_F}{R_c}$$

AVERAGING CIRCUIT: To convert it to an averaging circuit, we should have  $R_a = R_b = R_c = R$ .

Also, the gain by which each input is amplified must be equal to  $1/n$  over number of inputs ( $n$ ).

$$\frac{R_F}{R} = \frac{1}{n} = \frac{1}{3}$$


$$\therefore \text{output voltage } V_o = -\left(\frac{V_a + V_b + V_c}{3}\right)$$

↳ This is the negated average of three inputs.

Ans 4: INSTRUMENTATION AMPLIFIER: It is intended for precise, low-level signal amplification where low noise, low thermal and time drifts, high input resistance and accurate closed loop gain are required.



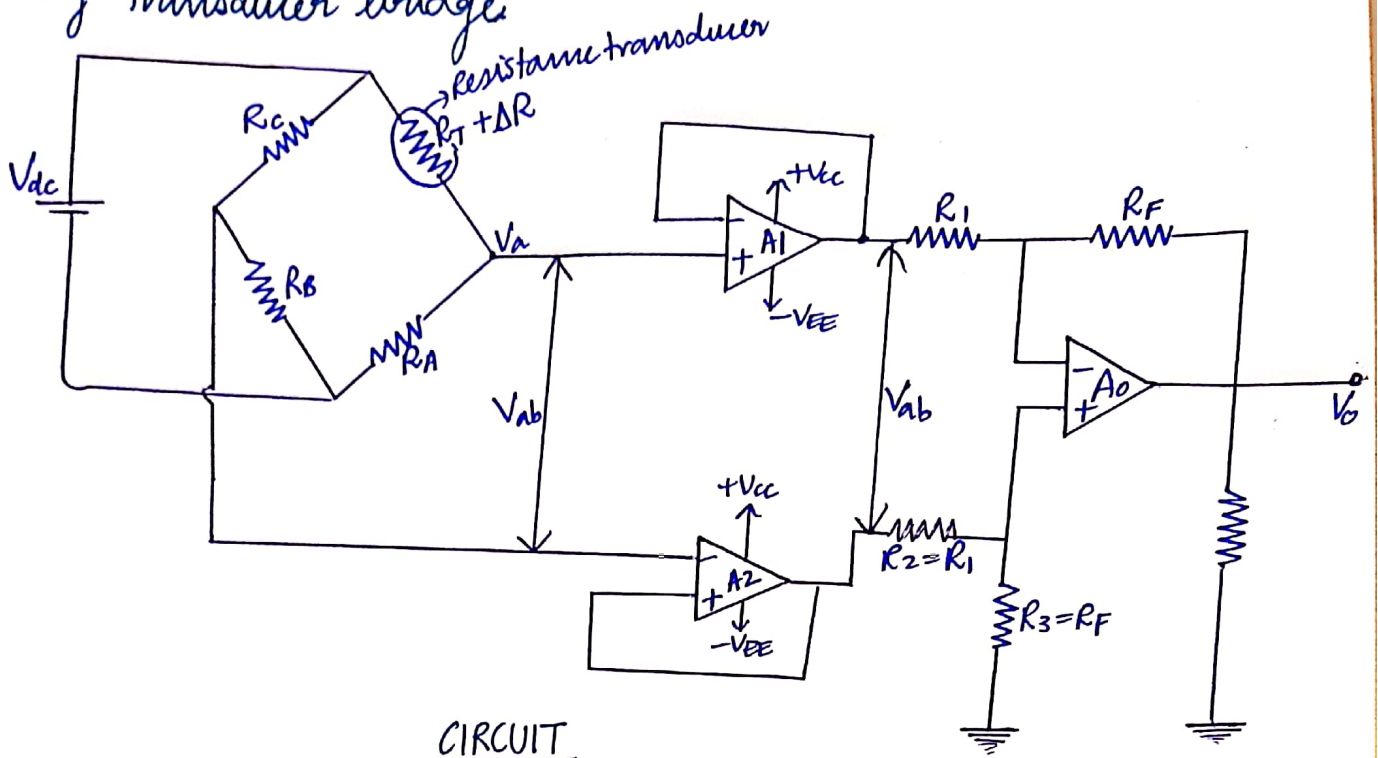In the figure, a simplified differential instrumentation amplifier using transducer bridge.



→ Resistors  $R_A, R_B, R_C$  and  $R_T$  are in balanced condition,  $\frac{R_C}{R_B} = \frac{R_T}{R_A}$

At this condition  $V_a = V_b$

But whenever there is change in resistance of transducer  $R_T$ , then  $V_a \neq V_b$ . Let the change in the resistance to  $R_T$  be  $\Delta R$ .

$$\therefore V_a = V_{dc} \left( \frac{R_A}{R_A + (R_T + \Delta R)} \right) \text{ and } V_b = V_{dc} \cdot \left( \frac{R_B}{R_B + R_C} \right)$$

$$\therefore V_{ab} = V_a - V_b = V_{dc} \left( \frac{R_A}{R_A + (R_T + \Delta R)} \right) - V_{dc} \left( \frac{R_B}{R_B + R_C} \right)$$

→ If  $R_A = R_B = R_C = R_T = R$ , then  $V_{ab} = V_{dc} \left( \frac{\Delta R}{2(2R + \Delta R)} \right)$

→ The output voltage  $V_{ab}$  of the bridge is then applied to the differential instrumentation amplifier consisting of three OPAMPS  $A_1, A_2, A_3$

→ The voltage follower  $A_1$  and  $A_2$  help in eliminating loading of the bridge circuit. Now, the third amplifier  $A_3$ , having gain  $\left( -\frac{R_F}{R_1} \right)$ , comes into picture to amplify  $V_{ab}$ , so the output  $V_o$ , can be given as,

$$V_o = \left(-\frac{R_F}{R_i}\right) V_{ab} = \frac{(\Delta R) V_{dc}}{2(2R + \Delta R)} \cdot \frac{R_F}{R_i}$$

$\therefore \Delta R$  is very small, so,  $2R + \Delta R \approx 2R$ ,  $\therefore V_o = \frac{R_F}{R_i} \cdot \frac{\Delta R}{4R} V_{dc}$

→ The equation indicates that  $V_o$  is directly proportional to the change in resistance  $\Delta R$  of the transducer  $R_T$ .  
It can be thermistor.

→ Some commonly used Instrument amplifiers are  $\mu A7425$ ,  $LH0036$  etc.

### Ans 1: CLASS B OUTPUT STAGE:

- It consists of complementary pair of transistor (an pnp and npn)
- They are connected such that both cannot conduct simultaneously

#### CIRCUIT OPERATION:

CASE ①: ( $V_I = 0$ ) → Both  $Q_n$  and  $Q_p$  in cut off ( $V_o = 0$ )


CASE ②:  $Q_n$  conducts (operates as emitter follower)

$V_I = +ve$   
 $V_I > 0.5V$  }  $V_o = V_I - V_{BE_n}$  (output follows  $V_I$ ). Thus,  $Q_n$  supplies load current.

Meanwhile, emitter base junction of  $Q_p$  will be reverse biased by  $V_{BE}$  of  $Q_n$  (approx  $0.7V$ ). and  $Q_p$  is cut off.

CASE ③: ( $V_I = -ve$ )  
and ( $V_I < -0.5V$ )

Class B  
output  
Stage

 

→  $Q_p$  is on and gets used as emitter follower.

→  $V_o = V_I + V_{BE_p}$  (output follows  $V_I$ )

→  $Q_p$  supplies the load current but  $Q_n$  is off

The circuit operates in push pull fashion as  $Q_n$  pushes (source) current into the load when  $V_I$  is present and  $Q_p$  pulls (sinks) current from the load when  $V_I$  is negative.



#### TRANSFER CHARACTERISTICS:

Both transistors are off in a range of  $V_I$  centered around zero and



So  $V_0 = 0$

  This deadband results in crossover distortion.



Deadband in class B transfer characteristics resulting in crossover distortion.

TRANSFER CHARACTERISTICS

- The effect of crossover distortion will be most pronounced when input signal amplitude is small.
- The distortion in audio power amplifiers gives unpleasant sounds

POWER CONVERSION EFFICIENCY:

- Neglect crossover distortion and let output sinusoidal have peak amplitude of  $\hat{V}_0$ .
- Average load power is  $P_L = \frac{(\frac{\hat{V}_0}{\sqrt{2}})^2}{R_L} = \frac{\hat{V}_0^2}{2R_L}$
- Average power drawn from each of the two power supplies,  $P_{S^+} = P_{S^-} = (I_{avg})V_{CC}$

→  $P_{S^+} = P_{S^-} = \left(\frac{\hat{V}_0}{\pi R_L}\right) V_{CC} \rightarrow I_{avg} = \frac{I_m}{\pi} = \frac{\hat{V}_0}{R_L \pi}$

→  $P_S (\text{total power supply}) = P_{S^+} + P_{S^-} \Rightarrow P_S = \frac{2\hat{V}_0 V_{CC}}{\pi R_L}$

→ efficiency ( $\eta$ ) =  $\frac{P_L}{P_S} = \frac{\left(\frac{\hat{V}_0^2}{2R_L}\right)}{\left(\frac{2\hat{V}_0}{\pi R_L}\right) V_{CC}} = \frac{\pi \hat{V}_0}{4 V_{CC}}$

→ When  $\hat{V}_0$  is max, i.e.,  $V_{CC} \Rightarrow \eta \% = \frac{\pi}{4} = 78.5\%$

Also, max average load power,  $P_{L \text{ max}} = \frac{V_{CC}^2}{2R_L}$   
(When  $\hat{V}_0 = V_{CC}$ )