

IAT 3

suchi.s@cmrit.ac.in [Switch account](#)



The name, email, and photo associated with your Google account will be recorded when you upload files and submit this form

* Required

Explain the working of 4 bit Carry Look Ahead Adder *

10 points

 Add file

Explain the working of 4 bit Shift Register *

10 points

 Add file

Explain the Manufacturing Test Principles *

10 points

 Add file

Explain 3T DRAM working principle & estimate area & power consumption 10 points

*

 Add file

Discuss FPGA Architecture *

10 points

 Add file



Submit

Clear form

This form was created inside of CMR Institute of Technology. [Report Abuse](#)

Google Forms

