

CBCS SCHEME



USN

--	--	--	--	--	--	--	--	--	--

17EE73

Seventh Semester B.E. Degree Examination, Feb./Mar. 2022 High Voltage Engineering

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- Define Townsend's first and secondary ionization coefficients. Derive an expression for the current growth in a gas discharge due to secondary mechanism. (08 Marks)
 - Explain the streams theory of breakdown in air at atmospheric pressure. (08 Marks)
 - The following observations were made in an experiment for determination of dielectric strength of transformer oil. Determine the power law equation.

Gap spacing (cm)	4	6	8	10
Breakdown voltage (kv)	88	135	165	212

(04 Marks)

OR

- Describe bubble theory and thermal mechanism of breakdown in liquid dielectrics. (08 Marks)
 - Classify the breakdown mechanism in solids and explain the electromechanical breakdown mechanism in solid dielectrics. (08 Marks)
 - A steady current of $600\mu\text{A}$ flows through the plane electrode separated by a distance of 0.5cm when a voltage of 10kV is applied. Determine the Townsend's first Ionization coefficient if a current of $60\mu\text{A}$ flows when the distance of separation is reduced to 0.1cm and the field is kept constant at the previous value. (04 Marks)

Module-2

- What are the different forms of high voltage and mention their applications. (04 Marks)
 - Explain the working of Cockcroft-Walton voltage multiplier circuit with schematic diagram. (08 Marks)
 - With the help of a neat sketch, explain the construction and working principle of cascading of transformers of three-units for producing very high AC voltage. (08 Marks)

OR

- Explain the construction and working of a three-electrode gap tripping circuit used for the impulse generator. (08 Marks)
 - With the help of a neat sketch, explain the working of impulse current generator circuit and its waveform. (08 Marks)
 - A 100KVA, 400V/250KV testing transformer has 8% leakage reactance and 2% resistance on 100KVA base. A cable has to be tested at 500KV using the above transformer as a resonant transformer at 50Hz. If the charging current of the cable at 500KV is 0.4A, find the series inductance required. Assume 2% resistance for the inductor to be used and the connecting leads. Neglect dielectric loss of the cable. What will be the input voltage to the transformer? (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Explain the working principle of generating voltmeter with a neat sketch. (06 Marks)
 b. Explain how peak value of high voltage AC is measured using Chubb-Fortescue method. (06 Marks)
 c. Explain the factors influencing the sparkover voltage of sphere gaps. (08 Marks)

OR

- 6 a. Explain the schematic arrangement of an impulse potential divider with an oscilloscope connected for measuring impulse voltages. (08 Marks)
 b. Explain with schematic diagrams how DC current can be measured using DC current transformers. (06 Marks)
 c. A Rogowski coil is required to measure impulse current of 8KA having rate of change of current of 10^{10} A/sec. The voltmeter is connected across the integrating circuit which reads 8 volts for full scale deflection. The input to the integrating circuit is from the Rogowski coil. Determine the mutual inductance of coil and R and C of the integrating circuit. (06 Marks)

Module-4

- 7 a. Explain the mathematical models for lightning discharges. (06 Marks)
 b. Explain the successive reflection lattice of a travelling wave. (06 Marks)
 c. Derive the expression for the voltage and current waves on long transmission lines and obtain the surge impedance of the line. (08 Marks)

OR

- 8 a. Explain the principle of insulation coordination in EHV and UHV systems. (10 Marks)
 b. Explain with suitable figures the principles and functioning of i) Expulsion gaps ii) Protector tubes. (10 Marks)

Module-5

- 9 a. Explain the high voltage Schering bridge for the $\tan \delta$ and capacitance measurement of insulators or bushings. (10 Marks)
 b. What are partial discharges? Explain the methods of balanced detection for locating partial discharges in electrical equipment. (10 Marks)

OR

- 10 a. Explain the method of impulse testing of high voltage transformers. What is the procedure adopted for locating the failure? (10 Marks)
 b. Explain with a schematic diagram, the synthetic testing procedure on valve units in HVDC systems. What are the different tests done using synthetic test circuit? (10 Marks)

CMRIT LIBRARY
 BANGALORE - 560 037
