 


CBCS SCHEME

18EC72



Seventh Semester B.E. Degree Examination, Feb./Mar. 2022

VLSI Design

Time: 3 hrs

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- With necessary circuit diagram, explain the operation of tristate inverter. Also realize a 2 : 1 multiplexer using tristate inverter. (08 Marks)
 - Implement a D flipflop using transmission gates and explain its operation with necessary timing diagram. (08 Marks)
 - Realize CMOS compound gate for the function $Y = A(B + C) + DE$. (04 Marks)

OR

- Explain the operation of MOSFET with necessary diagrams. Also derive the equation for drain current in linear and saturation region of operation. (10 Marks)
 - Draw the circuit of CMOS inverter and explain its DC transfer characteristics. (06 Marks)
 - Explain the following non-ideal effects channel length modulation, mobility degradation. (04 Marks)

Module-2

- Explain CMOS n-well fabrication process with necessary diagrams. (12 Marks)
 - What is scaling. Compute drain current, power, current density and power density for constant field and constant voltage scaling. (08 Marks)

OR

- Draw the layout of $Y = (A + B + C)D$ and estimate the area. (08 Marks)
 - Mention different types of MOSFET capacitances and explain with necessary diagrams and equations. (06 Marks)
 - With neat diagram, explain lambda based design rules for wires and contacts. (06 Marks)

Module-3

- Develop the RC delay model to compute the delay of the logic circuit and calculate the delay of unit sized inverter driving another unit inverter. (08 Marks)
 - Explain Cascode Voltage Switch Logic (CVSL). Also realize two input AND/NAND using CVSL. (06 Marks)
 - Explain linear delay model. Compare the logical efforts of the following gates with the help of schematic diagrams :
i) 2-input NAND gate ii) 3-input NOR gate. (06 Marks)

OR

- Explain : i) pseudo nMOS ii) ganged CMOS with necessary circuit examples. (06 Marks)
 - Estimate t_{pdf} and t_{pdr} of a 3-input NAND gate if the output is loaded with h identical gates. Use Elmore delay model. (08 Marks)
 - Explain skewed gates with an example. (06 Marks)

Module-4

- 7 a. With necessary circuit diagrams, explain resettable latches with
 i) synchronous reset
 ii) asynchronous reset. (08 Marks)
- b. Compute the output voltage V_{out} in the following pass transistor circuits. Assume $V_t = 0.7$.
 (Ref. Fig.Q7(b)).

 


Fig.Q7(b) (06 Marks)

- c. With necessary diagram, explain a D flipflop with two-phase non-overlapping clocks. (06 Marks)

OR

- 8 a. With necessary circuit diagram explain 3-bit dynamic shift register with depletion load. (08 Marks)
- b. Realize $F = \overline{A_1 A_2 A_3} + B_1 B_2$ using dynamic CMOS logic. Also explain the cascading problem in dynamic logic with necessary example. (08 Marks)
- c. Explain the general structure of ratioless synchronous dynamic logic with relevant diagram. (04 Marks)

Module-5

- 9 a. With necessary circuit diagram, explain the operation of three transistor DRAM cell. (08 Marks)
- b. Explain full CMOS SRAM cell with necessary circuit topology. (08 Marks)
- c. Explain the terms :
 i) Observability
 ii) Controllability
 iii) Fault coverage. (04 Marks)

CMRIT LIBRARY
 BANGALORE - 560 037

OR

- 10 a. What is a fault model? Explain stuck-at model with examples. (07 Marks)
- b. Mention the approaches used in design for testability. Explain scan based testing using necessary diagrams. (07 Marks)
- c. Draw the circuit of 3-bit BIST register and explain. (06 Marks)
