 


CBCS SCHEME



USN

--	--	--	--	--	--	--	--

15TE73

Seventh Semester B.E. Degree Examination, Feb./Mar. 2022

CMOS VLSI Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. With a neat diagram, explain the behavior of nMOS enhancement mode MOSFET in different regions and draw the V-I characteristics. (10 Marks)
- b. Explain the following:
 - i) Channel length modulation
 - ii) Threshold voltage-body effect. (06 Marks)

OR

- 2 a. Illustrate the nMOS fabrication with neat diagram. (10 Marks)
- b. Give the comparisons between CMOS and Bipolar Technology. (06 Marks)

Module-2

- 3 a. Obtain the CMOS circuit and stick diagram for the following function $F = \overline{(A + BC)D}$. (06 Marks)
- b. Using λ -based design rules, draw the layout for a nMOS 3-input NOR gate, using the following transistor L:W ratios:
 - i) P.U. transistor = 8:1
 - ii) P.D. transistors = 1:2, 1:2, 1:2 (10 Marks)

OR

- 4 a. For the following structure obtain C_m , C_p , C_g and C_t . Given that the relative values of capacitances are metal $1 = 0.075 \square C_g$, polysilicon $= 0.1 \square C_g$. (08 Marks)

 


Fig.Q.4(a)

- b. Derive the expressions for rise time and fall time delays of a CMOS inverters. What is the condition for symmetrical operation? (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Derive scaling factors for the following MOS parameters:
- Carrier density in channel, Q_{on}
 - Channel resistance, R_{on}
 - Gate delay, T_d
 - Switching energy per gate E_g
- Scaling method to be adopted is combined voltage and dimension method. (08 Marks)
- b. Explain a 4×4 barrel shifter with neat diagram. (08 Marks)

OR

- 6 a. How to implement arithmetic and logic operation with a standard adder? Explain with the help of logic expression. (06 Marks)
- b. Explain carry look ahead adder. (10 Marks)

Module-4

- 7 a. Explain the following:
- Pseudo nMOS logic
 - C^2 MOS logic. (06 Marks)
- b. Explain the structured design of a purity generator with necessary blocks and stick diagram. (10 Marks)

OR

- 8 a. Explain generic structure of FPGA with block diagram. (08 Marks)
- b. Explain placement and routing with respect to FPGA. (08 Marks)

Module-5

- 9 a. Explain with a neat diagram a 3 transistor dynamic RAM cell. (08 Marks)
- b. Explain pseudo static memory cell using circuit diagram. (08 Marks)

OR

- 10 a. Write a short notes on:
- Built In Self Test (BIST)
 - Scan design technique. (08 Marks)
- b. Write a short notes on:
- Stuck-at-faults
 - Short circuit and open circuit faults. (08 Marks)

CMRIT LIBRARY
BANGALORE - 560 037
