

USN 

--	--	--	--	--	--	--	--	--	--	--	--



## Internal Assessment Test 1 – December 2021

Sub:	Analog and Digital Electronics				Sub Code:	18CS33	Branch:	ISE		
Date:	17/12/2021	Duration:	90 min's	Max Marks:	50	Sem/Sec:	III / A,B and C		OBE	
<b>Answer any FIVE FULL Questions</b>								MARKS	CO	RBT
1	Define Implicants, Combinational Circuits. Explain prime and essential prime implicants with example. Find the minterm & maxterm expansion of $F(a,b,c,d)=a'(b'+d)+acd'$ . Show that $a'c + b'c' + ab = a'b' + bc + ac'$						10	CO3	L2	
2	What is K-map & explain limitations of K-map? Solve $F(A,B,C,D) = \Pi M(0,3,4,7,8,10,12,14). \Pi D(2,6)$ using K map to get minimum POS expression and implement using basic, NAND only and NOR only gates.						10	CO3	L2	
3	What is Quine- McCuskey Method? Find the minimum SOP for the function. $F(A, B, C, D) = \Sigma m(0,4,5,10,11,13,15) + \Sigma d(1, 10, 15)$ using Quine McCuskey method.						10	CO3	L1	
4	Consider the following logic function $F(A, B, C, D) = \Sigma m(0,4,5,10,11,13,14,15)$ . a) Find two different minimum circuits which implements F using AND and OR gates. Identify two hazards in each circuit. b) Find an AND-OR circuit for F which as no hazards. c) Find an OR- AND circuit for F which as no hazards.						10	CO3	L1	
5	What is Multiplexer? Build 8: 1 Mux using basic gates.						10	CO3	L3	
6	What is Buffer? Explain different three state buffers. Construct 8-to-1 MUX using two 4-to-1 MUXes, two three-state buffers, and one inverter.						10	CO3	L3	

Faculty Signature

CCI Signature

HOD Signature

USN 

--	--	--	--	--	--	--	--	--	--	--	--



## Internal Assessment Test 1 – December 2021

Sub:	Analog and Digital Electronics				Sub Code:	18CS33	Branch:	ISE		
Date:	17/12/2021	Duration:	90 min's	Max Marks:	50	Sem/Sec:	III / A,B and C		OBE	
<b>Answer any FIVE FULL Questions</b>								MARKS	CO	RBT
1	Define Implicants, Combinational Circuits. Explain prime and essential prime implicants with example. Find the minterm & maxterm expansion of $F(a,b,c,d)=a'(b'+d)+acd'$ . Show that $a'c + b'c' + ab = a'b' + bc + ac'$						10	CO3	L2	
2	What is K-map & explain limitations of K-map? Solve $F(A,B,C,D) = \Pi M(0,3,4,7,8,10,12,14). \Pi D(2,6)$ using K map to get minimum POS expression and implement using basic, NAND only and NOR only gates.						10	CO3	L2	
3	What is Quine- McCuskey Method? Find the minimum SOP for the function. $F(A, B, C, D) = \Sigma m(0,4,5,10,11,13,15) + \Sigma d(1, 10, 15)$ using Quine McCuskey method.						10	CO3	L1	
4	Consider the following logic function $F(A, B, C, D) = \Sigma m(0,4,5,10,11,13,14,15)$ . a) Find two different minimum circuits which implements F using AND and OR gates. Identify two hazards in each circuit. b) Find an AND-OR circuit for F which as no hazards. c) Find an OR- AND circuit for F which as no hazards.						10	CO3	L1	
5	What is Multiplexer? Build 8: 1 Mux using basic gates.						10	CO3	L3	
6	What is Buffer? Explain different three state buffers. Construct 8-to-1 MUX using two 4-to-1 MUXes, two three-state buffers, and one inverter.						10	CO3	L3	

Faculty Signature

CCI Signature

HOD Signature

**Scheme of Evaluation**  
**Internal Assessment Test 1 – December 2021**

<b>Sub:</b>	Analog and Digital Electronics						<b>Code:</b>	18CS33	
<b>Date:</b>	17/12/2021	<b>Duration:</b>	90mins	<b>Max Marks:</b>	50	<b>Sem:</b>	III	<b>Branch:</b>	ISE

**Note:** Answer Any five full questions.

Question No.	Description	Marks Distribution		Max Marks
1	<p><b>Implicants:</b> A group of one or more 1's which are adjacent a group of one or more 1s which are adjacent and can be combined on a Karnaugh Map is called an <b>implicants</b>.</p> <p><b>Combinational Circuit:</b> The output of the combinational circuit depends on the values at the input at any given time.</p> <p><b>Definition of Prime and Essential Prime Implicants:</b></p> <p><b>Problem Solution</b></p>	1M	10M	10M
2	<p><b>Karnaugh map/K map</b> is a method simplifying and manipulating switching functions. K map method is faster and easier to apply than other simplification methods.</p> <p><b>Limitations of K map:</b></p> <ul style="list-style-type: none"> <li>➤ Complexity of <b>K-map</b> simplification process increases with the increase in the number of variables</li> <li>➤ K map is manual technique and simplification process heavily depends on the human ability.</li> </ul> <p><b>Solving the function using K map</b></p> <p><b>Logic circuit diagram using NAND and NOR Gates</b></p>	1M 2M 3M 4M	10M	10M
3	<p>The Quine-McCluskey method reduces the minterm expansion (standard sum-of-products form) of a function to obtain a minimum sum of products.</p> <p><b>Steps</b></p> <p><b>Prime Implicate Chart</b></p> <p><b>Final expression</b></p>	2M 5M 3M	10M	10M

4		<b>Finding Static 1 and Static 0 Hazard</b> <b>Hazard free equation in terms of AND-OR</b> <b>Hazard free equation in terms of OR - AND</b>	4M 2M 2M	10M	10M
5		The multiplexer is a device that has multiple inputs and single line output. The select lines determine which input is connected to the output. <b>Implementation of 8:1 MUX using basic gates</b> <b>Block Diagram</b> <b>Truth Table</b> <b>Expression</b> <b>Logic Diagram</b>	2M  8M	10M	10M
6		A <b>buffer</b> has only a single input and a single output with behavior that is the opposite of an NOT gate. It simply passes its input, unchanged, to its output.  <b>Different types of three state buffers</b> <b>Implementing 8:1 MUX using 4:1 MUX and Buffers</b>	1M  4M 5M	10M	10M

**Scheme Of Evaluation Internal Assessment Test 1 – NOV 2021**

<b>Sub:</b>	Analog and Digital Electronics						<b>Code:</b>	18CS33	
<b>Date:</b>	17/12/2021	<b>Duration:</b>	90mins	<b>Max Marks:</b>	50	<b>Sem:</b>	III	<b>Branch:</b>	ISE

**Note:** Answer Any full five questions

**Q. 1** Define Implicants, Combinational Circuits. Explain prime and essential prime implicants with example. Find the minterm & maxterm expansion of  $F(a,b,c,d)=a'(b'+d)+acd'$ . Show that  $a'c + b'c' + ab = a'b' + bc + ac'$ .

**Implicants:**

A group of one or more 1's which are adjacent a group of one or more 1s which are adjacent and can be combined on a Karnaugh Map is called an **implicants**.

**Combinational Circuits:**

Combinational Circuits are circuits made up of different types of logic gates. The output of the combinational circuit depends on the values at the input at any given time.

**Prime and Essential Prime Implicants:**

A group of square or rectangle made up of bunch of adjacent minterms which is allowed by definition of K-Map are **called prime implicants (PI)**. Consider a Boolean function,  $F = AB + ABC + BC$ . Implicants. are AB, ABC and BC. Prime implicants.

Essential prime implicants (EPI) are those prime implicants which always appear in final solution.

Duplicate terms have been crossed out, because  $X + X = X$ . This expression can then be converted to decimal notation:

$$\begin{aligned}
 f &= a'b'c'd' + a'b'c'd + a'b'cd' + a'b'cd + a'bc'd + a'bcd + abcd' + ab'cd' \\
 &\quad 0000 \quad 0001 \quad 0010 \quad 0011 \quad 0101 \quad 0111 \quad 1110 \quad 1010 \\
 f &= \Sigma m(0, 1, 2, 3, 5, 7, 10, 14)
 \end{aligned}$$

The maxterm expansion for  $f$  can then be obtained by listing the decimal integers (in the range 0 to 15) which do not correspond to minterms of  $f$ :

$$f = \Pi M(4, 6, 8, 9, 11, 12, 13, 15)$$

Show that  $a'c + b'c' + ab = a'b' + bc + ac'$ .

We will find the minterm expansion of each side by supplying the missing variables. For the left side,

$$\begin{aligned}
 a'c(b + b') + b'c'(a + a') + ab(c + c') \\
 &= a'bc + a'b'c + ab'c' + a'b'c' + abc + abc' \\
 &= m_3 + m_1 + m_4 + m_0 + m_7 + m_6
 \end{aligned}$$

For the right side,

$$\begin{aligned}
 a'b'(c + c') + bc(a + a') + ac'(b + b') \\
 &= a'b'c + a'b'c + abc + a'bc + abc' + ab'c' \\
 &= m_1 + m_0 + m_7 + m_3 + m_6 + m_4
 \end{aligned}$$


Because the two minterm expansions are the same, the equation is valid.

**Q.2** What is K-map & explain limitations of K-map? Solve  $F(A,B,C,D) = \prod M(0,3,4,7,8,10,12,14) \cdot \prod D(2,6)$  using K map to get minimum POS expression and implement using basic, NAND only and NOR only gates.


**Karnaugh map/K map** is a method simplifying and manipulating switching functions. K map method is faster and easier to apply than other simplification methods.

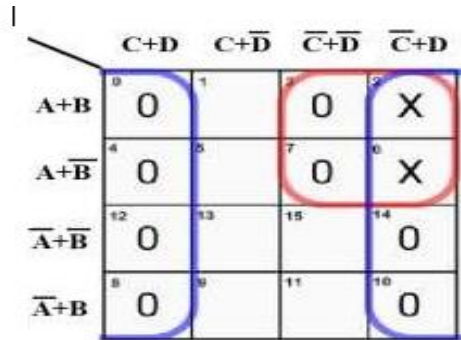**Limitations of K map:**

- Complexity of **K-map** simplification process increases with the increase in the number of variables
- K map is manual technique and simplification process heavily depends on the human ability.



$S = (A + \bar{C}) \cdot (D)$

 

**Q.3** What is Quine- McCuskey Method? Find the minimum SOP for the function.  $F(A, B, C, D) = \sum m(0,4,5,10,11,13,15) + \sum d(1, 10, 15)$  using Quine McCuskey method.

**The Quine-McCluskey** method provides a systematic simplification procedure which can be readily programmed for a digital computer. The Quine-McCluskey method reduces the minterm expansion (standard sum-of-products form) of a function to obtain a minimum sum of products.

**Petrick's method** is a technique for determining all minimum sum-of-products solutions from a prime implicant chart

$F(A, B, C, D) = \sum m(2, 3, 7, 9, 11, 13) + \sum d(1, 10, 15)$  using Quine McCuskey method.

Q. 3: QM. Mtd:


$$F(A, B, C, D) = \sum m(0, 4, 5, 10, 11, 13, 15) + \sum d(1, 10, 15)$$

Solution:

Sop: ?

Stage - I	Stage - II	Stage - III
ABCD	abcd	
0 0000	(0,1) 000 -	(0,1,4,5) 0 - 0 -
1 0001	(0,4) 0 - 0 0	(0,4,15) 0 - 0 - X
2 0100	(1,5) 0 - 0 1	
3 0101	(4,5) 0 1 0 -	
4 0110		
5 0111		
10 1010	(5,13) - 1 0 1	
11 1011	(10,11) 1 0 1 -	
13 1101	(11,15) 1 - 1 1	
15 1111	(13,15) 1 1 - 1	

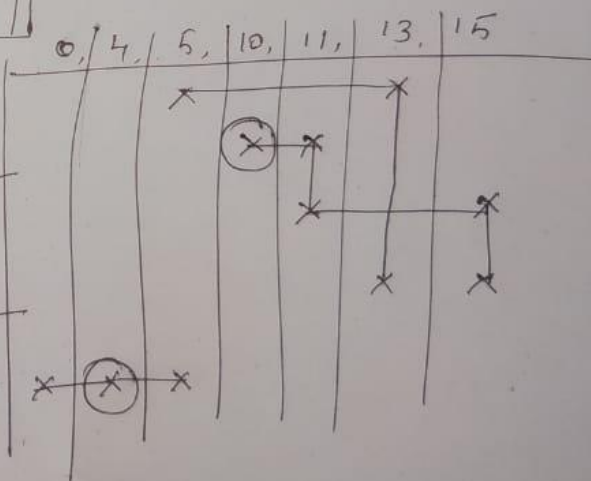$PI = (5, 13) \quad b\bar{c}d$   
 $(10, 11) \quad a\bar{b}c$   
 $(11, 15) \quad acd$   
 $(13, 15) \quad abc$   
 $(0, 1, 4, 5) \quad \bar{a}\bar{c}$



$$F_{PI} = F = \boxed{a\bar{b}c + abc + \bar{a}\bar{c}} \quad \text{Sop.}$$

$F_{PI} = a\bar{b}c, abc, \bar{a}\bar{c}$   
 $F_2 = bcd, \bar{a}bc, acd, abc, \bar{a}\bar{c}$





REDMI NOTE 6 PRO  
MI DUAL CAMERA



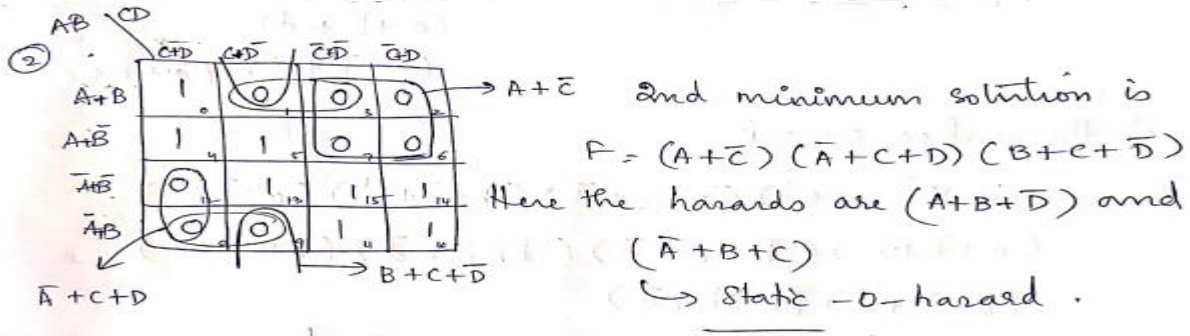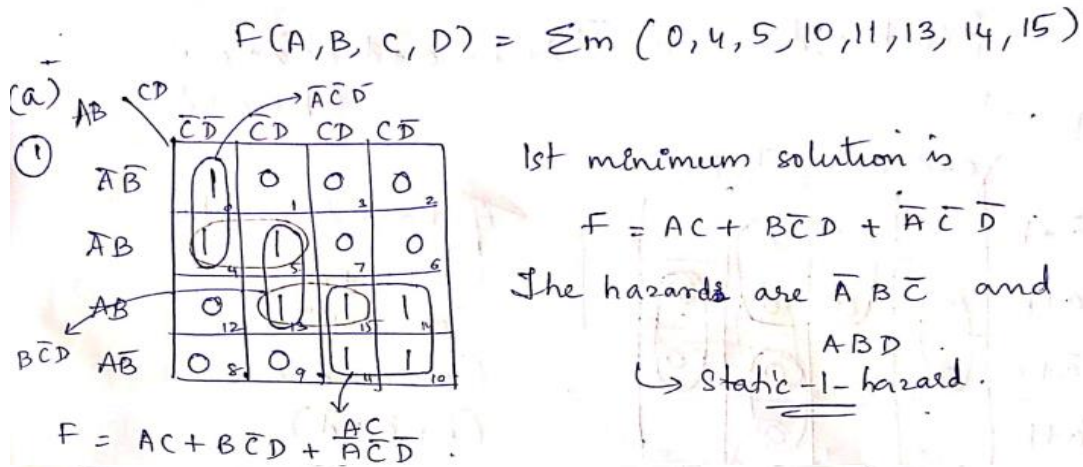**Q.4** Consider the following logic function  $F(A, B, C, D) = \sum m(0, 4, 5, 10, 11, 13, 14, 15)$ .

- Find two different minimum circuits which implements  $F$  using AND and OR gates. Identify two hazards in each circuit.
- Find an AND-OR circuit for  $F$  which as no hazards.
- Find an OR- AND circuit for  $F$  which as no hazards.



(b) AND-OR ckt for  $F$  which has no hazards:

$$F = AC + \bar{B}\bar{C}D + \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C} + ABD$$


(c) OR-AND ckt for  $F$  which has no hazards:

$$F = (A + \bar{C})(\bar{A} + C + D)(B + C + \bar{D})(A + B + \bar{D})(\bar{A} + B + C)$$

**Q.5 What is Multiplexer? Build 8: 1 Mux using basic gates.**

The multiplexer is a device that has multiple inputs and single line output. The select lines determine which input is connected to the output.

Block Diagram:

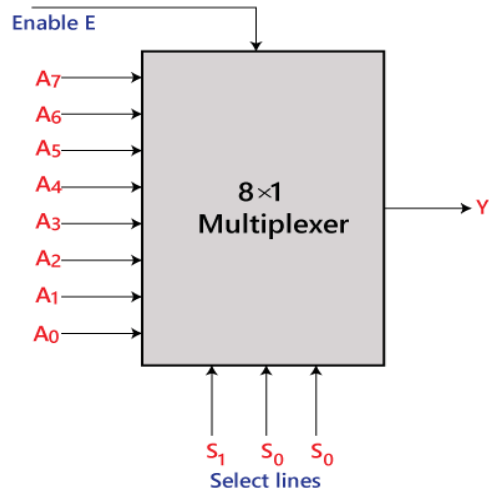

Truth Table:


INPUTS			Output
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y
0	0	0	A <sub>0</sub>
0	0	1	A <sub>1</sub>
0	1	0	A <sub>2</sub>
0	1	1	A <sub>3</sub>
1	0	0	A <sub>4</sub>
1	0	1	A <sub>5</sub>
1	1	0	A <sub>6</sub>
1	1	1	A <sub>7</sub>

The logical expression of the term Y is as follows:

$$Y = S_0' \cdot S_1' \cdot S_2' \cdot A_0 + S_0 \cdot S_1' \cdot S_2' \cdot A_1 + S_0' \cdot S_1 \cdot S_2' \cdot A_2 + S_0 \cdot S_1 \cdot S_2' \cdot A_3 + S_0' \cdot S_1' \cdot S_2 \cdot A_4 + S_0 \cdot S_1' \cdot S_2 \cdot A_5 + S_0' \cdot S_1 \cdot S_2 \cdot A_6 + S_0 \cdot S_1 \cdot S_2 \cdot A_7$$

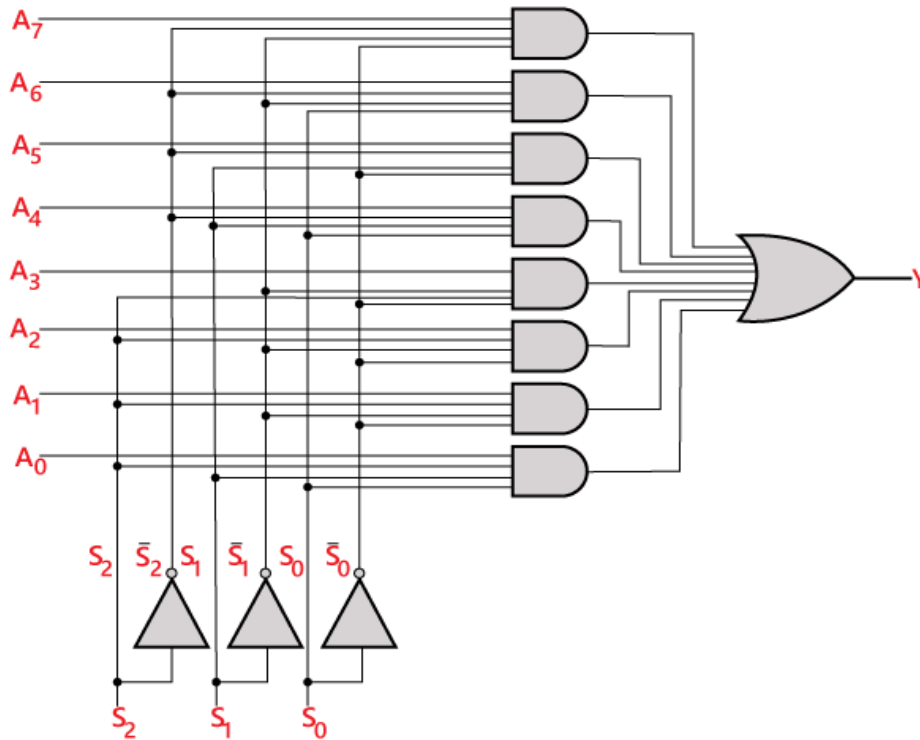Logical circuit of the above expression is given below:






**Q 6. What is Buffer? Explain different three state buffers. Construct 8-to-1 MUX using two 4-to-1 MUXes, two three-state buffers, and one inverter.**

A **buffer** has only a single input and a single output with behavior that is the opposite of an NOT gate. It simply passes its input, unchanged, to its output.

The following Figure shows the truth tables for four types of three-state buffers.

 

**Fig: Four kinds of three state buffers**

In Figures (a) and (b), the enable input B is not inverted, so the buffer output is enabled when B = 1 and disabled when B = 0. That is, the buffer operates normally when B = 1, and the buffer output is effectively an open circuit when B = 0. We use the symbol Z to represent this high-impedance state.

In Figure (b), the buffer output is inverted so that C = A' when the buffer is enabled.

The buffers in Figures (c) and (d) operate the same as in (a) and (b) except that the enable input is inverted, so the buffer is enabled when B = 0.

In the following Figure, the outputs of two three-state buffers are tied together. When  $B = 0$ , the top buffer is enabled, so that  $D = A$ ; when  $B = 1$ , the lower buffer is enabled, so that  $D = C$ .

