

USN

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|



Internal Assessment Test 2 – January 2022

| | | | | | |
|-------|--------------------------------|-----------|----------|------------|-------------------------|
| Sub: | Analog and Digital Electronics | Sub Code: | 18CS33 | Branch: | CSE |
| Date: | 25/1/2022 | Duration: | 90 min's | Max Marks: | 50 |
| | | | | Sem/Sec: | 3 rd / A,B,C |

Answer any FIVE FULL Questions

MARKS CO RBT

1 (a) Explain the operation of master and slave JK flip flop with truth table and timing diagram


[7] CO4 L4

ANS:


Master Slave SR Flip flop

| <i>S</i> | <i>R</i> | <i>Q</i> | <i>Q_{next}</i> | <i>Q_{next}'</i> |
|----------|----------|----------|-------------------------|--------------------------|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | × | × |
| 1 | 1 | 1 | × | × |

Truth Table

 

(b)

 


It is built from two gated SR latches: one a master, and the other a slave.

The master takes the flip-flop's inputs: S (set), R (reset), and C (clock).

 2. The clock input is fed to the latch's gate input.
3. The slave takes the master's outputs as inputs (Q to S and Q_n to R), and the complement of the flip-flop's clock input.
4. The slave's outputs are the flip-flop's outputs.
5. This difference in clock inputs between the two latches *disconnects* them and eliminates the transparency between the flip-flop's inputs and outputs.
6. The schematic below shows a master-slave SR flip-flop.
7. The two inputs S and R are used to set and reset the data respectively.
8. The clock input C is used to control both the master and slave latches making sure only one of the latches can set its data at any given time.
9. When C has the value 1, the master latch can set its data and the slave latch cannot. When C has the value 0, the slave can set its data and the master cannot

Given a rising-edge-triggered D flip-flop with the following inputs, sketch the waveform for Q . assume $Q=1$



[3]

CO4

L3

2

Derive the characteristic equations for the following latches and flip-flops in product of-sums form.

[10]


CO4

L3

- (a) S-R latch or flip-flop
- (b) Gated D latch
- (c) D flip-flop
- (d) J-K flip-flop
- (e) T flip-flop

ANS:

| INPUTS | | | OUTPUTS | REMARKS |
|--------|---|-----------------------------------|----------------------------------|---|
| S | R | Q _n (Present State) | Q _{n+1} (Next State) | States and Conditions |
| 0 | 0 | X | Q _n | Hold State condition S = R = 0 |
| 0 | 1 | X | 0 | Reset state condition S = 0, R = 1 |
| 1 | 0 | X | 1 | Set state condition S = 1, R = 0 |
| 1 | 1 | X | Indeterminate | Indeterminate state condition S = R = 1 |

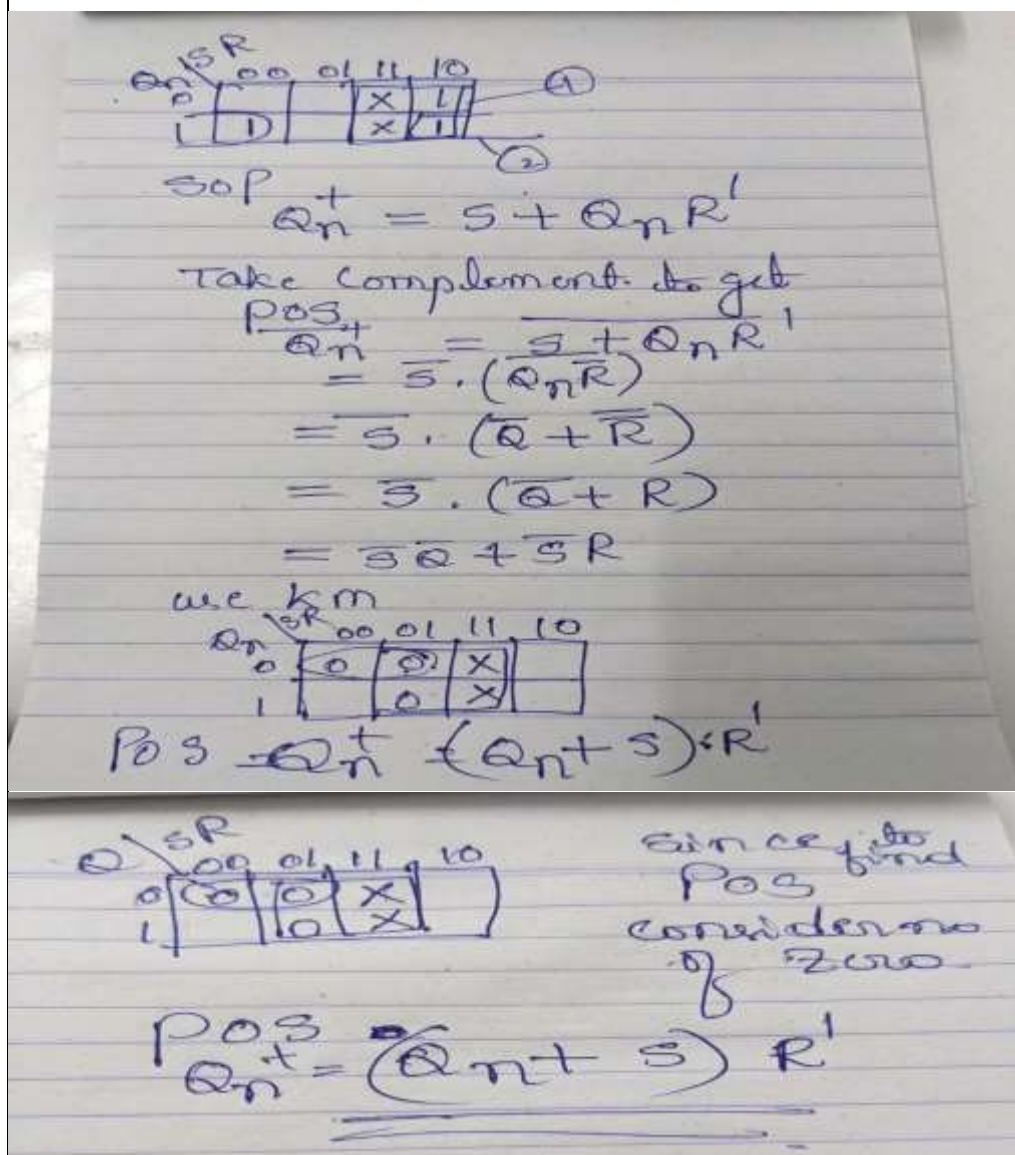


Gated D latch


| | | | |
|-----|------|-------|-------|
| D | Q | GDQ | Q^+ |
| L | Q' | 000 | 0 |
| G | Q' | 001 | 1 |
| | | 010 | 0 |
| | | 011 | 1 |
| | | 100 | 0 |
| | | 101 | 0 |
| | | 110 | 1 |
| | | 111 | 1 |

| | | | | |
|------|------|------|------|------|
| GD | 00 | 01 | 11 | 10 |
| Q | | | | |
| 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 |


$Q^+ = G'Q + GD$

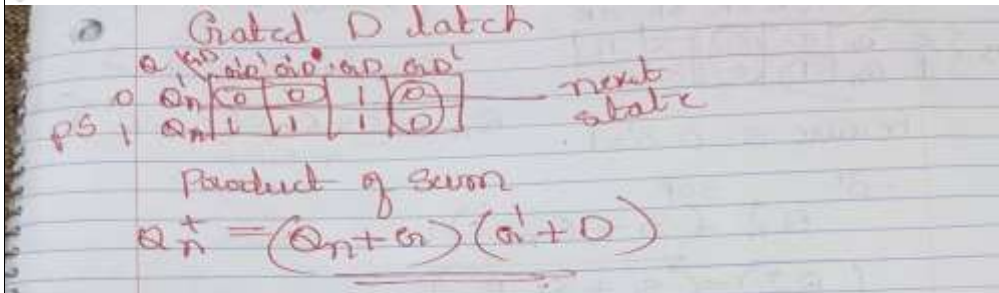

D flip flop:

 

(a) Rising-edge trigger

 


(b) Falling-edge trigger

| | |
|------|-------|
| DQ | Q^+ |
| 00 | 0 |
| 01 | 0 |
| 10 | 1 |
| 11 | 1 |


(c) Truth table

$Q^+ = D$

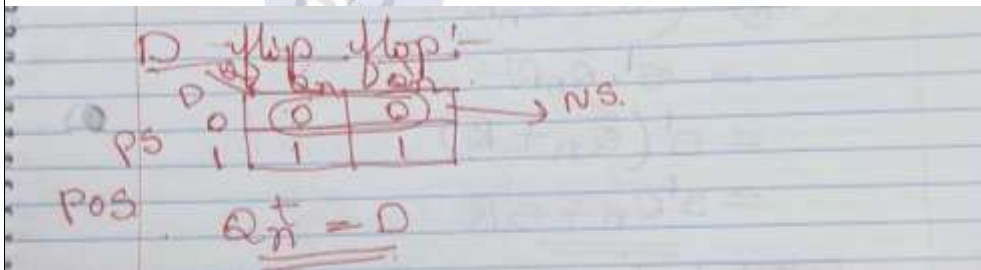


JK Flip Flop:

| INPUTS | | Q_n (Present State) | OUTPUTS Q_{n+1} (Next State) | REMARKS States and Conditions |
|--------|---|--------------------------|--------------------------------------|--------------------------------------|
| J | K | | | |
| 0 | 0 | X | Q_n | Hold State condition $J = K = 0$ |
| 0 | 1 | X | 0 | Reset state condition $J = 0, K = 1$ |
| 1 | 0 | X | 1 | Set state condition $J = 1, K = 0$ |
| 1 | 1 | X | Q'_n | Toggle state condition $J = K = 1$ |

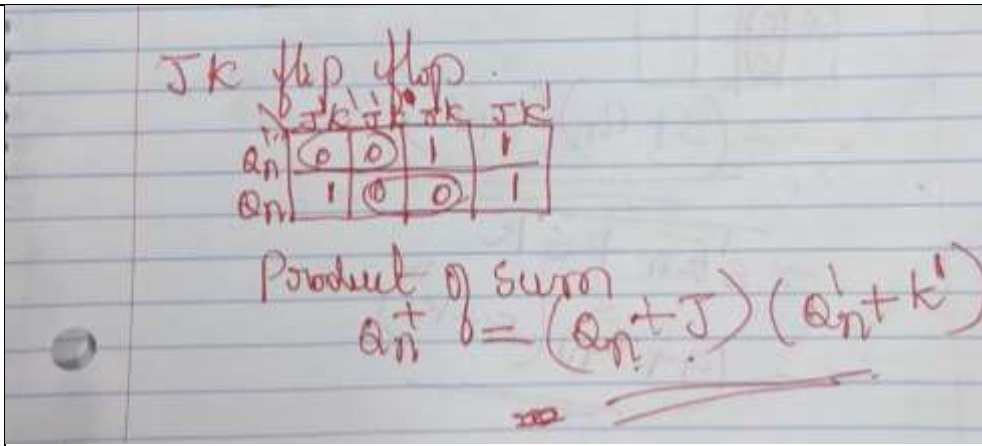


T Flip Flop :

 

| T | Q | Q ⁺ |
|---|---|----------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

(b)

$$Q^+ = TQ + TQ' = T \oplus Q$$

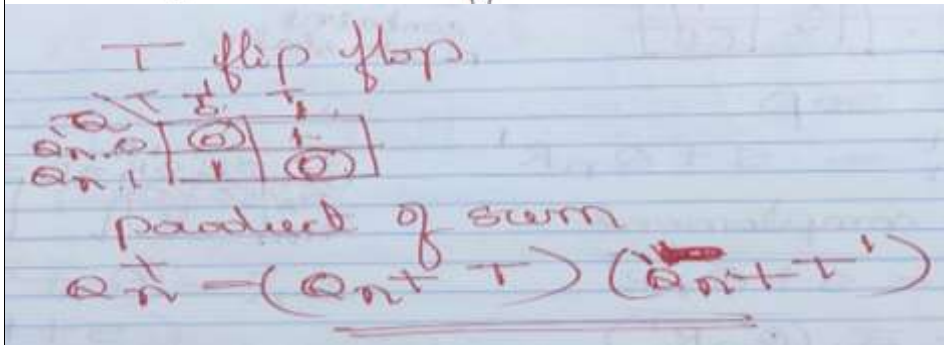

3

Write a structural VHDL module for a 4 bit adder using Full adder component.

[10]

CO5

L3

Full Adder

Library ieee;

use ieee.std_logic_1164.all;

```
entity fa is port(a,b,c:in bit; sum,carry:out bit);
end fa;
```

architecture data of fa is

begin

sum<= a xor b xor c;

carry <= ((a and b) or (b and c) or (a and c));

end data;

4bit adder



library IEEE;

use IEEE.STD_LOGIC_1164.all;

```
entity 4bitadder is
```

```
port(a : in STD_LOGIC_VECTOR(3 downto 0);
```

```
b : in STD LOGIC VECTOR(3 downto 0);
```
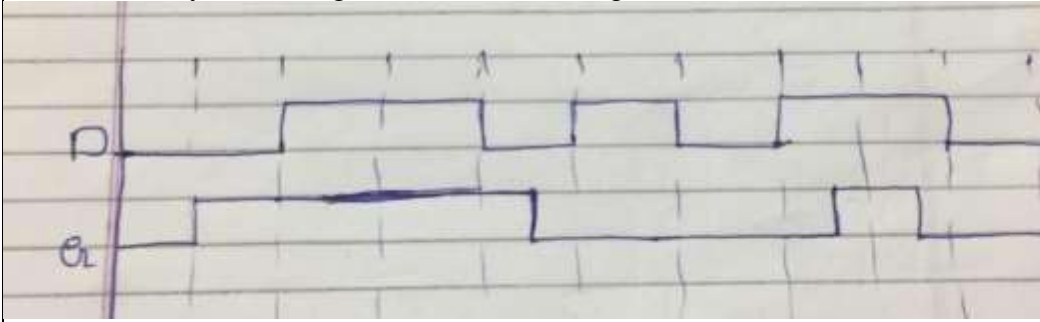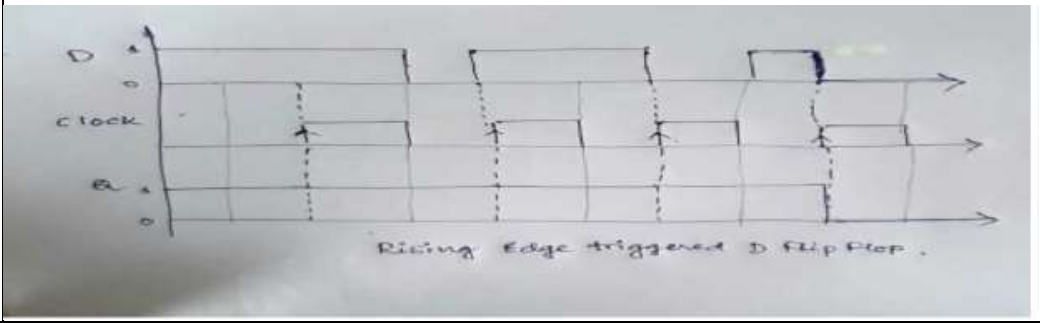
| | | | | |
|-------|--|------|-----|----|
| | <pre> ca : out STD_LOGIC; sum : out STD_LOGIC_VECTOR(3 downto 0)); end 4bitadder; architecture adder4 of 4bitadder is Component fa is port (a : in STD_LOGIC; b : in STD_LOGIC; c : in STD_LOGIC; sum : out STD_LOGIC; ca : out STD_LOGIC); end component; signal s : std_logic_vector (2 downto 0); signal temp: std_logic; begin temp<='0'; u0 : fa port map (a(0),b(0),temp, sum(0),s(0)); u1 : fa port map (a(1),b(1),s(0), sum(1),s(1)); u2 : fa port map (a(2),b(2),s(1), sum(2),s(2)); ue : fa port map (a(3),b(3),s(2), sum(3),ca); end adder4; </pre> | | | |
| 4 (a) | Explain edge-triggered D Flip Flop with truth table and timing diagram and why edge the trigger is important | [6] | CO4 | L4 |
| (b) | <p>Given a gated D latch with the following inputs, sketch the waveform for Q. assume initially Q=0 and gate is active when high.</p>  <p>ANS:</p>  <p>Rising Edge triggered D flip flop.</p> | [4] | CO4 | L3 |
| 5 | Design 3 bit Synchronous Down Counter using SR flip flop ANS: | [10] | CO4 | L3 |

Design 3-bit counter (down) synchronous
-ous counter using SR flip flop.


(1) Truth table, SR flip flop

| S | R | Q | Q ⁺ |
|---|---|---|----------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | X | X |

(2) Excitation table

| PS | NS | S | R |
|----|----|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | X | 0 |

(3) State Diagram

 

(4) Synthesis table

| CBA | C ⁺ B ⁺ A ⁺ | S _C R _C | S _B R _B | S _A R _A |
|-----|--|-------------------------------|-------------------------------|-------------------------------|
| 111 | 110 | X0 | X0 | 01 |
| 110 | 101 | X0 | 01 | 10 |
| 101 | 100 | X0 | 0X | 01 |
| 100 | 011 | 01 | 10 | 10 |
| 011 | 010 | 0X | X0 | 01 |
| 010 | 001 | 0X | 01 | 10 |
| 001 | 000 | 0X | 0X | 01 |
| 000 | 111 | 10 | 10 | 10 |

(5) To find S_CR_C, S_BR_B, S_AR_A

apply km method

| C | BA | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | X | X | X | X |

$S_C = \overline{CBA}$

| C | BA | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| 0 | 0 | 0 | X | X | X |
| 1 | 0 | 1 | 0 | 0 | 0 |

$R_C = CBA$

| C | BA | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| 0 | 0 | 1 | 0 | X | 0 |
| 1 | 0 | 1 | 0 | X | 0 |

$S_B = \overline{BA}$

| C | BA | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| 0 | 0 | 0 | X | 0 | 1 |
| 1 | 0 | 0 | X | 0 | 1 |


$R_B = BA$

| C | BA | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 |

$S_A = \overline{A}$

| C | BA | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 |

$R_A = A$

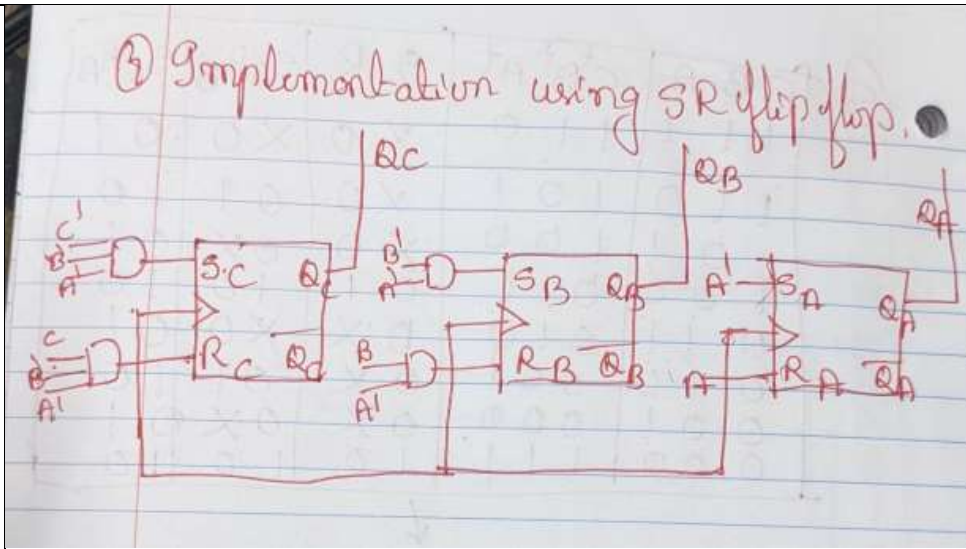

6

Write neat Sketch and Explain the working principle of Serial in parallel out (SIPO) with timing Diagram


[10]

CO4

L4,

ANS:

Serial-in to Parallel-out (SIPO) - the register is loaded with serial data, one bit at a time, with the stored data being available at the output in parallel form. For 'n' bit serial input data which need to be stored, the number of clock pulses required is equal to 'n'. and For 'n' bit parallel output data that need to be stored, the number of clock pulses required is zero. As no clock pulse is required for this operation.

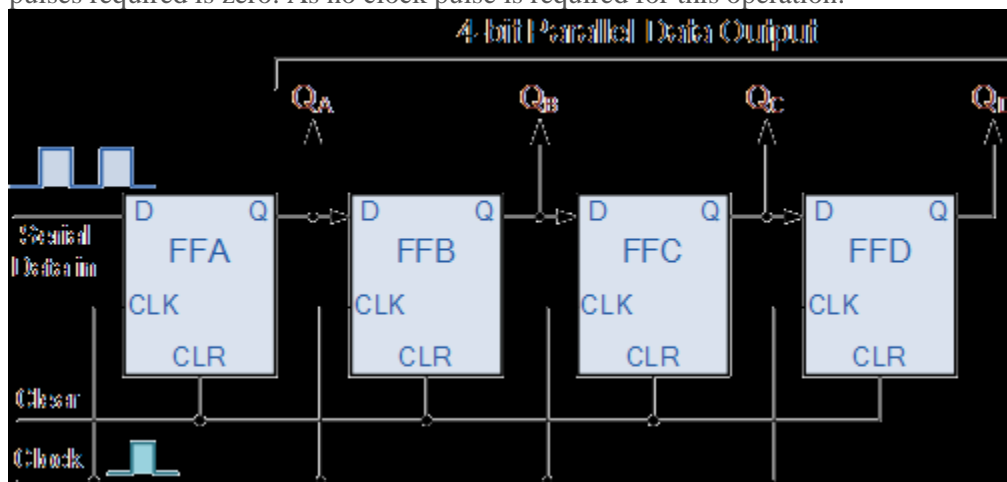

The operation is as follows. Let's assume that all the flip-flops (FFA to FFD) have just been RESET (CLEAR input) and that all the outputs QA to QD are at logic level "0" ie, no parallel data output.

If a logic "1" is connected to the DATA input pin of FFA then on the first clock pulse the output of FFA and therefore the resulting QA will be set HIGH to logic "1" with all the other outputs still remaining LOW at logic "0". Assume now that the DATA input pin of FFA has returned LOW again to logic "0" giving us one data pulse or 0-1-0.

The second clock pulse will change the output of FFA to logic "0" and the output of FF B and QB HIGH to logic "1" as its input D has the logic "1" level on it from QA. The logic "1" has now moved or been "shifted" one place along the register to the right as it is now at QA.


When the third clock pulse arrives this logic "1" value moves to the output of FF C (QC) and so on until the arrival of the fifth clock pulse which sets all the outputs QA to QD back again to logic level "0" because the input to FFA has remained constant at logic level "0".

The effect of each clock pulse is to shift the data contents of each stage one place to the right, and this is shown in the following table until the complete data value of 0-0-0-1

is stored in the register. This data value can now be read directly from the outputs of QA to QD.

Then the data has been converted from a serial data input signal to a parallel data output.

| Clock Pulse No | QA | QB | QC | QD |
|----------------|----|----|----|----|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 0 | 1 | 0 |
| 4 | 0 | 0 | 0 | 1 |
| 5 | 0 | 0 | 0 | 0 |

 

7 Design 3 bit Synchronous Counter for the following sequence 0,3,5,6,7 using D flip flop
ANS:

[10] CO4 L3

Design 3 bit synchronous counter - seq. 0, 3, 5, 6, 7.

① Truth table for D flip flop

| D | Q | Q' |
|---|---|----|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

② Excitation table for D flip flop

| P.S | N.S | D |
|-----|-----|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

③ 3 flip flops are required for 3 bit counter.


④ Synthesis table

| CBA | CB'A' | CB'A | CB'A' | D | D' | B | B' | A |
|-----|-------|------|-------|---|----|---|----|---|
| 0 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

⑤ State Diagram

```

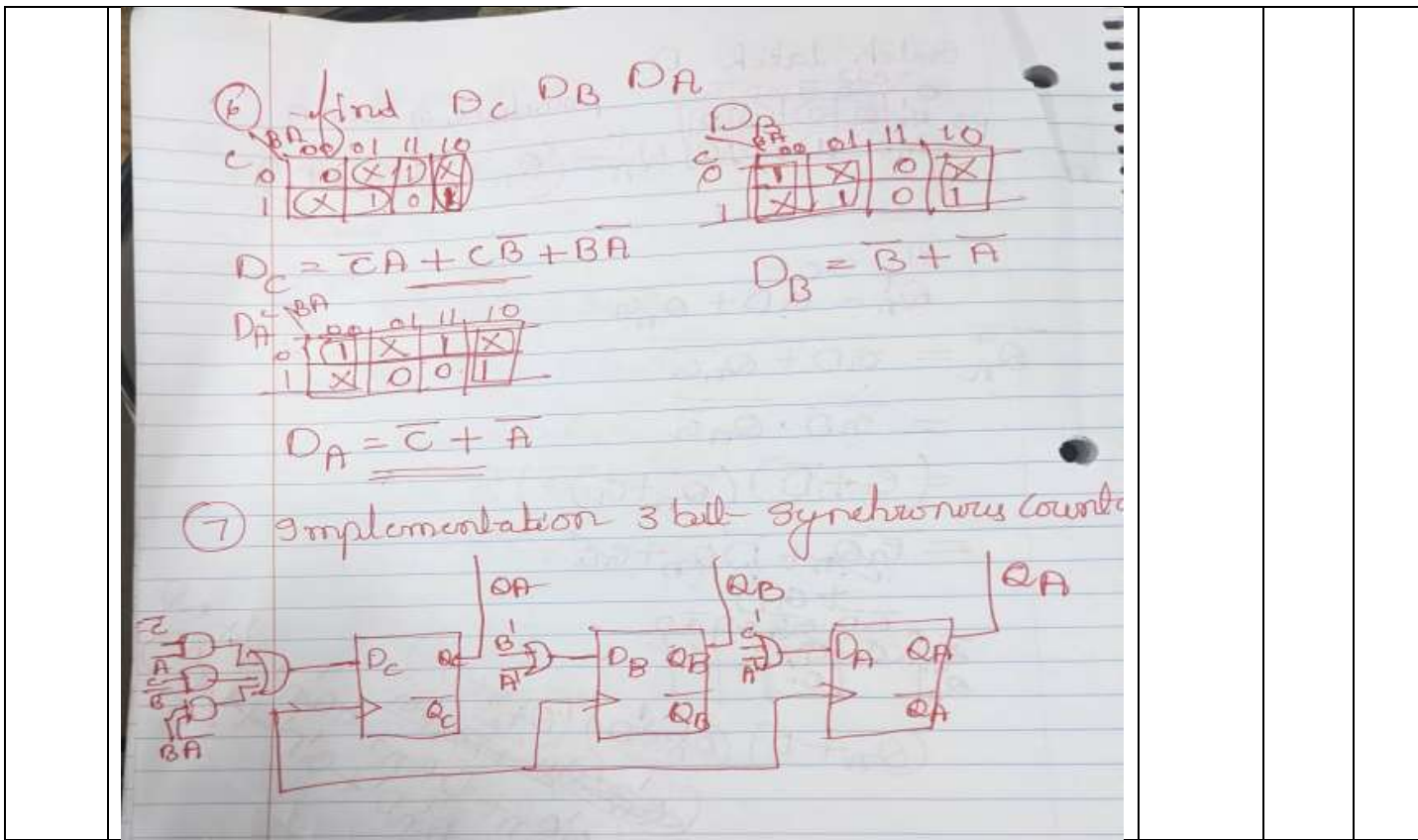    graph TD
      000((000)) --> 011((011))
      011 --> 101((101))
      101 --> 110((110))
      110 --> 011
      011 --> 000
  
```



| Course Outcomes | | Modul es cover ed | P O 1 | P O 2 | P O 3 | P O 4 | P O 5 | P O 6 | | P O 7 | P O 8 | P O 9 | P O 10 | P O 11 | P O 12 | P S O 1 | P S O 2 | P S O 3 | P S O 4 |
|-----------------|---|----------------------------|-------------|-------------|-------------|-------------|-------------|-------------|---|-------------|-------------|-------------|--------------|--------------|--------------|------------------|------------------|------------------|------------------|
| CO1 | Design and analyze application of analog circuits using photo devices, timer IC, power supply and regulator IC and op-amp. | 1 | 2 | 3 | 3 | 2 | 2 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 2 | 0 | 2 | 2 |
| CO2 | Explain the basic principles of A/D and D/A conversion circuits and develop the same | 1 | 2 | 2 | 3 | 2 | 2 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 2 | 0 | 2 | 2 |
| CO3 | Simplify digital circuits using Karnaugh Map, and Quine-McClusky Methods | 2 | 2 | 3 | 3 | 3 | 2 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 2 | 0 | 2 | 2 |
| CO4 | Explain Gates and flip flops and make us in designing different data processing circuits, registers and counters and compare the types. | 3, 4, 5 | 2 | 3 | 3 | 3 | 3 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 2 | 0 | 2 | 2 |
| CO5 | Develop simple HDL programs | 3, 4, 5 | 1 | 1 | 1 | 1 | 3 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 2 | 0 | 2 | 1 |

| COGNITIVE LEVEL | REVISED BLOOMS TAXONOMY KEYWORDS |
|-----------------|---|
| L1 | List, define, tell, describe, identify, show, label, collect, examine, tabulate, quote, name, who, when, where, etc. |
| L2 | summarize, describe, interpret, contrast, predict, associate, distinguish, estimate, differentiate, discuss, extend |
| L3 | Apply, demonstrate, calculate, complete, illustrate, show, solve, examine, modify, relate, change, classify, experiment, discover. |
| L4 | Analyze, separate, order, explain, connect, classify, arrange, divide, compare, select, explain, infer. |
| L5 | Assess, decide, rank, grade, test, measure, recommend, convince, select, judge, explain, discriminate, support, conclude, compare, summarize. |

| PROGRAM OUTCOMES (PO), PROGRAM SPECIFIC OUTCOMES (PSO) | | | | CORRELATION LEVELS | |
|--|--|------|--------------------------------|--------------------|----------------------|
| PO1 | Engineering knowledge | PO7 | Environment and sustainability | 0 | No Correlation |
| PO2 | Problem analysis | PO8 | Ethics | 1 | Slight/Low |
| PO3 | Design/development of solutions | PO9 | Individual and team work | 2 | Moderate/ Medium |
| PO4 | Conduct investigations of complex problems | PO10 | Communication | 3 | Substantial/ High |
| PO5 | Modern tool usage | PO11 | Project management and finance | | |
| PO6 | The Engineer and society | PO12 | Life-long learning | | |
| PSO1 | Develop applications using different stacks of web and programming technologies | | | | |
| PSO2 | Design and develop secure, parallel, distributed, networked, and digital systems | | | | |
| PSO3 | Apply software engineering methods to design, develop, test and manage software systems. | | | | |
| PSO4 | Develop intelligent applications for business and industry | | | | |
