



USN <input type="text"/>									
<b>Internal Assessment Test 2 – January 2022</b>									
Sub:	Analog and Digital Electronics				Sub Code:	18CS33	Branch:	ISE	
Date:	25/1/2022	Duration:	90 min's	Max Marks:	50	Sem/Sec:	III / A, B and C		
<b><u>Answer any FIVE FULL Questions</u></b>							MARKS	CO	RBT
1	Explain the structure of VHDL Program. Write VHDL Code for 4-bit parallel adder.					10	CO5	L2	
2	Construct SR latch using NOR gate. Show how SR latch can be used for switch de-bouncing.					10	CO4	L3	
3	a. With an example, explain the syntax of conditional signal assignment statement in VHDL.					4	CO5	L2	
	b. Construct binary counter which counts from 000 to 111 using three T flip flops.					6	CO4	L3	
4	Draw the logic diagram of Master Slave JK flip flop using NAND gates and explain the working with suitable timing diagram					10	CO4	L2	
5	Derive the characteristics equations for D, T, SR, JK FLIP-FLOPS					10	CO4	L1	
6	With neat sketch, explain the working principle of SISO & PIPO shift register.					10	CO4	L2	

Faculty Signature

CCI Signature

HOD Signature

USN <input type="text"/>									
<b>Internal Assessment Test 2 – January 2022</b>									
Sub:	Analog and Digital Electronics				Sub Code:	18CS33	Branch:	ISE	
Date:	25/1/2022	Duration:	90 min's	Max Marks:	50	Sem/Sec:	III / A, B and C		
<b><u>Answer any FIVE FULL Questions</u></b>							MARKS	CO	RBT
1	Explain the structure of VHDL Program. Write VHDL Code for 4-bit parallel adder.					10	CO5	L2	
2	Construct SR latch using NOR gate. Show how SR latch can be used for switch de-bouncing.					10	CO4	L3	
3	a. With an example, explain the syntax of conditional signal assignment statement in VHDL.					4	CO5	L2	
	b. Construct binary counter which counts from 000 to 111 using three T flip flops.					6	CO4	L3	
4	Draw the logic diagram of Master Slave JK flip flop using NAND gates and explain the working with suitable timing diagram					10	CO4	L2	
5	Derive the characteristics equations for D, T, SR, JK FLIP-FLOPS					10	CO4	L1	
6	With neat sketch, explain the working principle of SISO & PIPO shift register.					10	CO4	L2	

Faculty Signature

CCI Signature

HOD Signature

USN

**Internal Assessment Test 2 – January 2022**


Sub:	Analog and Digital Electronics	Sub Code:	18CS33	Branch:	ISE	
Date:	25/1/2022	Duration:	90 min's	Max Marks:	50	
					Sem/Sec:	III / A, B and C
						OBE

**Answer any FIVE FULL Questions**

		MARKS	CO	RBT			
1	<p>Explain the structure of VHDL Program. Write VHDL Code for 4-bit parallel adder..</p> <p><b>Solution:</b></p> <p>When we describe a system in VHDL, we must specify an entity and an architecture at the top level, and also specify an entity and architecture for each of the component modules that are part of the system. Each entity declaration includes a list of interface signals that can be used to connect to other modules or to the outside world. We will use entity declarations of the form:</p> <p><b>entity</b> entity-name <b>is</b> [port(interface-signal-declaration);] <b>end</b> [entity] [entity-name];</p> <p>The items enclosed in square brackets are optional. The interface-signal-declaration normally has the following form:  list-of-interface-signals: mode type [: _ initial-value]  {; list-of-interface-signals: mode type [: _ initial-value]};</p> <div style="border: 1px solid black; padding: 10px; text-align: center; margin: 10px 0;"> <p><b>Entity Architecture</b></p> <table style="margin: auto;"> <tr> <td style="border: 1px solid black; padding: 5px;">Entity Architecture Module 1</td> <td style="padding: 0 10px;">...</td> <td style="border: 1px solid black; padding: 5px;">Entity Architecture Module N</td> </tr> </table> <p><i>VHDL Program Structure</i></p> </div> <pre> entity Adder4 is   port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs         S: out bit_vector(3 downto 0); Co: out bit); -- Outputs end Adder4;  architecture Structure of Adder4 is   component FullAdder     port (X, Y, Cin: in bit; -- Inputs           Cout, Sum: out bit); -- Outputs   end component;   signal C: bit_vector(3 downto 1);   begin -- instantiate four copies of the FullAdder     FA0: FullAdder port map (A(0), B(0), Ci, C(1), S(0));     FA1: FullAdder port map (A(1), B(1), C(1), C(2), S(1));     FA2: FullAdder port map (A(2), B(2), C(2), C(3), S(2));     FA3: FullAdder port map (A(3), B(3), C(3), Co, S(3));   end Structure; </pre>	Entity Architecture Module 1	...	Entity Architecture Module N	10	CO5	L2
Entity Architecture Module 1	...	Entity Architecture Module N					

Construct SR latch using NOR gate. Show how SR latch can be used for switch debouncing.

**Solution:**

 

From this, the flip-flop has two inputs: R and S and two outputs: Q and  $\bar{Q}$  and it is clear from the representation that the outputs are complementary to each other. Let us try to analyze the different possibilities of inputs and their corresponding outputs.

An important point to note here is that for a NOR gate, Logic '1' is a dominating input and if any one of its input is Logic '1' (HIGH), then the output is Logic '0' (LOW), irrespective of the other input. With this in mind, let us analyze the above circuit.

**Case 1: R = 0 and S = 0**

In the first case, the inputs of both the NOR gates are Logic '0'. As neither of them are dominating inputs, they have no effect on the output. So, the output retains their previous states i.e., there is no change in the output. This condition is called as Hold Condition or No Change Condition.

**Case 2: R = 0 and S = 1**

In this case, the 'S' input is 1, which means the output of the NOR Gate B will become 0. As a result, both the inputs of NOR Gate A become 0 and hence the output of the NOR Gate A and thus the value of Q is 1 (HIGH). As '1' at input S makes the output to switch to one of its stable states and sets it to '1', the S input is known as SET input.


**Case 3: R = 1 and S = 0**

In this case, the 'R' input is 1, which means the output of the NOR Gate A will become 0 i.e., Q is 0 (LOW). As a result, both the inputs of NOR Gate B become 0 and hence the output of the NOR Gate B is 1 (HIGH). As '1' at input R makes the output to switch to one of its stable states and resets it to '0', the R input is known as RESET input.

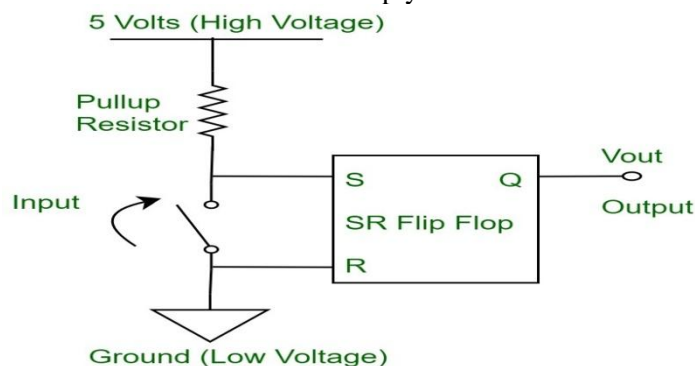**Case 4: R = 1 and S = 1**

This input condition is forbidden as it forces outputs of both NOR Gates to become 0, which is a violation of complementary outputs. Even if this input condition is applied, if the next inputs become R = 0 and S = 0 (hold condition), then it causes a 'race condition' between the NOR Gates, which causes an unstable or unpredictable state at the output.

Hence, the input condition R = 1 and S = 1 is simply not used.



#### Switch Debouncing

Use of S-R Flip Flop Latch circuit. The circuit when introduced in the output part of the switch, it will retain the voltage level of the input as the output state. Thus, latching to the input, when change in state is introduced. This method is useful, but adds to the bulkiness of the simple circuit.

3 a. With an example, explain the syntax of conditional signal assignment statement in VHDL.

```


signal_name <= expression_1 when condition_1 else
                expression_2 when condition_2 else
                expression_3 ;
architecture COND of BRANCH is
begin
    Z <= A when X > 5 else
        B when X < 5 else
        C;
end COND;

```

4 CO5 L2

b. Construct binary counter which counts from 000 to 111 using three T flip flops.

6 CO4 L3

 

Binary Counter

Present State			Next State			Flip-Flop Inputs		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	T <sub>C</sub>	T <sub>B</sub>	T <sub>A</sub>
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

		C	
BA		0	1
00	0	0	
01	0	0	
11	1	1	
10	0	0	

*T<sub>C</sub>*

		C	
BA		0	1
00	0	0	
01	1	1	
11	1	1	
10	0	0	

*T<sub>B</sub>*


Truth Table and K Map





TC, TB, and TA are now derived from the table as functions of C, B, and A. By inspection, T<sub>A</sub> = 1. Using K-maps for T<sub>C</sub> and T<sub>B</sub>, we will get T<sub>C</sub> = BA and T<sub>B</sub> = A.

4 Draw the logic diagram of Master Slave JK flip flop using NAND gates and explain the working with suitable timing diagram

 10 CO4 L2

**Solution:**



Case	Inputs			Outputs		Remark
	CLK	J	K	$Q_{n+1}$	$\bar{Q}_{n+1}$	
I	x	0	0	$Q_n$	$\bar{Q}_n$	No change
II		0	0	$Q_n$	$\bar{Q}_n$	No change
III		0	1	0	1	Reset
IV		1	0	1	0	Set
V		1	1	$\bar{Q}_n$	$Q_n$	Toggle

Truth table of Master slave JK FF

When the clock pulse is true, the slave flip flop will be in the isolated state, and the system's state may be affected by the J and K inputs. The "slave" remains isolated until the CP is 1. When the CP set to 0, the master flip-flop passes the information to the slave flip flop to obtain the output.


The master flip flop responds first from the slave because the master flip flop is the positive level trigger, and the slave flip flop is the negative level trigger.

The output  $Q'=1$  of the master flip flop is passed to the slave flip flop as an input K when the input J set to 0 and K set to 1. The clock forces the slave flip flop to work as reset, and then the slave copies the master flip flop.

When  $J=1$ , and  $K=0$ , the output  $Q=1$  is passed to the J input of the slave. The clock's negative transition sets the slave and copies the master.

The master flip flop toggles on the clock's positive transition when the inputs J and K set to 1. At that time, the slave flip flop toggles on the clock's negative transition.

 The flip flop will be disabled, and Q remains unchanged when both the inputs of the JK flip flop set to 0




### SR Flip flop

1. Truth Table for SR flip-flop


S	R	$Q_n$	$Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1		invalid
1	1		invalid

4. K-map Simplification

 

Excitation Table for SR flip-flop

Outputs		Inputs	
$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

 


(a) SR flip-flop

### D-Flipflop


1. Truth Table for D Flip-Flop

Input	Outputs	
D	$Q_n$	$Q_{n+1}$
0	0	0
0	1	0
1	0	1
1	1	1

 

Excitation Table for D Flip Flop

Outputs		Input
$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

 


(b) D flip-flop

### T-flipflop

Truth Table for T Flip Flop


Input	Outputs	
T	$Q_n$	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

4. K-map Simplification

 


Excitation Table for T Flip Flop

Outputs		Input
$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

 

(d) T flip-flop


### K-map Simplification

 

### JK-Flipflop

Truth Table for JK Flip-Flop


Inputs		Outputs	
J	K	$Q_n$	$Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

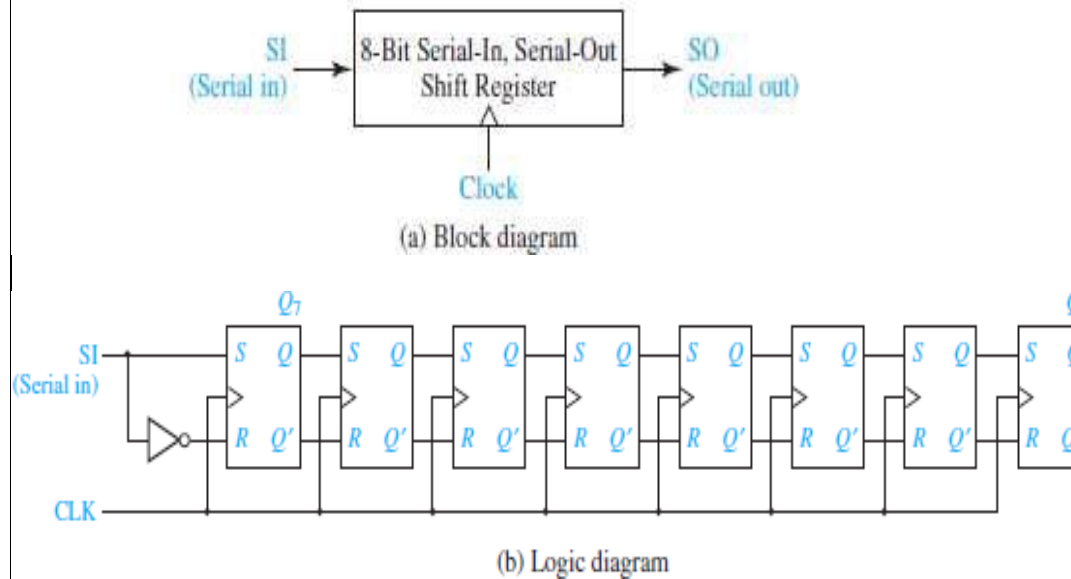**Solution:****8-Bit Serial-in, Serial-out Shift Register**

The following Figure

illustrates an 8-bit serial-in, serial-out shift register. Serial in means that data is shifted into the first flipflop one bit at a time, and the flip-flops cannot be loaded in parallel. Serial out means that data can only be read out of the last flip-flop and the outputs from the other flip-flops are not connected to terminals of the integrated circuit.

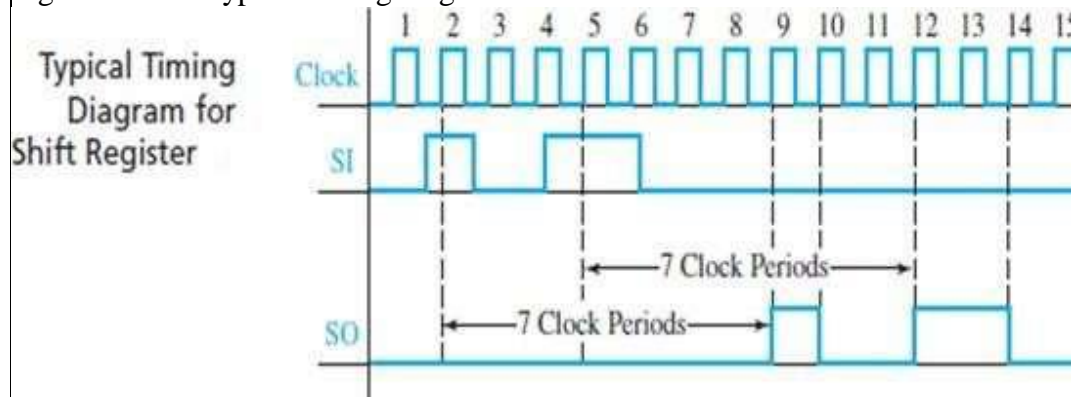The inputs to the first flip-flop are  $S = SI$  and  $R = SI'$ . Thus, if  $SI = 1$ , a 1 is shifted into the register when it is clocked, and if  $SI = 0$ , a 0 is shifted in. The following Figure shows a typical timing diagram.





The following Figure (a) shows a 4-bit parallel-in, parallel-out shift register.

Parallel-in implies that all four bits can be loaded at the same time, and parallel-out implies that all bits can be read out at the same time. The shift register has two control inputs, shift enable ( $Sh$ ) and load enable ( $L$ ). If  $Sh = 1$  (and  $L = 1$  or  $L = 0$ ), clocking the register causes the serial input ( $SI$ ) to be shifted into the first flip-flop, while the data in flip-flops  $Q_3, Q_2$ , and  $Q_1$  are shifted right. If  $Sh = 0$  and  $L = 1$ , clocking the shift register will cause the four data inputs ( $D_3, D_2, D_1, D_0$ ) to be loaded in parallel into the flip-flops. If  $Sh = L = 0$ ,



clocking the register causes no change of state.

## PIPO shift register

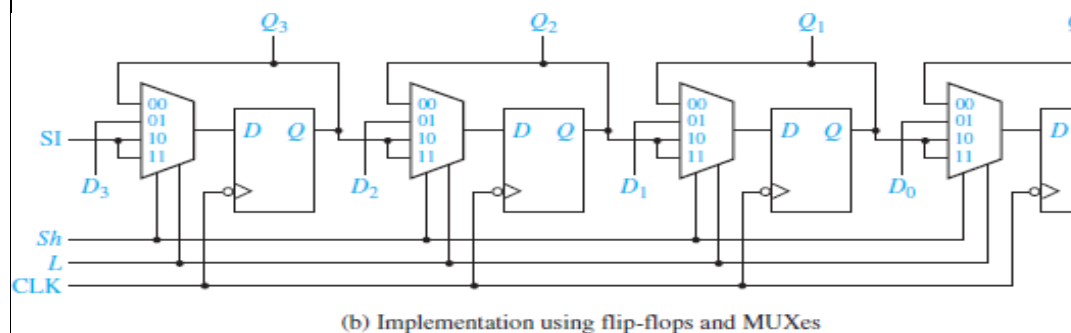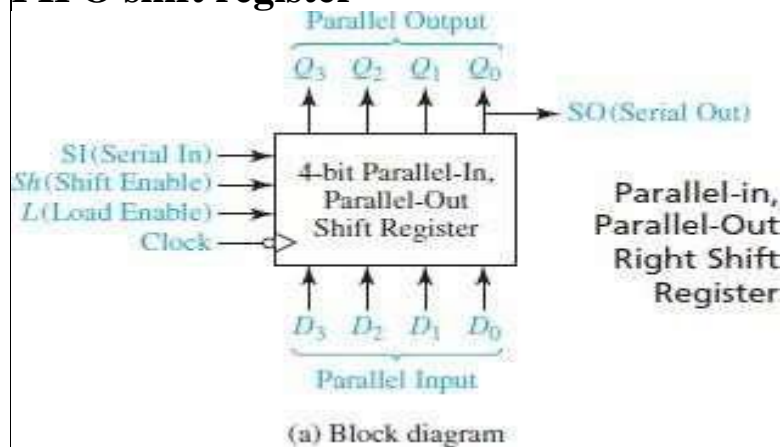

The following Table summarizes the operation of this shift register. All state changes occur immediately following the falling edge of the clock.

Shift Register Operation

Inputs		Next State				Action
Sh (Shift)	L (Load)	$Q_3^+$	$Q_2^+$	$Q_1^+$	$Q_0^+$	
0	0	$Q_3$	$Q_2$	$Q_1$	$Q_0$	No change
0	1	$D_3$	$D_2$	$D_1$	$D_0$	Load
1	X	SI	$Q_3$	$Q_2$	$Q_1$	Right shift

The shift register can be implemented using MUXes and D flip-flops, as shown in the above Figure (b).

For the first flip-flop, when  $Sh = L = 0$ , the flip-flop  $Q_3$  output is selected by the MUX, so  $Q_3^+ = Q_3$  and

no state change occurs. When  $Sh = 0$  and  $L = 1$ , the data input  $D_3$  is selected and loaded into the flip-flop.

When  $Sh = 1$  and  $L = 0$  or  $1$ ,  $SI$  is selected and loaded into the flip-flop. The second MUX selects  $Q_2$ ,

$D_2$ , or  $Q_3$ , etc. **The next-state equations for the flip-flops are**

$$Q_3^+ = Sh' \cdot L' \cdot Q_3 + Sh' \cdot L \cdot D_3 + Sh \cdot SI$$

$$Q_2^+ = Sh' \cdot L' \cdot Q_2 + Sh' \cdot L \cdot D_2 + Sh \cdot Q_3$$

$$Q_1^+ = Sh' \cdot L' \cdot Q_1 + Sh' \cdot L \cdot D_1 + Sh \cdot Q_2$$

$$Q_0^+ = Sh' \cdot L' \cdot Q_0 + Sh' \cdot L \cdot D_0 + Sh \cdot Q_1$$