

--	--	--	--	--	--	--	--	--	--

Internal Assessment Test 1– Dec 2021

Sub:	POWER ELECTRONICS AND INSTRUMENTATION				Sub Code:	18EC36	Branch:	ECE		
Date:	20-12-2021	Duration:	1.5 hour	Max Marks:	50	Sem/Sec:	3 rd sem /A,B,C,D		OBE	
<u>ANSWER ANY 5 FULL QUESTIONS</u>								MARKS	CO	RBT
1	With necessary sketches, explain the static V-I characteristics of SCR and its operation. Show the effect of various gate currents.						10	CO1	L2	
2	What is Commutation? Differentiate between Natural and Forced Commutation. Discuss in detail Class A commutation.						10	CO1	L1	
3	Describe the operation of UJT with neat sketches. Explain how a UJT firing circuit for an SCR works.						10	CO1	L2	
4	Explain the working of a single phase half wave controlled rectifier for RL load with necessary sketches. Explain the effect of freewheeling diode.						10	CO2	L2	
5	A step down chopper has a resistive load of $R = 15 \text{ ohm}$ and input voltage $E_{dc} = 200\text{V}$. When the chopper remains ON, its voltage drop is 2.5 V . The chopper frequency is 1 KHz . If the duty cycle is 50% , determine: (a) Average output voltage (b) RMS Output voltage (c) Chopper Efficiency						10	CO2	L3	
6 a	Explain the working of a single phase full wave controlled rectifier for resistive load with necessary sketches. Also derive the expression for RMS load voltage.						5	CO2	L2	
6 b	If the half wave controlled rectifier has a purely resistive load of R and delay angle is $\alpha = \pi/3$, Determine:- (a) Rectification Efficiency (b) Ripple factor						5	CO2	L3	
7a	Explain the principle of operation of Step Down Chopper (Buck Converter) with necessary circuit diagram and wave forms.						5	CO2	L2	
7b	Describe the classification of choppers						5	CO2	L1	
8a	Explain the working of a Resistance firing circuit with necessary circuit diagram and waveforms.						5	CO1	L2	
8b	What are the different Turn ON methods of a Thyristor?						5	CO1	L1	


29/12/21

Power Electronics (18EC36) ①

Internal Assessment test-1. (Dec 2021)

Answer Key.

Q.1. Static VI characteristics of SCR.

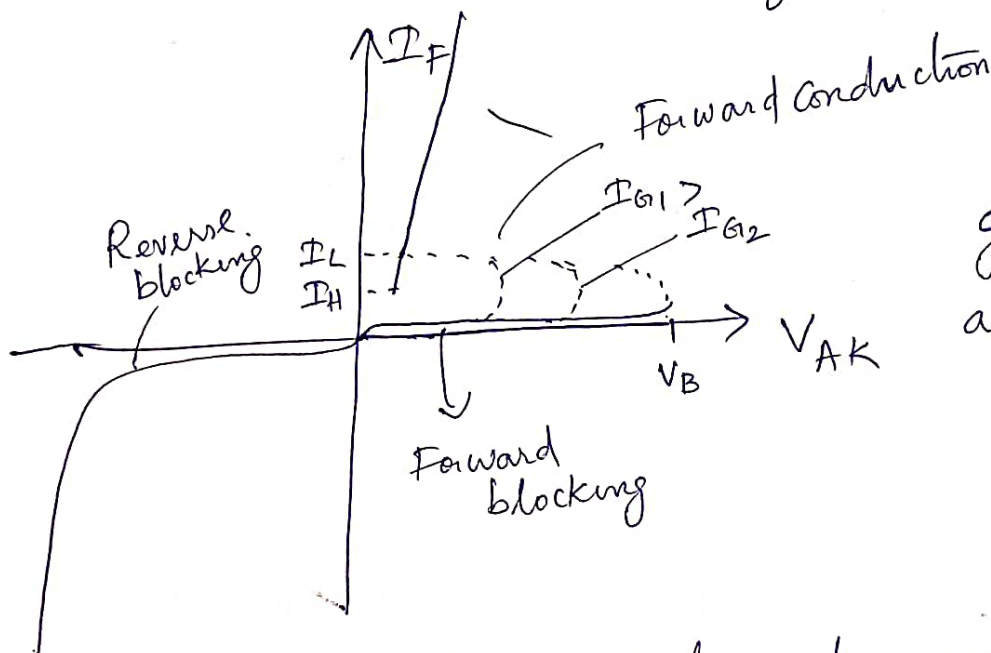

graph with all marking (5m)

explanation and definition of I_L & I_H (5m)

10m.

Q.2. Commutation is the process of turning off an SCR (1m)

Natural and Forced Commutation (4m)

Class A commutation working (3m) +
Waveform (2m)

10m.


Q.3 UJT operation with v-I graph (5m)

UJT firing circuit (2m) + working (3m)

10m.

(2)

Q.4

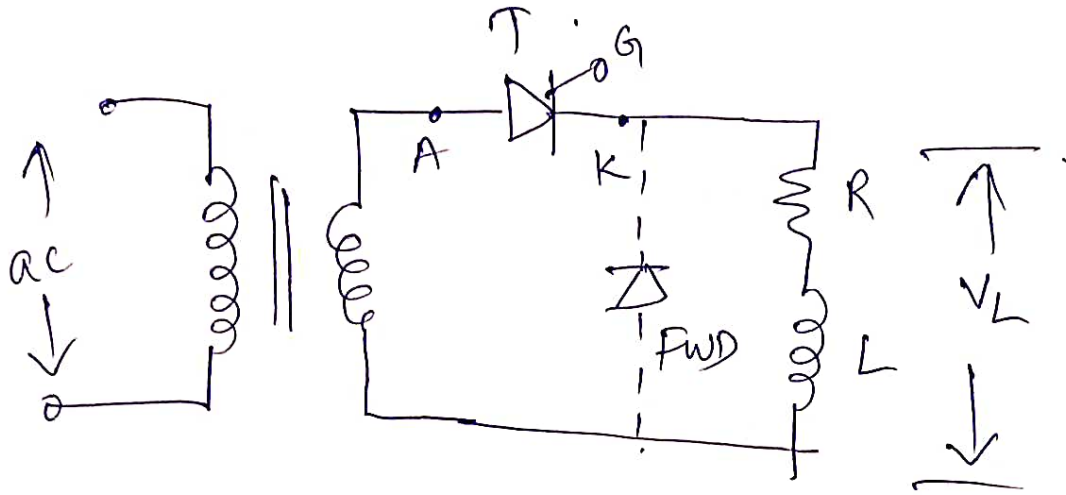

Current + waveforms (3m)

Explanation (3m)

Free wheeling diode working + waveform (4m)

10m

Q.5

$$R = 15 \quad E_{dc} = 200V \quad E_{drop} = 2.5V$$

(a) Average output voltage $E_o = \alpha (E_{dc} - E_{drop})$ (1m)

$$E_o = \underline{98.75V} \quad (2m)$$

(b) RMS output voltage $E_{o,rms} = \sqrt{\alpha} (E_{dc} - E_{drop})$ (1m)


$$E_{o,rms} = \underline{139.653V} \quad (2m)$$

(c) chopper efficiency $\eta = \frac{P_o}{P_i}$ derivation (2m)

$$\eta = \underline{98.74\%} \quad (2m)$$

10m

Q6a

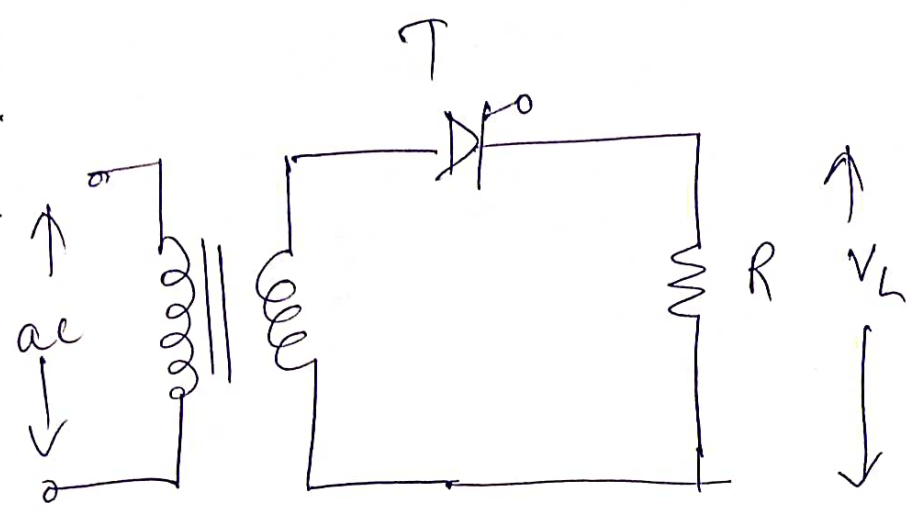

Current diagram (~~2m~~) + Working and waveforms (~~2m~~) (3m)

Expression for RMS load voltage (0.2m)

$$E_{rms} = \frac{1}{2\pi} \int_0^{\pi} (E_m \sin \omega t)^2 d\omega t$$

0.5m ~~1.0m~~

$$E_{rms} = E_m \left[\frac{\pi - \alpha}{4\pi} + \frac{\sin 2\alpha}{8\pi} \right]^{1/2}$$

Q6b $\alpha = \frac{\pi}{3}$

Rectification efficiency $\eta = \frac{P_{dc}}{P_{ac}} = \frac{(0.239 E_m)^2}{(0.485 E_m)^2}$


$= 24.25\%$ (3m)

Ripple factor (γ) = $\sqrt{\left(\frac{E_{rm}}{I_{dc}}\right)^2 - 1} = 1.77$

(2m)

0.5m

Q.7a Step down chopper (Buck Converter).

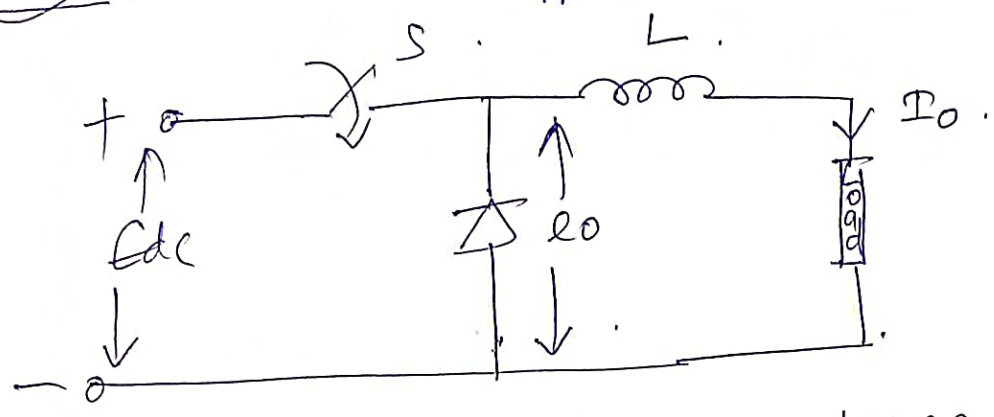

Current diagram + waveforms (3M)

Explanation and ~~the~~ expression $E_o = \alpha E_{dc}$ (2M)

5M

Q7b classification of chopper

- Line commutated
- AC link chopper.
- DC chopper.

Step up/down chopper (1M)

class A, B, C, D, E (1M)

First, Two, four quadrant chopper (2M)


According to commutation (1M)

5M

5

Q
8a

R-firing circuit

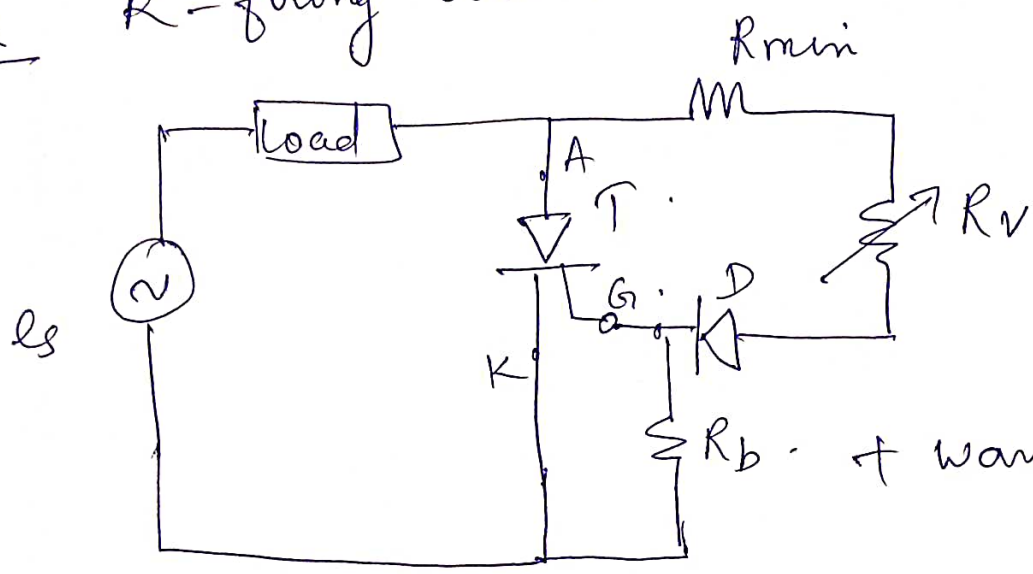

Working (2m)

+ waveforms (3m)

5m

8b Turn ON methods . (Explanation in one line)

Forward voltage triggering

Thermal triggering

Radiation Triggering

5m

$\frac{dv}{dt}$ Triggering

Gate Triggering

- DC
- AC
- pulse