
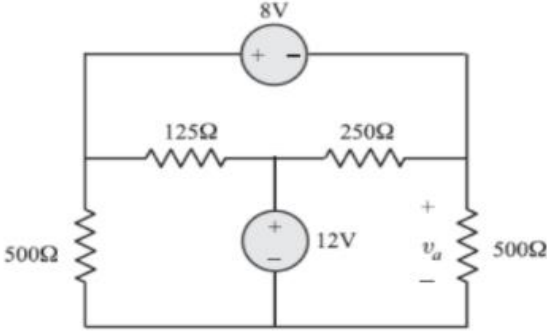
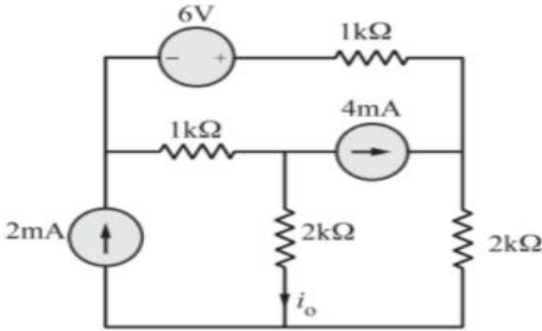
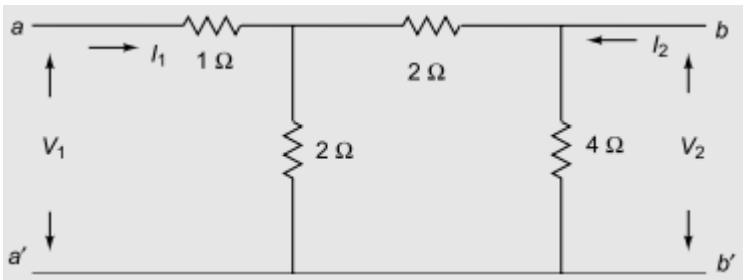
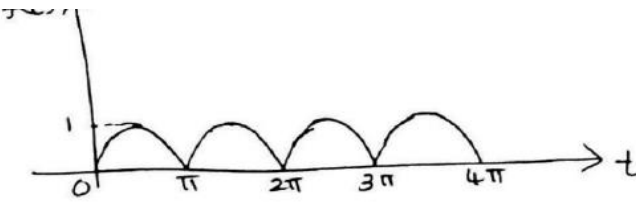
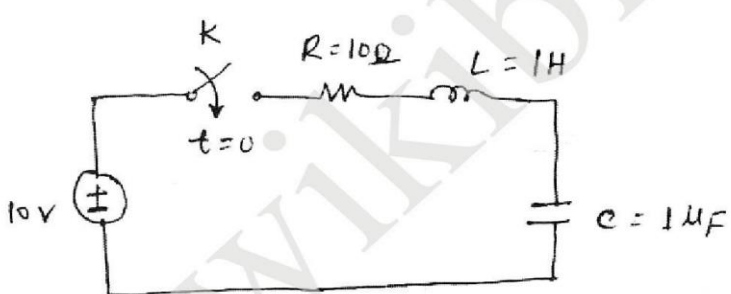
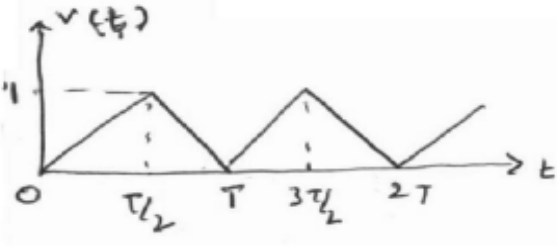
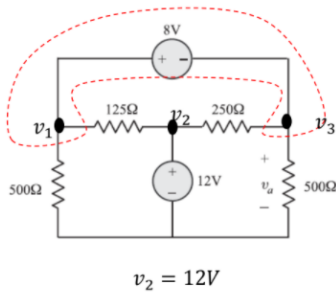


Internal Assessment Test II – Jan. 2022


Sub:	Network Theory				Sub Code:	18EC32	Branch:	ECE	
Date:	24-01-2022	Duration:	90 Minutes	Max Marks:	50	Sem / Sec:	3/A,B,C,D		OBE
Answer any FIVE FULL Questions							MARKS	CO	RBT
1	Determine V_a in the given circuit (Fig.1).					[10]	CO1	L3	
 <p>Fig.1</p>									
2	Determine i_o in the given circuit (Fig.2).					[10]	CO1	L3	
 <p>Fig.2</p>									
3	For the network shown in Fig.3, obtain 'z' and 'y' parameters					[10]	CO5	L3	
 <p>Fig. 3</p>									
4	(a).Obtain the relationship between 'y' and 'h' parameters					[5]	CO5	L2	
	(b).Obtain the reciprocity condition for ABCD parameters.					[5]	CO5	L2	

5	<p>Derive the expression for the resonant frequency of the circuit where R_L resistance in inductor branch and R_C resistance in the capacitor branch. Also show that the circuit will resonate at all frequencies if $R_L = R_C$.</p>	[10]	CO5	L2
6	<p>a. Obtain the Laplace transform of (i). Unit step function, (ii). Unit impulse function. b. Find the Laplace transform of the periodic function as shown in the Fig.6</p>  <p style="text-align: center;">Fig.6</p>	[4] [6]	CO4 CO4	L2 L3
7	<p>Determine the loop current in the Fig.7 using Laplace transform when switch is closed ($t = 0$).</p>  <p style="text-align: center;">Fig. 7</p>	[10]	CO4	L3
8	<p>a. State and prove initial and final value theorem. b. Find the Laplace transform of the periodic function as shown in the Fig. 8.</p>  <p style="text-align: center;">Fig.8</p>	[4] [6]	CO4 CO4	L2 L3

Ques 1. Find v_o in the circuit shown

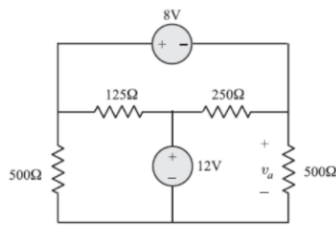

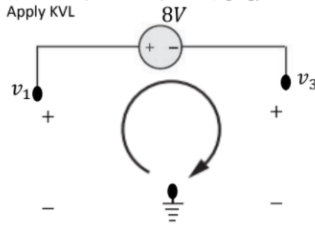1) Inside Supernode equation (v_1, v_3)
Apply KVL



$$v_1 - 8 - v_3 = 0 \quad (\text{By KVL})$$

$$v_1 - v_3 = 8$$

2) Here v_1 and v_3 are forming super-node and $v_2 = 12V$ is forming is just an independent node

Supernode equation (v_1, v_3)

$$\left(\frac{v_1 - v_2}{125}\right) + \frac{v_1 - 0}{500} + \frac{v_3 - v_2}{250} + \frac{v_3 - 0}{500} = 0$$

$$\left(\frac{v_1 - 12}{5}\right) + \frac{v_1 - 0}{20} + \frac{v_3 - 12}{10} + \frac{v_3 - 0}{20} = 0$$

$$v_1 \left(\frac{1}{5} + \frac{1}{20}\right) + v_3 \left(\frac{1}{10} + \frac{1}{20}\right) = \frac{12}{5} + \frac{12}{10}$$

$$v_1 \left(\frac{5}{20}\right) + v_3 \left(\frac{3}{20}\right) = \frac{36}{10}$$



$$\Rightarrow v_1 (0.25) + v_3 (0.15) = 3.6$$

solving

$$v_1 = 12V$$

$$v_3 = v_o = 4V$$

Ques 2. Find i_o in the circuit shown

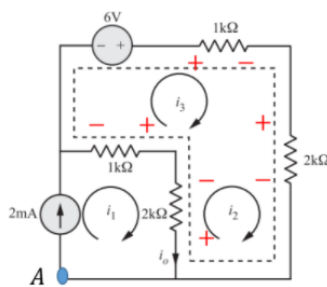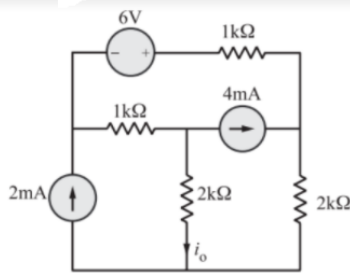

mesh1

KCL at node A

$$2m - i_1 = 0 \quad \Rightarrow i_1 = 2mA$$

Supermesh (mesh2 and mesh3)

$$6 - 1k(i_3) - 2ki_2 - 2k(i_2 - i_1) - 1k(i_3 - i_1) = 0$$

$$6 - 1k(i_3) - 2ki_2 - 2k(i_2 - 2m) - 1k(i_3 - 2m) = 0$$

$$12 - 4ki_2 - 2ki_3 = 0 \quad \Rightarrow 2i_2 + i_3 = 6m$$

Solving

$$i_2 = \frac{10}{3} mA$$

KCL at node D

$$-i_o + (i_1 - i_2) = 0 \Rightarrow -i_o = 2m - \frac{10}{3}m \Rightarrow i_o = \frac{-4}{3}m$$

KCL at node B

$$-i_3 + i_2 - 4m = 0$$

$$-i_3 + i_2 = 4m$$

$$-i_3 + \frac{10}{3}m = 4m$$

$$i_3 = \frac{2}{3} mA$$


KCL at node C

$$4m + i_o - (i_1 - i_3) = 0$$

$$4m + i_o - (2m - \frac{2}{3}m) = 0$$

$$\Rightarrow i_o = \frac{-4}{3}m$$

Q.NO3:

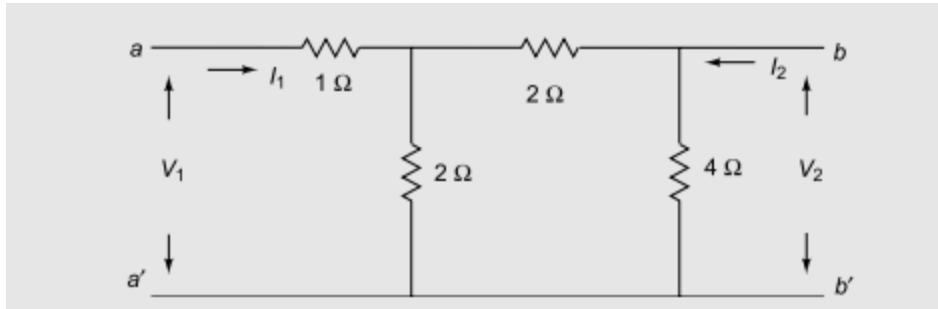

Solution $Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$

When $b-b'$ is short circuited, $V_2 = 0$ and the network looks as shown in Fig. 16.8(a).

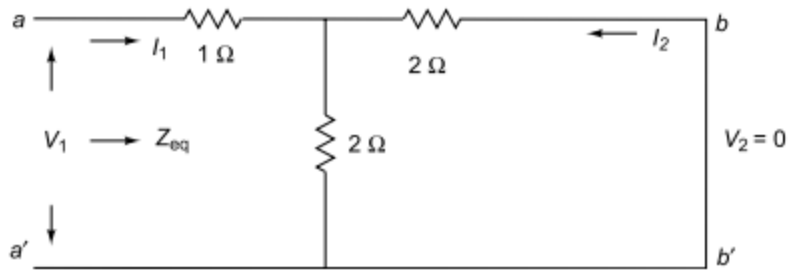


Fig. 16.8 (a)

$$V_1 = I_1 Z_{eq}$$

$$Z_{eq} = 2 \Omega$$

$$\therefore V_1 = I_1 \cdot 2$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{1}{2} \text{ U}$$


$$Y_{21} = \left. \frac{I_2}{V_2} \right|_{V_2=0}$$

With port $b-b'$ short circuited, $-I_2 = I_1 \times \frac{2}{4} = \frac{I_1}{2}$

$$\therefore -I_2 = \frac{V_1}{4}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -\frac{1}{4} \text{ U}$$

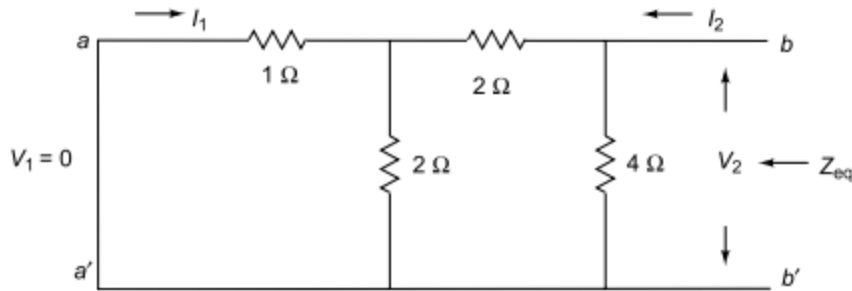Similarly, when port $a-a'$ is short circuited, $V_1 = 0$ and the network looks as shown in Fig. 16.8 (b).



$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

$$V_2 = I_2 Z_{\text{eq}}$$

where Z_{eq} is the equivalent impedance as viewed from $b-b'$.

$$Z_{\text{eq}} = \frac{8}{5} \Omega$$

$$V_2 = I_2 \times \frac{8}{5}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{5}{8} \text{ U}$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

With $a-a'$ short circuited, $-I_1 = \frac{2}{5} I_2$

Since $I_2 = \frac{5V_2}{8}$

$$-I_1 = \frac{2}{5} \times \frac{5}{8} V_2 = \frac{V_2}{4}$$

$$\therefore Y_{12} = \frac{I_1}{V_2} = -\frac{1}{4} \text{ U}$$

The describing equations in terms of the admittance parameters are

$$I_1 = 0.5 V_1 - 0.25 V_2$$

$$I_2 = -0.25 V_1 + 0.625 V_2$$

Ques 4: a)

Eqⁿ for h^0 parameter:

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

from (1)

$$I_1 = \left(\frac{1}{h_{11}} \right) V_1 + \left(\frac{-h_{12}}{h_{11}} \right) V_2 \quad \text{--- (3)}$$

using (3) in (2) we have

$$I_2 = h_{21} \left[\frac{1}{h_{11}} V_1 + \left(\frac{-h_{12}}{h_{11}} \right) V_2 \right] + h_{22} V_2$$

$$= \left(\frac{h_{21}}{h_{11}} \right) V_1 + \left(h_{22} - \frac{h_{12} h_{21}}{h_{11}} \right) V_2$$

$$I_2 = \left(\frac{h_{21}}{h_{11}} \right) V_1 + \left(\frac{h_{22} h_{11} - h_{12} h_{21}}{h_{11}} \right) V_2 \quad \text{--- (4)}$$

Comparing (3) & (4) with (A) & (B)

$$Y_{11} = \frac{1}{h_{11}}$$

$$Y_{21} = \frac{h_{21}}{h_{11}}$$

$$Y_{12} = \frac{-h_{12}}{h_{11}}$$

$$Y_{22} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{11}}$$

Ques 4B:

④ Condition for reciprocity for ABCD parameter:

$$\text{Eq}^{\text{I}}: V_1 = AV_2 + B(-I_2) \quad \text{--- ①}$$

$$I_1 = CV_2 + D(-I_2) \quad \text{--- ②}$$

Consider fig ①, $V_1 = V_S$, $V_2 = 0$ and $I_2' = +I_2$

$$\text{Eq ①: } V_S = BI_2' \Rightarrow \frac{V_S}{I_2'} = B \quad \text{--- ③}$$

Consider fig ②, $V_2 = V_S$, $V_1 = 0$ and $I_1' = -I_2$

$$\text{Eq ①: } 0 = AV_S - BI_2 \quad \text{--- ④} \Rightarrow I_2 = \frac{AV_S}{B} \quad \text{--- ④}$$

$$\text{Eq ②: } -I_1' = CV_S - DI_2 \quad \text{--- ⑤}$$

using ④ in ⑤.

$$-I_1' = CV_S - D\left(\frac{A}{B}\right)V_S$$



$$\therefore -I_1' = \frac{BC - AD}{B} V_S$$

$$\Rightarrow \frac{V_S}{I_1'} = \frac{B}{AD - BC}$$

The n/w is said to be reciprocal if, $\frac{V_S}{I_1'} = \frac{V_S}{I_2'}$

$$\Rightarrow \frac{B}{AD - BC} = B \Rightarrow \boxed{AD - BC = 1}$$


condition

Ques 5:

Antiresonance Circuit: Case 2-> Practical Circuit for parallel resonance with RL & RC

Resonance in a Two Branch RL and RC Parallel Circuit

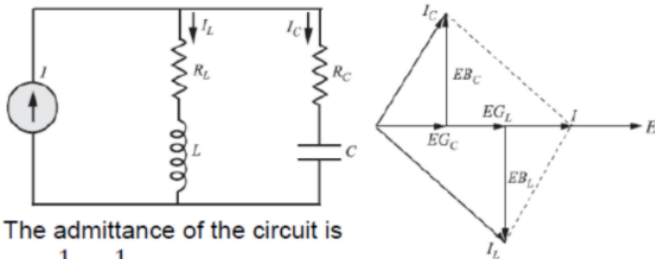Consider the two branch parallel circuit shown in Fig. A Let E be the voltage across each of the parallel circuit shown in the figure. The vector diagram at resonance is shown in Figure B.



The admittance of the circuit is

$$Y = \frac{1}{Z_L} + \frac{1}{Z_C}$$

$$Y = \frac{1}{R_L + j\omega L} + \frac{1}{R_C + \frac{j}{\omega C}} \quad (1)$$

$$Y = \frac{1}{R_L + j\omega L} \left(\frac{R_L - j\omega L}{R_L - j\omega L} \right) + \frac{1}{R_C - \frac{j}{\omega C}} \left(\frac{R_C + \frac{j}{\omega C}}{R_C + \frac{j}{\omega C}} \right)$$

At resonance, $\omega = \omega_0$

$$Y = \frac{R_L}{R_L^2 + \omega_0^2 L^2} - \frac{j\omega_0 L}{R_L^2 + \omega_0^2 L^2} + \frac{R_C}{R_C^2 + \frac{1}{\omega_0^2 C^2}} + \frac{j}{\omega_0 C} \quad (2)$$

$$Y = \frac{R_L}{R_L^2 + \omega_0^2 L^2} + \frac{R_C}{R_C^2 + \frac{1}{\omega_0^2 C^2}} - \frac{j\omega_0 L}{R_C^2 + \omega_0^2 L^2} + \frac{j}{\omega_0 C} \quad (2)$$

$$Y = G_L + G_C - j(B_L - B_C) \quad (3)$$

For resonance, $\omega = \omega_0$

$$B_L = B_C$$

$$\Rightarrow \frac{\omega_0 L}{R_L^2 + \omega_0^2 L^2} = \frac{1}{\omega_0 C} \quad (4)$$

$$\Rightarrow \frac{\omega_0 L}{R_L^2 + \omega_0^2 L^2} = \frac{\omega_0 C}{\omega_0^2 C^2 R_C^2 + 1}$$

$$\Rightarrow L(\omega_0^2 C^2 R_C^2 + 1) = (R_L^2 + \omega_0^2 L^2)C$$

$$\Rightarrow \omega_0^2 (C^2 R_C^2 L - L^2 C) = R_L^2 C - L$$


$$\Rightarrow \omega_0^2 = \frac{R_L^2 C - L}{C^2 R_C^2 L - L^2 C}$$

$$\Rightarrow \omega_0^2 = \frac{1}{LC} \frac{R_L^2 C - L}{R_C^2 C - L} \quad (4)$$

$$\Rightarrow \omega_0^2 = \frac{1}{LC} \frac{R_L^2 - \frac{L}{C}}{R_C^2 - \frac{L}{C}} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 - \frac{L}{C}}{R_C^2 - \frac{L}{C}}} \quad (5)$$

Resonance in a Two Branch RL and RC Parallel Circuit Cont...
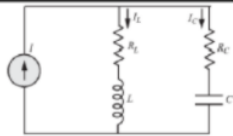
$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 - \frac{L}{C}}{R_C^2 - \frac{L}{C}}}$$



This is the expression for resonant frequency. It is to be noted that

1) resonance is not possible for certain combination of circuit elements unlike in a series circuit where resonance is always possible.

2) resonance is also possible by varying of R_L or R_C .

Consider the case where

$$R_L^2 < \frac{L}{C} < R_C^2$$

Or,

$$R_C^2 < \frac{L}{C} < R_L^2$$

In both the cases, the quantity under radical is negative and therefore resonance is not possible.

3) If, $R_L = R_C = R = \sqrt{\frac{L}{C}}$

Then, $\omega_0 = \frac{1}{\sqrt{LC}}$
as in R, L, C series circuit.

If, $R_L = R_C = R = \sqrt{\frac{L}{C}}$

Or, $R_L^2 = R_C^2 = R^2 = \frac{L}{C} = X_L X_C \quad (6)$

now, $Y = G_L + G_C - j(B_L - B_C)$

$$Y = \frac{R_L}{R_L^2 + \omega_0^2 L^2} + \frac{R_C}{R_C^2 + \frac{1}{\omega_0^2 C^2}} - \frac{j\omega_0 L}{R_L^2 + \omega_0^2 L^2} + \frac{j}{\omega_0 C}$$

$$Y = \frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} - \frac{jX_L}{X_L X_C + X_L^2} + \frac{jX_C}{X_L X_C + X_C^2}$$

$$Y = \frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} - \frac{j}{X_C + X_L} + \frac{j}{X_C + X_L}$$

$$Y = \frac{R}{R^2 + X_L^2} + \frac{R}{R^2 + X_C^2} \quad (7)$$


$$Y = \frac{R(R^2 + X_C^2) + R(R^2 + X_L^2)}{(R^2 + X_L^2)(R^2 + X_C^2)}$$

$$Y = \frac{1}{R} \quad (8) \quad \because y = 1/z$$

$$Z = R = \sqrt{\frac{L}{C}} \quad (9) \quad \text{from (6)}$$

Ques 6: a

1) Unit Step function

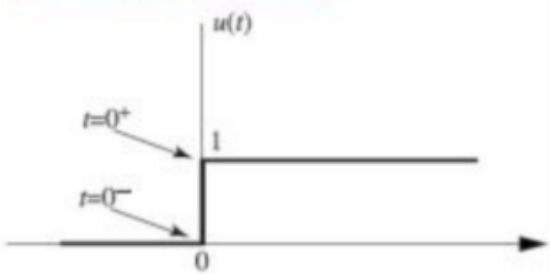

$$u(t - 0) = u(t) = \begin{cases} 1; & t \geq 0^+ \\ 0; & t \leq 0^- \end{cases}$$


Laplace transform of $u(t)$

Given $x(t) = u(t)$

$$\text{Then } L\{x(t)\} = \int_0^{\infty} x(t)e^{-st} dt = \int_0^{\infty} e^{-st} dt = \frac{1}{s}$$

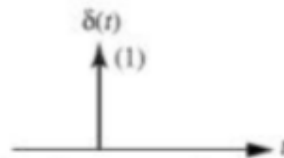2) Impulse function

$$\frac{du(t)}{dt} = \delta(t) = \begin{cases} \infty; & t = 0 \\ 0; & t \neq 0 \end{cases}$$



Note: Impulse function is only **defined at a point** in time domain, not before and after that

Area under an impulse is **unity**.

$$\int_0^{\infty} \delta(t) dt = 1$$


Laplace transform of $\delta(t)$

Given $x(t) = \delta(t)$

$$\text{Then } L\{x(t)\} = \int_0^{\infty} x(t)e^{-st} dt = \int_0^{\infty} \delta(t) e^{-st} dt = \int_0^{\infty} \delta(t) dt = 1$$

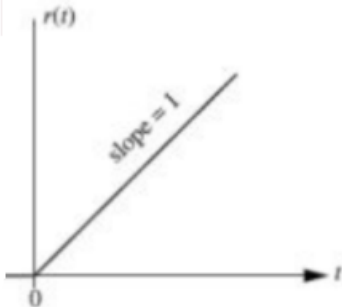3) Ramp function

$$\int u(t) dt = r(t) = \begin{cases} t; & t \geq 0 \\ 0; & t \leq 0 \end{cases}$$





Given $x(t) = r(t)$


$$\begin{aligned} \text{Then } L\{x(t)\} &= \int_0^{\infty} x(t) e^{-st} dt \\ &= \int_0^{\infty} t e^{-st} dt \\ &= \left[\frac{t e^{-st}}{s} \right]_0^{\infty} + \frac{1}{s} \int_0^{\infty} e^{-st} dt \\ &= \frac{1}{s^2} \end{aligned}$$

Ques 6B:

Solu: We know that

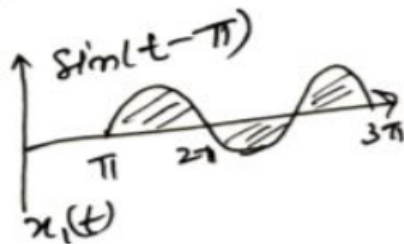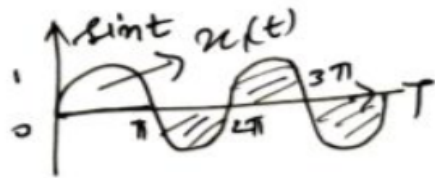
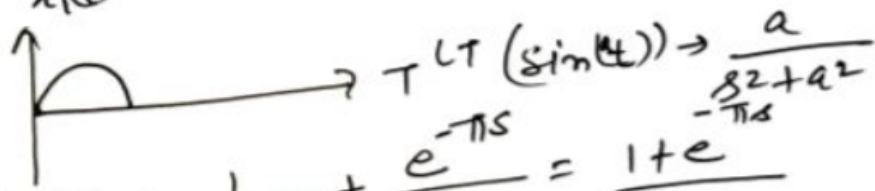
$$\begin{aligned} \oplus x(t) &= \sin t + \sin(t - \pi) \\ \text{OR} \\ &= \sin t \cdot u(t) + \sin(t - \pi) \cdot u(t) \end{aligned}$$



$$X_1(s) = \frac{1}{s^2+1} + \frac{e^{-\pi s}}{s^2+1} = \frac{1+e^{-\pi s}}{s^2+1}$$

$$\begin{aligned} X(s) &= \frac{1}{1-e^{-Ts}} \cdot X_1(s) \\ &= \frac{1}{1-e^{-Ts}} \left(\frac{1+e^{-\pi s}}{1+s^2} \right) \end{aligned}$$

Ques 8A:

Initial-value theorem

The initial-value theorem allows us to find the initial value $x(0)$ of the function $x(t)$, directly from its Laplace transform $X(s)$

If $x(t)$, is a causal signal, then $x(0) = \lim_{s \rightarrow \infty} sX(s)$

Proof: To prove this theorem, we use time differentiation property

$$\Rightarrow L\left\{\frac{d}{dt}x(t)\right\} = sX(s) - x(0) = \int_0^{\infty} \frac{d}{dt}x(t)e^{-st} dt$$

Taking the limit $s \rightarrow \infty$ on both sides of above equation
If we let $s \rightarrow \infty$ then the integral on the right side of equation vanishes due to damping factor, e^{-st}

$$\lim_{s \rightarrow \infty} (sX(s) - x(0)) = 0$$

$$\Rightarrow x(0) = \lim_{s \rightarrow \infty} sX(s)$$

Final-value theorem

The final-value theorem allows us to find the final value $x(\infty)$ of the function $x(t)$, directly from its Laplace transform $X(s)$

If $x(t)$, is a causal signal, then $x(\infty) = \lim_{s \rightarrow 0} sX(s)$

Proof: To prove this theorem, we use time differentiation property

$$\Rightarrow L\left\{\frac{d}{dt}x(t)\right\} = sX(s) - x(0) = \int_0^{\infty} \frac{d}{dt}x(t)e^{-st} dt$$

Taking the limit $s \rightarrow 0$ on both sides of above equation
If we let $s \rightarrow 0$ then the integral on the right side of equation reduces to


$$\lim_{s \rightarrow 0} (sX(s) - x(0)) = \int_0^{\infty} \frac{dx(t)}{dt} dt$$

$$\lim_{s \rightarrow 0} sX(s) - x(0) = x(t) \Big|_0^{\infty}$$

$$\lim_{s \rightarrow 0} sX(s) - x(0) = x(\infty) - x(0)$$

$$\Rightarrow x(\infty) = \lim_{s \rightarrow 0} sX(s)$$

Ques8 B

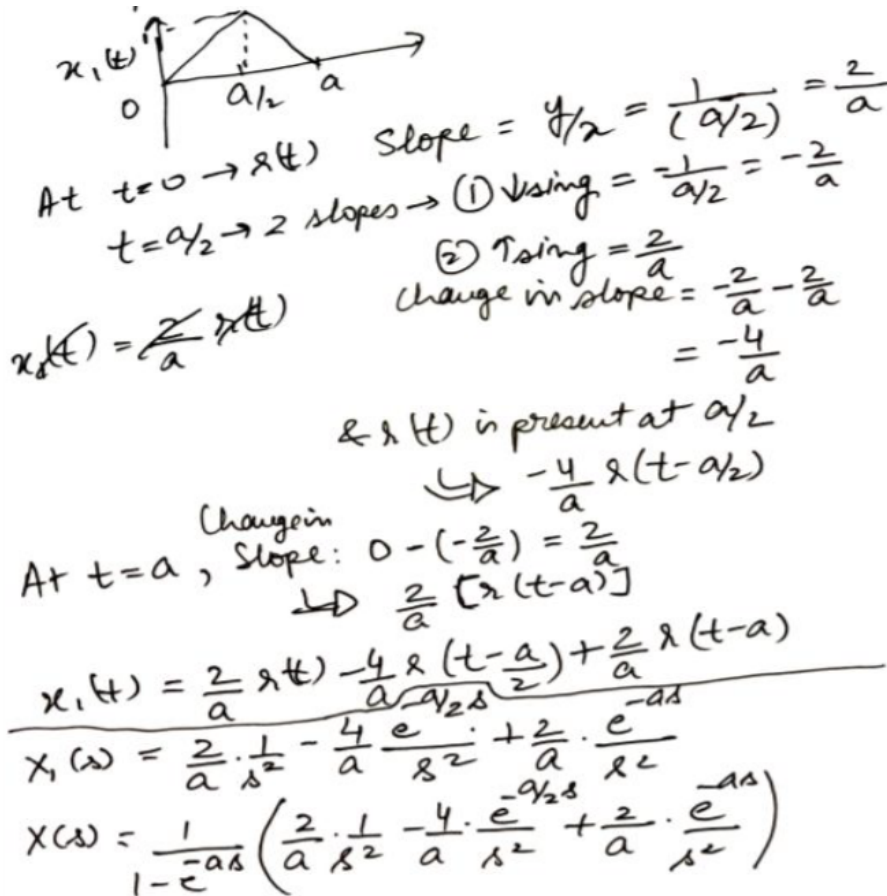

$x_1(t)$ is a triangular pulse starting at $t=0$, peaking at $t=a/2$, and ending at $t=a$.
 At $t=0 \rightarrow x(t)$ Slope = $\frac{1}{2} = \frac{1}{(a/2)} = \frac{2}{a}$
 At $t=a/2 \rightarrow 2$ slopes \rightarrow (1) \downarrow slope = $-\frac{1}{a/2} = -\frac{2}{a}$
 (2) \uparrow slope = $\frac{2}{a}$
 Change in slope = $-\frac{2}{a} - \frac{2}{a} = -\frac{4}{a}$
 $x_2(t) = \frac{2}{a} x(t)$
 & $x(t)$ is present at $a/2$
 $\hookrightarrow -\frac{4}{a} x(t - a/2)$
 At $t=a$, Change in Slope: $0 - (-\frac{2}{a}) = \frac{2}{a}$
 $\hookrightarrow \frac{2}{a} [x(t-a)]$
 $x_1(t) = \frac{2}{a} x(t) - \frac{4}{a} x(t - \frac{a}{2}) + \frac{2}{a} x(t-a)$
 $X_1(s) = \frac{2}{a} \cdot \frac{1}{s^2} - \frac{4}{a} \frac{e^{-a/2s}}{s^2} + \frac{2}{a} \frac{e^{-as}}{s^2}$
 $X(s) = \frac{1}{1-e^{-as}} \left(\frac{2}{a} \cdot \frac{1}{s^2} - \frac{4}{a} \cdot \frac{e^{-a/2s}}{s^2} + \frac{2}{a} \cdot \frac{e^{-as}}{s^2} \right)$