

Internal Assessment Test - I

Sub:	DIGITAL SYSTEM DSEISIGN						Code:	18EE35				
Date:	17/12/2021	Duration:	90 mins	Max Marks:	50	Sem:	3 rd	Branch:	EEE			
Answer Any FIVE FULL Questions												
								Marks	OBE			
									CO	RBT		
1	Simplify the following expression using Quine- McCluskey method. $F(a,b,c,d) = \sum m(7,9,12,13,14,15) + \sum d(4,11)$ and implement using only NAND gates .								10	CO1	L3	
2	a.Define combinational circuits and list the various steps involved in the designing of combinational circuits. b.Define Minterm,maxterm ,Literal,Canonical SOP and Canonical POS..								5	CO1	L2	
3	Simply boolean expression using k-Map (a) $F_1(a,b,c,d) = \sum m(2,3,4,5,13,15) + \sum d(8,9,10,11)$ (b) $F_2(a,b,c,d) = \pi M(1,4,5,11,12,13,15) + \pi d(3,9,10)$								10	CO1	L3	
4	Implement $f(a,b,c,d) = ad + bc' + bd$ using 4:1 MUX using a and b as select lines.								10	CO2	L3	
5	Implement the following function i) $F_1(A,B,C,D) = \sum m(0,2,6,10,11,12,13) + \sum d(3,8,14)$ using 74LS151(8:1 MUX) considering lower order input as select inputs. ii) $F_2(A,B,C,D) = \sum m(0,2,3,4,6,7,9,11,13,15) + \sum d(3,8,14)$ using 74LS153(4:1 MUX) considering higher order input as select inputs.								10	CO2	L3	
6	a.Implement the following function pairs using 74138 decoder. i. $f_1 = (a,b,c) = \Sigma(0,2,4)$; ii. $f_2 = (a,b,c) = \Sigma(1,2,4,5,7)$ b.Design and implement a 2 Bit digital comparator using basic gates								4	CO2	L3	
									6	CO2	L3	

5	Implement the following function iii) $F_1(A,B,C,D) = \sum m(0,2,6,10,11,12,13) + \sum d(3,8,14)$ using 74LS151(8:1 MUX) considering lower order input as select inputs. iv) $F_2(A,B,C,D) = \sum m(0,2,3,4,6,7,9,11,13,15) + \sum d(3,8,14)$ using 74LS153(4:1 MUX) considering higher order input as select inputs.	10	CO2	L3
6	a.Implement the following function pairs using 74138 decoder. i. $f_1(a,b,c) = \Sigma(0,2,4)$; ii. $f_2(a,b,c) = \Sigma(1,2,4,5,7)$	4	CO2	L3
	b.Design and implement a 2 Bit digital comparator using basic gates	6	CO2	L3

I'AT-1

$$\textcircled{1} \quad F(a, b, c, d) = \sum m(7, 9, 12, 13, 14, 15) + \sum d(4, 11)$$

	(2)	(2)	(2)
-d ₄	0100	0100	(4, 12) - 100
-m ₇	0111	0111	(9, 11) 10-1 ✓
-m ₉	1001	1001	(9, 13) 1-01 ✓
-d ₁₁	1011	1011	(12, 13) 110- ✓
-m ₁₂	1000	1100	(12, 14) 11-0 ✓
-m ₁₃	1100	1101	
-m ₁₄	1100	1110	(7, 15) - 111
-m ₁₅	1111	1111	(11, 15) 1-11 ✓
		m ₁₅ 1111	(13, 15) 11-1 ✓
			(14, 15) 111- ✓

$$\begin{aligned} & \checkmark (9, 11, 13, 15) 1 - - 1 \\ & \checkmark (12, 13, 14, 15) 1 1 - - \\ & (4, 12) - 100 \\ & \checkmark (7, 15) - 111 \end{aligned}$$

$$f = AD + AB + BCD$$

	d ₄	m ₇	m ₉	d ₁₁	m ₁₂	m ₁₃	m ₁₄	m ₁₅
(9, 11, 13, 15)	✓	✓						✓
(12, 13, 14, 15)							✓	✓
(4, 12)				✓				
(7, 15)					✓			

2 a) Definition - 2

steps involved - 3

b) Each definition 1 mark.

3) (a) $F_1(a, b, c, d) = \sum m(2, 3, 4, 5, 13, 15) + \sum d(8, 9, 10, 11)$

$$F_1 = A'B'C' + B'C + AD$$

CD					
AB				1	1
	1	1			
			1		
X	X	X	X		

(5 marks)

(b)

CD			
AB			
	0	X	
0	0		
0	0	0	
X	0		X

$$F_2 = (C + D')(B' + C)(A' + D')$$

(5 marks)

$$4) f(a, b, c, d) = ad + bc' + bd$$

$$\cancel{a'b'c'd'} + \cancel{abc'd'} +$$

$$\cancel{ad(b+b')}(c+c') + (a+a')bc'(d+d') + (a+a')b(c+c')d$$


$$= (\cancel{ad} + \cancel{b+b'} + \cancel{c+c'}) +$$

$$= ab'c'd + ab'cd + abc'd + abc'd + a'b'cd + abc'd' + a'b'cd$$

$$cd' cd cd' cd = \sum(4, 5, 7, 9, 11, 12, 13, 15)$$

	D_0	D_1	D_2	D_3	
D_0	0	1	2	3	0
D_1	4	5	6	7	$c'd' + c'd + cd = c' + d$
D_2	8	9	10	11	$c'd + cd = d$
D_3	12	13	14	15	$c'd' + c'd + cd = c' + d$

(4)

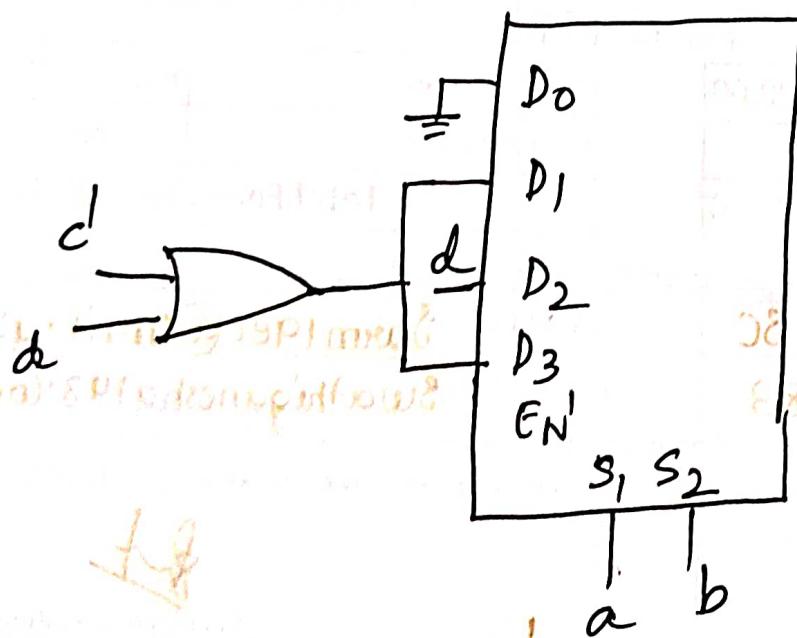

(2)


P105|S1|d1

Output: d

$$(5) \quad (i) \quad F_1(A, B, C, D) = \sum m(0, 2, 6, 10, 11, 12, 13) + \sum d(3, 8, 14)$$


In A, B, C, D , $[B, C, D]$ is select lines

	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
A'	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	0	1	1	A	A	1	0
	1	1						

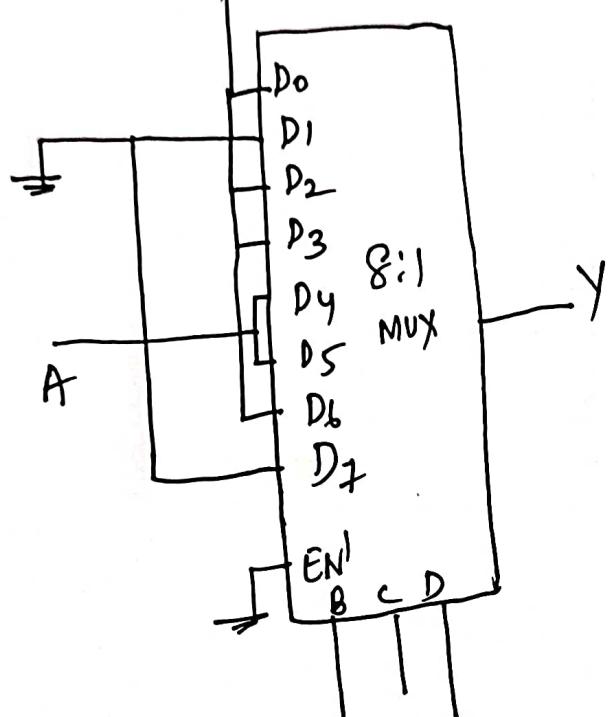


(5 marks)
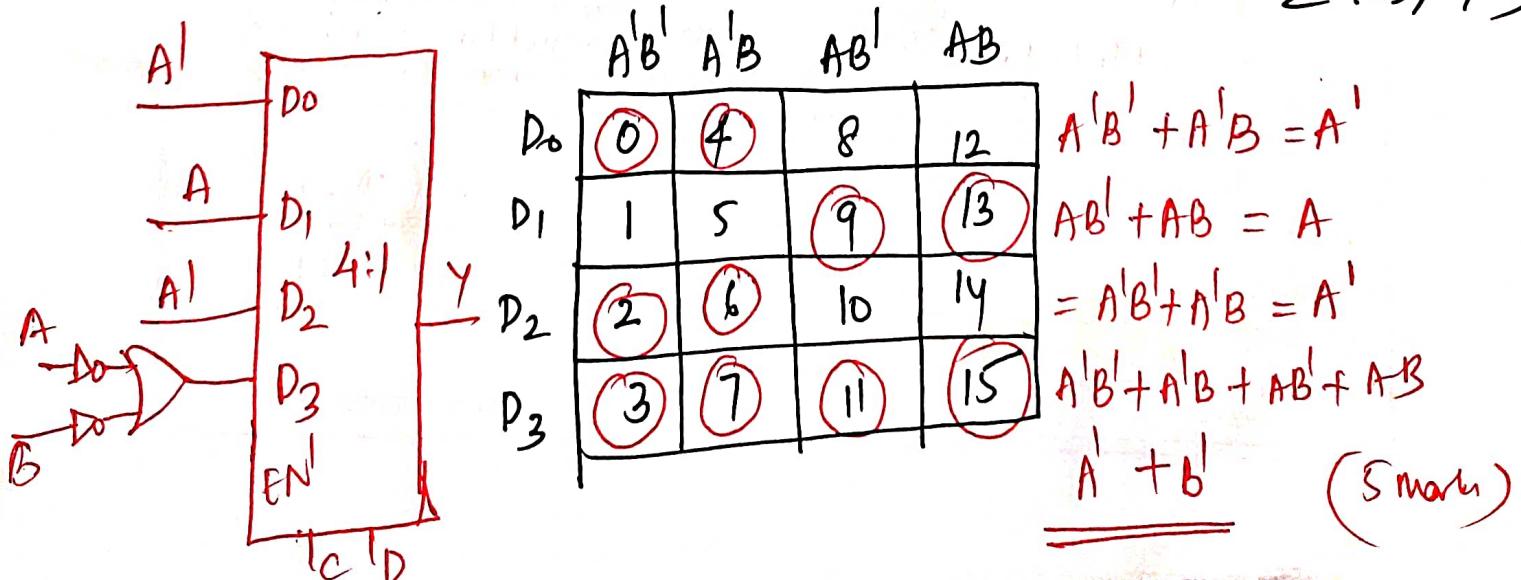
$$(ii) \quad F_2(A, B, C, D) = \sum m(0, 2, 3, 4, 6, 7, 9, 11, 13, 15) + \sum d(3, 8, 14)$$



$$6) a) f_1(a, b, c) = \sum(0, 2, 4)$$

$$f_2(a, b, c) = \sum(1, 2, 4, 5, 7)$$

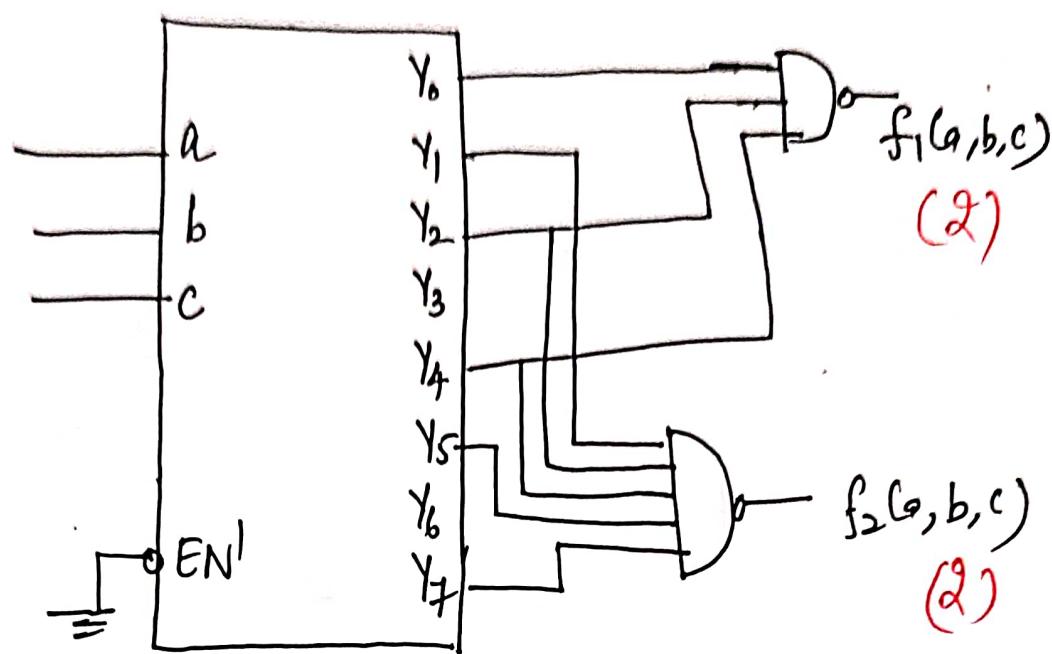

$$b) A > B = A_0 B_1' B_0 + A_1 B_1' + A_1 A_0' B_0 \quad (2)$$

$$A = B = (A_0 \odot B_0) (A_1 \odot B_1) \quad (2)$$

$$A < B = A_1' A_0' B_0 + A_0' B_1 B_0 + A_1' B_1 \quad (2)$$