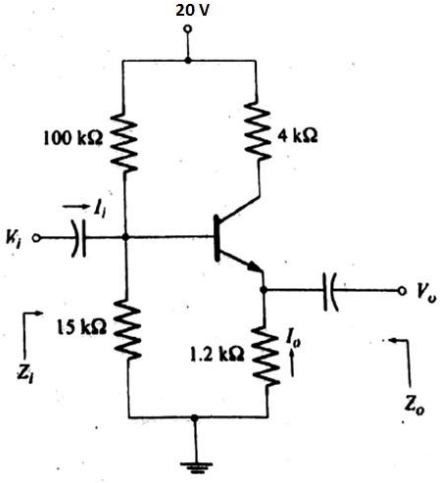


Internal Assessment Test - II

Sub:	ANALOG ELECTRONIC CIRCUITS	Code:	18EE34							
Date:	25/01/2022	Duration:	90 mins	Max Marks:	50	Sem:	3rd	Branch:	EEE	
Answer <b>Any FIVE FULL</b> Questions										
								Marks	OBE	
									CO	RBT
1.	Define h parameter and obtain an equivalent h parameter model of CE, CC and CB configurations. Also write generalized h-parameter equations.		10							
2.	<p>For the Emitter Follower circuit shown below, determine the following:</p> <p>a) <math>r_e</math> b) <math>Z_i</math> c) <math>Z_o</math> d) <math>A_v</math> and e) <math>A_I</math> Take <math>\beta = 90</math> and <math>r_o = \infty</math></p> <div style="text-align: center;">  </div>		10							
3.	A transistor in CE mode has h-parameters $h_{ie} = 1.1K\Omega$ , $h_{re} = 2 \times 10^{-4}$ , $h_{fe} = 100$ and $h_{oe} = 20 \mu A / V$ . Determine equivalent CB parameters.		10							
4.	Draw the circuit diagram of Common Emitter amplifier with fixed biasing. Also draw its AC equivalent $r_e$ model. Derive the expression for input impedance, output impedance, voltage gain and current gain.		10							
5.	Derive equations for Miller Input Capacitance and Miller output capacitance with appropriate diagrams.		10							
6.	State and prove Millers Theorem.		10							
7.	What are the advantages of h parameters? Explain the relationship using circuit and equations between the parameters of hybrid model and the $r_e$ model for CE and CB configuration.		10							


## Solution

1.

Hybrid means mixed. Here we have mixed parameters.


In hybrid model, the transistor is modelled based on what is happening at its terminals without regard for the physical process taking place inside the transistor.

CE:

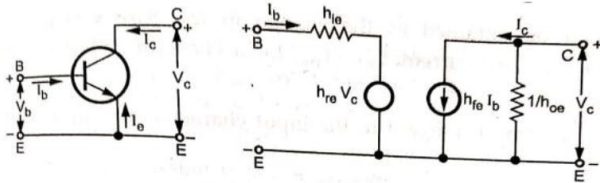


$$\begin{aligned} v_1 &= h_i i_1 + h_r v_2 \\ i_2 &= h_f i_1 + h_o v_2 \end{aligned} \quad \Rightarrow \quad \begin{aligned} V_b &= h_{ie} I_b + h_{re} V_c \\ I_c &= h_{fe} I_b + h_{oe} V_c \end{aligned}$$

CC:

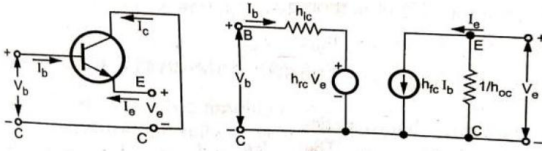

$$\begin{aligned} v_1 &= h_i i_1 + h_r v_2 \\ i_2 &= h_f i_1 + h_o v_2 \end{aligned} \quad \Rightarrow \quad \begin{aligned} V_b &= h_{ic} I_b + h_{rc} V_e \\ I_e &= h_{fc} I_b + h_{oc} V_e \end{aligned}$$

CB:

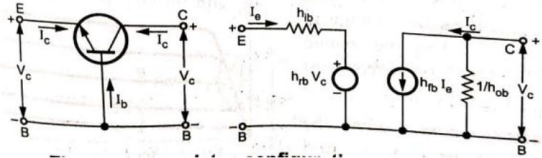

$$\begin{aligned} v_1 &= h_i i_1 + h_r v_2 \\ i_2 &= h_f i_1 + h_o v_2 \end{aligned} \quad \Rightarrow \quad \begin{aligned} V_e &= h_{ib} I_e + h_{rb} V_c \\ I_c &= h_{fb} I_e + h_{ob} V_c \end{aligned}$$

2.

a)  $I_E = 1.23 \text{ mA}$   
 $r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.23 \text{ mA}} = 21.13 \Omega$

b)  $Z_b = \beta(r_e + R_E) = 100(21.13 \Omega + 1.2 \text{ k}\Omega) = 122.11 \text{ k}\Omega$   
 $Z_i = R_B \parallel Z_b$   
 $R_B = 100 \text{ k}\Omega \parallel 15 \text{ k}\Omega = 13.04 \text{ k}\Omega$   
 $Z_i = 13.04 \text{ k}\Omega \parallel 122.11 \text{ k}\Omega = 11.78 \text{ k}\Omega$   
 $Z_o = R_E \parallel r_e = 1.2 \text{ k}\Omega \parallel 21.13 \Omega = 20.76 \Omega$


c)  $A_V = 1$

$$A_i = -\frac{A_v Z_i}{R_E} = -\frac{(0.983)(11.78 \text{ k}\Omega)}{1.2 \text{ k}\Omega} = -9.65$$

3.

solution  
 $h_{ib} = \frac{h_{ie}}{1+h_{fe}}$ ,  $h_{sb} = \frac{h_{ie} h_{oe} - h_{re}}{1+h_{fe}}$   
 $h_{fb} = \frac{-h_{fe}}{1+h_{fe}}$ ,  $h_{ob} = \frac{h_{oe}}{1+h_{fe}}$

4.

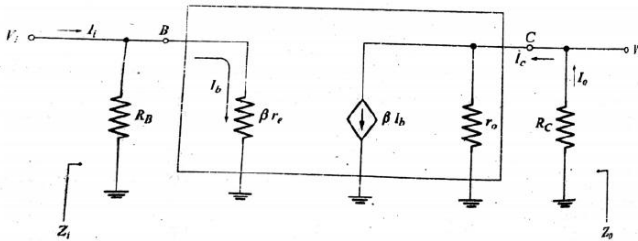

Input Impedance ( $Z_i$ ):


$$Z_i = R_B \parallel \beta r_e$$

If  $R_B \geq 10\beta r_e$   $Z_i = \beta r_e$

Output Impedance ( $Z_o$ ):

Reduce  $V_i = 0$  to find output impedance.

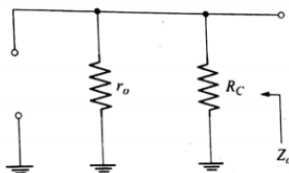$V_i = 0$ ,  $I_i = 0$ ,  $I_b = 0$ . Therefore  $\beta I_b = 0$



$$Z_o = r_o \parallel R_C$$

If  $r_o \geq 10R_C$  (or)  $r_o = \infty$ ,  $Z_o = R_C$

### Voltage Gain ( $A_v$ ):

$$V_o = -\beta I_b [r_o \parallel R_C]$$

From the input circuit,

$$V_i = I_b [\beta r_e]$$

Voltage Gain,  $A_v = \frac{V_o}{V_i}$

$$= \frac{-\beta I_b [r_o \parallel R_C]}{I_b [\beta r_e]}$$

$$A_v = -\frac{r_o \parallel R_C}{r_e} \quad (\text{or}) \quad A_v \approx -\frac{R_C}{r_e}$$

### Current Gain ( $A_i$ ):

$$A_i = \frac{I_o}{I_i}$$

$$V_o = -I_o R_C$$

$$I_o = \frac{-V_o}{R_C}$$

$$I_i = \frac{V_i}{Z_i}$$


$$A_i = \left[ \frac{-V_o}{R_C} \right] \div \left[ \frac{V_i}{Z_i} \right]$$

$$= - \left[ \frac{V_o}{V_i} \right] \left[ \frac{Z_i}{R_C} \right]$$

$$A_i = -\frac{A_v Z_i}{R_C}$$

5.
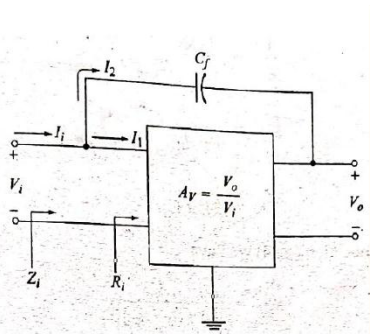
### Miller Input Capacitance ( $C_{Mi}$ )



$$\text{Let } R_i = \frac{V_i}{I_i} \Rightarrow I_i = \frac{V_i}{R_i}$$

$$\text{and } Z_i = \frac{V_i}{I_i} \Rightarrow I_i = \frac{V_i}{Z_i}$$

Apply KCL at input node,

$$I_i = I_1 + I_2$$

$$I_2 = \frac{V_i - V_o}{X_{C_f}}$$

$$= \frac{V_i - A_v V_i}{X_{C_f}} \quad [\because V_o = A_v V_i]$$

$$\frac{V_i}{Z_i} = \frac{V_i}{R_i} + \frac{[1 - A_v] V_i}{X_{C_f}}$$

By Eliminating  $V_i$ ,

$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{\left[ \frac{X_{C_f}}{1 - A_v} \right]}$$

$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{C_{Mi}}}$$

$$\text{where } X_{C_{Mi}} = \frac{X_{C_f}}{1 - A_v}$$

$$X_{C_f} = \frac{1}{2\pi f C_f}$$


$$X_{C_{Mi}} = \frac{1}{2\pi f [1 - A_v] C_f}$$

$$X_{C_{Mi}} = \frac{1}{2\pi f C_{Mi}}$$

$$\text{where } C_{Mi} = [1 - A_v] C_f$$

where  $C_{Mi}$  is Miller input capacitance

# Miller Output Capacitance ( $C_{Mo}$ )

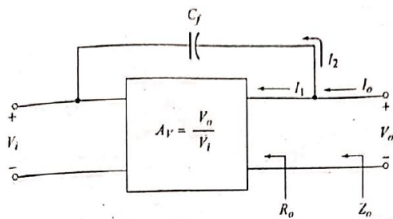

$$\text{Let } R_o = \frac{V_o}{I_1} \Rightarrow I_1 = \frac{V_o}{R_o}$$

$$\text{and } Z_o = \frac{V_o}{I_o} \Rightarrow I_o = \frac{V_o}{Z_o}$$

Apply KCL at output node,

Usually  $R_o$  is large, so  $V_o/R_o$  neglected

$$I_o = I_1 + I_2$$

$$I_2 = \frac{V_o - V_i}{X_{C_f}}$$

Using  $V_i = \frac{V_o}{A_v}$  we have

$$I_2 = \frac{V_o - \frac{V_o}{A_v}}{X_{C_f}} = \frac{V_o \left[1 - \frac{1}{A_v}\right]}{X_{C_f}}$$

$$I_o = \frac{V_o}{R_o} + \frac{V_o \left[1 - \frac{1}{A_v}\right]}{X_{C_f}}$$

$$\text{Now } I_o \approx \frac{V_o \left[1 - \frac{1}{A_v}\right]}{X_{C_f}}$$

$$Z_o = \frac{V_o}{I_o} = \frac{X_{C_f}}{\left[1 - \frac{1}{A_v}\right]}$$

$$Z_o = \frac{1}{2\pi f \left[1 - \frac{1}{A_v}\right] C}$$


$$Z_o = \frac{1}{2\pi f C_{Mo}}$$

$$\text{where } C_{Mo} = \left[1 - \frac{1}{A_v}\right] C_f$$

where  $C_{Mo}$  is Miller output Capacitance

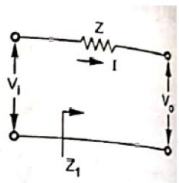6.

Miller's Theorem states that, the effect of resistance  $Z$  on the input circuit is a ratio of input voltage  $V_i$  to the current  $I$  which flows from the input to the output.




Therefore,

$$Z_1 = \frac{V_i}{I}$$

$$\text{where, } I = \frac{V_i - V_o}{Z} = \frac{V_i \left[1 - \frac{V_o}{V_i}\right]}{Z} = \frac{V_i [1 - A_v]}{Z}$$

$$\therefore Z_1 = \frac{Z}{1 - A_v} = \frac{Z}{1 - K} \quad \left[ \because \frac{V_o}{V_i} = A_v = K \right]$$

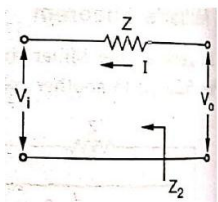Miller's Theorem states that, the effect of resistance  $Z$  on the output circuit is a ratio of output voltage  $V_o$  to the current  $I$  which flows from the output to the input.



Therefore,

$$Z_2 = \frac{V_o}{I}$$

$$\text{where, } I = \frac{V_o - V_i}{Z} = \frac{V_o \left[1 - \frac{V_i}{V_o}\right]}{Z} = \frac{V_o \left[1 - \frac{1}{A_v}\right]}{Z}$$


$$= \frac{V_o \left[\frac{A_v - 1}{A_v}\right]}{Z}$$

$$\therefore Z_2 = \frac{V_o}{I} = \frac{Z}{\left[\frac{A_v - 1}{A_v}\right]} = \frac{Z A_v}{A_v - 1} = \frac{Z \cdot K}{K - 1}$$

$$\left[ \because \frac{V_o}{V_i} = A_v = K \right]$$

7.

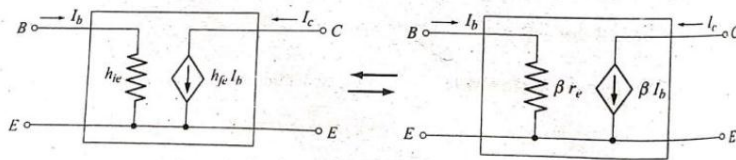**Relation between the parameters of Hybrid model and  $r_e$  model for CE configuration.**




By comparing the two models,

$$h_{ie} = \beta r_e$$

$$h_{fe} = \beta$$

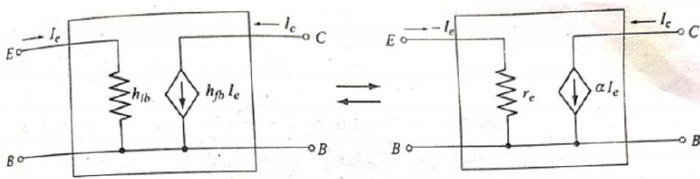**Relation between the parameters of Hybrid model and  $r_e$  model for CB configuration.**



By comparing,

$$h_{ib} = r_e$$

$$h_{fb} = -\alpha (\alpha \approx 1).$$

**Benefits of h-parameter**

- Easy to measure
- Can be obtained from the transistor characteristic curves
- Convenient to use in circuit analysis and design.
- Most of the transistor manufacturers specify the h-parameter.