

USN										
-----	--	--	--	--	--	--	--	--	--	--




CMR
INSTITUTE OF
TECHNOLOGY






Internal Assessment Test - III


Sub:	Electric Circuit Analysis						Code:	18EE32	
Date:	07/03/2022	Duration:	90 mins	Max Marks:	50	Sem:	3 rd	Branch:	EEE

Answer Any FIVE FULL Questions

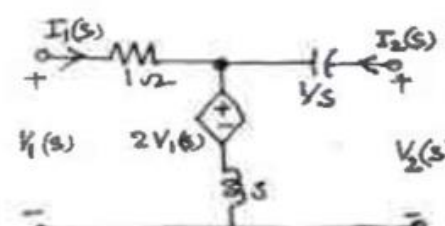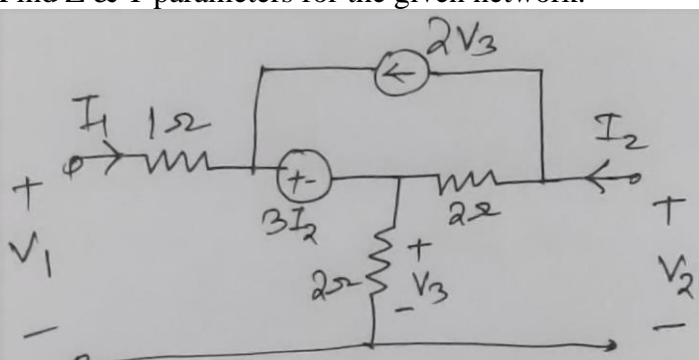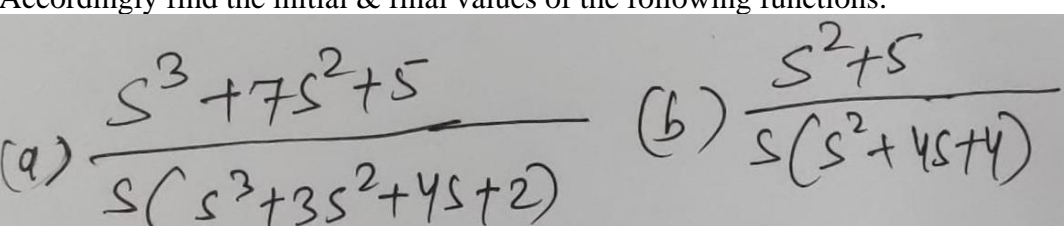
		Marks	OBE	
			CO	RBT
1	Find Transmission Line Parameters for the given network. 	10	CO6	L3
2	Find Z & T parameters for the given network. 	10	CO6	L3
3	a) Determine the line currents for a delta connected load of $Z_{ab}=10 \angle 60^\circ \Omega$, $Z_{bc} = 20 \angle 90^\circ \Omega$ and $Z_{ca}=25 \angle 30^\circ \Omega$. Assume 3-phase 400V, ABC sequence. b) A three phase, 400V, 4 wire system has a star connected load with $Z_A=(10+j0)\Omega$, $Z_B = (15+j10)\Omega$, $Z_C=(0+j5)\Omega$. Find the line currents & current through neutral wire.	4 6	CO6	L3 L3
4	Determine the line currents, neutral current, Real & Reactive Power in an unbalanced star connected load supplied from a symmetrical 3 phase, 440V system. The branch impedances are $Z_R = 4 \angle 30^\circ \Omega$ $Z_Y=10 \angle 45^\circ \Omega$ and $Z_B=10 \angle 60^\circ \Omega$. The phase sequence is RYB	10	CO6	L3
5	State & prove Initial & Final Value Theorem for any function $x(t)$. Accordingly find the initial & final values of the following functions: 	10	CO5	L3

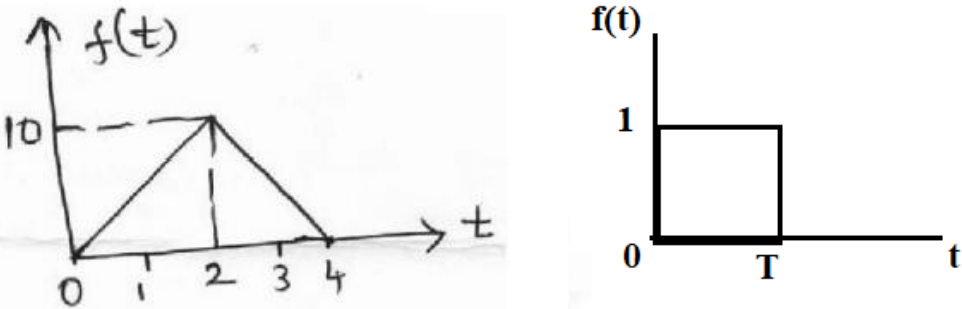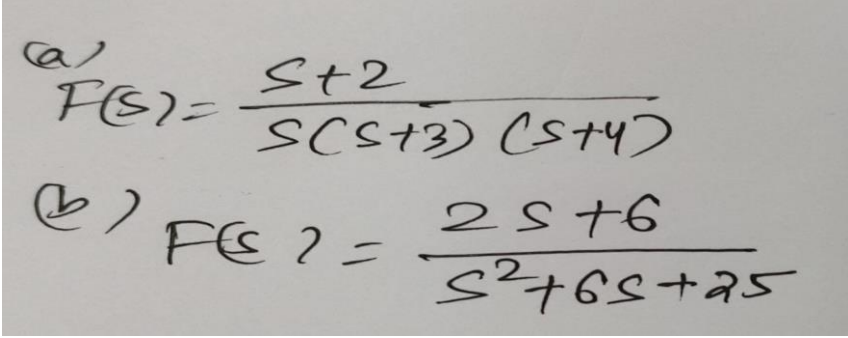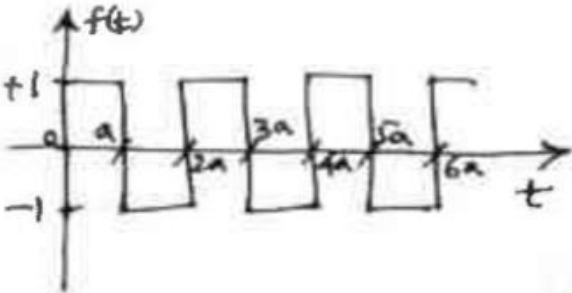6	<p>Find the Laplace transform of the function given by the following waveforms.</p> 	10 (7+3)	CO5	L3
7	<p>a) Find Inverse Laplace of following functions:</p> 	7	CO5	L3
	<p>b) Find Laplace of the following functions: (i) $\delta(t)$ (ii) $u(t)$ (iii) $\sin \omega t$</p>	3	CO5	L2
8	<p>(a) Find Laplace Transform of the given Periodic function:</p> 	8	CO5	L3
	<p>(b) Draw the following functions: (i) $tu(t-T)$ (ii) $(t-T)u(t-T)$ (iii) $u(-t)$ (iv) $tu(t+T)$</p>	2	CO5	L3

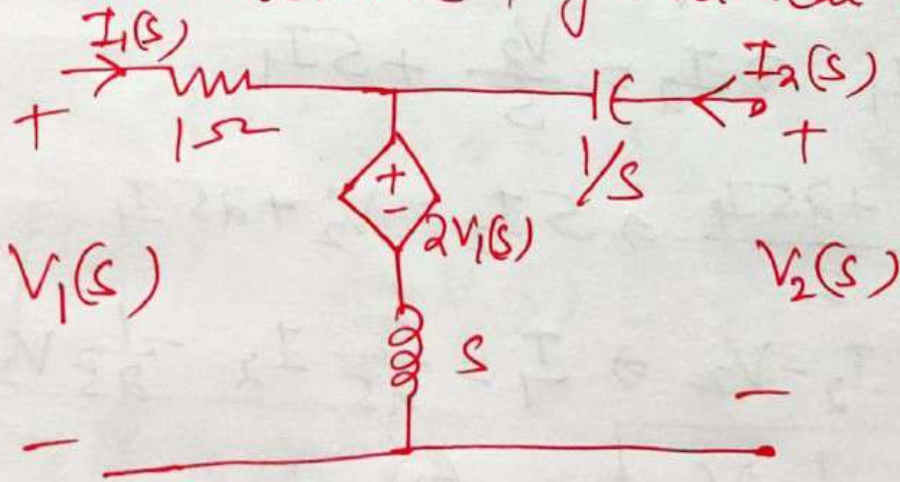Q: For the given network find V -Parameters.
 Is this network symmetrical?



Ans:

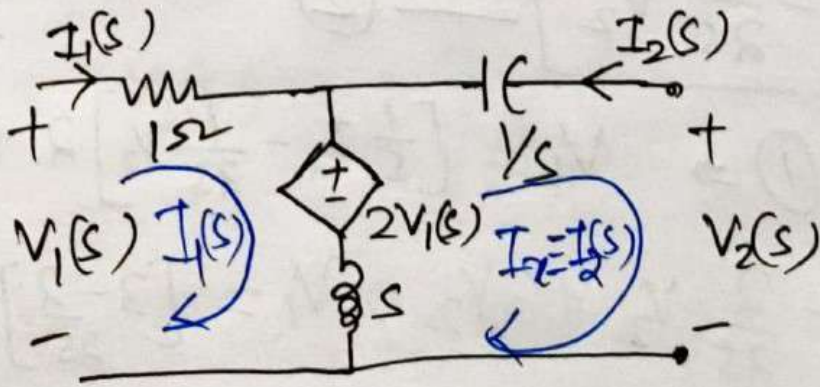

$$I_x = -I_2(s)$$

Mesh I_1 eqn $\Rightarrow V_1(s) - I_1(s) - 2V_1(s) - s(I_1(s) - I_2(s)) = 0$

$$\Rightarrow V_1(s) - I_1(s) - 2V_1(s) - sI_1(s) + sI_2(s) = 0 \quad [I_2 = -I_2]$$

$$\Rightarrow V_1(s) - I_1(s) - 2V_1(s) - sI_1(s) - sI_2(s) = 0$$

$$\Rightarrow -V_1(s) - I_1(s)[s+1] - sI_2(s) = 0$$

$$\Rightarrow \boxed{I_1(s) = -V_1(s) - sI_2(s)} \quad \text{--- ①}$$

Mesh I_2 eqn

$$[I_2 = -I_2]$$

$$-V_2(s) - s(I_2(s) - I_1(s)) + 2V_1(s) - I_2(s) \frac{1}{s} = 0$$

$$\Rightarrow -V_2(s) - sI_2(s) + sI_1(s) + 2V_1(s) - \frac{I_2(s)}{s} = 0$$

$$\Rightarrow -V_2(s) + sI_2(s) + sI_1(s) + 2V_1(s) + \frac{I_2(s)}{s} = 0$$

$$\Rightarrow \left(s + \frac{1}{s}\right) I_2(s) + sI_1(s) + 2V_1(s) - V_2(s) = 0$$

$$\Rightarrow \left(\frac{s^2+1}{s}\right) I_2(s) = V_2(s) - 2V_1(s) - sI_1(s)$$

$$\Rightarrow \boxed{I_2(s) = \frac{s}{s^2+1} V_2(s) - \frac{2s}{s^2+1} V_1(s) - \frac{s^2}{s^2+1} I_1(s)} \quad \text{--- ②}$$

Putting ② in ① we get:

$$I_1(s) = -V_1(s) - s \left[\frac{s}{s^2+1} V_2(s) - \frac{2s}{s^2+1} V_1(s) - \frac{s^2}{s^2+1} I_1(s) \right]$$

$$\Rightarrow I_1(s) = -V_1(s) - \frac{s^2}{s^2+1} V_2(s) + \frac{2s^2}{s^2+1} V_1(s) + \frac{s^3}{s^2+1} I_1(s)$$

$$\Rightarrow I_1(s) = V_1(s) \left[\frac{2s^2}{s^2+1} - 1 \right] - \frac{s^2}{s^2+1} V_2(s) + \frac{s^3}{s^2+1} I_1(s)$$

$$\Rightarrow I_1(s) - I_1(s) \left(\frac{s^3}{s^2+1} \right) = V_1(s) \left[\frac{2s^2 - s^2 - 1}{s^2+1} \right] - \frac{s^2}{s^2+1} V_2(s)$$

$$\Rightarrow I_1(s) \left[1 - \frac{s^3}{s^2+1} \right] = V_1(s) \left[\frac{s^2-1}{s^2+1} \right] - \left(\frac{s^2}{s^2+1} \right) V_2(s)$$

$$\Rightarrow I_1(s) \left[\frac{s^2+1-s^3}{s^2+1} \right] = V_1(s) \left[\frac{s^2-1}{s^2+1} \right] - \left(\frac{s^2}{s^2+1} \right) V_2(s)$$

$$\Rightarrow I_1(s) = \frac{V_1(s) [s^2-1]}{(s^2+1)} \times \frac{(s^2+1)}{-s^3+s^2+1} - \left(\frac{s^2}{s^2+1} \right) \times \frac{s^2+1}{-s^3+s^2+1} V_2(s)$$

$$\Rightarrow \boxed{I_1(s) = \left[\frac{s^2-1}{-s^3+s^2+1} \right] V_1(s) - \left[\frac{s^2}{-s^3+s^2+1} \right] V_2(s)} \quad \text{--- (3)}$$

Y-Parameter \Rightarrow

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$\boxed{Y_{11} = \frac{s^2-1}{-s^3+s^2+1}}$$

$$\boxed{Y_{12} = \frac{-s^2}{-s^3+s^2+1} = \frac{s^2}{s^3-s^2-1}}$$

Putting (3) in (2) \Rightarrow

$$I_2(s) = \frac{s}{s^2+1} V_2(s) - \frac{2s}{s^2+1} V_1(s) - \frac{s^2}{s^2+1} I_1(s)$$

$$\Rightarrow I_2(s) - \left(\frac{s}{s^2+1} \right) V_2(s) - \frac{2s}{s^2+1} V_1(s) = -\frac{s^2}{s^2+1} I_1(s)$$

$$I_2(s) = \frac{s}{s^2+1} V_2(s) - \frac{2s}{s^2+1} V_1(s) - \frac{s^2}{s^2+1} \left[\frac{s^2-1}{-s^3+s^2+1} V_1(s) - \frac{s^2}{-s^3+s^2+1} V_2(s) \right]$$

$$\Rightarrow I_2(s) = \frac{s}{s^2+1} V_2(s) - \frac{2s}{s^2+1} V_1(s) - \frac{s^2(s^2-1)}{(s^2+1)(-s^3+s^2+1)} V_1(s) + \frac{s^4}{(s^2+1)(-s^3+s^2+1)} V_2(s)$$

$$\Rightarrow I_2(s) = V_2(s) \left[\frac{s}{s^2+1} + \frac{s^4}{(s^2+1)(-s^3+s^2+1)} \right] - V_1(s) \left[\frac{2s}{s^2+1} + \frac{s^2(s^2-1)}{(s^2+1)(-s^3+s^2+1)} \right]$$

$$\Rightarrow I_2(s) = V_2(s) \left[\frac{s(-s^3+s^2+1) + s^4}{(s^2+1)(-s^3+s^2+1)} \right] - V_1(s) \left[\frac{2s(-s^3+s^2+1) + s^4 - s^2}{(s^2+1)(-s^3+s^2+1)} \right]$$

$$\Rightarrow I_2(s) = V_2(s) \left[\frac{-s^4 + s^3 + s + s^4}{(s^2+1)(-s^3+s^2+1)} \right] - \left[\frac{-2s^4 + 2s^3 + 2s + s^4 - s^2}{(s^2+1)(-s^3+s^2+1)} \right] V_1(s)$$

$$\Rightarrow I_2(s) = V_2(s) \left[\frac{s^3 + s}{(s^2+1)(-s^3+s^2+1)} \right] - \left[\frac{-s^4 + 2s^3 - s^2 + 2s}{(s^2+1)(-s^3+s^2+1)} \right] V_1(s)$$

$$\Rightarrow I_2(s) = V_1(s) \left[\frac{s^4 - 2s^3 + s^2 - 2s}{(s^2+1)(-s^3+s^2+1)} \right] + V_2(s) \left[\frac{s(s^2+1)}{(s^2+1)(-s^3+s^2+1)} \right]$$

$$\Rightarrow I_2(s) = V_1(s) \left[\frac{s^3(s-2) + s(s-2)}{(s^2+1)(-s^3+s^2+1)} \right] + \frac{s}{(-s^3+s^2+1)} V_2(s)$$

$$\Rightarrow I_2(s) = V_1(s) \left[\frac{(s^3+s)(s-2)}{(s^2+1)(-s^3+s^2+1)} \right] + \left[\frac{s}{-s^3+s^2+1} \right] V_2(s)$$

$$= V_1(s) \left[\frac{s(s^2+1)(s-2)}{(s^2+1)(-s^3+s^2+1)} \right] + \left(\frac{s}{-s^3+s^2+1} \right) V_2(s)$$

$$\Rightarrow I_2(s) = \left[\frac{s(s-2)}{-s^3+s^2+1} \right] V_1(s) + \left(\frac{s}{-s^3+s^2+1} \right) V_2(s)$$

Comparing with $I_2 = Y_{21} V_1 + Y_{22} V_2$

$$Y_{21} = \frac{s(s-2)}{-s^3+s^2+1}, \quad Y_{22} = \frac{s}{-s^3+s^2+1}$$


$$\Rightarrow Y_{11} = \frac{s^2-1}{-s^3+s^2+1}, \quad Y_{12} = \frac{s^2}{s^3-s^2-1}$$

$$Y = \begin{bmatrix} \frac{s^2-1}{-s^3+s^2+1} & \frac{s^2}{s^3-s^2-1} \\ \frac{s(s-2)}{-s^3+s^2+1} & \frac{s}{-s^3+s^2+1} \end{bmatrix}$$

Here $Y_{11} \neq Y_{22}$ & $Y_{21} \neq Y_{12}$ So not symmetric.

A.

Q:

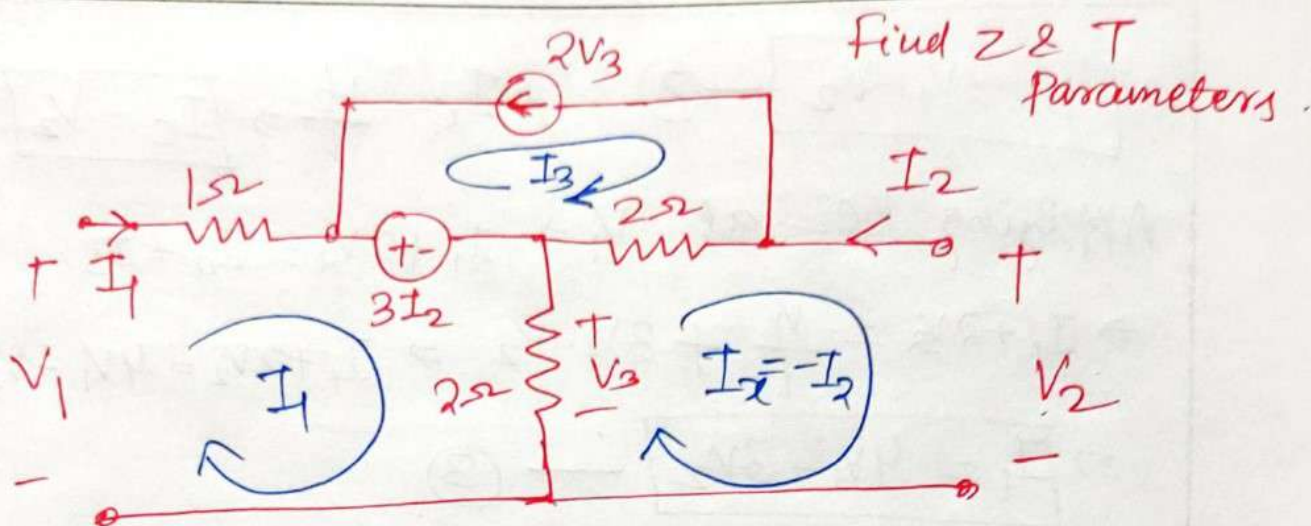

Ans.: Applying Mesh Analysis in I_1 Mesh

$$\Rightarrow V_1 - I_1 - 3I_2 - 2(I_1 - I_x) = 0$$

$$\Rightarrow V_1 - I_1 - 3I_2 - 2I_1 + 2I_x = 0$$

$$\Rightarrow V_1 - I_1 - 3I_2 - 2I_1 - 2I_2 = 0$$

$$\Rightarrow \boxed{V_1 = 3I_1 + 5I_2} \quad \text{--- (1)} \quad [I_x = -I_2]$$

From I_3 Mesh: $I_3 = -2V_3$ & $V_3 = 2(I_1 - I_x)$

$$\Rightarrow I_3 = -2 \times 2(I_1 - I_x) = -4(I_1 + I_2)$$

$$\Rightarrow \boxed{I_3 = -4I_1 - 4I_2} \quad \text{--- (2)}$$

From I_x Mesh: $-V_2 - 2(I_x - I_1) - 2(I_x - I_3) = 0$

$$\Rightarrow -V_2 - 2I_x + 2I_1 - 2I_x + 2I_3 = 0$$

$$\Rightarrow V_2 = -2(-I_2) + 2I_1 - 2(-I_2) + 2I_3$$

Putting I_3 value from (2) \Rightarrow

$$V_2 = 2I_2 + 2I_1 + 2I_2 + 2(-4I_1 - 4I_2)$$

$$V_2 = 4I_2 + 2I_1 - 8I_1 - 8I_2 \Rightarrow \boxed{V_2 = -6I_1 - 4I_2} \quad (3)$$

From (1) & (3)

$$V_1 = 3I_1 + 5I_2$$

$$V_2 = -6I_1 - 4I_2$$

Comparing with
Z-Parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

So $Z_{11} = 3, Z_{12} = 5, Z_{21} = -6, Z_{22} = -4$

$$\boxed{[Z]} = \begin{bmatrix} 3 & 5 \\ -6 & -4 \end{bmatrix} \Rightarrow \Delta Z = \begin{vmatrix} 3 & 5 \\ -6 & -4 \end{vmatrix} = -12 - (-30)$$

$$\Rightarrow \Delta Z = 18$$

$$A = \frac{Z_{11}}{Z_{21}} = \frac{3}{-6} \Rightarrow \boxed{A = -\frac{1}{2}}, \quad B = \frac{\Delta Z}{Z_{21}} = \frac{18}{-6} \Rightarrow \boxed{B = -3}$$

$$\boxed{B = -3}, \quad \boxed{C = \frac{1}{Z_{12}} = \frac{1}{5}}, \quad D = \frac{Z_{22}}{Z_{21}} = \frac{-4}{-6} \Rightarrow \boxed{D = \frac{2}{3}}$$

$$[T] = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \Rightarrow \boxed{[T]} = \begin{bmatrix} -\frac{1}{2} & -3 \\ \frac{1}{5} & \frac{2}{3} \end{bmatrix}$$

Q: Determine the line currents & total power supplied to a delta connected load of $Z_{ab} = 10/60^\circ \Omega$, $Z_{bc} = 20/90^\circ \Omega$, $Z_{ca} = 25/30^\circ \Omega$. Assume 3-Phase 400V, ABC sequence.

Ans: Sequence: ABC, $V_L = 400V$

$$V_{AB} = V_L \angle 0 = 400 \angle 0$$

$$V_{BC} = V_L \angle -120 = 400 \angle -120$$


$$V_{CA} = V_L \angle 120 = 400 \angle 120$$

Phase Currents:

$$I_{ab} = \frac{V_{AB}}{Z_{ab}} = \frac{400 \angle 0}{10/60} = 40 \angle 60^\circ$$

$$I_{bc} = \frac{V_{BC}}{Z_{bc}} = \frac{400 \angle -120}{20/90} = 20 \angle -210 = 20 \angle 210^\circ$$
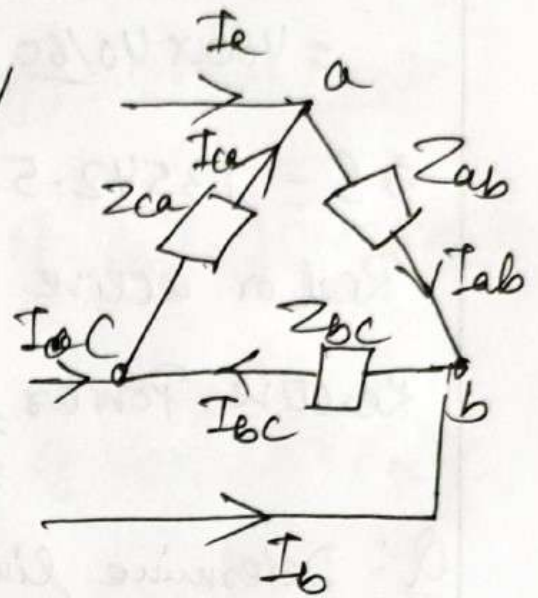
$$I_{ca} = \frac{V_{CA}}{Z_{ca}} = \frac{400 \angle 120}{25/30} = 16 \angle 90^\circ$$



$$Z_{ab} = 10/60^\circ$$

$$Z_{bc} = 20/90^\circ$$

$$Z_{ca} = 25/30^\circ$$

Line Currents: KCL at a $\Rightarrow I_a + I_{ca} = I_{ab}$

$$\Rightarrow I_a = I_{ab} - I_{ca} = 40 \angle 60 - 16 \angle 90 \Rightarrow I_a = 54.44 \angle -68.44^\circ$$

KCL at b $\Rightarrow I_{ab} + I_b = I_{bc} \Rightarrow I_b = I_{bc} - I_{ab} = 20 \angle 210 - 40 \angle 60$

$$\Rightarrow I_b = 58.18 \angle 129.89^\circ$$

KCL at c $\Rightarrow I_c + I_{bc} = I_{ca} \Rightarrow I_c = I_{ca} - I_{bc} = 16 \angle 90 - 20 \angle 210$

$$\Rightarrow I_c = 18.33 \angle 19.1^\circ$$

Power: $S = \cancel{V_{AB} I_{AB}^*} + \cancel{V_{BC} I_{BC}^*}$

$$S = V_{AB} I_{AB}^* + V_{BC} I_{BC}^* + V_{CA} I_{CA}^*$$

$$= 400 \angle 0^\circ \times [40 \angle -60^\circ]^* + 400 \angle -120^\circ \times [20 \angle -210^\circ]^* + 400 \angle 120^\circ \times [16 \angle 90^\circ]^*$$

$$= 400 \times 40 \angle 60^\circ + 400 \angle -120^\circ \times 20 \angle 210^\circ + 400 \angle 120^\circ \times 16 \angle -90^\circ$$

$$\Rightarrow S = 13542.56 + 25056.4j \quad \text{VA}$$

Real or active Power $P = 13542.56 \text{ W} = \text{Re}[S] \leftarrow$ Real Part of S


Reactive Power $Q = \text{Im}[S] = 25056.4 \text{ VAR} \leftarrow$ Imaginary Part of S .

Q: A 3-Phase 400V 4 wire system has a star connected load with $Z_A = (10 + j0) \Omega$, $Z_B = (15 + j10) \Omega$, $Z_C = (0 + j5) \Omega$ - Find line currents & current through neutral wire.

Ans: 3-Phase Star:

At balanced source side
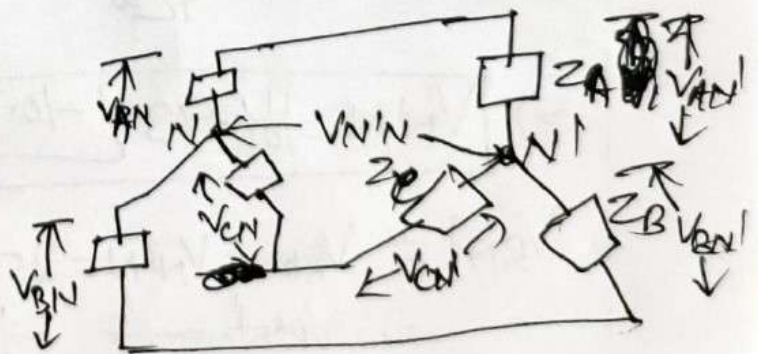
$$V_p = \frac{V_L}{\sqrt{3}}, \quad V_L = 400V$$



Line Voltages are: Considering Phase sequence as ABC.

$$V_{AB} = V_L \angle 0 = 400 \angle 0, \quad V_{BC} = 400 \angle -120, \quad V_{CA} = 400 \angle 120$$

Phase Voltages: $V_p = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94$

* angle of phase voltages lags 30° to line voltage.

$$V_{AN} = 230.94 \text{ [angle lags by } 30^\circ \text{ to } V_{AB}] = 230.94 \angle 0 - 30$$

$$\Rightarrow V_{AN} = 230.94 \angle -30$$

$$V_{BN} = 230.94 \text{ [angle } 30^\circ \text{ lags by } V_{BC}] = 230.94 \angle 120 - 30$$

$$\Rightarrow V_{BN} = 230.94 \angle -150$$

$$V_{CN} = 230.94 \text{ [angle } 30^\circ \text{ lags by } V_{CA}] = 230.94 \angle 120 - 30$$

$$\Rightarrow V_{CN} = 230.94 \angle 90$$

Neutral Shift Voltage:

$$V_{N'N} = \frac{V_{AN} Y_A + V_{BN} Y_B + V_{CN} Y_C}{Y_A + Y_B + Y_C} = \frac{\frac{V_{AN}}{Z_A} + \frac{V_{BN}}{Z_B} + \frac{V_{CN}}{Z_C}}{\frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C}}$$

$$\Rightarrow V_{N'N} = \frac{\frac{230.94 \angle -30}{10 + j0} + \frac{230.94 \angle -150}{15 + j10} + \frac{230.94 \angle 90}{0 + j5}}{\frac{1}{10 + j0} + \frac{1}{15 + j10} + \frac{1}{0 + j5}}$$

$$\Rightarrow \boxed{V_{N'N} = 199.4 \angle 46.29}$$

Actual Phase Voltages

$$V_{AN'} = V_{AN} - V_{N'N} = 230.94 \angle -30 - 199.4 \angle 46.29 \Rightarrow \text{---}$$

$$\boxed{V_{AN'} = 266.95 \angle -76.52}$$

$$V_{BN'} = V_{BN} - V_{N'A} = 230.94 \angle -150 - 199.4 \angle 46.29$$

$$\Rightarrow \boxed{V_{BN'} = 426.02 \angle -142.45}$$

$$V_{CN'} = V_{CN} - V_{N'A} = 230.94 \angle 90 - 199.4 \angle 46.29$$

$$\Rightarrow \boxed{V_{CN'} = 162.85 \angle 147.78}$$

Line Currents = Phase Currents:

$$I_a = \frac{V_{AN'}}{Z_a} = \frac{266.95 \angle -76.52}{10 + j0} \Rightarrow \boxed{I_a = 26.695 \angle -76.52}$$

$$I_b = \frac{V_{BN'}}{Z_b} = \frac{426.02 \angle -142.45}{15 + j10} \Rightarrow \boxed{I_b = 23.63 \angle -176.14}$$

$$I_c = \frac{V_{CN'}}{Z_c} = \frac{162.85 \angle 147.78}{0 + j5} \Rightarrow \boxed{I_c = 32.57 \angle 57.78}$$

Current through Neutral wire:

$$I_N = -(I_a + I_b + I_c) = -1 \times [26.695 \angle -76.52 + 23.63 \angle -176.14 + 32.57 \angle 57.78]$$

$$\Rightarrow \boxed{I_N = 0.012 \angle -160}$$

Q: Determine line currents in an unbalanced star connected load supplied from symmetrical 3 phase, 440V system. The branch impedances are $Z_R = 4 \angle 30^\circ$, $Z_Y = 10 \angle 45^\circ$ & $Z_B = 10 \angle 60^\circ$. The phase sequence is RYB.

Ans: 3-Phase Star


At source side phase

$$\text{Voltage } V_p = \frac{V_L}{\sqrt{3}}$$

& lags the line voltage by

30° .

$$V_L = 440V.$$

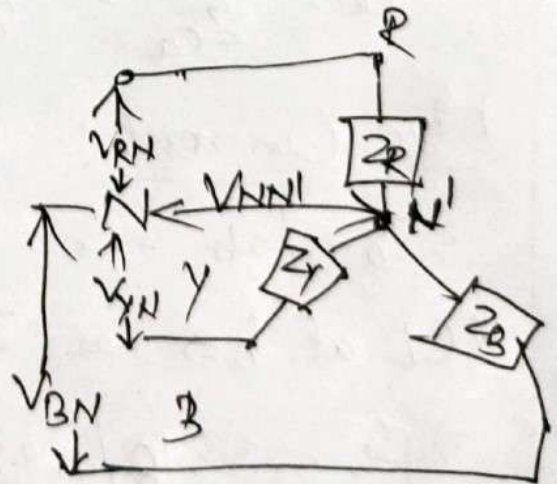

Sequence in R-Y-B $\Rightarrow V_{RY} = \frac{\text{Line Voltage}}{\sqrt{3}} = 440/\sqrt{3}$

$$V_{YB} = 440/\sqrt{3} \angle 120^\circ, \quad V_{BR} = 440/\sqrt{3} \angle 240^\circ$$

Phase Voltage = $V_p = \frac{V_L}{\sqrt{3}} = 254.03 \text{ V}$

$$V_{RN} = 254.03 \text{ [angle in } 30^\circ \text{ lagging of } V_{RY}] = 254.03 \angle 0-30^\circ$$

$$V_{YN} = 254.03 \text{ [angle in } 30^\circ \text{ lagging of } V_{YB}] = 254.03 \angle 120-30^\circ$$

$$\Rightarrow V_{YN} = 254.03 \angle -150^\circ$$

$$V_{BN} = 254.03 \text{ [angle in } 30^\circ \text{ lagging of } V_{BR}] = 254.03 \angle 240-30^\circ$$

$$\Rightarrow V_{BN} = 254.03 \angle 90^\circ$$

$$Z_R = 4 \angle 30^\circ, \quad Z_Y = 10 \angle 45^\circ, \quad Z_B = 10 \angle 60^\circ$$

Neutral Shift Voltage:

$$V_{N'N} = \frac{V_{RN} Y_R + V_{YN} Y_Y + V_{BN} Y_B}{Y_R + Y_Y + Y_B} = \frac{\frac{V_{RN}}{Z_R} + \frac{V_{YN}}{Z_Y} + \frac{V_{BN}}{Z_B}}{\frac{1}{Z_R} + \frac{1}{Z_Y} + \frac{1}{Z_B}}$$

$$= \frac{\frac{254.03 \angle -30^\circ}{4 \angle 30^\circ} + \frac{254.03 \angle -150^\circ}{10 \angle 45^\circ} + \frac{254.03 \angle 90^\circ}{10 \angle 60^\circ}}{\frac{1}{4 \angle 30^\circ} + \frac{1}{10 \angle 45^\circ} + \frac{1}{10 \angle 60^\circ}}$$

$$\Rightarrow V_{N'N} = 104.93 \angle -10.78^\circ$$

Actual Phase Voltages

$$V_{RN'} = V_{RN} - V_{N'N} = 254.03 \angle -30^\circ - 104.93 \angle -10.78^\circ$$

$$\Rightarrow V_{RN'} = 158.75 \angle -42.56^\circ$$

$$V_{YN'} = V_{YN} - V_{N'N} = 254.03 \angle -150 - 104.93 \angle -10.78$$

$$\Rightarrow V_{YN'} = 340.45 \angle -161.61$$

$$V_{BN'} = V_{BN} - V_{N'N} = 254.03 \angle 90 - 104.93 \angle -10.78$$

$$\Rightarrow V_{BN'} = 292.42 \angle 110.63$$

Line Currents = Phase Currents

~~I_a~~ $I_R = \frac{V_{RN'}}{Z_R} = \frac{158.75 \angle -42.56}{4 \angle 30}$

$$\Rightarrow I_R = 39.68 \angle -72.56$$

$$I_Y = \frac{V_{YN'}}{Z_Y} = \frac{340.45 \angle -161.61}{10 \angle 45} = 34.04 \angle -206.61$$

$$I_B = \frac{V_{BN'}}{Z_B} = \frac{292.42 \angle 110.63}{10 \angle 60} \Rightarrow I_B = 29.24 \angle 50.63$$

(iii) Initial Value Theorem:-

- It is used to find initial value of a function.
- If $x(t)$ is a function, this can be used to find $x(0)$ if $X(s)$ is given.

$$\text{If } L\{x(t)\} = X(s), \text{ then } x(0) = \lim_{s \rightarrow \infty} sX(s)$$

Scanned with CamScanner

Proof:- We know:- $L\left\{\frac{dx(t)}{dt}\right\} = sX(s) - x(0)$

$$L\left\{\frac{dx(t)}{dt}\right\} = \int_0^{\infty} \frac{dx(t)}{dt} e^{-st} dt = sX(s) - x(0)$$

Applying $\lim_{s \rightarrow \infty}$ on both sides we get:-

$$\Rightarrow \lim_{s \rightarrow \infty} \int_0^{\infty} \frac{dx(t)}{dt} e^{-st} dt = \lim_{s \rightarrow \infty} [sX(s) - x(0)]$$

$$\Rightarrow 0 = \lim_{s \rightarrow \infty} [sX(s)] - x(0) \left[e^{-st} \Big|_{s \rightarrow \infty} = 0 \right]$$

$$\Rightarrow \boxed{x(0) = \lim_{s \rightarrow \infty} sX(s)}$$

(iii) Final Value Theorem:-

- It is used to find the final value of function.
- If $x(t)$ is a function, this can be used to find $x(\infty)$ if $X(s)$ is given.

$$\text{If } L\{x(t)\} = X(s), \text{ then } \lim_{t \rightarrow \infty} x(t) = \lim_{s \rightarrow 0} sX(s)$$

Proof:- $L\left\{\frac{dx(t)}{dt}\right\} = \int_0^{\infty} \frac{dx(t)}{dt} e^{-st} dt = sX(s) - x(0)$

Taking $\lim_{s \rightarrow 0}$ both the sides we get:-

$$\lim_{s \rightarrow 0} \int_0^{\infty} \frac{dx(t)}{dt} e^{-st} dt = \lim_{s \rightarrow 0} [sX(s) - x(0)] \quad \text{--- (1)}$$

$$\Rightarrow \int_0^{\infty} \frac{dx(t)}{dt} \left[\lim_{s \rightarrow 0} e^{-st} \right] dt = \int_0^{\infty} \frac{dx(t)}{dt} \cdot 1 dt = [x(t)]_0^{\infty}$$
$$= x(\infty) - x(0) \quad \text{--- (2)}$$

Scanned with CamScanner

Applying this in (1) we get:-

$$x(\infty) - x(0) = \lim_{s \rightarrow 0} [sX(s) - x(0)] = \lim_{s \rightarrow 0} sX(s) - x(0)$$

$$\Rightarrow \boxed{x(\infty) = \lim_{s \rightarrow 0} sX(s)}$$

Q: Using Initial & final value theorem find $f(0)$ & $f(\infty)$ for following functions.

(i) $\frac{s^2 + 7s + 5}{s(s^2 + 3s^2 + 4s + 2)}$ (ii) $\frac{s(s+4)(s+8)}{(s+1)(s+6)}$

Ans: (i) $F(s) = \frac{s^2 + 7s + 5}{s(s^2 + 3s^2 + 4s + 2)}$

Initial Value theorem \neq

$$f(0) = \lim_{s \rightarrow \infty} s F(s) = \lim_{s \rightarrow \infty} s \cdot \frac{s^2 + 7s + 5}{s(s^2 + 3s^2 + 4s + 2)}$$

$$= \lim_{s \rightarrow \infty} \frac{s^3 [1 + \frac{7}{s} + \frac{5}{s^2}]}{s^3 [1 + \frac{3}{s} + \frac{4}{s^2} + \frac{2}{s^3}]} = \frac{1 + \frac{7}{\infty} + \frac{5}{\infty^2}}{1 + \frac{3}{\infty} + \frac{4}{\infty^2} + \frac{2}{\infty^3}}$$

$\Rightarrow f(0) = 1$

Final value theorem:

$$f(\infty) = \lim_{s \rightarrow 0} s F(s) = \lim_{s \rightarrow 0} s \cdot \frac{s^2 + 7s + 5}{s(s^2 + 3s^2 + 4s + 2)}$$

$$\Rightarrow f(\infty) = \frac{0^2 + 7 \cdot 0 + 5}{0^2 + 3 \cdot 0^2 + 4 \cdot 0 + 2} \Rightarrow f(\infty) = \frac{5}{2}$$

(ii) $F(s) = \frac{s(s+4)(s+8)}{(s+1)(s+6)}$

Initial Value Theorem:

$$f(0) = \lim_{s \rightarrow \infty} s F(s) = \lim_{s \rightarrow \infty} s \cdot \frac{s(s+4)(s+8)}{(s+1)(s+6)}$$

$$f(0) = \lim_{s \rightarrow \infty} \frac{s^2 \cdot s(1 + \frac{4}{s})(1 + \frac{8}{s})}{s(1 + \frac{1}{s})s(1 + \frac{6}{s})} = \lim_{s \rightarrow \infty} \frac{s^2 (1 + \frac{4}{s})(1 + \frac{8}{s})}{s^2 (1 + \frac{1}{s})(1 + \frac{6}{s})}$$


$$\Rightarrow f(0) = \frac{\infty^2 [1 + \frac{4}{\infty}] [1 + \frac{8}{\infty}]}{(1 + \frac{1}{\infty})(1 + \frac{6}{\infty})} \Rightarrow f(0) = \infty$$

Final Value Theorem:


$$f(\infty) = \lim_{s \rightarrow 0} s \cdot F(s) = \lim_{s \rightarrow 0} s \cdot \frac{s(s+4)(s+8)}{(s+1)(s+6)}$$

$$= \lim_{s \rightarrow 0} \frac{s^2 (s+4)(s+8)}{(s+1)(s+6)} = \frac{0^2 (0+4)(0+8)}{(0+1)(0+6)}$$


$\Rightarrow f(\infty) = 0$

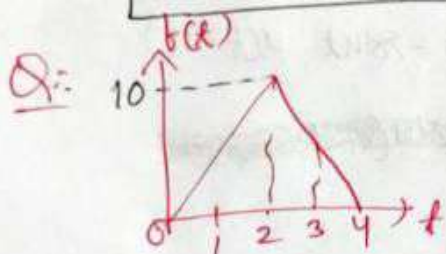

Find Laplace of $f(t)$.

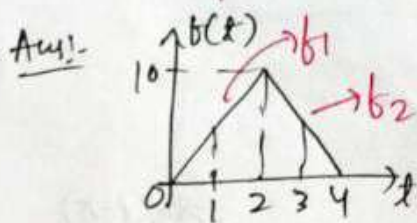


b_1

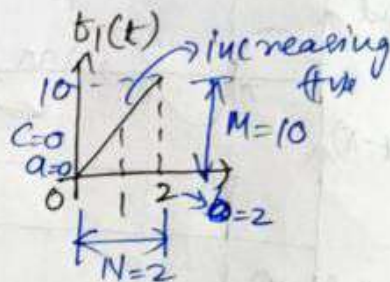

$$b_1 = +\frac{M}{N}(t-c)[u(t-a) - u(t-b)]$$

$$\Rightarrow b_1 = \frac{10}{2}(t-0)[u(t-0) - u(t-2)]$$
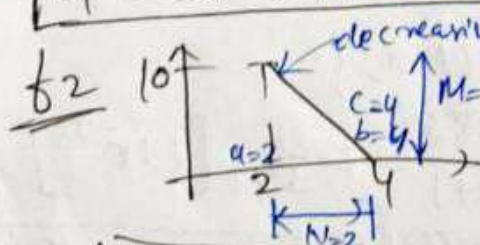
$$\Rightarrow \boxed{b_1 = 5t u(t) - 5t u(t-2)}$$



$$b_2 = -\frac{M}{N}(t-c)[u(t-a) - u(t-b)]$$

$$\Rightarrow b_2 = -\frac{10}{2}(t-4)[u(t-2) - u(t-4)]$$

$$\Rightarrow \boxed{b_2 = -5(t-4)u(t-2) - 5(t-4)u(t-4)}$$

$$f(t) = b_1(t) + b_2(t) = 5t u(t) - 5t u(t-2) - 5(t-4)u(t-2) - 5(t-4)u(t-4)$$

$$= 5t u(t) - 5u(t-2)[t + t-4] - 5t u(t-4)$$

$$= 5t u(t) - 5u(t-2)(2t-4) - 5t u(t-4)$$

$$= 5t u(t) - 10u(t-2)(t-2) - 5t u(t-4)$$

$$\Rightarrow f(t) = 5t u(t) - 10u(t-2) - 5t u(t-4)$$

$$\Rightarrow F(s) = L\{5t u(t)\} - L\{10u(t-2)\} - L\{5t u(t-4)\}$$

$$\Rightarrow \boxed{F(s) = \frac{5}{s^2} - \frac{10e^{-2s}}{s^2} - \frac{5e^{-4s}}{s^2}}$$


$$\Rightarrow \boxed{F(s) = \frac{5}{s^2} [1 - 2e^{-2s} - e^{-4s}]}$$

Q.3 $f(t)$



Find Laplace of following wave form.

Ans:

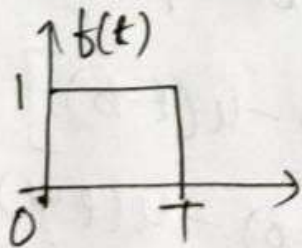

$$b(t) = 1 [u(t) - u(t-T)]$$

Taking Laplace

$$b(t) = u(t) - u(t-T)$$

$$F(s) = L\{b(t)\} = L\{u(t)\} - L\{u(t-T)\}$$

$$\Rightarrow F(s) = \frac{1}{s} - \frac{e^{-s}}{s} \Rightarrow \boxed{F(s) = \frac{1}{s}(1 - e^{-s})}$$

Q: Find inverse Laplace of following:

(i) $\frac{s^2+5}{s(s^2+4s+4)}$ (ii) $\frac{2s+6}{s^2+6s+25}$

Ans: $\frac{s^2+5}{s(s^2+4s+4)} = \frac{s^2+5}{s(s^2+2\cdot s\cdot 2+2^2)}$

$F(s) = \frac{s^2+5}{s(s+2)^2} \Rightarrow$ using partial fraction

$$\frac{s^2+5}{s(s+2)^2} = \frac{A_1}{s} + \frac{A_2}{(s+2)^2} + \frac{A_3}{(s+2)}$$

$$\Rightarrow A_1 = \left. \frac{s^2+5}{s(s+2)^2} \right|_{s=0} \Rightarrow A_1 = \frac{5}{4}$$

$$A_2 = \left. (s+2)^2 \cdot \frac{s^2+5}{s(s+2)^2} \right|_{\substack{s+2=0 \\ s=-2}} \Rightarrow A_2 = \frac{(-2)^2+5}{-2} = \frac{9}{-2} = -\frac{9}{2}$$

$$A_3 = \left. \frac{d}{ds} \left[(s+2)^2 \cdot \frac{s^2+5}{s(s+2)^2} \right] \right|_{s=-2} = \left. \frac{d}{ds} \left[\frac{s^2+5}{s} \right] \right|_{s=-2}$$

$$\Rightarrow A_3 = \left. \frac{s \left[\frac{d}{ds}(s^2+5) \right] - (s^2+5) \frac{d}{ds}s}{s^2} \right|_{s=-2} = \left. \frac{\frac{d}{dx}(u) = \frac{u \frac{dv}{dx} - v \frac{du}{dx}}{v^2}}{s^2} \right|_{s=-2} = \frac{2s^2 - s^2 - 5}{s^2} \Big|_{s=-2} = \frac{s^2-5}{s^2} \Big|_{s=-2}$$

$$A_3 = \frac{(-2)^2-5}{(-2)^2} \Rightarrow A_3 = -\frac{1}{4}$$

$$\text{So } F(s) = \frac{s^2+5}{s(s+2)^2} = \frac{A_1}{s} + \frac{A_2}{(s+2)^2} + \frac{A_3}{s+2}$$

$$\Rightarrow F(s) = \frac{5/4}{s} + \frac{-9/2}{(s+2)^2} + \frac{-1/4}{s+2}$$

Inverse Laplace

$$\Rightarrow L^{-1}[F(s)] = L^{-1}\left[\frac{5/4}{s}\right] - L^{-1}\left[\frac{9/2}{(s+2)^2}\right] - L^{-1}\left[\frac{1/4}{s+2}\right]$$

$$\Rightarrow \cancel{f(t) = \frac{5}{4}u(t)}$$

$$f(t) = \frac{5}{4}u(t) - \frac{9}{2}t e^{-2t} - \frac{1}{4}e^{-2t}u(t)$$

$$\begin{cases} L^{-1}\left[\frac{1}{s}\right] = u(t) \\ L^{-1}\left[\frac{1}{(s+a)^2}\right] = t e^{-at}u(t) \\ L^{-1}\left[\frac{1}{(s+a)}\right] = e^{-at}u(t) \end{cases}$$

ii) $F(s) = \frac{2s+6}{s^2+6s+25}$

$$= \frac{2s+6}{s^2+2\cdot 3\cdot s+3^2+4^2} = \frac{2(s+3)}{s^2+2\cdot 3\cdot s+9+16}$$

$$F(s) = \frac{2(s+3)}{(s+3)^2+4^2}$$

$$\left[L^{-1}\left[\frac{s+a}{(s+a)^2+b^2}\right] = \cos bt e^{-at} \right]$$

inverse Laplace

$$L^{-1}[F(s)] = L^{-1}\left[\frac{2(s+3)}{(s+3)^2+4^2}\right] \Rightarrow \cancel{f(t) = 2e^{-3t} \sin 4t}$$

$$f(t) = 2e^{-3t} \cos 4t$$