
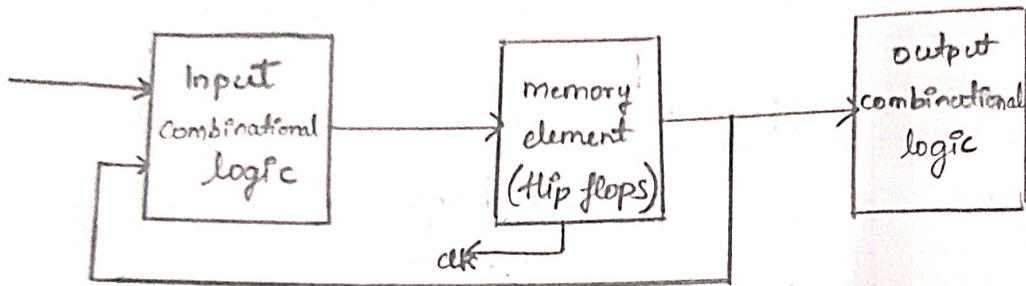


Internal Assessment Test - III

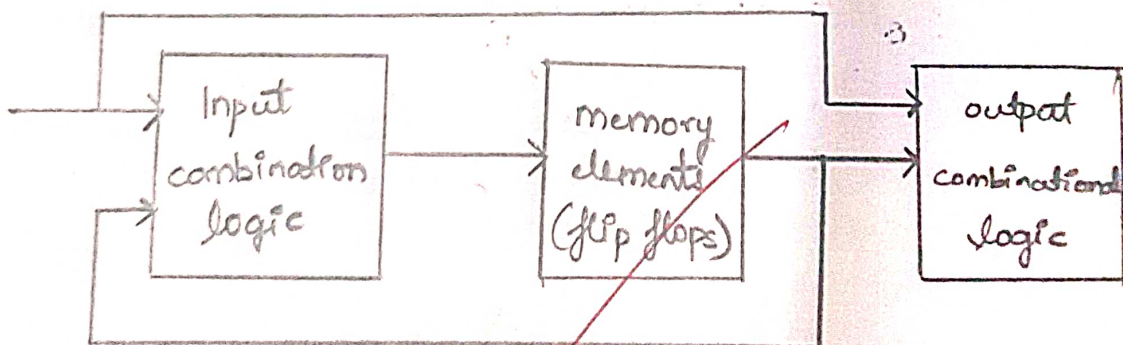1) Moore: when the output of the sequential circuit is depend on the only present of state of sequential circuit it is known as moore model.



Mealy model: when the output of the sequential circuit is depend on the both present state and inputs of sequential circuit it is known as mealy model.



Moose model.

i) Its output function is depend on the present state.

ii) Inputs will not effect the function of output.

iii) Number of ~~states~~ ^{state} requi-
-red to implementing
the same function is
more.


Mealy model.

i) Its output function is depend on both present and input states.

iii) Inputs will effect the function of output.

iii) less number of states
required for implementing the
same function.

3)

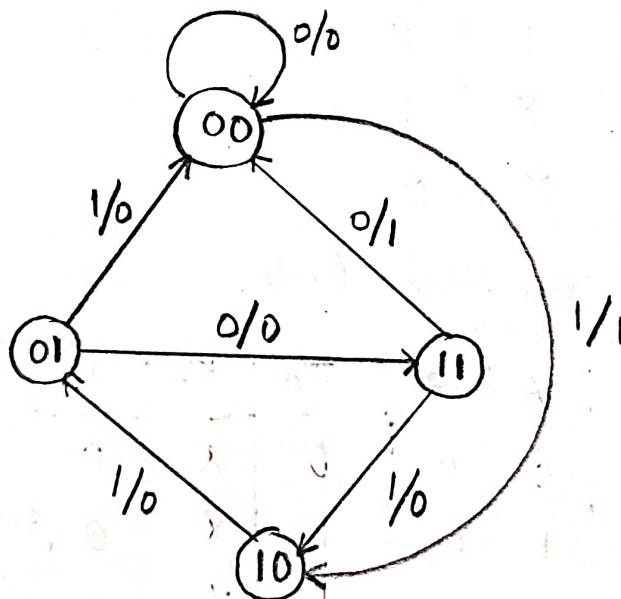

No of flip flop required $\Rightarrow 4$ states $\Rightarrow 2^2 = 2$ flip flops.

Step 1:

Write the state table.

Present stage		Next stage				output	
A	B	$x=0$		$x=1$		$x=0$	$x=1$
		A	B	A	B		
0	0	0	0	1	0	0	1
0	1	1	1	0	0	0	0
1	0	1	0	0	1	1	0
1	1	0	0	1	0	1	0

step 2: write excitation table of JK

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

step 3: write transition table.

Present stage			Next stage		output				
A	B	X	A	B	J_A	K_A	J_B	K_B	Y
0	0	0	0	0	0	X	0	X	0
0	0	1	1	0	1	X	0	X	1
0	1	0	1	1	1	X	X	0	0
0	1	1	0	0	0	X	X	1	0
1	0	0	1	0	X	0	0	X	1
1	0	1	0	1	X	1	1	X	0
1	1	0	0	0	X	1	X	1	1
1	1	1	1	0	X	0	X	1	0

step 4: write the k-map.

	00	01	11	10
A	0	1	0	1
X	1	1	1	1

$$\begin{aligned} J_A &= \bar{B}X + BX \\ &= B \oplus X \end{aligned}$$

	00	01	11	10
A	1	1	1	1
X	0	1	0	1

$$K_A = B \oplus X$$

	00	01	11	10
A	0	0	1	1
X	0	1	1	1

$$J_B = AX$$




	00	01	11	10
A	1	1	1	0
X	1	1	1	1

$$\begin{aligned} K_B &= B + X \\ K_B &= X + A\bar{X} \end{aligned}$$

	00	01	11	10
A	0	1	0	0
X	1	0	0	1

$$Y = \bar{B}X + A\bar{X}$$

10 Step 5: draw sequential circuit.

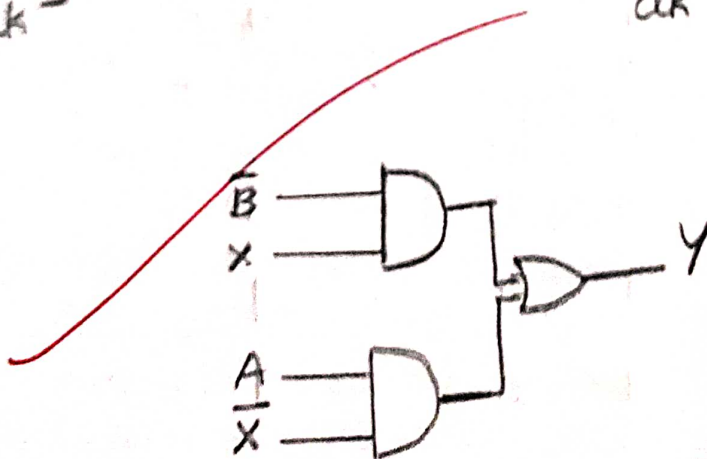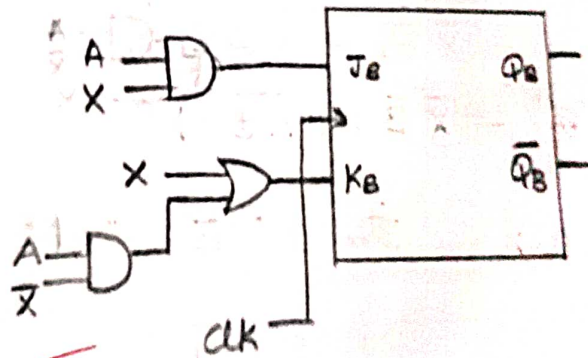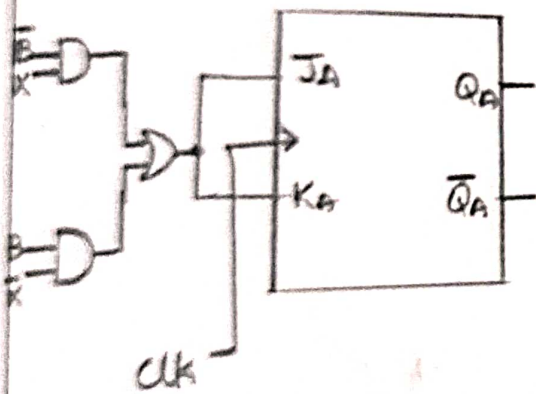

4)

step 1: write equations

$$J_A = B$$

$$J_B = \bar{X}$$

$$K_A = \bar{X}B$$

$$K_B = A \oplus X$$

$$F = A \oplus B$$

step 2: write transition equations,

$$\Rightarrow JK \Rightarrow Q^+ = J\bar{Q} + KQ$$

$$\begin{aligned} Q_A^+ &= J_A \bar{Q}_A + K_A Q_A \\ &= B \bar{Q}_A + \bar{X}B \cdot Q_A \\ &= B \bar{Q}_A + (X + \bar{B}) Q_A \\ &= B \bar{A} + (X + \bar{B}) A \end{aligned}$$

$$\begin{aligned} Q_B^+ &= J_B \bar{Q}_B + K_B Q_B \\ &= \bar{X} \bar{Q}_B + (A \oplus X) Q_B \end{aligned}$$

$$Q_B^+ = \bar{X} \bar{B} + (A \oplus X) B$$


step 3: write ~~the~~ state table.

Present stage		Next state				output
A	B	x=0		x=1		y = A ⊕ B
		A	B	A	B	
0	0	0	1	0	0	0
0	1	1	0	1	0	1
1	0	1	1	1	0	1
1	1	0	0	1	1	0


draw state table:

Present state	Next state		output
	b	a	
a	b	a	0
b	d	c	1
c	d	c	1
d	a	d	0

steps: draw state diagram:

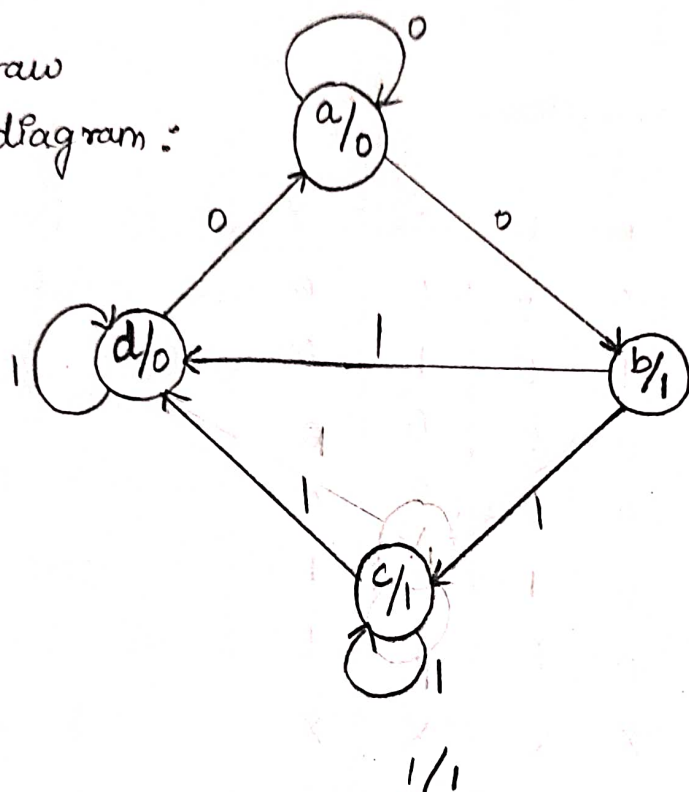

10

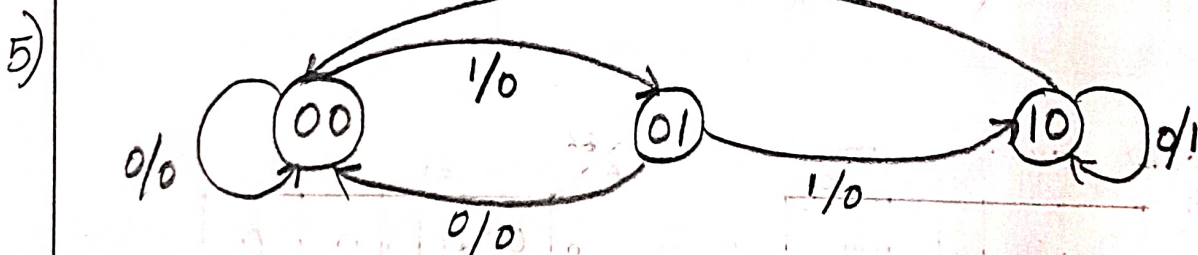

write state table:

Present stage		Next stage				output	
A	B	x=0		x=1		x=0	x=1
		A	B	A	B	A	B
0	0	0	0	0	1	0	0
0	1	0	0	1	0	0	0
1	0	1	0	0	0	1	1

Write excitation table of D

Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

Step 3: write transition table:

Present			Next		output		
A	B	X	A	B	D_A	D_B	Y
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	0	0
0	1	1	1	0	1	0	0
1	0	0	1	0	1	0	1
1	0	1	0	0	0	0	1
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X


A \ BX	00	01	11	10
0	0	0	1	0
1	1	0	X	X

$$D_A = BX + \bar{X}$$

A \ BX	01	10	11	10
0	0	1	0	0
1	0	0	X	X

$$D_B = \bar{A}\bar{B}X$$

A \ BX	00	01	11	10
0	0	0	0	0
1	1	1	X	X

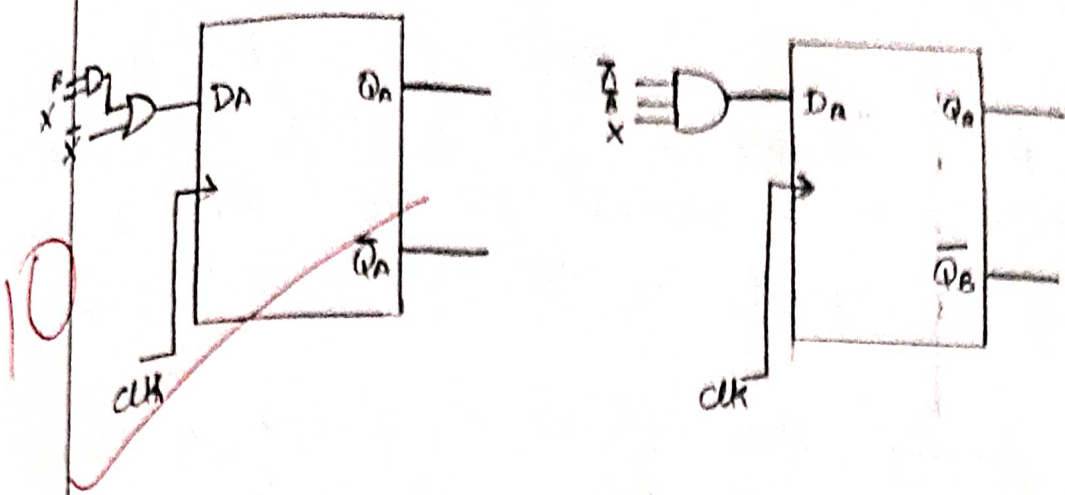

2) Write short notes on EPROM, flash memory & different types of RAM and ROM.

→ EPROM:

(Erasable Programming Read only memory).


EPROM uses a mos circuitry. It stores a 1's or 0's in packet of charge in the Ic chip layer. It is used by EPROM programmer. The special effect in EPROM is the data storage can be erased by exposing it to UV light through quartz in the chip for 15-20 minutes.

The data erasable is not selected, if erased the entire data is lost. but it can reprogrammed. It is suitable for experimental project, college laboratories because it can reprogram data many times over.

Flash memory:

Flash memory is a type of read write memories. It is possible to read a single cell, but while writing it is possible for entire block of cells. Flash memory is depend on transistor with trapped charge.

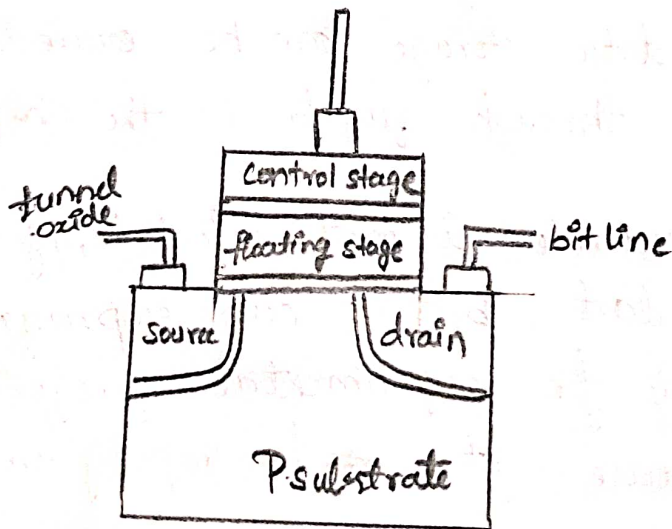The floating stage works in presence & absence of charge. In absence of charge it works like the normal mosfet. If +ve charge in control stage it makes a channel between drain and source and current passes. If floating stage is negative it shields the charge somewhat from control stage, and create a P-substrate between source and drain.



RAM (Random access memory).



i) static RAM.

ii) Dynamic RAM

ROM (Read only memory).

i) PROM (Programming Read only memory)

ii) EPROM (Erasable Programming read only memory.)

10