

Scheme of Evaluation
Internal Assessment Test 3


Sub:	Power Electronics					Code:	18EE53		
Date:	25.01.2022	Duration:	90mins	Max Marks:	50	Sem:	V	Branch:	EEE

Note: Answer Any Five Questions

Question #	Description
1a	<p>Explain the operation of step-up chopper. Draw the relevant waveform. Derive an expression for average output voltage.</p> <ul style="list-style-type: none"> ➤ Step-up chopper is a static device whose average output DC voltage is greater than its input DC voltage. ➤ A converter can be used to step-up a dc voltage and an arrangement for step-up operation. When switch SW is closed for time t, the inductor current rises and energy is stored in the inductor L. ➤ If the switch is opened for time t_1, the energy stored in the inductor is transferred to load through diode D and the inductor current falls <div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"> <p>Step-up Chopper</p> <p>(a) Step-up arrangement</p> </div> <div style="text-align: center;"> <p>(b) Current waveform</p> </div> </div> <div style="text-align: center; margin-top: 20px;"> </div>


Mode 1: Switch is ON

- When chopper (CH) is switched ON, the current will flow through the closed path formed by supply source V_s , inductor L and chopper CH.
- During this period, no current will flow through the load.
- Only source current i_s will flow and the value of load current i_o will be ZERO during the ON period.
- Also, during the T_{ON} period, energy is stored in the inductor L .
- This energy storage in L is essential to boost the load output voltage above the source voltage.
- Therefore, a large value of L is essential in a step-up chopper.

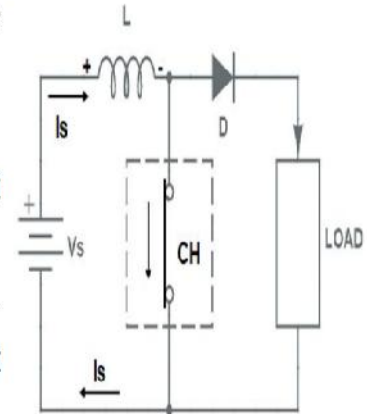

Mode 2: Switch is OFF

- When the chopper CH is switched OFF, the current through the L can not reduce instantaneously rather it decays exponentially.
- Due to this behavior of L , it will force the current through the diode D and load for the entire time period T_{OFF} .
- Since, the current through the inductor L tends to decrease, the polarity of the emf induced in inductor L is reversed as shown in above figure.
- As a result, the voltage across the load becomes equal to the sum of source voltage and emf induced in inductor.
- Thus, the output voltage exceeds the source voltage V_s .
- The load / output voltage may be written as below.

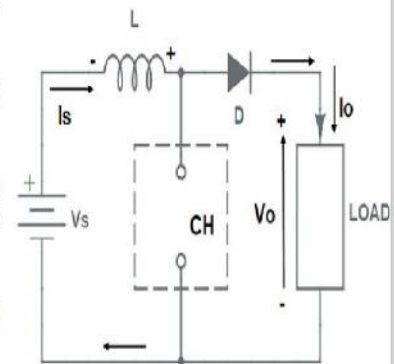

$$V_o = V_s + L(di/dt)$$

Average Output Voltage Equation

When the converter is turned on, the voltage across the inductor is

$$v_L = L \frac{di}{dt} \Rightarrow di = \frac{v_L}{L} dt = \frac{V_s}{L} t_1$$

and this gives the peak-to-peak ripple current in the inductor as

$$\Delta I = \frac{V_s}{L} t_1$$

The average output voltage is

$$\begin{aligned} v_o &= V_s + L \frac{\Delta I}{t_2} & \Delta I &= \frac{V_s}{L} t_1 \\ &= V_s \left(1 + \frac{t_1}{t_2} \right) = V_s \left(1 + \frac{k\tau}{(1-k)\tau} \right) & t_1 &= k\tau \\ &= V_s \frac{1}{1-k} & t_2 &= (1-k)\tau \end{aligned}$$

$$v_o = V_s \frac{1}{1-k}$$

K value can be changed from 0 to 1.

1

1b

A step-up chopper has an input voltage of 220V and output voltage is 640V. If the non-conducting time of thyristor is 100µsec. Calculate the pulse width of the output voltage. If the pulse width is halved, for constant frequency operation. Calculate the new output voltage.

$$1b) V_s = 220V; V_a = 640V; T_{off} = 100\mu\text{sec}$$

Step-up-chopper:

$$V_a = \frac{V_s}{1-K}$$

$$640 = \frac{220}{1-K}$$

$$640 - 640K = 220$$

$$-640K = 220 - 640$$

$$\boxed{K = 0.656}$$

$$K = \frac{T_{on}}{T_{on} + T_{off}} = \frac{T_{on}}{T}$$

$$T_{off} = 100\mu\text{s}$$

$$0.656 = \frac{T_{on}}{T_{on} + 100 \times 10^{-6}}$$

$$\boxed{T_{on} = 191\mu\text{sec}}$$

Pulse width is halved,

$T_{on} \Rightarrow \text{half}$

Constant frequency; T is constant

$$T = T_{on} + T_{off}$$

$$T = 191\mu\text{s} + 100\mu\text{sec}$$

$$\boxed{T = 291\mu\text{s}}$$

$$T_{on} \text{ is half; } T_{on} = \frac{191}{2} = 95.5\mu\text{s}$$


$$K = \frac{T_{on}}{T} = \frac{95.5}{291} = \underline{\underline{0.328}}$$

New
o/p Voltage.

$$\boxed{V_a = \frac{220}{1-0.328} = 327.38V}$$

Explain working of step-down chopper. Draw the relevant waveform. Derive an expression for average and output rms voltage.

Step-down Chopper with RL Load

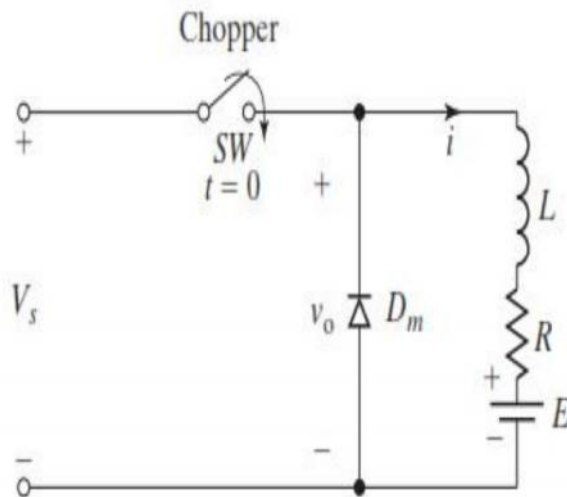

➤A dc-dc converter with an RL load is shown in Figure.

➤The operation of the converter can be divided into two modes.

➤During mode 1, the converter is switched on and the current flows from the supply to the load.

➤During mode 2, the converter is switched off and the load current continues to flow through freewheeling diode D

2a

1

Modes of Operation


Current may be

- Continuous
- Discontinuous

Assumption

load current rises linearly.

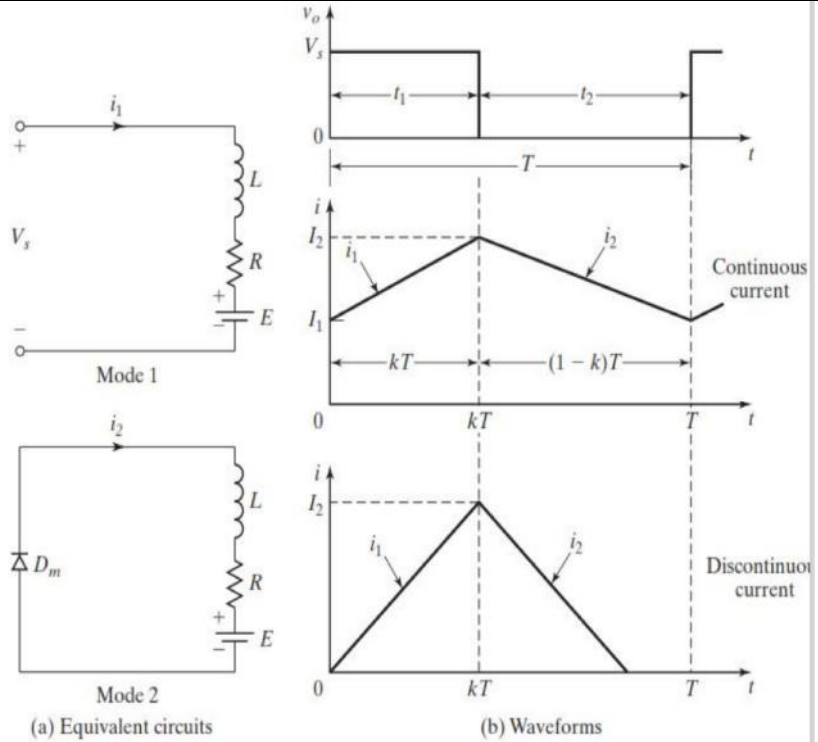
However, the current flowing through an RL load rises or falls exponentially with a time constant.



(a) Equivalent circuits

(b) Waveforms

The load time constant $(\tau = L/R)$

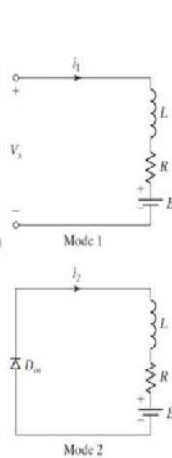

The load current for mode 1 can be found from

$$V_s = Ri_1 + L \frac{di_1}{dt} + E$$

which with initial current $i_1(t = 0) = I_1$ gives the load current as

$$i_1(t) = I_1 e^{-tR/L} + \frac{V_s - E}{R} (1 - e^{-tR/L}) \quad (5.19)$$

This mode is valid $0 \leq t \leq t_1 (=kT)$; and at the end of this mode, the load current becomes

$$i_1(t = t_1 = kT) = I_2 \quad (5.20)$$

The load current for mode 2 can be found from

$$0 = Ri_2 + L \frac{di_2}{dt} + E$$

With initial current $i_2(t = 0) = I_2$ and redefining the time origin (i.e., $t = 0$) at the beginning of mode 2, we have

$$i_2(t) = I_2 e^{-tR/L} - \frac{E}{R} (1 - e^{-tR/L}) \quad (5.21)$$

This mode is valid for $0 \leq t \leq t_2 [(1 - k)T]$. At the end of this mode, the load current becomes

$$i_2(t = t_2) = I_3 \quad I_3 = I_1 \quad (5.22)$$

A step-down chopper with resistive load of 20Ω and the input voltage is $200V$. When the converter switch remains ON its voltage drop is $1V$ and chopping frequency is $2KHz$, if the duty cycle is 50% determine, 1) Average output Voltage 2) RMS output voltage 3) Chopper efficiency. 4) effective input resistance.

2b) Step down chopper:
 $R = 20 \Omega$; $V_s = 200V$; $V_T = 1V$.
 $f = 2kHz$; $K = 50\% = 0.5$

1) Average o/p Voltage:

$$V_o = K V_s = 0.5 [200 - 1]$$

$$V_o = 0.5 \times 199 = 99.5V$$

2) Rms o/p Voltage:

$$V_o = \sqrt{K} \times (V_s - V_T)$$

$$= \sqrt{0.5} \times [200 - 1]$$

$$V_o = 140.7V$$

3) Converter efficiency:

$$\eta = P_o / P_i$$

$$P_o = K \frac{V_s^2}{R} = \frac{K [V_s - V_T]^2}{R}$$

$$= \frac{0.5 \times (199)^2}{20} = 990W$$

$$R_i = \frac{20}{0.5} = 40 \Omega$$

$$P_i = V_s I_s$$

$$= V_s \times \frac{V_s - V_T}{R_i}$$

$$P_i = 200 \times \frac{199}{40} = 995W$$

$$\eta = \frac{990}{995} = 99.5\%$$

2b

1

1

1

1

1


With circuit diagram and waveforms, explain the operation of class D chopper and Four quadrant chopper.

Class D Chopper

- The load voltage is always negative.
- The load current is either positive or negative
- S3 and D2 operate to yield both a negative voltage and a load current.
- When S3 is closed, a negative current flow through the load.
- When S3 is opened, the load current freewheels through diode D2.
- S2 and D3 operate to yield a negative voltage and a positive load current.
- When S2 is closed, a positive load current flow.
- When S2 is opened, the load current freewheels through diode D3.
- It is important to note that the polarity of E must be reversed for this circuit to yield a negative voltage and a positive current.
- This is a negative two-quadrant converter.
- This converter can also operate as a rectifier or as an inverter.
- The load voltage is always negative.
- The load current is either positive or negative
- S3 and D2 operate to yield both a negative voltage and a load current.
- When S3 is closed, a negative current flow through the load. • When S3 is opened, the load current freewheels through diode D2
- S2 and D3 operate to yield a negative voltage and a positive load current. • When S2 is closed, a positive load current flow.
- When S2 is opened, the load current freewheels through diode D3.
- It is important to note that the polarity of E must be reversed for this circuit to yield a negative voltage and a positive current.

3


3

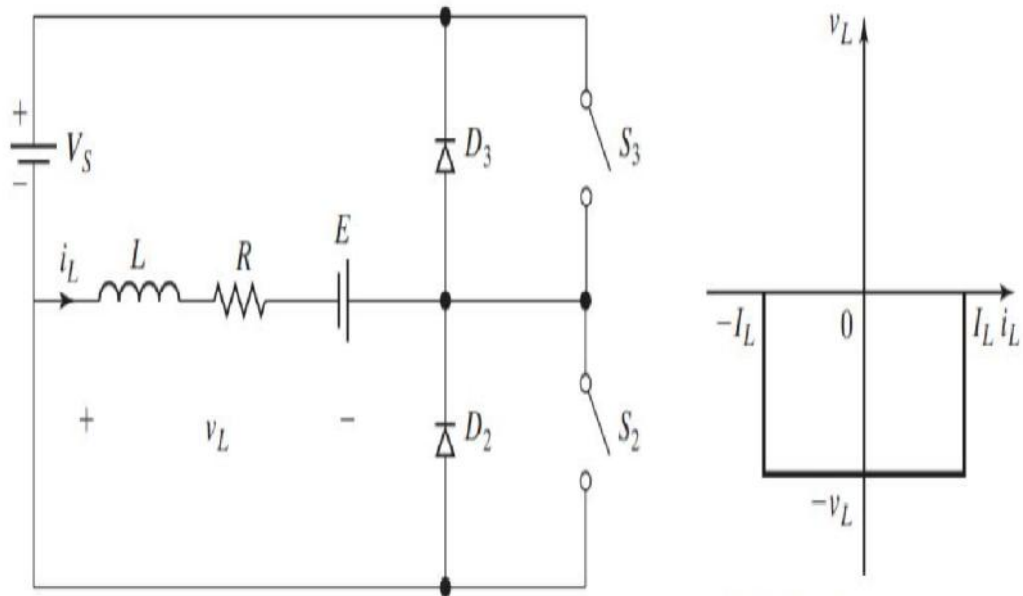

2

Four-quadrant converter / Class E Chopper

- The load current is either positive or negative
- The load voltage is also either positive or negative.
- One first and second quadrant converter and one third and fourth quadrant converter can be combined to form the four-quadrant converter.
- For operation in the fourth quadrant, the direction of the battery E must be reversed.
- This converter forms the basis for the single-phase full-bridge inverter.

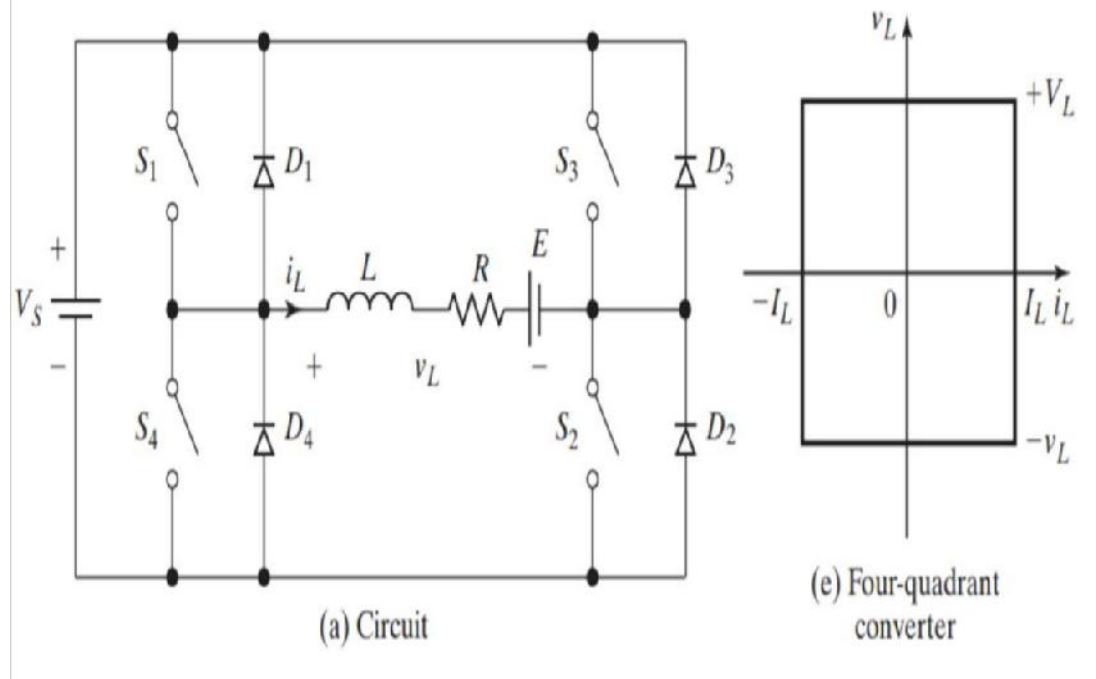


With the neat circuit diagram and waveforms, Explain the operation of single-phase full bridge inverter supplying resistive a load.


Single Phase Bridge Inverter

- Full bridge single phase inverter is a switching device that **generates a square wave AC output voltage** on the application of **DC input** by adjusting the **switch turning ON and OFF** based on the appropriate switching sequence, where the output voltage generated is of the form **$+V_s, -V_s$, Or 0** .
- **A single-phase bridge voltage-source inverter (VSI)**
- It consists of four choppers ($Q_1 D_1, Q_2 D_2, Q_3 D_3, Q_4 D_4$).
- When transistors Q_1 and Q_2 are turned on simultaneously, the input voltage V_s appears across the load.
- If transistors Q_3 and Q_4 are turned on at the same time, the voltage across the load is reversed and is $-V_s$.


Single Phase Bridge Inverter

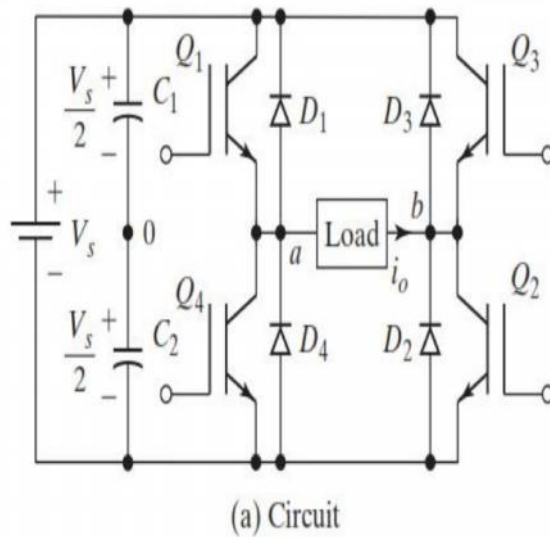

Mode 1

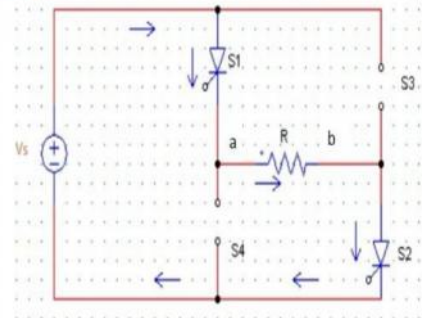

Mode 2

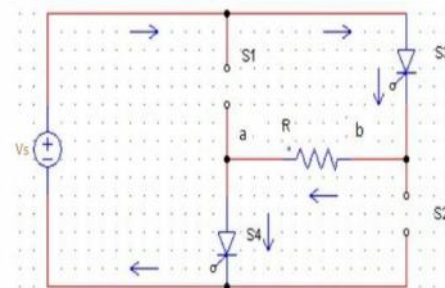

Mode 1 (0 to T/2):-


- During this mode switch **S1** and switch **S2** are **ON** and switch **S3** and switch **S4** are **OFF** From period 0 to T/2.
- Current flowing path during this mode is $V_s - S1 - a - R(\text{load resistor}) - b - S2 - V_s$.

- Voltage across the load resistor is positive V_s . ($V_o = V_s$)

Mode 2 (T/2 to T):-

- During this mode switch **S3** and switch **S4** are **ON** and switch **S1** and switch **S2** are **OFF** From period T/2 to T.
- Current flowing path during this mode is $V_s - S3 - b - R(\text{load resistor}) - a - S4 - V_s$.

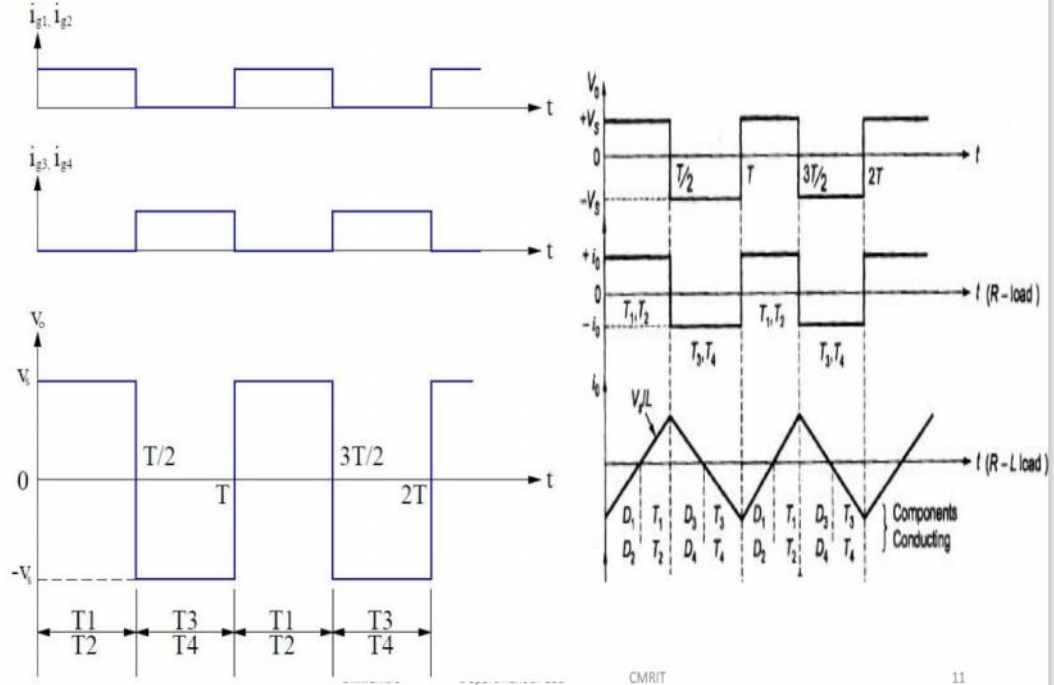- Voltage across the load resistor is negative V_s . ($V_o = -V_s$)



2

Switching States of single phase full bridge inverter

Switch States for a Single-Phase Full-Bridge Voltage-Source Inverter

State	State No.	Switch State*	v_{ao}	v_{bo}	v_o	Components Conducting
S_1 and S_2 are on and S_4 and S_3 are off	1	10	$V_S/2$	$-V_S/2$	V_S	S_1 and S_2 if $i_o > 0$ D_1 and D_2 if $i_o < 0$
S_4 and S_3 are on and S_1 and S_2 are off	2	01	$-V_S/2$	$V_S/2$	$-V_S$	D_4 and D_3 if $i_o > 0$ S_4 and S_3 if $i_o < 0$
S_1 and S_3 are on and S_4 and S_2 are off	3	11	$V_S/2$	$V_S/2$	0	S_1 and D_3 if $i_o > 0$ D_1 and S_3 if $i_o < 0$
S_4 and S_2 are on and S_1 and S_3 are off	4	00	$-V_S/2$	$-V_S/2$	0	D_4 and S_2 if $i_o > 0$ S_4 and D_2 if $i_o < 0$
$S_1, S_2, S_3,$ and S_4 are all off	5	off	$-V_S/2$ $V_S/2$	$V_S/2$ $-V_S/2$	$-V_S$ V_S	D_4 and D_3 if $i_o > 0$ D_1 and D_2 if $i_o < 0$

2

With the neat circuit diagram and waveforms, Explain the 180° mode of operation for three phase inverter. Give the expression for line and phase voltages for one cycle.

Three Phase Bridge Inverters


- A three-phase output can be obtained from a configuration of **six transistors and six diodes**.
- Two types of control signals can be applied to the transistors:
 - 180° conduction or 120° conduction.
- The 180° conduction has better utilization of the switches and is the preferred method.
- This circuit topology is often known as a three-phase bridge inverter and is used in many applications, including renewable energy systems.
- The rectifier converts the ac voltage of the wind generator to a dc voltage and the voltage source inverter (VSI) converts the dc voltage into three-phase ac voltages to match with ac grid voltage and frequency.

1

5

2

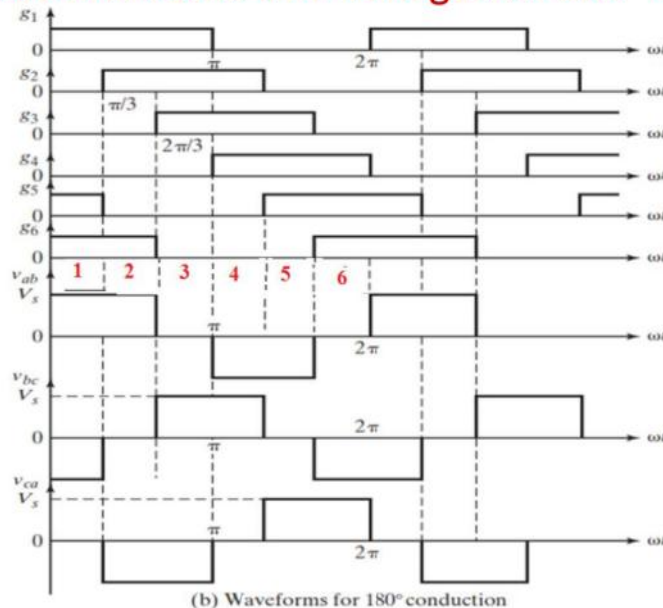Gate Pulse and Line Voltages for 180° Conduction



Thus, the resulting ac output line voltages are


$V_s, 0, \text{ and } -V_s$

$V_{ab} - Q1 Q6 +V_s$
& $Q3 Q4 -V_s$

$V_{bc} - Q3 Q2 +V_s$
& $Q5 Q6 -V_s$

$V_{ca} - Q5 Q4 +V_s$
& $Q1 Q2 -V_s$

Phase Voltages for 180° Conduction

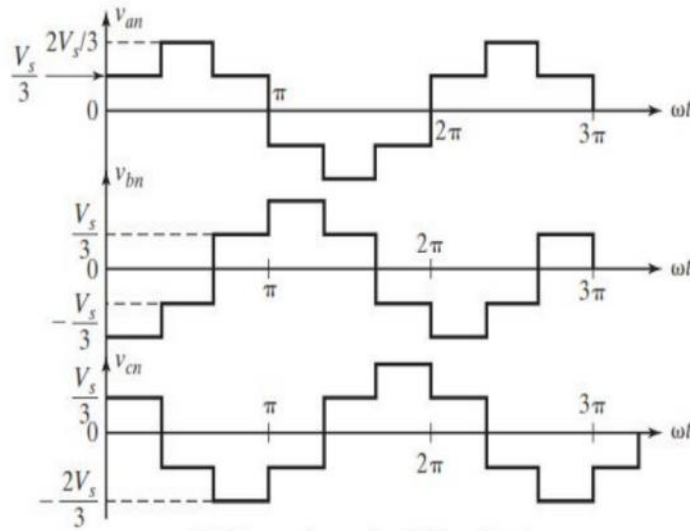

(b) Phase voltages for 180° conduction

- Phase voltages are step wave with step height $V_s/3$
- Line Voltages are quasi square wave with voltages $V_s, 0, -V_s$

15

2

Switching States for Three Phase bridge Inverter 180° mode

TABLE Switch States for Three-Phase Voltage-Source Inverter

State	State No.	Switch States	v_{ab}	v_{bc}	v_{ca}
$S_6, S_1,$ and S_5 are on and $S_3, S_4,$ and S_2 are off	1	101	V_s	$-V_s$	0
$S_1, S_2,$ and S_6 are on and $S_4, S_5,$ and S_3 are off	2	100	V_s	0	$-V_s$
$S_2, S_3,$ and S_1 are on and $S_5, S_6,$ and S_4 are off	3	110	0	V_s	$-V_s$
$S_3, S_4,$ and S_2 are on and $S_6, S_1,$ and S_5 are off	4	010	$-V_s$	V_s	0
$S_4, S_5,$ and S_3 are on and $S_1, S_2,$ and S_6 are off	5	011	$-V_s$	0	V_s
$S_5, S_6,$ and S_4 are on and $S_2, S_3,$ and S_1 are off	6	001	0	$-V_s$	V_s
$S_1, S_3,$ and S_5 are on and $S_4, S_6,$ and S_2 are off	7	111	0	0	0
$S_4, S_6,$ and S_2 are on and $S_1, S_3,$ and S_5 are off	8	000	0	0	0

2

Mode 1; From 0 to 60°;


During mode 1 for $0 \leq \omega t < \pi/3$, transistors Q_1 , Q_5 , and Q_6 conduct

$$R_{\text{eq}} = R + \frac{R}{2} = \frac{3R}{2}$$

$$i_1 = \frac{V_s}{R_{\text{eq}}} = \frac{2V_s}{3R}$$

$$v_{an} = v_{cn} = \frac{i_1 R}{2} = \frac{V_s}{3}$$

$$v_{bn} = -i_1 R = -\frac{2V_s}{3}$$

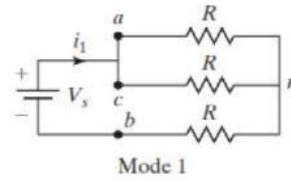

Mode 2; From 60° to 120°;


During mode 2 for $\pi/3 \leq \omega t < 2\pi/3$, transistors Q_1 , Q_2 and Q_6 conduct

$$R_{\text{eq}} = R + \frac{R}{2} = \frac{3R}{2}$$

$$i_2 = \frac{V_s}{R_{\text{eq}}} = \frac{2V_s}{3R}$$

$$v_{an} = i_2 R = \frac{2V_s}{3}$$
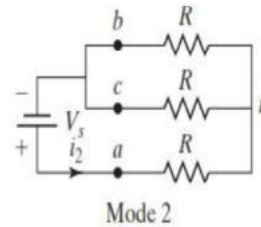
$$v_{bn} = v_{cn} = \frac{-i_2 R}{2} = -\frac{V_s}{3}$$



Mode 3; From 120° to 180°;


During mode 3 for $2\pi/3 \leq \omega t < \pi$, transistors Q_1 , Q_2 , and Q_3 conduct

$$R_{\text{eq}} = R + \frac{R}{2} = \frac{3R}{2}$$

$$i_3 = \frac{V_s}{R_{\text{eq}}} = \frac{2V_s}{3R}$$

$$v_{an} = v_{bn} = \frac{i_3 R}{2} = \frac{V_s}{3}$$

$$v_{cn} = -i_3 R = -\frac{2V_s}{3}$$

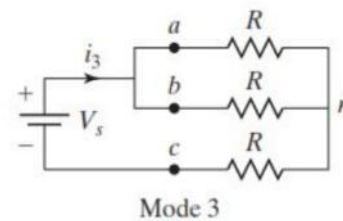

RMS output Voltage (Line – Line) & Phase

The line-to-line rms voltage can be found from

$$V_L = \left[\frac{2}{2\pi} \int_0^{2\pi/3} V_s^2 d(\omega t) \right]^{1/2} = \sqrt{\frac{2}{3}} V_s = 0.8165V_s$$

$$V_L = 0.8165V_s$$

The rms value of line-to-neutral voltages can be found from the line voltage,

$$V_p = \frac{V_L}{\sqrt{3}} = \frac{\sqrt{2}V_s}{3} = 0.4714V_s$$

$$V_p = 0.4714V_s$$

RMS Value of Fundamental Line Voltage & Phase Voltage

From v_{ab} Eq , the rms n th component of the line voltage is

$$V_{Ln} = \frac{4V_s}{\sqrt{2}n\pi} \sin \frac{n\pi}{3}$$

which, for $n = 1$, gives the rms fundamental line voltage.

$$V_{L1} = \frac{4V_s \sin 60^\circ}{\sqrt{2}\pi} = 0.7797V_s$$

$$V_{p1} = \frac{V_{L1}}{\sqrt{3}} = \frac{0.7797V_s}{\sqrt{3}}$$

$$V_{n1} = 0.45 V_s$$

6

A single-phase full bridge inverter has a resistive load of 4 and dc input voltage is $V_s = 24V$. Determine

1. RMS output voltage at fundamental frequency
2. Output power
3. Average and peak current of each transistor
4. Peak reverse blocking voltage of each transistor
5. THD, DF, HF and DF of LOH

6) $V_S = 24V$; $R = 4\Omega$.

1) RMS o/p Voltage @ fundamental frequency,

$$V_{o1} = 0.90 \times 24 = \underline{\underline{21.6V}}$$

2) O/P Power = $P_0 = V_S^2 / R = \frac{24^2}{4} = \underline{\underline{144W}}$

3) Peak transistor current $I_p = \frac{24}{4} = \underline{\underline{6A}}$

Average current of each transistor

$$I_Q = 0.5 \times 6 = \underline{\underline{3A}}$$

4) Peak reverse blocking voltage of each transistor

$$V_{BR} = 24V.$$

$$5) \text{ THD} = \frac{1}{V_{o1}} \sqrt{\sum_{n=2}^{\infty} V_{on}^2}$$

$$= \frac{\sqrt{V_o^2 - V_{o1}^2}}{V_{o1}} = \frac{\sqrt{24^2 - 21.6^2}}{21.6}$$

$$= 0.4843$$

$$\text{THD} = 48.43\%$$

Distortion factor (DF)

$$\text{DF} = \frac{0.048 \times V_s}{V_{o1}} = \frac{0.048 \times 24}{21.6} = 5.33\%$$

HF & DF of LOH

3rd harmonics ; $n=3$

$$\text{HF} = \frac{V_{o3}}{V_{o1}} = \frac{V_{on}}{V_{o1}} = \frac{7.2}{21.6} = 0.3333$$

$$V_{o3} = \frac{V_{o1}}{3} = 7.2$$

$$\boxed{\text{HF}_3 = 33.33\%}$$

$$\text{DF}_3 = \frac{V_{o3}}{V_{o1} \times n^2} = \frac{V_{o1}}{3 \times V_{o1} \times 3^2} = \frac{1}{3^3} = 0.3704$$

$$\boxed{\text{DF}_3 = 3.704\%}$$

Explain the voltage control of single-phase inverter using 1) multiple pulse width modulation 2) sinusoidal pulse width modulation


Features of Multi pulse width modulation

- The order of harmonics is the same as that of single-pulse modulation.
- The distortion factor is reduced significantly compared with that of single-pulse modulation.
- However, due to larger number of switching on and off processes of power transistors, the switching losses would increase.
- With larger values of p , the amplitudes of LOH would be lower, but the amplitudes of some higher order harmonics would increase.
- However, such higher order harmonics produce negligible ripple or can easily be filtered out.

7a

2. Multi Pulse Width Modulation

Output Voltage $V_o = V_s (g1- g4)$

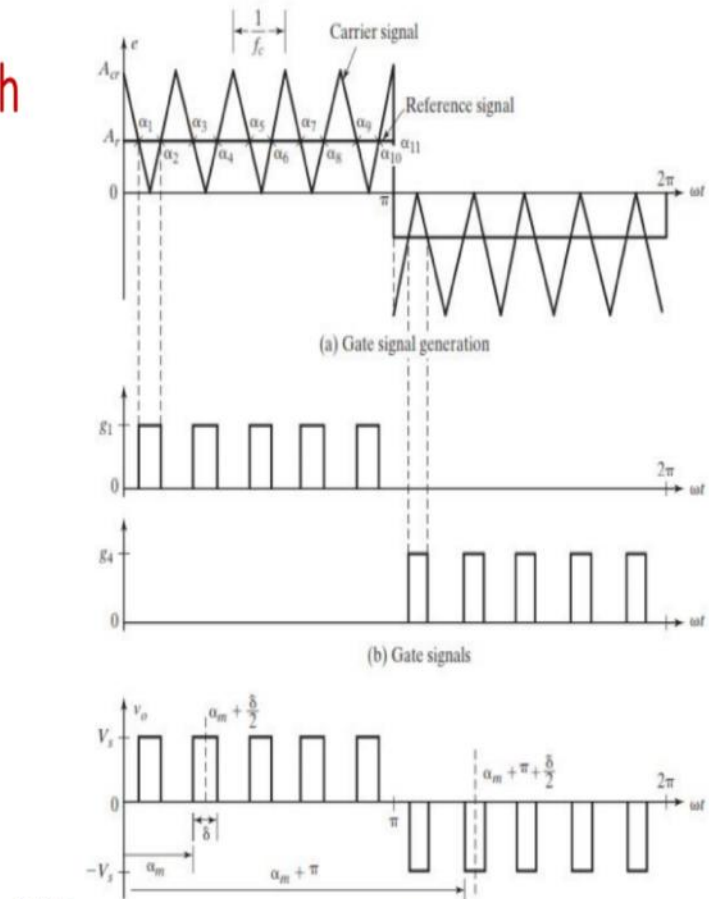

Sinusoidal Pulse Width Modulation

- Since the desired output voltage is a sine wave, a reference sinusoidal signal is used as the reference signal.
- Instead of maintaining the width of all pulses the same as in the case of multiple-pulse modulation, the width of each pulse is varied in proportion to the amplitude of a sine wave evaluated at the center of the same pulse.
- The DF and LOH are reduced significantly.
- The gating signals are generated by comparing a sinusoidal reference signal with a triangular carrier wave of frequency f_c .
- This sinusoidal pulse-width modulation (SPWM) is commonly used in industrial applications.
- The frequency of reference signal f_r determines the inverter output frequency f_o ; and its peak amplitude A_r , controls the modulation index M , then controls RMS output voltage.

2


Sinusoidal Pulse Width Modulation

✓ Comparing the bidirectional carrier signal v_{cr} with two sinusoidal reference signals v_r and $-v_r$ shown in produces gating signals g_1 and g_4 , respectively.

✓ Unidirectional triangular wave if preferred

Output Voltage $V_o = V_s (g_1 - g_4)$

Dr.X.CI

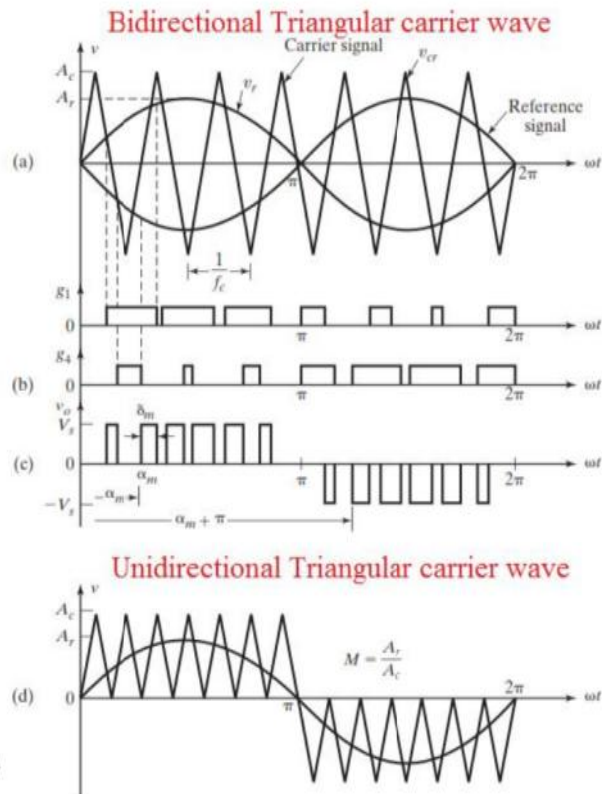

With the neat circuit diagram and waveforms, Explain the operation of current source inverter.


1

Current Source Inverter

- In VSI, the inverters are fed from a voltage source and the load current is forced to fluctuate from positive to negative, and vice versa.
- To cope with inductive loads, the power switches with freewheeling diodes are required
- In a current-source inverter (CSI), the input behaves as a current source.
- The output current is maintained constant irrespective of load on the inverter and the output voltage is forced to change.


2

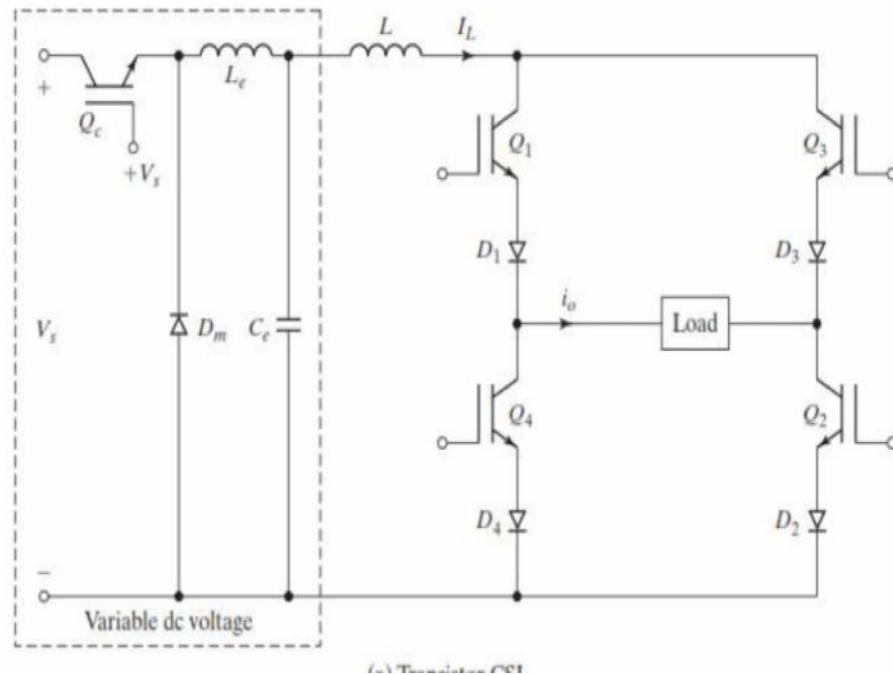Current Source Inverter (CSI) – Single Phase



7b

Gate Pulse & Output Current Waveform

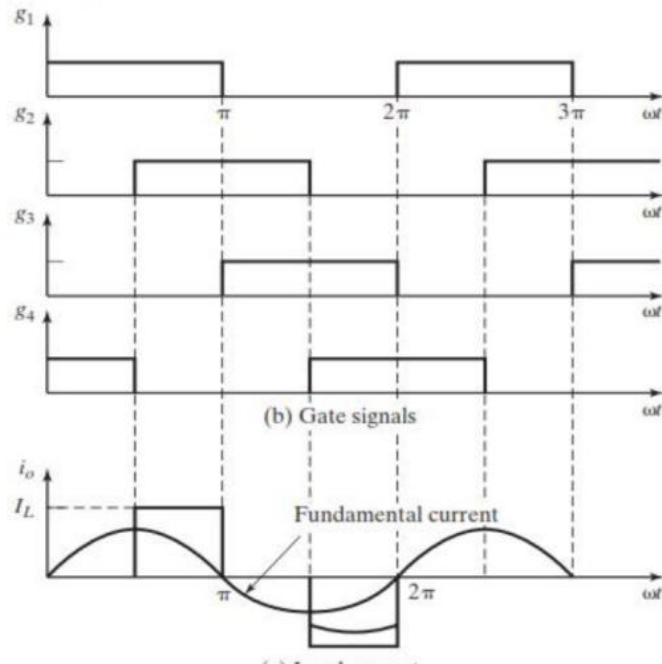

Current Source Inverter

- Because there must be a continuous current flow from the source, two switches must always conduct—one from the upper and one from the lower switches.
- The conduction sequence is 12, 23, 34, and 41.
- The switch states are shown in Table 6.6.

TABLE Switch States for a Full-Bridge Single-Phase Current-Source Inverter (CSI)

State	State No.	Switch State $S_1S_2S_3S_4$	i_o	Components Conducting
S_1 and S_2 are on and S_4 and S_3 are off	1	1100	I_L	S_1 and S_2 D_1 and D_2
S_3 and S_4 are on and S_1 and S_2 are off	2	0011	$-I_L$	S_3 and S_4 D_3 and D_4
S_1 and S_4 are on and S_3 and S_2 are off	3	1001	0	S_1 and S_4 D_1 and D_4
S_3 and S_2 are on and S_1 and S_4 are off	4	0110	0	S_3 and S_2 D_3 and D_2