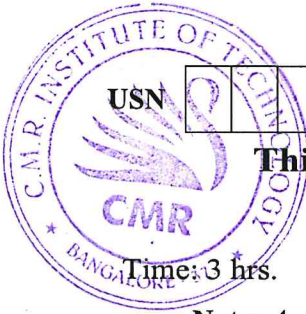


# CBCS SCHEME



18EE35

Third Semester B.E. Degree Examination, Feb./Mar. 2022

## Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Explain the definition of combinational logic. Convert the given Boolean expression into minterm canonical form and maxterm canonical form.

$$F(x, y, z) = X + \bar{x}\bar{z}(y + z). \quad (08 \text{ Marks})$$

- b. Simplify the function :

$$Y = f(a, b, c, d) = \sum m(2, 3, 4, 5, 13, 15) + \sum d(8, 9, 10, 11) \text{ using Karnaugh map.} \quad (06 \text{ Marks})$$

- c. Simplify the function :

$$Y = f(a, b, c, d) = \pi M(0, 4, 5, 7, 8, 9, 11, 12, 13, 15) \text{ using the Karnaugh map.} \quad (06 \text{ Marks})$$

OR

- 2 a. Simplify using the Quine – McClusky minimization technique :

$$Y = f(a, b, c, d) = \sum m(0, 2, 8, 10). \quad (08 \text{ Marks})$$

- b. Using the Quine – McClusky method, obtain all the prime implicants for the following Boolean function :

$$f(a, b, c, d) = \pi M(0, 2, 3, 4, 5, 12, 13) + dc(8, 10). \quad (12 \text{ Marks})$$

### Module-2

- 3 a. With the aid of general structure, clearly distinguish between a decoder and encoder.

(06 Marks)

- b. Implement the following Boolean function using 4 : 1 multiplexer.

$$F(A, B, C) = \sum m(1, 3, 5, 6) \quad (06 \text{ Marks})$$

- c. Implement full subtractor using a decoder and two NAND gates and write its truth table.

(08 Marks)

OR

- 4 a. What is carry look ahead adder? Explain general organization of it.

(06 Marks)

- b. Write a truth table for two – bit magnitude comparator. Write the Karnaugh map for each output of two bit magnitude comparator and the resulting equation.

(14 Marks)

### Module-3

- 5 a. What is a Flip-Flop? Discuss the working principle of SR Flip Flop with its truth table. Also highlight the role of SR Flip Flop in switch debouncer circuit.

(12 Marks)

- b. Explain the operation of Master - Slave JK flip-flop along with its circuit diagram.

(08 Marks)

OR

- 6 a. Draw and explain the working of Positive and Negative edge triggered D flip-flop.

(12 Marks)

- b. Derive the characteristic equations for D, JK, T and SR flip flops.

(08 Marks)

**Module-4**

- 7 a. Explain with suitable logic and timing diagram :  
 i) Serial-in serial-out shift register (10 Marks)  
 ii) Parallel-in parallel out shift register. (10 Marks)
- b. Compare Registers and Counters. Explain the working of 4-bit Asynchronous counter using JK flip-flops. (10 Marks)

**OR**

- 8 a. Describe the block diagram of a MOD – 7 Johnson counter and explain its operation. Give the count sequence table and the decoding logic used to identify the various states. (10 Marks)
- b. Design a MOD – 5 synchronous binary counter using clocked J-K flip-flops. (10 Marks)

**Module-5**

- 9 a. With a suitable example, explain Mealy and Moore model in a sequential circuit analysis. (08 Marks)
- b. A sequential circuit has one input and one output. The state diagram is as shown in Fig.Q9(b). Design a sequential circuit with 'T' flip-flop.

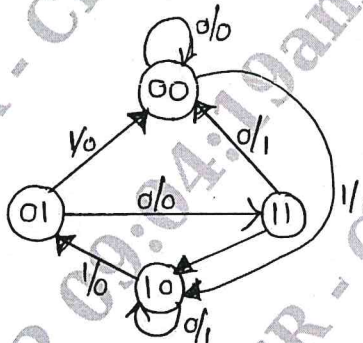


Fig.Q9(b)

(12 Marks)

**OR**

- 10 a. With a basic structure, explain clearly Programmable Read Only Memories (PROMS) and EPROM. (13 Marks)
- b. Write short note on :  
 i) Read only and Read/Write memories  
 ii) Flash memory. (07 Marks)

\*\*\*\*\*

CMRIT LIBRARY  
 BANGALORE - 560 037