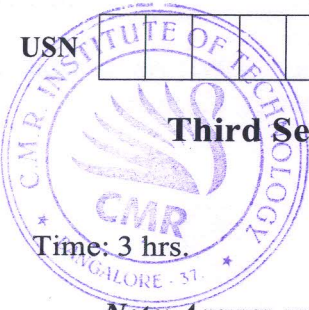


# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EE34



**Third Semester B.E. Degree Examination, Feb./Mar. 2022**

## Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 80

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Draw and explain series negative clipper with the help of output waveform and transfer characteristics. (04 Marks)
- b. Derive an expression for  $S(iC_O)$  and  $S(V_{BE})$  for fixed bias. (06 Marks)
- c. Determine the following for the fixed-bias configuration of Fig.Q1(c).
  - (i)  $I_{BQ}$  and  $I_{CQ}$
  - (ii)  $V_{CEQ}$
  - (iii)  $V_B$  and  $V_C$

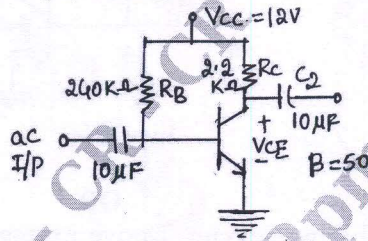


Fig.Q1(c)

(06 Marks)

OR

- 2 a. Explain Emitter bias circuit, with the help of BE loop and CE loop. Write necessary equation. (08 Marks)
- b. Design a suitable circuit represented by the box shown in Fig.Q2(b), which had input and output waveforms as indicated.

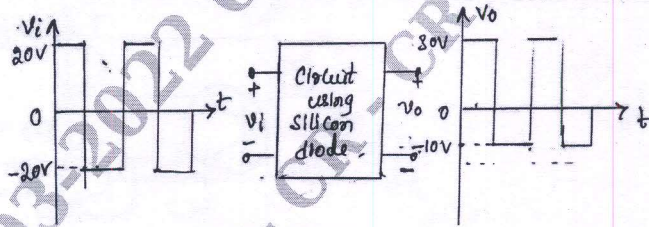


Fig.Q2(b)

(04 Marks)

- c. Fig.Q2(c) shows the transistor switch check whether the circuit works properly.

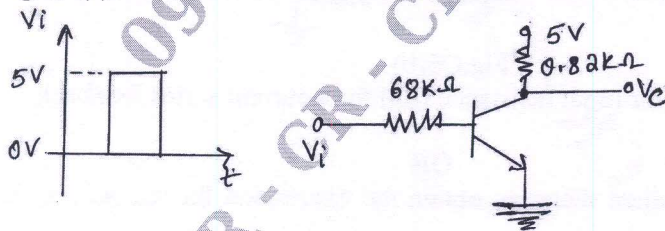


Fig.Q2(c)

$V_{CE} = 0.7V$   
 $V_{CE(SAT)} = 0.15V$   
 $I_{CEO} = 10 \mu A$   
 $\beta_{dc} = h_{FE} = 125$

(04 Marks)

### Module-2

- 3 a. Define h-parameters. Hence derive h-parameter model of a CE – BJT. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- b. For the common base configuration of Fig.Q3(b).  $I_E = 4 \text{ mA}$ ,  $\alpha = 0.991$ . An ac signal of  $3 \text{ mV}$  is applied between the base and emitter terminals. If  $R_L = 610 \Omega$ . Calculate  
 (i)  $r_v$  and  $z_i$                       (ii)  $A_v$  and  $A_i$

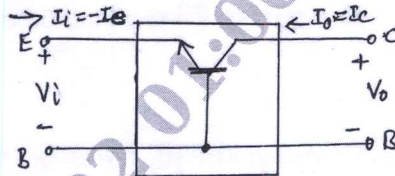


Fig.Q3(b)

(04 Marks)

- c. For the circuit shown in Fig.Q3(c),  
 (i) Determine  $r_e$                       (ii) Find  $z_i$ ,  $z_o$ ,  $A_v$  and  $A_i$  (with  $r_o = \infty \Omega$ )

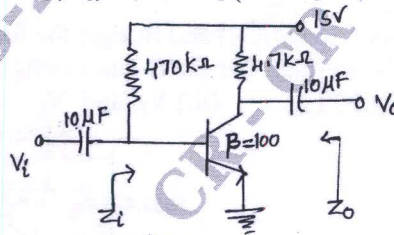


Fig.Q3(c)

(06 Marks)

OR

- 4 a. Draw the emitter follower circuit. Derive expression for (i)  $z_i$  (ii)  $z_o$  (iii)  $A_v$  using  $r_e$  model. (08 Marks)  
 b. Derive the expressions for Miller's effect capacitance. (08 Marks)

**Module-3**

- 5 a. Explain the need of cascading amplifier? Draw and explain the block diagram of two stage cascade amplifier. (06 Marks)  
 b. For the amplifier circuit shown in Fig.Q5(b), calculate  $z_i$ ,  $z_o$ ,  $A_i$  and  $A_v$ .

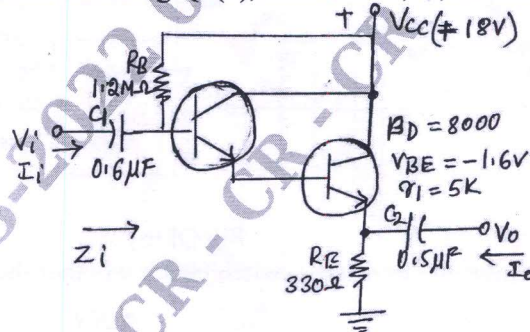


Fig.Q5(b)

(04 Marks)

- c. Derive the expression for input resistance ( $R_{if}$ ) for a current series feedback. (06 Marks)

OR

- 6 a. With necessary equivalent diagram, obtain the expression for  $z_{in}$ ,  $A_v$ ,  $z_o$  for a Darlington Emitter follower. (10 Marks)  
 b. An amplifier with open loop voltage gain of 1000 deliver 10W of power output at 10% second harmonic distortion when  $i_p$  is 10 mV. If 40 dB negative feedback is applied and output power is to remain at 10W, determine required input signal  $V_s$  and second harmonic distortion with feedback. (06 Marks)

**Module-4**

- 7 a. Show that series fed directly coupled class A power amplifiers has a maximum power efficiency of 25%. (10 Marks)  
 b. With a neat diagram, Explain the working of R-C phase shift oscillator. (06 Marks)

**OR**

- 8 a. Compare RC phase shift oscillator with wein bridge oscillator. (04 Marks)  
 b. The following data are available for the Colpitts oscillator.  
 $C_1 = 1 \text{ nF}$ ,  $C_2 = 99 \text{ nF}$ ,  $L = 1.5 \text{ mH}$   
 $L_{RFC} = 0.5 \text{ mH}$ ,  $C_c = 10 \text{ }\mu\text{F}$ ,  $h_{fc} = 110$   
 (i) Calculate the frequency of oscillation  
 (ii) Check to make sure that the condition for oscillation is satisfied. (06 Marks)  
 c. Calculate the peak power dissipated in each transistor of a class B, push pull power amplifier if  $V_{CC} = 15\text{V}$  and  $R_L = 5\Omega$ . (06 Marks)

**Module-5**

- 9 a. Draw JFET amplifier using fixed bias configuration. Derive  $z_i$ ,  $z_o$ ,  $A_v$  for small signal model. (10 Marks)  
 b. For the JFET amplifier shown in Fig.Q9(b).  
 (i) Calculate  $z_i$  and  $z_o$  (ii) Calculate  $A_v$  (iii) Find  $V_o$  if  $V_i = 25\text{mV(rms)}$

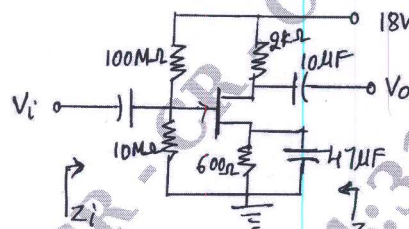


Fig.Q9(b)

$$\begin{aligned} I_{DSS} &= 12 \text{ mA} \\ V_p &= -3 \text{ V} \\ V_{os} &= 10 \text{ }\mu\text{s} \\ V_{GSQ} &= -1 \text{ V} \end{aligned}$$

CMRIT LIBRARY  
 BANGALORE - 560 030 (06 Marks)

**OR**

- 10 a. Explain the structure of the Depletion mode MOSFET. (08 Marks)  
 b. Define Transconductance  $g_m$ . Derive an expression for  $g_m$ . (04 Marks)  
 c. List the difference between FET and BJT. (04 Marks)

\*\*\*\*\*