



Third Semester B.E. Degree Examination, Feb./Mar. 2022 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Three impedances are connected in delta. Obtain expressions for their star connected equivalent. (06 Marks)
- b. Reduce the network shown in Fig.Q.1(b) to a single voltage source in series with a resistance using source shift and source transformations. (06 Marks)

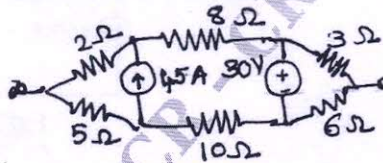


Fig. Q.1(b)

- c. In the circuit shown in Fig.Q.1(c), determine V_2 which result in zero current through 4Ω resistor use mesh current analysis. (08 Marks)

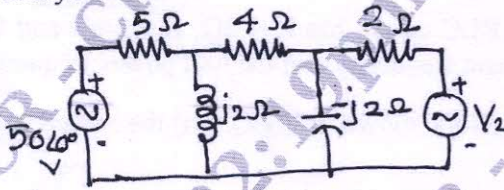


Fig. Q.1(c)

OR

- 2 a. Write short note on the following:
 - i) Active and Passive elements. (06 Marks)
 - ii) Concept of Ideal and practical sources. (07 Marks)
- b. Find the current I in 28Ω resistor by Mesh analysis in Fig.Q.2(b).

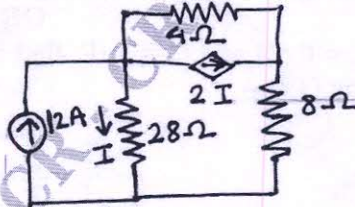


Fig. Q.2(b)

- c. Find the power dissipated in 10Ω resistor by node voltage method in Fig.Q.2(c). (07 Marks)

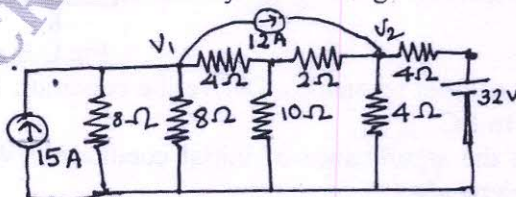


Fig. Q.2(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, $42+8=50$, will be treated as malpractice.

Module-2

- 3 a. State and explain superposition theorem. (06 Marks)
 b. State and explain Reciprocity theorem. (06 Marks)
 c. Find the value of R_L shown in Fig.Q.3(c) at which maximum power is transferred across ab. What is the maximum power transferred? (08 Marks)

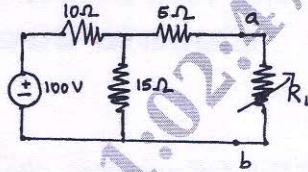


Fig.Q.3(c)

OR

- 4 a. State and prove the maximum power transfer theorem, for ac networks. (07 Marks)
 b. Find the Thevenin's equivalent circuit of the network shown in Fig.Q.4(b) across load. (06 Marks)

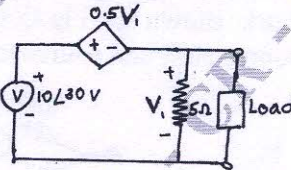


Fig.Q.4(b)

- c. State and explain Norton's theorem. (06 Marks)

- 5 a. A series RLC circuit has $R = 2\Omega$, $L = 2\text{mH}$ and $C = 10\mu\text{F}$. Calculate Q factor, band width, the resonant frequency and the half power frequencies. (10 Marks)

- b. In the network shown in Fig.Q.5(b) the switch is closed at $t = 0$. Determine i , di/dt and $\frac{d^2i}{dt^2}$ at $t = 0^+$. (10 Marks)

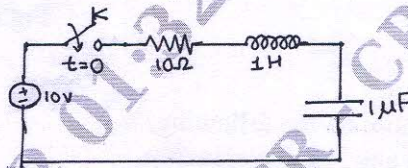


Fig.Q.5(b)

OR

- 6 a. If $R = 25\Omega$, $L = 0.5\text{H}$ and $C = 5\mu\text{F}$, find the W_{ar} , Q and the band width for the circuit as shown in the Fig.Q.6(a). (08 Marks)

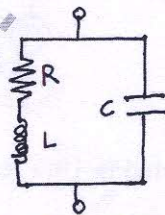


Fig.Q.6(a)

- b. Explain parallel resonance. Derive the condition for parallel resonance when RL connected parallel to RC. (06 Marks)
 c. What is the significance of initial conditions? Write a note on initial conditions in basic circuit elements. (06 Marks)

Module-4

- 7 a. State and prove initial and final value theorem in Laplace transformation. (10 Marks)
 b. Find the Laplace transformation of unit step, unit impulse and unit ramp function. (10 Marks)

OR

- 8 a. In the R.C. series circuit shown in Fig.Q.8(a) the switch is closed at $t = 0$, obtain the expression for the current. (10 Marks)

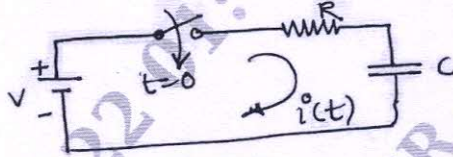


Fig.Q.8(a)

- b. Find the inverse Laplace transform

i) $\frac{s^2 + 5}{s(s^2 + 4s + 4)}$

ii) $\frac{2s + 6}{s^2 + 6s + 25}$

(10 Marks)

Module-5

- 9 a. A star load with $Z_A = (3 + j0)\Omega$, $Z_B = (2 + j3)\Omega$ and $Z_C = (2 - j1)\Omega$ is connected to 3 phase, 4 wire 100V system with the phase sequence as ACB. Find the line currents including the neutral. (10 Marks)
 b. Find the transmission parameters for the circuit shown in Fig.Q.9(b). (10 Marks)

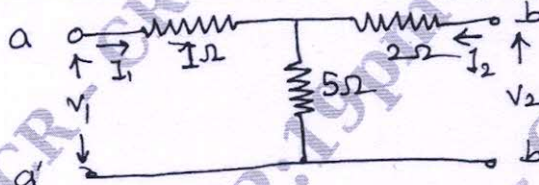


Fig.Q.9(b)

OR

- 10 a. For the networks shown in Fig.Q.10(a), find Z-parameters. (10 Marks)

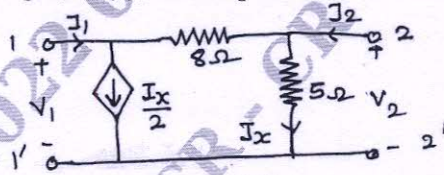


Fig.Q.10(a)

- b. Determine the line currents and total power supplied to a delta connected load of $Z_{ab} = 10 \angle 60^\circ \Omega$, $Z_{bc} = 20 \angle 90^\circ \Omega$ and $Z_{ca} = 25 \angle 30^\circ \Omega$. Assume a 3-phase, 400V ABC system. (10 Marks)
