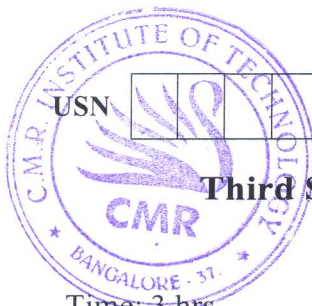


CBCS SCHEME



USN

--	--	--	--	--	--	--	--

17EE34

Third Semester B.E. Degree Examination, Feb./Mar. 2022

Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the working of series positive clipper circuit which clips off positive part of the input above V_R . Draw the waveforms and transfer characteristics. Neglect V_r . (05 Marks)
- b. For the collector to base bias circuit $V_{CC} = 10\text{ V}$, $R_C = 4.7\text{ K}\Omega$, $R_B = 220\text{ K}\Omega$ and $\beta = 100$. Calculate the location of Q-point. (05 Marks)
- c. For the fixed bias circuit, derive expressions for $S_{I_{CO}}$, $S_{V_{BE}}$ and S_{β} . Also obtain the relations between $S_{I_{CO}}$ and $S_{V_{BE}}$ and $S_{I_{CO}}$ and S_{β} . (10 Marks)

OR

- 2 a. Calculate the output voltage V_0 for the clamper circuit as shown in Fig.Q2(a). The input voltage V_i is also shown. Frequency $V_i = 1\text{ kHz}$.

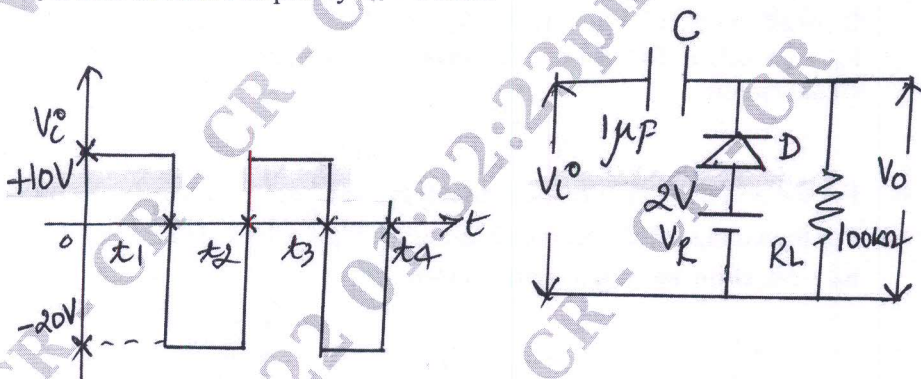


Fig.Q2(a)

(10 Marks)

- b. For the voltage divider bias circuit, derive expressions for $S_{V_{BE}}$. Also obtain the relation between $S_{V_{BE}}$ and $S_{I_{CO}}$. (10 Marks)

Module-2

- 3 a. For the transistor amplifier in general form, derive expressions for A_I , Z_i , A_V , A_{VS} , A_{IS} and Z_o . Use h-parameter model. (10 Marks)
- b. A single stage common emitter amplifier has $R_S = 1\text{ K}\Omega$, $R_L = 2\text{ K}\Omega$, $R_1 = 50\text{ K}\Omega$, $R_2 = 2\text{ K}\Omega$, $R_C = 2\text{ K}\Omega$, $h_{fe} = 50$, $h_{ie} = 1.1\text{ K}\Omega$, $h_{oe} = h_{re} = 0$, $V_{CC} = 10\text{ V}$, $R_E = 470\ \Omega$, $C_E = 47\ \mu\text{F}$, $C_1 = C_2 = 0.01\ \mu\text{F}$. Draw the circuit diagram and determine A_I , Z_i , A_V , A_{IS} and A_{VS} and Z'_o . (10 Marks)

OR

- 4 a. Explain the working of common collector or emitter follower configuration. Develop expressions for A_I , Z_i , A_V and Y_o using approximate and exact hybrid model. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- b. For the amplifier circuit as shown in Fig.Q4(b), $h_{fe} = 100$, $h_{ie} = 3.37 \text{ K}\Omega$, $h_{re} = h_{oe} = 0$. Determine A_I , Z_I , A_V , A_{I_S} .

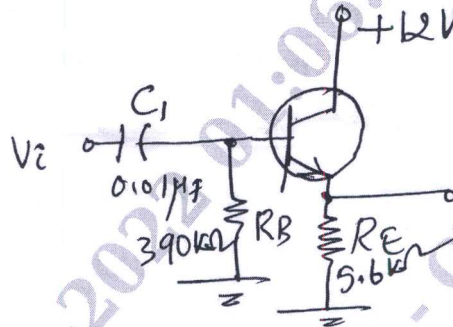


Fig.Q4(b)

(10 Marks)

Module-3

- 5 a. Draw the circuit of cascode amplifier. State its merits. Develop h-parameter model using approximate model. (08 Marks)
- b. Consider a 2-stage RC coupled CE-CE amplifier. The component values are $R_S = 1 \text{ K}\Omega$, $R_{C_1} = 15 \text{ K}\Omega$, $R_{E_1} = 100 \Omega$, $R_1 = 200 \text{ K}\Omega$, $R_2 = 20 \text{ K}\Omega$, $C_{E_1} = 47 \mu\text{F}$, $C_1 = C_2 = 0.1 \mu\text{F}$ and for II stage $R_{C_2} = 4 \text{ K}\Omega$, $R_{E_2} = 330 \Omega$, $C_{E_2} = 47 \mu\text{F}$, $C'_1 = C'_2 = 0.1 \mu\text{F}$, biasing resistors of II stage, $R_3 = 47 \text{ K}\Omega$ and $R_4 = 4.7 \text{ K}\Omega$, $h_{ie} = 1.2 \text{ K}\Omega$, $h_{fe} = 50$, $h_{re} = 2.5 \times 10^{-4}$ and $h_{oe} = 25 \mu\text{A/V}$. Determine the overall A_V , A_{V_S} and Z_o . Draw the circuit diagram and small signal circuit. (12 Marks)

OR

- 6 a. For the current series feedback topology, obtain expressions for R_{if} and R'_{of} . (10 Marks)
- b. For the voltage series feedback circuit of Fig.Q6(b), calculate A_V , β , D , R_i , R_{if} , R_{of} and R'_{of} , $h_{fe} = 50$. Draw the small signal model.

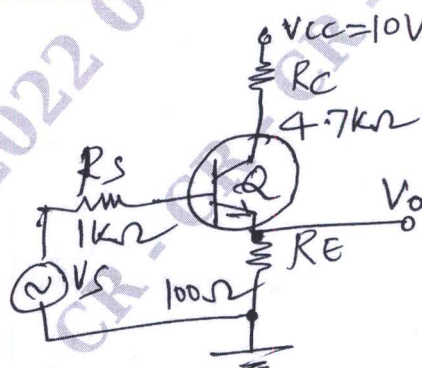


Fig.Q6(b)

(10 Marks)

Module-4

- 7 a. For the transformer coupled class-A amplifier, explain DC and AC operations, AC and DC, output and input power efficiency, maximum efficiency and power dissipation. (10 Marks)
- b. The input signal V_s is given by $V_s = 1.75 \sin(600t)$ is fed to a power amplifier and regulating o/p current is $i_o = 15 \sin 600t + 1.5 \sin 1200t + 1.2 \sin 1800t + 0.5 \sin 2400t$. Determine percentage increase in power due to distortion. (05 Marks)
- c. Explain cross-over distortion in class-B push pull amplifier. (05 Marks)

OR

- 8 a. Explain the expression for gain with feedback in oscillators. What is the value of $A\beta$ to generate oscillations? Thus, explain principle of oscillations. (06 Marks)
- b. State Barkhausen criteria for sustained oscillations. (04 Marks)
- c. Derive an expression for frequency of oscillations in Colpitt's oscillator and h_{fe} min required for transistor. (10 Marks)

Module-5

- 9 a. Explain construction of n-channel D-MOSFET. Draw and explain transfer characteristics and drain characteristics. (10 Marks)
- b. Explain biasing for zero current drift and derive condition for zero drift. (10 Marks)

OR

- 10 a. For the JFET with fixed bias circuit, obtain expressions for Z_i , Z_o , A_v . Compare the result for exact analysis and when $r_d \gg R_D$. (10 Marks)
- b. For the JFET amplifier as in Fig.Q10(b), determine A_v , Z_i , Z_o and Z'_o . For FET, $g_m = 2 \text{ mA/V}$, $r_d = 10 \text{ K}\Omega$.

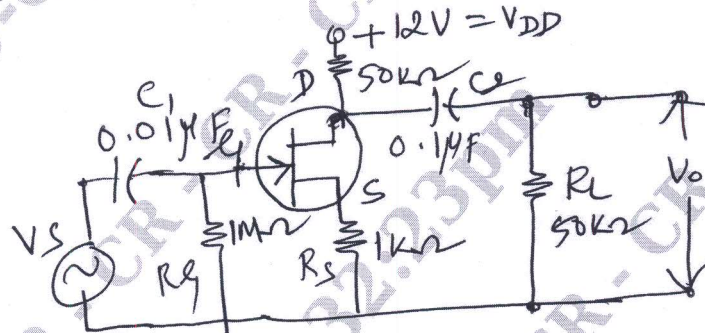


Fig.Q10(b)

(10 Marks)
