 


CBCS SCHEME



17EE35

Third Semester B.E. Degree Examination, Feb./Mar. 2022 Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Convert the following Boolean function into their proper canonical form:
(i) $f = \bar{a}b + \bar{b}c$ (ii) $f(x, y, z) = (x+y)(y+z)$ (08 Marks)
b. Simplify the following function using K-map:
i) $f(w, x, y, z) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 4)$
ii) $f(a, b, c, d) = \sum m(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$ (12 Marks)

OR

- 2 a. Define combinational logic, canonical SOP, canonical POS and PI, with examples. (08 Marks)
b. Simplify using Q-M method $y=f(w, x, y, z) = \sum m(0, 2, 8, 10)$. Verify the answer with K-map. (12 Marks)

Module-2

- 3 a. What are Multiplexers? Implement the following using 8:1 multiplexers.
 $f(a, b, c, d) = \sum m(2, 3, 5, 6, 7)$ (08 Marks)
b. Design 2-bit comparator circuit, truth table, K-map and logic circuit. (12 Marks)

OR

- 4 a. Explain the carry look ahead adder. (10 Marks)
b. Design 16:1 multiplexer using 8:1 mux. (05 Marks)
c. Write a short note on encoders. (05 Marks)

Module-3

- 5 a. Explain the working of Master-Slave JK flip-flop with functional table and timing diagram. (10 Marks)
b. Explain working of 3-bit binary ripple counter with the logic and timing diagram. (10 Marks)

OR

- 6 a. Explain the 4 modes of operation of universal shift register with suitable logic diagram. (10 Marks)
b. Design mod-6 synchronous counter using JK-flipflop. (10 Marks)

Module-4

- 7 a. With the help of block diagram, explain Mealy and Moore model. (08 Marks)

- b. Design a sequential circuit using D flip-flop. [Refer Fig.Q7(b)].

 


Fig.Q7(b)

(12 Marks)

OR

- 8 a. Write procedure for design of clocked synchronous sequential circuit. (08 Marks)
 b. Analyse the following sequential circuit and draw the state diagram. [Refer Fig.Q8(b)]

 


Fig.Q8(b)

CMRIT LIBRARY
BANGALORE - 560 037

(12 Marks)

Module-5

- 9 a. Explain briefly history of HDL and structure of HDL. (10 Marks)
 b. List the classification of VHDL data types and explain with examples. (10 Marks)

OR

- 10 a. Mention styles/types of HDL description. Explain behavioral type with Fulladder example in both VHDL and varilog. (12 Marks)
 b. Explain varilog data types. (08 Marks)
