 


CBCS SCHEME

15EC33



USN

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, Feb./Mar. 2022 Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define the following terms :
i) Canonical forms
ii) Truth Table
iii) Prime Implicant
iv) Max term. (08 Marks)
- b. Simplify the function using K-Map $f(w, x, y, z) = wx + \bar{y}z + w\bar{x}\bar{y} + \bar{w}xyz$. (08 Marks)

OR

- 2 a. Simplify using K-Map and implement it using NAND only.
 $f(w, x, y, z) = \Sigma m(2, 6, 7, 8, 9, 10, 12, 13) + dc(0, 1, 4)$ (08 Marks)
- b. Simplify using QM method the function
 $f(a, b, c, d) = \Sigma m(1, 3, 6, 8, 9, 10, 12, 14) + dc(7, 13)$ (08 Marks)

Module-2

- 3 a. Design 3:8 NAND decoder with active low enable and realize full adder using it. (08 Marks)
- b. Design 2-bit comparator with necessary truth and K-Map. (08 Marks)

OR

- 4 a. Implement the Boolean function using MUX
i) 8:1 MUX a, b, c as select lines
ii) 4:1 MUX with c, d as select lines
 $f(a, b, c, d) = \Sigma m(1, 2, 6, 7, 9, 11, 12, 14, 15)$ (08 Marks)
- b. With a note diagram explain carry lookahead adder. (08 Marks)

Module-3

- 5 a. Explain M/s JK flip-flop (master/slave with neat diagram, truth table and timing diagram. (08 Marks)
- b. Derive the characteristics equation of JK flip-flop and T flip-flop. (08 Marks)

OR

- 6 a. Explain the following terms :
i) Latch
ii) Pulse – Triggered
iii) Edge – Triggered
iv) Characteristics equation of D-Flip-flop. (08 Marks)
- b. Differentiate between :
i) Sequential Logic circuit and combinational logic circuit
ii) Flip Flop and Latch. (08 Marks)

Module-4

- 7 a. Explain with a neat diagram universal shift Register along with control modes. (08 Marks)
- b. Design MOD – 8 asynchronous counter using T-flip-flop. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR


- 8 a. Design 3-bit synchronous down counter using T-flip-flop. (08 Marks)
 b. Design the synchronous counter using D-flip-flop to count the sequence 2 – 4 – 1 – 5 – 0. (08 Marks)

Module-5

- 9 a. Explain Mealy machine model and Moore machine model. (08 Marks)
 b. Design a synchronous counter using T flip-flops to count the sequence 6 – 5 – 4 – 3 – 2 – 1. (08 Marks)

OR

 - 10 a. Analyse the synchronous circuit as in Fig Q10(a).
 i) Derive the excitation and output equations
 ii) Write the state equations
 iii) Construct transition table and state table
 iv) Draw the state diagram



CMRIT LIBRARY
 BANGALORE - 560 037

Fig Q10(a)

- b. Define the following terms :
 i) State table
 ii) Transition table
 iii) Excitation table
 iv) State Diagram.
