

USN

--	--	--	--	--	--	--	--

First/Second Semester B.E. Degree Examination, Feb./Mar. 2022 Basic Electrical Engineering

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. State and explain Kirchhoff's laws and ohm's law. (06 Marks)
 b. Find :
 i) Voltage drop across $4\ \Omega$
 ii) Supply voltage for the networks shown in Fig.Q1(b).

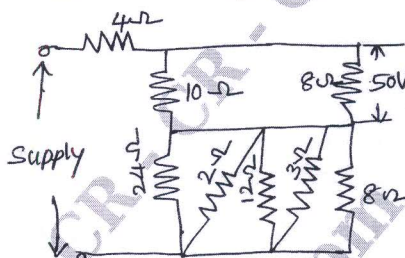


Fig.Q1(b)

(08 Marks)

- c. Define the following :
 i) Average value of alternating current ii) Form factor iii) Peak factor. (06 Marks)

OR

- 2 a. Two resistance $20\ \Omega$ and $40\ \Omega$ are connected in parallel. A resistance of $10\ \Omega$ is connected in series with the combination. A voltage of 200V is applied across the circuit. Find the current in each resistance and voltage across $10\ \Omega$. Find also the power consumed in all the resistors. (08 Marks)
 b. Derive the expression for RMS value average current of a sinusoidally varying quantity. (08 Marks)
 c. Two alternating currents in a parallel circuit are represented by $i_1 = 5\sin \omega t$ and $i_2 = 10 \sin(\omega t + 60^\circ)$. Find the resultant current. (04 Marks)

Module-2

- 3 a. Show that a pure inductance does not consume any power draw the waveforms of voltage, current, power when an alternating voltage is applied to pure inductance. (08 Marks)
 b. A coil of resistance $10\ \Omega$ and inductance 0.1H is connected in series with a $150\ \mu\text{F}$ capacitor across a 200V , 50Hz supply. Calculate :
 i) Inductive reactance
 ii) Capacitive reactance
 iii) Impedance
 iv) Current
 v) Power factor
 vi) Voltage across coil
 vii) Voltage across capacitor. (08 Marks)
 c. An inductive coil takes a current of 33.24a from 230V , 50Hz supply, if the resistance of coil is $6\ \Omega$. Calculate inductance of the coil and power taken by the coil. (04 Marks)

OR

- 4 a. In a three phase star connection, show that $V_L = \sqrt{3}V_{ph}$ also draw vector diagram of line voltage and phase voltage. (07 Marks)
- b. What are the advantages and three phase system over a single phase system? (07 Marks)
- c. A delta connected load consist of a resistance of 10Ω and capacitance of $100\mu F$ in each phase. A supply of $410V$ at $50Hz$ a applied to the load. Find line current, power consumed by the load and power factor. (06 Marks)

Module-3

- 5 a. Derive the EMF equation of a transformer. (06 Marks)
- b. A single phase transformer working at 0.8 power factor has an efficiency at 94% at both $\frac{3}{4}$ full load and pull load of $600KW$. Find the efficiency at $\frac{1}{2}$ full load unity power factor. (08 Marks)
- c. Primary winding of a transformer is connected to a $240V$, $50Hz$. The secondary winding has 1500 turns and the maximum value of core flux is $0.00207 \omega b$. Find secondary induced emf, number of turns in primary and cross sectional area of core. If max value of flux density is 0.465 Tesla. (06 Marks)

OR

- 6 a. Explain plate Earthing. (06 Marks)
- b. With circuit diagram and switching table, explain two-way control of lamp. (08 Marks)
- c. What are the precaution to be taken against electric shock? (06 Marks)

Module-4

- 7 a. Draw a neat sketch of DC machine and name the parts and briefly explain the function of each. (10 Marks)
- b. A 4-pole, $220V$, Lap connected DC shunt motor has 36 slots, each slot containing 16 conductors, it draws a current of $40A$ from the supply. The field resistance and armature resistance are 110Ω and 0.1Ω respectively. The motor develops an output power of $6KW$. Flux per pole is $40Mwb$. Calculate : i) speed ii) torque developed by the armature iii) shaft torque. (10 Marks)

OR

- 8 a. EMF generated in the armature of a shunt generator is $625V$. When delivering its full current of $400A$ to an external circuit. The field current is $6A$ and armature resistance is 0.06Ω . What is the terminal voltage? (06 Marks)
- b. Sketch the various characteristic of DC motor (shunt). (08 Marks)
- c. What is the significance of back EMF in a DC motor? (06 Marks)

Module-5CMRIT LIBRARY
BANGALORE - 560 037

- 9 a. Derive the EMF equation of an alternator. (06 Marks)
- b. 4-pole, $1500rpm$, star connected alternator has 9 slot/pole, and 8 conductor per slot. Find the flux per pole to give a terminal voltage of $3300V$. Take the winding factor as unity. (07 Marks)
- c. A 6 pole, star connected alternator has a 90 slot and 8 conductor per slot, and rotates at $1000rpm$. The flux per pole is $50 mwb$. Find the induced emf across its lines. Take the winding factor of 0.97 . (07 Marks)

OR

- 10 a. Mention the advantages and disadvantages of a squirrel cage and slip ring induction motors. (07 Marks)
- b. Why starter is required for a three phase induction motor? (07 Marks)
- c. A 6 pole induction motor is supplied by a 10 pole alternator. Which is driven at $600rpm$. If the motor is running at $970rpm$, find the slip. (06 Marks)