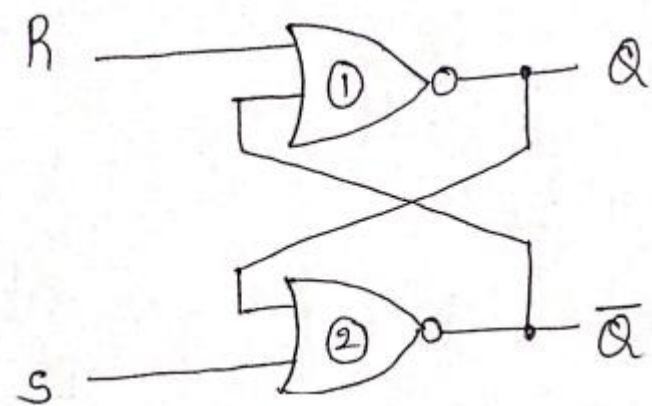
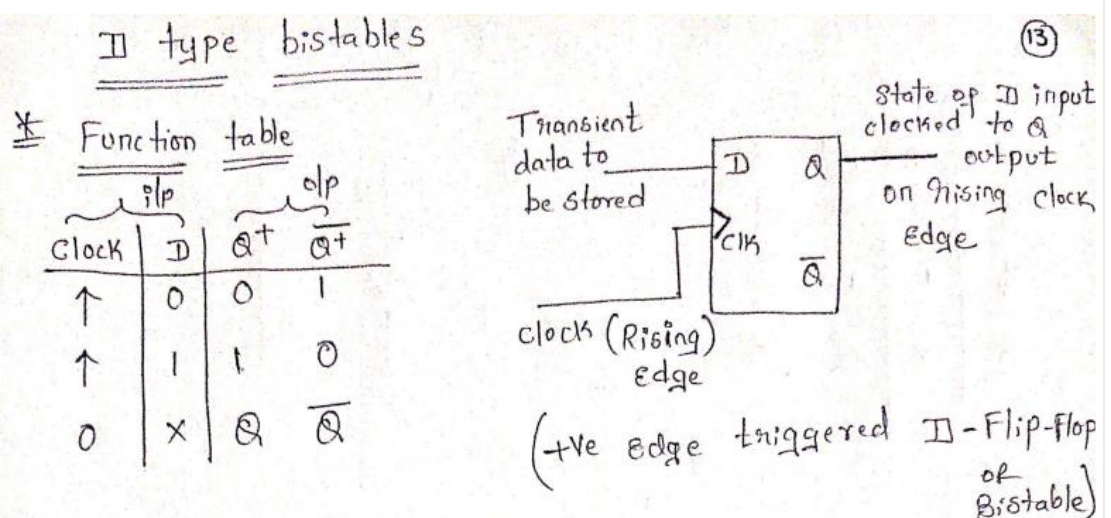


Internal Assessment Test - I

Sub:	Basic Electronics	Code:	21ELN14
Date:	25-01-2022	Duration:	90 mins
		Max Marks:	50
		Sem:	I
		Sec:	I, J, K, L, M, N, O
Answer Any FIVE FULL Questions			

		Marks	OBE	
			CO	RB T
1.	Explain the following logic gates with their symbols, truth table. a. XOR Gate b. AND Gate c. OR Gate d. NAND Gate. NOR Gate 2 MARKS FOR EACH SYMBOL, TRUTH TABLE, OPERATION	[10]	CO2	L1
2.a	Define bistable circuits. Explain R-S bistable using NOR gates. Mention one disadvantage of R-S bistable. CIRCUIT 1 MARKS DEFINITION 1 MARKS OPERATIONS 3 MARKS DISADVANTAGE 1 MARKS	[06]	CO2	L2
				
2.b	Write the logic symbol and truth table of D and JK bistable. 2 MARKS FOR EACH TABLE	[04]	CO2	L2
				

* Positive edge triggered JK-Flip Flop / JK-bistable (14)

Function table

clk	J	K	Q^+	\bar{Q}^+
↑	0	0	Q	\bar{Q}
↑	0	1	0	1
↑	1	0	1	0
↑	1	1	\bar{Q}	Q
0	x	x	Q	\bar{Q}

Comment


No change in state of the Q output on next clock transition

$\bar{Q}=0$, on next clock transition

$Q=1$, on next clock transition

Q output changes to the opposite state on the next clock transition

No change in o/p

 

3. Perform the following Conversions.

2 MARKS FOR EACH


- (i) $(1011011)_2 \rightarrow (?)_{16}$ (ii) $(1234.56)_{16} \rightarrow (?)_2$
- (iii) $(101110100.1101)_2 \rightarrow (?)_{16}$ (iv) $(ABCD.EF)_{16} \rightarrow (?)_2$
- (v) $(988.86)_{16} \rightarrow (?)_2$

[10] CO2 L2

4. Realize a full adder circuit using two half adder and a OR gate, with truth table and logic expressions.

CIRCUIT - 3 MARKS, EXPLANATION- 3 MARKS, TRUTH TABLE AND BOOLEAN SIMPLIFICATION- 4 MARKS

[10] CO2 L3

 


5. With neat circuit diagram explain the operation of 8:1 Multiplexer.

CIRCUIT – 3 MARKS , EXPLANATION- 3 MARKS, TRUTH TABLE AND BOOLEAN EXPRESSION- 4 MARKS

[10]

CO2

L2

 


6. What is a shift register? Explain the working of SISO shift register with neat diagram and waveforms. **DEFINITION- 1, CIRCUIT – 2 MARKS , EXPLANATION- 3 MARKS, OPERATION TABLE AND WAVEFORM- 4 MARKS**

[10]

CO2

L3

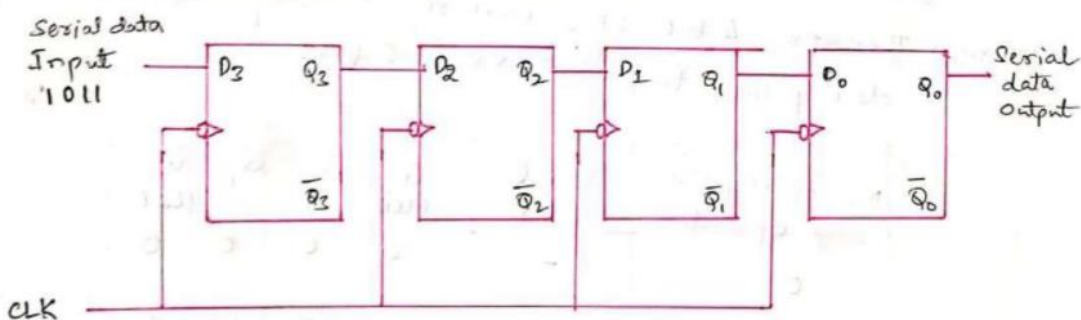
1) Serial In - Serial Out shift register:



NO. of Negative edge of clock	Serial input	Q ₃ (MSB)	Q ₂	Q ₁	Q ₀ (LSB)
0	-	0	0	0	0
1	1	1	0	0	0
2	1	1	1	0	0
3	0	0	1	1	0
4	1	1	0	1	1
5	-	1	0	1	1
6	-	1	1	1	1
7	-	1	1	1	1

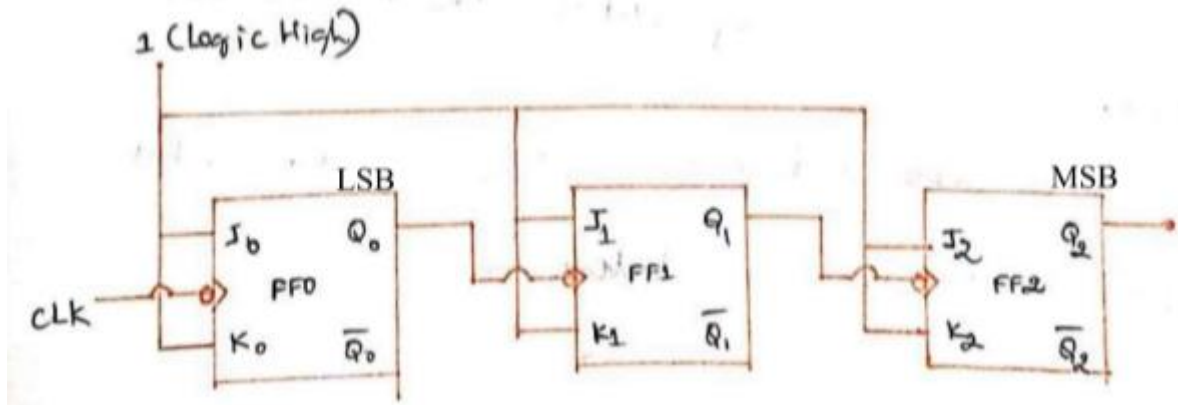7. Explain the operation 3-bit ripple UP counter with relevant diagram and waveforms. [10] CO2 L4

CIRCUIT – 2 MARKS, EXPLANATION- 4 MARKS, OPERATION TABLE AND WAVEFORM- 4 MARKS



Truth table of 3-bit ripple counter.

CLK	Q_2	Q_1	Q_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

