



**Module-4**

- 7 a. What are the three different models for writing a module body in VHDL? Give example for any one model. (06 Marks)
- b. Derive characteristic equation for JK, T, D and SR flip flop. (08 Marks)
- c. Give VHDL code for 4:1 multiplexer using conditional assign statement. (06 Marks)

OR

- 8 a. Using structural model, write VHDL code for Half Adder. (06 Marks)
- b. Derive the excitation table for JK and SR flip flop. How SR flip flop is converted to T flip flop? (08 Marks)
- c. With logic diagram, explain JK flip flop. (06 Marks)

**Module-5**

- 9 a. Define counter. Design synchronous counter for the sequence 0, 4, 1, 2, 6, 0, 4 using JK flip-flop. (08 Marks)
- b. What is shift register? With a neat diagram, explain 4 bit parallel in serial out shift register. (08 Marks)
- c. Write a note on sequential parity checker. (04 Marks)

OR

- 10 a. With a neat diagram, explain ring counter. (06 Marks)
- b. Design and implement MOD 5 synchronous counter using JK flip-flop. Explain with timing diagram. (08 Marks)
- c. Write a note on parallel adder with accumulator. (06 Marks)

.....

USN

VTU Solution– March 2022

Sub:	Analog and Digital Electronics			Sub Code:	18CS33	Branch:	ISE
Date:		Duration:	3 Hrs	Max Marks:	100	Sem/Sec:	III / A, B and C

**Answer any FIVE FULL Questions**

MARKS	CO	RBT
-------	----	-----


1 a. What is biasing? Mention different BJT biasing techniques. Explain voltage divider bias.

**Solution:**

Transistor Biasing is the establishment of suitable dc-values such as  $I_C$ ,  $V_{CE}$ ,  $I_B$ , etc., by using a dc-source. When BJT is properly biased, amplification of signal takes place. There are mainly three types of biasing a transistor: Base bias or Fixed bias, Collector-to-Base bias, Voltage-divider bias.

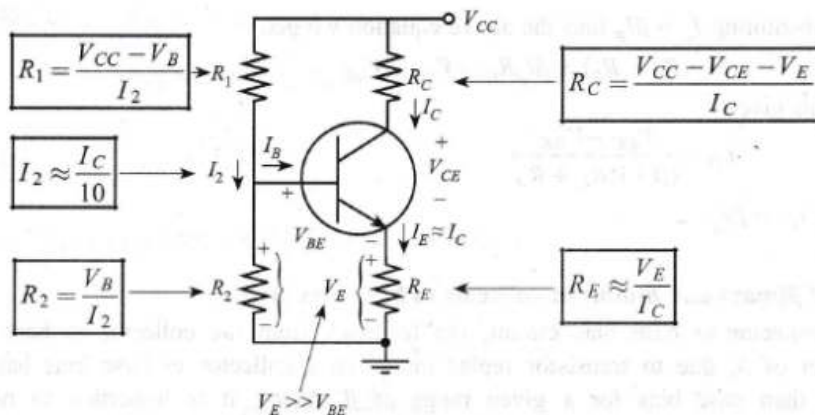**VOLTAGE DIVIDER (EMITTER CURRENT) BIAS CIRCUIT:**

Voltage divider bias is the most stable of the three basic transistor biasing circuits. A voltage divider circuit is shown in the following Figure.



There is an emitter resistor  $R_E$  connected in series with Emitter terminal, so that the total dc load in series with the transistor is  $(R_C + R_E)$ . Resistors  $R_1$  and  $R_2$  constitutes a voltage  $V_B$ .

Applying KVL to the loop  $V_{CC}$ ,  $R_1$ , and  $R_2$ , we get;

$$V_{CC} - I_1 R_1 - I_2 R_2 = 0 \quad \text{Or,} \quad I_1 R_1 + I_2 R_2 = V_{CC} \quad (5)$$

We have;  $I_1 = I_2 + I_B$

Voltage divider bias circuits are normally designed to have a voltage divider current  $I_2$  very much greater than transistor base current  $I_B$ . i.e.,  $I_2 \gg I_B$ . Hence,  $I_1 \approx I_2$  ----- (6)

Using 6 in 5;  $I_2 R_1 + I_2 R_2 = V_{CC}$  i.e.,  $I_2 (R_1 + R_2) = V_{CC}$  Or,  $I_2 = (V_{CC}) / (R_1 + R_2)$

$V_B$  is the voltage across  $R_2$ . i.e.,  $V_B = I_2 R_2$  Or,  $V_B = (V_{CC} * R_2) / (R_1 + R_2)$

$V_E$  is the voltage across  $R_E$ . i.e.,  $V_E = I_E R_E$

Applying KVL to the base-emitter loop;  $V_B - V_{BE} - V_E = 0$  i.e.,  $V_{BE} = V_B - V_E$

Or,  $V_E = V_B - V_{BE}$  i.e.,  $I_E R_E = V_B - V_{BE}$  Hence,  $I_E = (V_B - V_{BE}) / R_E$

Applying KVL to the collector-emitter loop;  $V_{CC} - I_C R_C - V_{CE} - I_C R_E = 0$  [ $I_E \approx I_C$ ]

i.e.,  $V_{CE} = V_{CC} - I_C (R_C + R_E)$

8	CO1	L2
---	-----	----

b. Explain relaxation oscillator


6

CO1

L3

**Solution:**

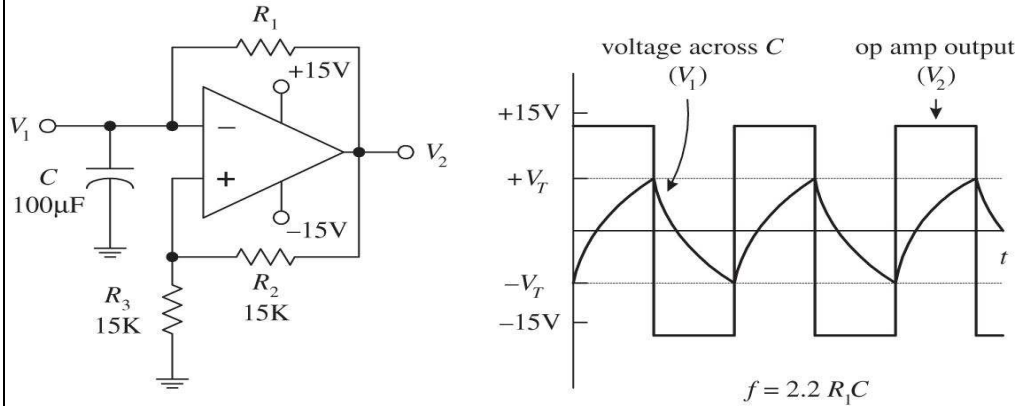**Simple Square-Wave Relaxation Oscillator**



Oscillator generally refers to the circuit which produces periodic and repetitive output like a sine wave or square wave. An oscillator can be a mechanical or electronic construction that produces oscillation depending on a few variables.

c. Write a note on opto coupler


6

**Construction:**

All optocouplers consist of two elements: a light source (a LED) and a photosensor (a photoresistor, photodiode, phototransistor, silicon-controlled rectifier (SCR), or triac); which are separated by a dielectric (non-conducting) barrier.

 
**Working Principle:**

When input current is applied to the LED, it switches ON and emits infrared light; the photosensor then detects this light and allows current to flow through the output side of the circuit; conversely, when the LED is off, no current will flow through the photosensor. By this method, the two flowing currents are electrically isolated. It consists of LED and photodiode; where the circuits are isolated electrically. In the following Figure, LED is forward biased, photodiode is reverse biased and output exists across  $R_2$ .




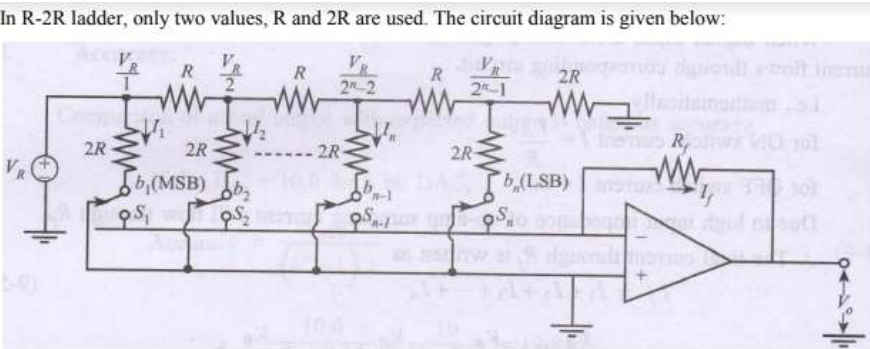The Figure describes the basic operation of an optocoupler. When current is not being applied via Pin 1, the LED is off, and the circuit connected to Pins 4 and 5 is experiencing no current flow. When power is applied to the input circuit, the LED switches on, the sensor detects the light, closes the switch and initiates current flow in the output circuit, as shown in the Figure



2	<p>a. Explain active filter. List advantages of active filters over passive filters.</p> <p><b>Solution:</b>  Filter is a frequency selective circuit commonly used in signal processing that passes signal of specified range of frequencies and blocks the signals of frequencies outside the band. Active filters are attractive due to their –</p> <ul style="list-style-type: none"> <li>• Flexibility in gain control</li> <li>• Small component size</li> <li>• No loading Problem</li> <li>• Pass band gain</li> <li>• Use of the inductors can be avoided</li> </ul> <p>Filters are useful in many areas of applications, such as Communication and Signal Processing. They are found in electronic systems like Radio, Television, Telephones, Radars, satellites, and Biomedical instruments.</p> <p>Active filters offer the following advantages over Passive filters:</p> <ul style="list-style-type: none"> <li>• Gain and frequency adjustment flexibility</li> <li>• No loading problem &amp; No insertion loss</li> <li>• Size and weight</li> <li>• Cost.</li> </ul> <p>Most commonly used active filters are –</p> <ul style="list-style-type: none"> <li>• Low-pass filter, High-pass filter, Band-pass filter, Band-stop filter (Band-reject filter), and All-pass filter.</li> </ul>	06	CO1	L2
	<p>b. Explain with diagram, R-2R ladder type D to A converter</p> <p><b>Solution:</b></p>  <p>In R-2R ladder, only two values, R and 2R are used. The circuit diagram is given below:</p> <p>Each binary bit connects switch either to ground (non-inverting input) or to the inverting terminal of Op-Amp. Due to virtual ground, both the positions of the switches are at ground potential, and currents through the resistances are constant.</p> <p>The current flowing through each of 2R resistances;</p> $I_1 = \frac{V_R}{2R} \quad I_2 = \frac{V_R/2}{2R} = \frac{V_R}{4R} \quad I_3 = \frac{V_R/4}{2R} = \frac{V_R}{8R} \quad I_n = \frac{V_R/(2^n - 1)}{2R}$ <p>But, <math>V_0 = -I_f R_f = -R_f (I_1 + I_2 + \dots + I_n)</math></p> <p>i. e., <math>V_0 = -R_f \left[ \frac{V_R}{2R} b_1 + \frac{V_R}{4R} b_2 + \dots + \frac{V_R}{2^n R} b_n \right]</math></p> <p>Or, <math>V_0 = -\frac{V_R}{R} R_f [b_1 2^{-1} + b_2 2^{-2} + \dots + b_n 2^{-n}]</math></p> <p>If <math>R_f = R</math>; <math>V_0 = -V_R [b_1 2^{-1} + b_2 2^{-2} + \dots + b_n 2^{-n}]</math></p>	8	CO1	L2
	<p>c. Define op-amp. Explain the performance parameters of op-amp.</p> <p><b>Solution:</b>  An Op-Amp is a direct-coupled high gain, high bandwidth differential amplifier with very high value of input impedance and very low value of output impedance.</p>	06		

	<p>The ideal Op-Amp model was derived to simplify circuit calculations. The ideal Op-Amp model makes three assumptions:</p> <ol style="list-style-type: none"> <li>1. Input resistance (impedance), <math>R_i = \infty</math></li> <li>2. Output resistance (impedance), <math>R_o = 0</math></li> <li>3. Open-loop (differential voltage) gain, <math>A_d = \infty</math></li> </ol> <p>Based on these three assumptions, other assumptions can be derived:</p> <ol style="list-style-type: none"> <li>1. Since <math>R_i = \infty</math>, <math>I_i = I_{in} = 0</math></li> <li>2. Since <math>R_o = 0</math>, <math>V_o = A_d * V_d</math></li> <li>3. Zero DC input and output offset voltages</li> <li>4. Bandwidth and slew rate are also infinite, as no frequency dependencies are assumed.</li> <li>5. Drift is also zero, as there is no changes in performance over time, temperature, power supply variations, and so on</li> <li>6. Since output voltage depends only on differential input voltage, it rejects any voltage common to both inputs. Hence, common mode gain = 0</li> </ol>			
3	<p>a. Explain don't care conditions with an example.</p> <p><b>Solution:</b></p> <p>The Don't Care conditions allow us to replace the empty cell of a K-Map to form a grouping of the variables which is larger than that of forming groups without don't care. While forming groups of cells, we can consider a Don't Care cell as 1 or 0 or we can also ignore that cell. Therefore, the "Don't Care" condition can help us to form a larger group of cells.</p> <p><b>Minimise the following function in SOP minimal form using K-Maps:</b></p> <div style="background-color: #e0e0e0; padding: 10px; margin: 10px 0;"> <math display="block">f = m(1, 5, 6, 11, 12, 13, 14) + d(4)</math> </div> <p><b>Explanation:</b></p> <p>The SOP K-map for the given expression is:</p>	4	CO3	L2

 

therefore, SOP minimal is,

$$f = BC' + BCD' + A'C'D + AB'CD$$


- b. Reduce the following function using k Map  $S = F(A, B, C, D) = \sum m(0,1,4,8,9,10) + d(2,11)$

8


CO3

L2

Solution:

 
 
$$S = \bar{A}\bar{C}\bar{D} + \bar{B}\bar{D} + \bar{B}C$$




$$S = \bar{A}\bar{C}\bar{D} + \bar{B}\bar{D} + \bar{B}C$$

- c. Using QM method, simplify the expression  $f(p,q,r,s) = \sum m(0,3,5,6,7,11,14)$

8

Solution:

 

4

a. Explain entered variable map method

5

CO3

L2

**Solution:**

**Minimization procedure for VEM** – Now, let's see how to find SOP expression if a VEM is given.

1. Write all the variables(original and complimented forms are treated as two different variables) in the map as 0, leave 0's, minterms and don't cares as it is and obtain the SOP expression.
2. (a) Select one variable and make all occurrences of that variable as 1, write minterms (1's) as don't cares, leave 0's and don't cares as it is. Now, obtain the SOP expression.  
(b) Multiply the obtained SOP expression with the concerned variable.
3. Repeat step 2 for all the variables in the k-map.
4. SOP of VEM is obtained by ORing all the obtained SOP expressions.


b. Apply QM method to find the essential prime implicants for the Boolean expression  $f(a,b,c,d) = \sum m(1,3,6,7,9,10,12,13,14,15)$

7

CO1


L2



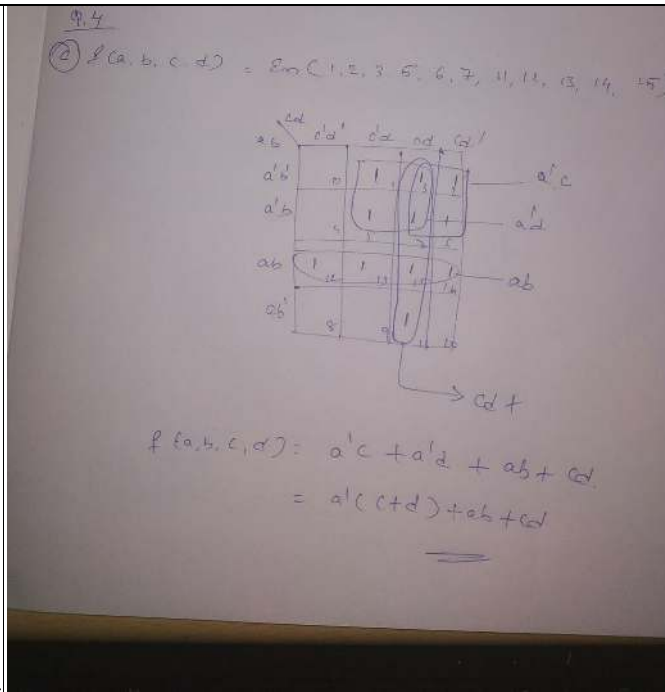

c. For the below expression, draw the logic diagram using AOI logic for minimal sum. Obtain minimal sum using K-map

8

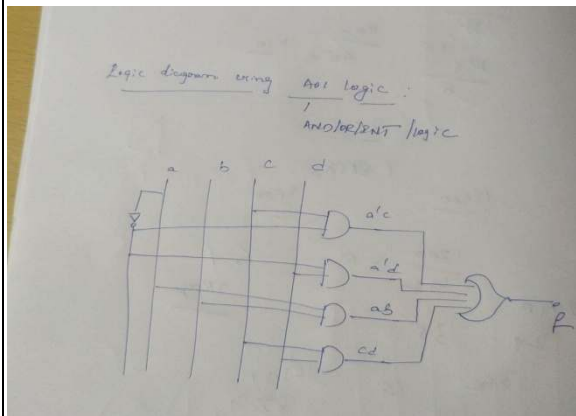

5 a. What is hazard? List the types of hazards. Explain static 0 and static 1 hazard.

6

CO4

L2

**Solution:**

**HAZARDS & HAZARD COVERS**

- The unwanted switching transient that may appear at the output of a circuit are called **hazards**.
- The hazards cause the circuit to malfunction.
- The main cause of hazards is the different propagation delays at different paths.
- Here we consider, 1) Static-1 hazard 2) Static-0 hazard & 3) Dynamic hazard.

**STATIC-1 HAZARD**

- In a combinational circuit, if output goes momentarily 0 when it should remain a 1, the hazard is known as **static-1 hazard** (Figure: 3.34).
- Static-1 hazard occurs when
  - $Y = A + A'$  type of situation appears in a logic circuit.
  - 'A' makes a transition 1→0
- Here is how static-1 hazard occurs:
  - > An  $A + A'$  condition should always generate 1 at the output, i.e. static-1.
  - > But the NOT gate output takes finite time to become 1 following 1→0 transition of A.
  - > Thus for OR gate, there are 2 zeros appearing at its input for the small duration, resulting a 0 at its output.
  - > The width of this zero is in nanosecond order and is called a **glitch**.
- In combinational circuits, static-1 hazard may not cause any serious problem. But in sequential circuit, static-1 hazard may cause major malfunctioning.

 


Figure 3.34: Static-1 hazard

**STATIC-0 HAZARD**

- In a combinational circuit, if output goes momentarily 1 when it should remain a 0, the hazard is known as **static-0 hazard** (Figure: 3.36).
- Static-0 hazard occurs when
  - $Y=AA'$  type of situation appears in a logic circuit.
  - 'A' makes a transition  $0 \rightarrow 1$ .
- Here is how static-0 hazard occurs:
  - An  $AA'$  condition should always generate 0 at the output, i.e. static-0.
  - But the NOT gate output takes finite time to become 0 following  $0 \rightarrow 1$  transition of A.
  - Thus for AND gate, there are 2 ones appearing at its input for the small duration, resulting a 1 at its output.
  - The width of this zero is in nanosecond order and is called a **glitch**.

 


Figure 3.36: Static-0 hazard

 


Figure 3.37: Static-0 hazard and its cover

b. Differentiate between combinational and sequential circuit.

6

CO4

L1


**Solution:**

Combinational Circuit	Sequential Circuit
1 It does not contain memory elements.	It contains memory elements.
2 Output depends on the present state of input only.	Output depends not only on the present inputs but also on the past history of inputs.
3 Its behavior is described by the set of output functions.	Its behavior is described by the set of next-state (memory) functions and the set of output functions.
4 Do not use the Feedback path.	Use Feedback path.
5 Does not require a clock signal.	Most sequential circuits use a clock signal.
6 Faster than the sequential circuit.	Slower than the combinational circuit.
7 <b>Example:</b> Adder, Subtractor, MUX, Encoders, etc.	<b>Example:</b> Flip Flops, Registers, Counters, etc.

c. Implement the following using PLA A=(1,2,4,6) B=(0,1,6,7) C=(2,6)

8

**Solution:**

 


6 a. Implement the following function using 8:1 multiplexer  
 $F(a,b,c,d) = \sum m(0,1,5,6,8,10,12,15)$

7 CO5 L3

**Solution:**

Implementation Table :

	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
$\bar{a}$	0	1	2	3	4	5	6	7
a	8	9	10	11	12	13	14	15
	1	$\bar{a}$	a	0	a	$\bar{a}$	$\bar{a}$	a

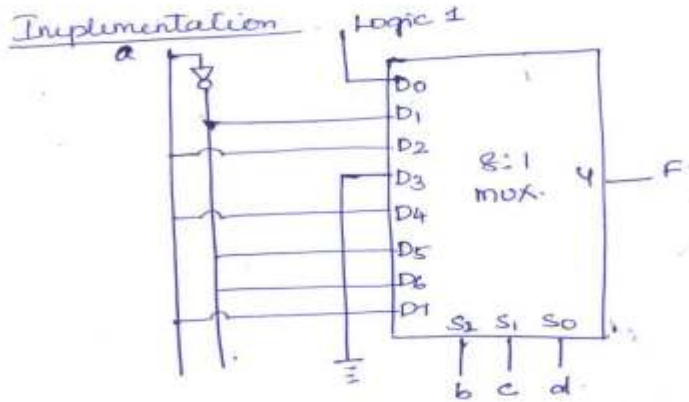

b. What is programmable logic array? How does PLA differ from PAL?


6 CO5 L2

**Solution:**

A programmable logic array (PLA) is a kind of programmable logic device used to implement combinational logic circuits.

S.NO	<p>PLA</p> <p>PAL</p> <ol style="list-style-type: none"> <li>PLA stands for Programmable Logic Array. While PAL stands for Programmable Array Logic.</li> <li>PLA speed is lower than PAL. While PAL's speed is higher than PLA.</li> <li>The complexity of PLA is high. While PAL's complexity is less.</li> <li>The cost of PLA is also high. While the cost of PAL is low.</li> <li>Programmable Logic Array is less available. While Programmable Array Logic is more available than Programmable Logic Array.</li> </ol>			
------	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--	--	--

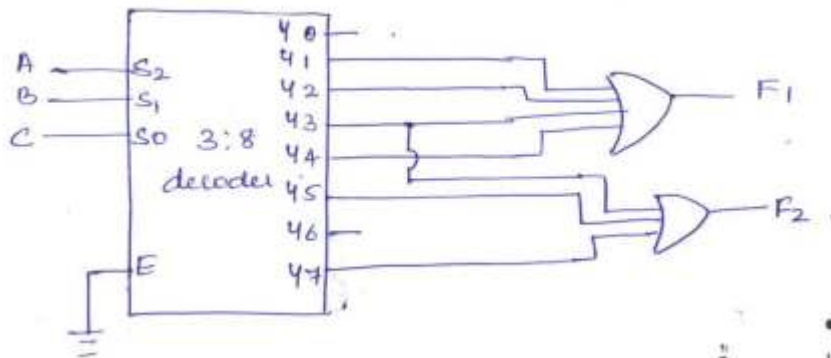c. Realize the following using 3:8 decoder  
 i)  $f(a,b,c) = \sum m(1,2,3,4)$     ii)  $f(a,b,c) = \sum m(3,5,7)$



7

7	<p>a. What are the three different models for writing a module body in VHDL?          Give example for any one model</p> <p><b>Solution:</b></p> <p>The difference between these styles is based on the type of concurrent statements used:</p> <ul style="list-style-type: none"> <li>A <u>dataflow</u> architecture uses only concurrent signal assignment statements.</li> <li>A <u>behavioral</u> architecture uses only process statements.</li> <li>A <u>structural</u> architecture uses only component instantiation statements.</li> </ul>	6	CO2	L2
---	---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	---	-----	----

```

library ieee;
use ieee.std_logic_1164.all;

entity half_adder is
port (a, b: in std_logic;
      sum, carry_out: out std_logic);
end half_adder;

architecture dataflow of half_adder is
begin
sum <= a xor b;
carry_out <= a and b;
end dataflow;

```

b. Derive characteristics equations for JK,T,D and SR flip flop

8

CO4


L2

**Solution:**


**SR Flip-Flop:**




**D Flip-Flop:**

 

**JK Flip-Flop:**

 

**T Flip-Flop:**

 

The characteristic equations for the latches and flip-flops discussed so far are:

$Q^+ = S + R'Q$ ( $SR = 0$ )	(S-R latch or flip-flop)
$Q^+ = GD + G'Q$	(gated D latch)
$Q^+ = D$	(D flip-flop)
$Q^+ = D \cdot CE + Q \cdot CE'$	(D-CE flip-flop)
$Q^+ = JQ' + K'Q$	(J-K flip-flop)
$Q^+ = T \oplus Q = TQ' + T'Q$	(T flip-flop)

c. Give VHDL code for 4:1 multiplexer using conditional assign statement.

**Solution:**

```

library IEEE; use IEEE.STD_LOGIC_VECTOR_1164.all;
entity mux4 is
port(d0, d1,
      d2, d3: in STD_LOGIC_VECTOR(3 downto 0);
      s: in STD_LOGIC_VECTOR(1 downto 0);
      y: out STD_LOGIC_VECTOR(3 downto 0));
end;
architecture synth1 of mux4 is
begin
y <=& d0 when s = &quot;00&quot;; else
d1 when s = &quot;01&quot;; else
d2 when s = &quot;10&quot;; else
d3;
end;

```

6



8

a. Using structural model, write VHDL code for Half Adder.

6

CO5

L2

**Solution:**

```

library ieee;
use ieee.std_logic_1164.all;

entity half_adder is          -- Entity declaration
  port (a, b: in std_logic;
        sum, carry_out: out std_logic);
end half_adder;

architecture structure of half_adder is  -- Architecture body

  component xor_gate          -- xor component declaration
    port (i1, i2: in std_logic;
          o1: out std_logic);
  end component;

  component and_gate          -- and component declaration
    port (i1, i2: in std_logic;
          o1: out std_logic);
  end component;

begin
  u1: xor_gate port map (i1 => a, i2 => b, o1 => sum);
  u2: and_gate port map (i1 => a, i2 => b, o1 => carry_out);
-- We can also use Positional Association
-- => u1: xor_gate port map (a, b, sum);
-- => u2: and_gate port map (a, b, carry_out);
end structure;

```

b. Derive the excitation table for JK flip flop and SR flip flop. How SR flip flop is converted to T flip flop.

8

CO5

L2

**Solutions:**

S	R	Present state $Q_n$	Next state $Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

} Invalid states

$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

*Excitation table of SR flip flop*

J	K	Present state $Q_n$	Next state $Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


Truth table of JK flip flop

$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Excitation table of JK flip flop

c. With logic diagram explain JK flip flop.

Solution:

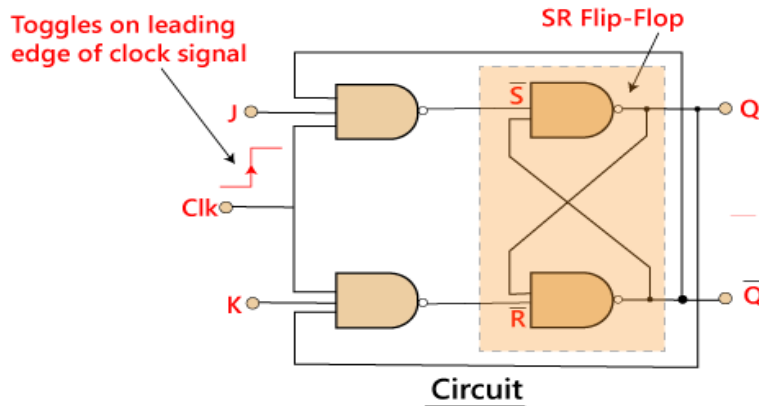

In SR flip flop, both the inputs 'S' and 'R' are replaced by two inputs J and K. It means the J and K input equates to S and R, respectively.

The two 2-input AND gates are replaced by two 3-input NAND gates. The third input of each gate is connected to the outputs at Q and Q'. The cross-coupling of the SR flip-flop permits the previous invalid condition of (S = "1", R = "1") to be used to produce the "toggle action" as the two inputs are now interlocked.

If the circuit is "set", the J input is interrupted from the "0" position of Q' through the lower NAND gate. If the circuit is "RESET", K input is interrupted from 0 positions of Q through the upper NAND gate. Since Q and Q' are always different, we can use them to control the input. When both inputs 'J' and 'K' are set to 1, the JK toggles the flip flop as per the given truth table.

Truth Table:

Same as for SR Latch	Clock	Input		Output		Description	
	Clk	J	K	Q	Q'		
	X	0	0	1	0	Memory no change	
	X	0	0	0	1		
	$\overline{\downarrow}$	0	1	1	0	Reset Q>>0	
	X	0	1	0	1		
	$\overline{\downarrow}$	1	0	0	0	1	Set Q>>1
	X	1	0	1	0	0	
Toggle action	$\overline{\downarrow}$	1	1	0	1	Toggle	
	$\overline{\downarrow}$	1	1	1	0		

9

a. Define counter. Design synchronous counter for the sequence 0,4,1,2,6,0,4 using JK flip flop.

8

**Solutions:**

$0 \rightarrow 4 \rightarrow 1 \rightarrow 2 \rightarrow 6 \rightarrow 0$

Present State			Next State			$J_2, K_2$		$J_1, K_1$		$J_0, K_0$	
$Q_2$	$Q_1$	$Q_0$	$Q_2^+$	$Q_1^+$	$Q_0^+$						
0	0	0	1	0	0	1	X	0	X	0	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	1	0	1	X	X	0	0	X
0	1	1	X	X	X	X	X	X	X	X	X
1	0	0	0	0	1	X	1	0	X	1	X
1	0	1	X	X	X	X	X	X	X	X	X
1	1	0	0	0	0	X	1	X	1	0	X
1	1	1	X	X	X	X	X	X	X	X	X

$J_2 = \overline{Q_0}$

$Q_1 \backslash Q_0$	00	01	11	10
0	1	0	X	1
1	X	X	X	X

$K_2 = Q_2$

$Q_1 \backslash Q_0$	00	01	11	10
0	X	X	X	X
1	1	X	X	1

$J_1 = \overline{Q_1} \overline{Q_0}$

$Q_1 \backslash Q_0$	00	01	11	10
0	0	1	X	X
1	X	X	X	0

$K_1 = Q_2$

$Q_1 \backslash Q_0$	00	01	11	10
0	X	X	X	0
1	X	X	X	1

$J_0 = Q_2 \overline{Q_1} \overline{Q_0}$

$Q_1 \backslash Q_0$	00	01	11	10
0	0	X	X	0
1	1	X	X	0

$\rightarrow J_0$

$K_0 = \overline{Q_1}$

$Q_1 \backslash Q_0$	00	01	11	10
0	X	X	X	X
1	X	X	X	X

$\rightarrow K_0$

b. What is shift register? With a neat diagram, explain 4 bit parallel in serial out shift register.

8

CO4

L2

**Solution:**


A shift register is a digital memory circuit found in calculators, computers, and data-processing systems. Bits (binary digits) enter the shift register at one end and emerge from the other end.

**Parallel-in to Serial-out (PISO) Shift Register**

The Parallel-in to Serial-out shift register acts in the opposite way to the serial-in to parallel-out one above. The data is loaded into the register in a parallel format in which all the data bits enter their inputs simultaneously, to the parallel input pins  $P_A$  to  $P_D$  of the register. The data is then read out sequentially in the normal shift-right mode from the register at  $Q$  representing the data present at  $P_A$  to  $P_D$ .


This data is outputted one bit at a time on each clock cycle in a serial format. It is important to note that with this type of data register a clock pulse is not required to parallel load the register as it is already present, but four clock pulses are required to unload the data.

 **4-bit Parallel-in to Serial-out Shift Register**



c. Write a note on sequential parity checker.

**Solutions:**

 

The sequential circuit must *remember* whether the total number of 1 inputs received is even or odd; therefore, only two states are required. We will designate these states as  $S_0$  and  $S_1$ , corresponding respectively to an even number of 1's received and an odd number of 1's received. We will start the circuit in state  $S_0$  because initially zero 1's have been received, and zero is an even number.

As indicated in state graph (above Figure), if the circuit is in state  $S_0$  (even number of 1's received) and  $X = 0$  is received, the circuit must stay in  $S_0$  because the number of 1's received is still even. However, if  $X = 1$  is received, the circuit goes to state  $S_1$  because the number of 1's received is then odd.

Similarly, if the circuit is in state  $S_1$  (odd number of 1's received) a 0 input causes no state change, but a 1 causes a change to  $S_0$  because the number of 1's received is then even.

The output  $Z$  should be 1 whenever the circuit is in state  $S_1$  (odd number of 1's received). The output is listed below the state on the state graph.

4

CO4

L2

10

a. With a neat diagram, explain ring counter

**Solutions:**

Working of Ring Counter

Ring counter's state needs to be set before the operation. Since ring counter circulates 1 through all stages, and there are no external inputs except the clock signal. So we need to set its state to initial state 1000 manually. We need to set the first stage flip-flop and clear the rest of the stages to obtain the state 1000. The preset input pin is designed to do this function. The schematic of ring counter is given below:

6

CO5

L2





Step 4

K-map simplification

For  $J_C$

$Q_B Q_A$ \ $Q_C$	00	01	11	10
0	0	0	1	0
1	x	x	x	x

$J_C = Q_B Q_A$

For  $K_C$

$Q_B Q_A$ \ $Q_C$	00	01	11	10
0	x	x	x	x
1	1	x	x	x

$K_C = 1$

For  $K_B$

$Q_B Q_A$ \ $Q_C$	00	01	11	10
0	x	x	1	0
1	x	x	x	x

$K_B = Q_A$

For  $J_A$

$Q_B Q_A$ \ $Q_C$	00	01	11	10
0	1	x	x	1
1	0	x	x	x


$J_A = \bar{Q}_C$

For  $K_A$

$Q_B Q_A$ \ $Q_C$	00	01	11	10
0	x	1	1	x
1	x	x	x	x

$K_A = 1$

Step 5 Logic Diagram

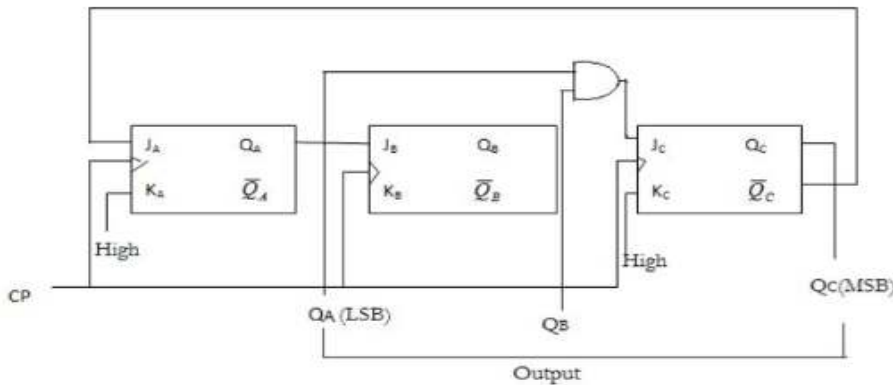


c. Write a note on parallel adder with accumulator.

Solution:

 **Parallel Adder with Accumulator:**

In computer circuits, it is frequently desirable to store one number in a register of flip-flops (called an accumulator) and add a second number to it, leaving the result stored in the accumulator.

One way to build a parallel adder with an accumulator is to add a register to the adder as shown in the following Figure.



Suppose that the number  $X = x_n \dots x_2 x_1$  is stored in the accumulator. Then, the number  $Y = y_n \dots y_2 y_1$  is applied to the full adder inputs, and after the carry has propagated through the adders, the sum of X and Y

<p>appears at the adder outputs. An add signal (Ad) is used to load the adder outputs into the accumulator flip-flops on the rising clock edge. If <math>s_i = 1</math>, the next state of flip-flop <math>x_i</math> will be 1. If <math>s_i = 0</math>, the next state of flip-flop <math>x_i</math> will be 0. Thus, <math>x_i^+ = s_i</math>, and if <math>Ad = 1</math>, the number X in the accumulator is replaced with the sum of X and Y, following the rising edge of the clock.</p> <p>Observe that the adder with accumulator is an iterative structure that consists of a number of identical cells. Each cell contains a full adder and an associated accumulator flip-flop. Cell <math>i</math>, which has inputs <math>c_i</math> and <math>y_i</math> and outputs <math>c_{i+1}</math> and <math>x_i</math>, is referred to as a typical cell.</p> <p>Before addition can take place, the accumulator must be loaded with X. This can be accomplished in several ways. The easiest way is to first clear the accumulator using the asynchronous clear inputs on the flip-flops, and then put the X data on the Y inputs to the adder and add to the accumulator in the normal way. Alternatively, we could add multiplexers at the accumulator inputs so that we could select either the Y input data or the adder output to load into the accumulator. This would eliminate the extra step of clearing the accumulator but would add to the hardware complexity.</p>		
----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--	--