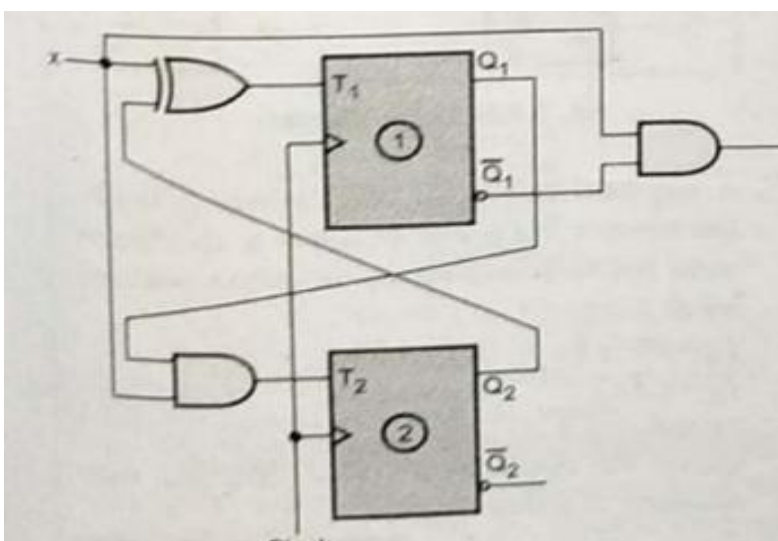
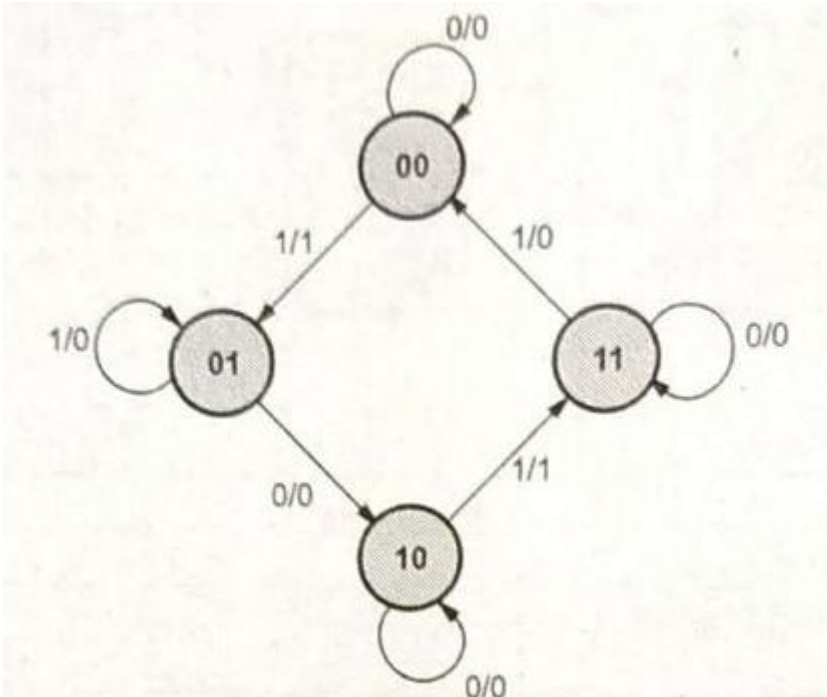
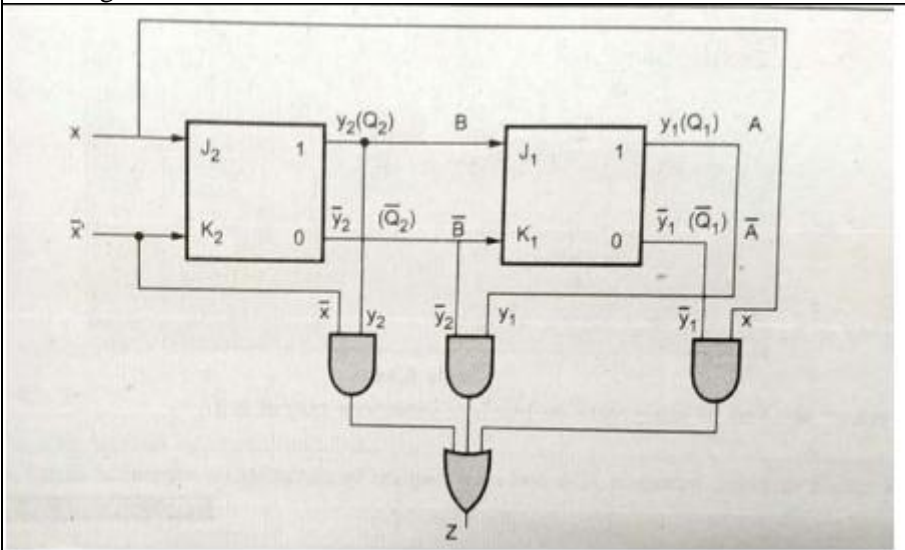


Internal Assessment Test - IV

Sub:	DIGITAL SYSTEM DSEIGN						Code:	18EE35		
Date:	21/03/2022	Duration:	3 HRS	Max Marks:	100	Sem:	3 rd	Branch:	EEE	
Answer Any 10 Questions										
								Marks	OBE	
									CO	RBT
1	Find a minimum SOP solution using Quine-McCluskey method $F(a,b,c,d)=\sum m(2,3,4,5,13,15) +d(8,9,10,11).$						10	CO1	L3	
2	Staircase light is controlled by two switches; one at the top of the stair and the other at the bottom of the stair: (a) Make a truth table for this system. (b) Write the logic equations in the POS form. (c) Realize the circuit using basic gates. (d) Realize the circuit using minimum number of NAND gates.						10	CO1	L2	
3	Simplify the following using K-map and define combinational logic: $Y=f(a,b,c,d)= \pi M (0,4,5,7,8,9,11,12,13,15).$						10	CO1	L3	
4	Simplify using K-Map $Y=f(a,b,c,d,e)=\sum m(1,3,4,6,9,11,12,14,17,19,20,22,25,27,28,30)+ \sum d(8,10,24,26)$						10	CO1	L3	
5	Differentiate synchronous and asynchronous counter. Mention the four different modes of operation shift registers.						10	CO3	L3	
6	Design a Mod 6 ripple counter using T flip-flop.						10	CO3	L3	
7	Design a synchronous counter with counting sequence 3,2,5,1,0,3...using D-flipflops						10	CO3	L3	
8	With a neat logic diagram explain the different modes of operation of universal shift register						10	CO3	L3	
9	Analyse the following sequential logic circuit shown in the figure below. Obtain the excitation and output equation, transition table and state table. Also draw a state diagram.						10	CO4	L3	
										

10	<p>Construct a sequential circuit by obtaining the state and excitation table for the given diagrams using JK flipflop</p> 	10	CO4	L3
----	---	----	-----	----

11	<p>Analyse the following sequential logic circuit shown in the figure below. Obtain the excitation and output equation, transition table and state table. Also draw a state diagram</p> 	10	CO4	L3
----	---	----	-----	----

CCI

HOD\

SOLUTION

1.

on : Step 1 : List all minterms in binary form.

Minterms	Binary representation			
m_2	0	0	1	0
m_3	0	0	1	1
m_4	0	1	0	0
m_5	0	1	0	1
m_{13}	1	1	0	1
m_{15}	1	1	1	1
dm_8	1	0	0	0
dm_9	1	0	0	1
dm_{10}	1	0	1	0
dm_{11}	1	0	1	1

Step 2 : Arrange the minterms according to number of 1's.

Minterms	Binary representation			
m_2	0	0	1	0
m_4	0	1	0	0
m_8	1	0	0	0
m_3	0	0	1	1
m_5	0	1	0	1
m_9	1	0	0	1
m_{10}	1	0	1	0
m_{11}	1	0	1	1
m_{13}	1	1	0	1
m_{15}	1	1	1	1

Step 3 :

Minterm	Binary representation			
2, 3 ✓	0	0	1	-
2, 10 ✓	-	0	1	0
4, 5	0	1	0	-
8, 10 ✓	1	0	-	0
8, 9 ✓	1	0	0	-
3, 11 ✓	-	0	1	1
5, 13	-	1	0	1
9, 13 ✓	1	-	0	1
9, 11 ✓	1	0	-	1
10, 11 ✓	1	0	1	-
13, 15 ✓	1	1	-	1
11, 15 ✓	1	-	1	1

Step 4 :

Minterm				Binary representation			
2,	3,	10,	11	-	0	1	-
8,	9,	10,	11	1	0	-	-
9,	11,	13,	15	1	-	-	1

Step 5 :

Prime implicants				Binary representation			
\bar{a}	b	\bar{c}	4, 5	0	1	0	-
b	\bar{c}	d	5, 13	-	1	0	1
\bar{b}	c		2, 3, 10, 11	-	0	1	-
a	\bar{b}		8, 9, 10, 11	1	0	-	-
a	d		9, 11, 13, 15	1	-	-	1

Step 6 :

Prime implicants	m_2	m_3	m_4	m_5	m_{13}	m_{15}	dm_3	dm_5	dm_{10}	dm_{11}
$\bar{a} b \bar{c}$ 4, 5			⊙	⊙						
$b \bar{c} d$ 5, 13				*	*					
$\bar{b} c$ 2, 3, 10, 13	⊙	⊙			⊙				⊙	
$a \bar{b}$ 8, 9, 10, 11							*	*	*	*
$a d$ 9, 11, 13, 15					⊙	⊙		⊙		⊙

$\therefore Y = \bar{b}c + \bar{a}b\bar{c} + ad$

2.

 


Fig.(a) Circuit diagram

a. The truth table for the system is illustrated in given truth table

S1	S2	L
0	0	0
0	1	1
1	0	1
1	1	0

b. The logic equation for given system is specified by $L = S_1 \bar{S}_2 + S_1 S_2$

c. Realization of given case, the circuit using AND-OR gates is demonstrated in fig (b)



 


Fig.(b) Logic Diagram for the system

3.

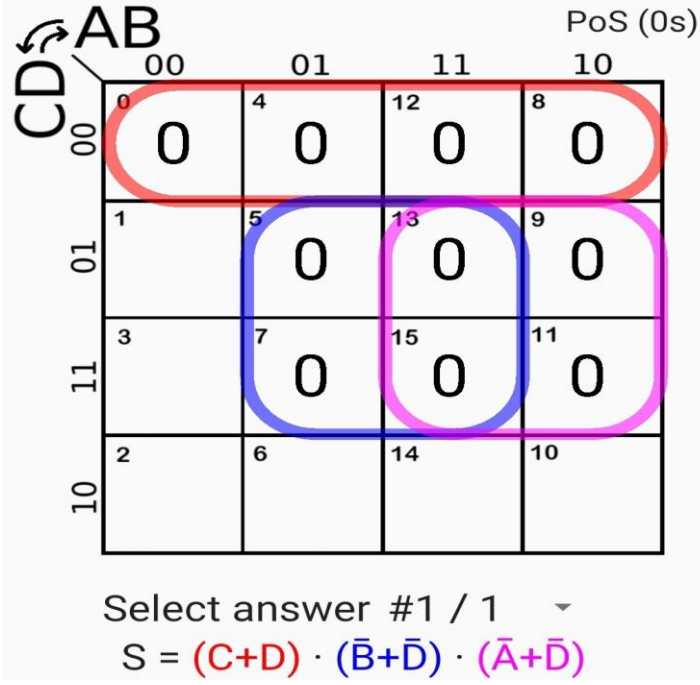

4.

 

5.

Difference between Synchronous and Asynchronous Counter

S.No.	Synchronous Counter	Asynchronous Counter
1.	In the synchronous counter there are continuous clock input signals with flip-flops used to produce the output.	In Asynchronous counters there are different clock signals used to produce the output.
2.	In the synchronous counter, the operation is faster.	In Asynchronous counter the operation is slower.
3.	Synchronous counter is also known as Parallel counter.	Asynchronous counter is also known as Serial counter.
4.	Synchronous counter produces less error than asynchronous counter.	Asynchronous counter produces more errors than a synchronous counter.
5.	Design of the Synchronous counter is complex.	Design of the Asynchronous counter is simple.
6.	Synchronous counters can work with a flexible number of count sequences.	Asynchronous counters can work with a fixed number of count sequences.

There are four basic modes of operation based on the movement of data in the Registers and they are:

- Serial In – Serial Out (SISO) Mode.
- Serial In – Parallel Out (SIPO) Mode.
- Parallel In – Serial Out (PISO) Mode.
- Parallel In – Parallel Out (PIPO) Mode.

6.

Solution :

Step 1 : Determine the number of flip-flop required. Here, counter goes through 0 - 5 states, i.e., total 6 states. Thus $N = 6$ and for $2^n \geq N$ we need $n = 3$, i.e. 3 flip-flops.


Step 2 : Type of flip-flops to be used : T


Step 3 : Write the truth table for counter

CLK	A	B	C	Output of reset logic Y
0	0	0	0	1
1	0	0	1	1
2	0	1	0	1
3	0	1	1	1
4	1	0	0	1
5	1	0	1	1
-	1	1	0	0
-	1	1	1	0


Valid states: 0, 1, 2, 3, 4, 5
Invalid states: -, -

Step 4 : Derive reset logic

 

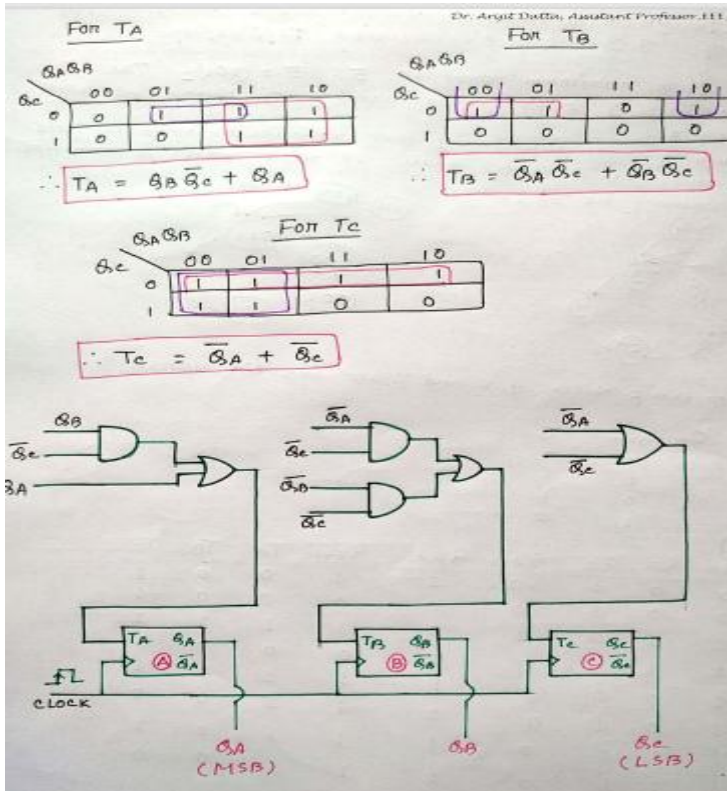

8.

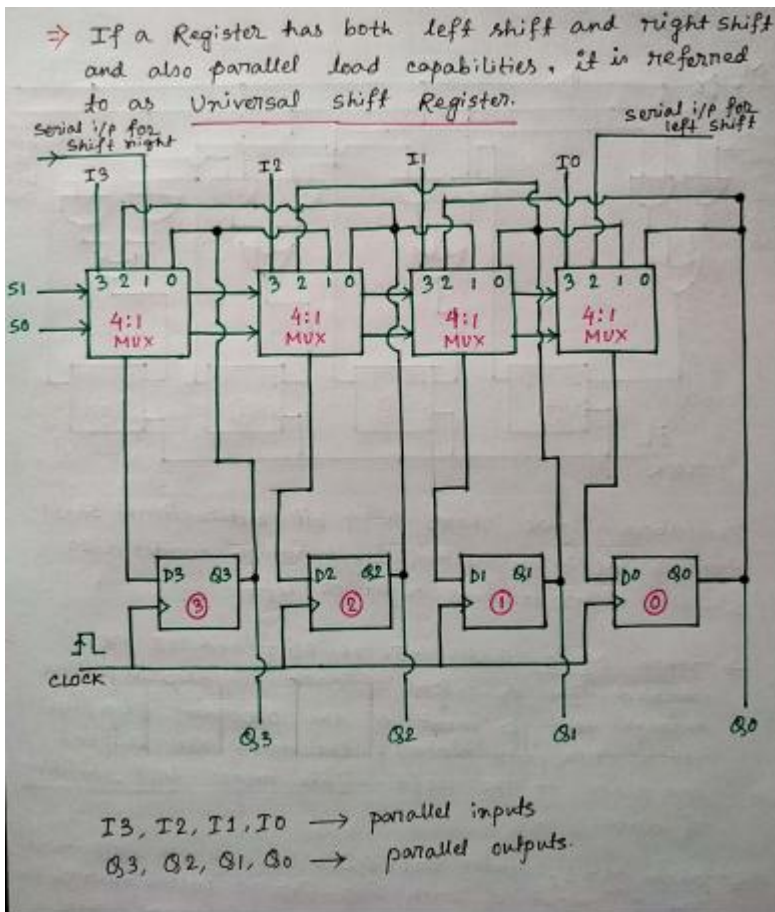

→ It consists of 4 flip-flops and 4 Multiplexers. The four Multiplexers have two common select inputs S_1 and S_0 , and they select appropriate input for D flip-flop. The below table shows the register operation depending on the select lines of multiplexer.

Mode Control		Register Operation
S_1	S_0	
0	0	No change
0	1	Shift Right
1	0	Shift Left
1	1	parallel Load

- When $S_1 S_0 = 00$, input 0 is selected and the present value of the register is applied to the D inputs of the flip-flops. This results no change in Register value.
- When $S_1 S_0 = 01$, input 1 is selected and circuit connections are such that it operates as a right shift Register.
- When $S_1 S_0 = 10$, input 2 is selected and circuit connections are such that it operates as a left shift Register.
- Finally when $S_1 S_0 = 11$, the binary information on the parallel input lines is transferred into the register simultaneously and it is a parallel load operation.

9.

Sol : Step 1 : Excitation and output equations.

$$Z = x\bar{Q}_1$$

$$T_1 = x\bar{Q}_2 + \bar{x}Q_2 = x \oplus Q_2$$

$$T_2 = xQ_1$$

Step 2 : Transition equations

The transition equation for T flip-flop is,

$$Q^+ = T \oplus Q$$

$$Q_1^+ = x \oplus Q_2 \oplus Q_1$$

$$Q_2^+ = xQ_1 \oplus Q_2$$

Step 3 : Next state map for each flip-flop

For Q_1^+

	x	0	1
$Q_2 Q_1$	00	0	1
	01	1	0
	10	1	0
	11	0	1

For Q_2^+

	x	0	1
$Q_2 Q_1$	00	0	0
	01	0	1
	10	1	1
	11	1	0

K-Map not required

Step 4 : Excitation table


Present state		Next state				Output Z	
Q_2	Q_1	$x = 0$		$x = 1$		$x = 0$	$x = 1$
		Q_2^+	Q_1^+	Q_2^+	Q_1^+		
0	0	0	0	0	1	0	1
0	1	0	1	1	0	0	0
1	0	1	1	1	0	0	1
1	1	1	0	0	1	0	0

Step 5 : State table

Assuming a = 00, b = 01, c = 10 and d = 11 we have

Present state	Next state		Output Z	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	1
b	b	c	0	0
c	d	c	0	1
d	c	b	0	0

Step 6 : State diagram

 

10.

Sol. :

Step 1 : State table

Present state	Next state	Output			
		x = 0	x = 1		
A	B	A, B	A, B	Y	Y
0	0	0 0	0 1	0	1
0	1	1 0	0 1	0	0
1	0	1 0	1 1	0	1
1	1	1 1	0 0	0	0

Table 5.5.27

Step 2 : K-map simplification :

$$D_A = \bar{x}B + A\bar{B}$$

 


Fig. 5.5.37 (a)

$$D_B = \bar{x}AB + x\bar{A} + x\bar{B}$$

 


Fig. 5.5.37 (b)


$$Y = x \bar{B}$$

For Y

	AB	00	01	11	10
x	0	0	0	0	0
	1	1	0	0	1

Fig. 5.5.37 (z)

Sequential circuit :

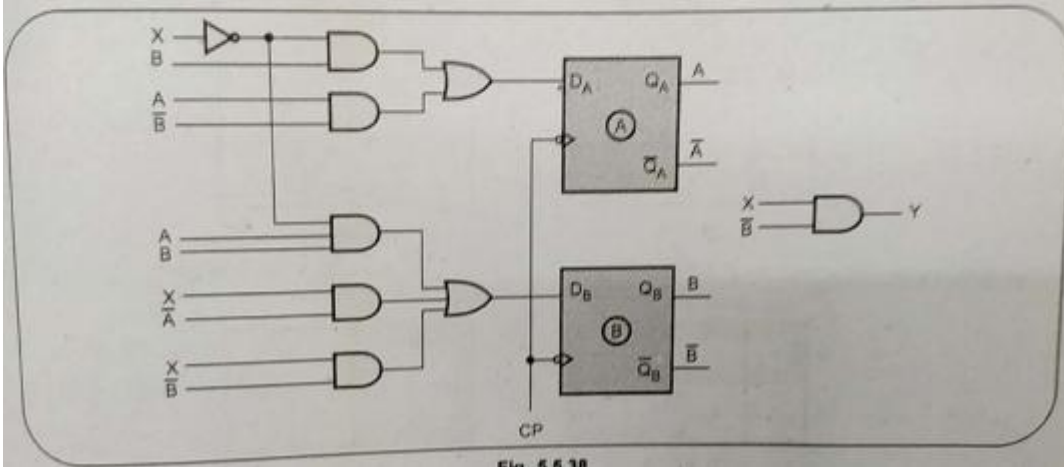

11.

Fig. 5.3.13

Sol. : The flip-flop input equations and output equations are,

$$J_2 = x \quad J_1 = y_2 \quad \text{and} \quad z = \bar{x}y_2 + \bar{y}_2y_1 + \bar{y}_1x$$

$$K_2 = \bar{x} \quad K_1 = \bar{y}_2$$

For JK flip-flop, $Q^+ = J\bar{Q} + \bar{K}Q$

$$\begin{aligned} J_2^+ = Q_2^+ &= J_2\bar{Q}_2 + \bar{K}_2Q_2 \\ &= x\bar{Q}_2 + xQ_2 = x\bar{y}_2 + xy_2 \end{aligned}$$

$$\begin{aligned} J_1^+ = Q_1^+ &= J_1\bar{Q}_1 + \bar{K}_1Q_1 \\ &= y_2\bar{Q}_1 + \bar{y}_2Q_1 \\ &= y_2\bar{y}_1 + y_2y_1 \\ &= y_2(\bar{y}_1 + y_1) = y_2 \end{aligned}$$

Next-state maps of each flip-flop.

		For J_2^+		For J_1^+	
	x	0	1	0	1
y_2y_1	00	0	1	0	0
	01	0	1	0	0
	10	0	1	1	1
	11	0	1	1	1
		$J_2^+ = x$		$J_1^+ = y_2$	

K-Map is not required

Fig. 5.3.13 (a)

Present state		Next state				Output z	
		x = 0		x = 1		x = 0	x = 1
y_2	y_1	y_2^+	y_1^+	y_2^+	y_1^+		
0	0	0	0	1	0	0	1
0	1	0	0	1	0	1	1
1	0	0	1	1	1	1	1
1	1	0	1	1	1	1	0