

IAT IV

①

Numericals.

(2b) Given Data. $\beta_{\min} = 10$

$$\beta_{\max} = 60.$$

$$R_C = 5\Omega; V_{CC} = 100V; V_{BB} = 8V$$

$$V_{CE}(\text{sat}) = 2.5V, V_{BE}(\text{sat}) = 1.75V$$

(i) $R_B = ?$ (ii) Forced $\beta = ?$ (iii) Total power loss.

$$ODF = 5$$

in saturation

(i) To find R_B in saturation.

$$I_{CS} = \frac{V_{CC} - V_{CE}(\text{sat})}{R_C} = \frac{100 - 2.5}{5} = 19.5A$$

$$I_{BS} = \frac{I_{CS}}{\beta} = \frac{I_{CS}}{\beta_{\min}} = \frac{19.5}{10} = 1.95A.$$

$$ODF = \frac{I_B}{I_{BS}} \Rightarrow I_B = ODF \times I_{BS} \\ = 5 \times 1.95 = 9.75A.$$

$$\boxed{I_B = 9.75A}$$

$$I_B = \frac{V_B - V_{BE}(\text{sat})}{R_B} \Rightarrow R_B = \frac{V_B - V_{BE}(\text{sat})}{I_B}$$

$$\boxed{R_B = 0.641A} \quad = \frac{8 - 1.75}{9.75} = 0.641A.$$

(2)

$$(ii) \text{ Forced } \beta = \beta_{\text{forced}} = \frac{I_{CS}}{I_B} = \frac{19.5}{9.75} = 2.$$

$$\boxed{\beta_{\text{forced}} = 2}$$

(iii) Total power loss.

$$P_T = V_{BE(\text{sat})} I_B + V_{CE(\text{sat})} I_{C(\text{sat})}$$

$$= (1.75 \times 9.75) + (2.5 \times 19.5)$$

$$\boxed{P_T = 65.8125 \text{ watts}}$$

(4b) Anti Saturation Control.

$V_{CC} = 100V, R_C = 1.5\Omega; V_{d1} = 2.1V; V_{d2} = 0.9$

$V_{d2} = 0.9V; V_{BE(sat)} = 0.7V; V_B = 15V$

$R_B = 2.5\Omega, \beta = 16.$

- 1) I_C without clamping.
- 2) I_C with clamping.
- 3) V_{CE} (CE clamping voltage).

(i) I_C without clamping.

$I_C = \beta I_B.$

$I_B = I_1 = \frac{V_B - V_{d1} - V_{BE}}{R_B} = \frac{15 - 2.1 - 0.7}{2.5}$

$I_B = 4.88 A.$

$I_C = \beta I_B = 16 \times 4.88 = 78.08 A.$

$I_C = 78.08 A$

(ii) ~~I_C~~ V_{CE} (Collector Emitter Clamping Voltage)

$V_{CE} = V_{BE} + V_{d1} - V_{d2} = 0.7 + 2.1 - 0.9$

$V_{CE} = 1.9V$

(iii) I_c with clamping.

$$I_c = \frac{\beta}{\beta + 1} (I_1 + I_L)$$

$$I_1 = I_B = 4.88 \text{ A.}$$

$$I_L = \frac{V_{cc} - V_{CE}}{R_c} = \frac{100 - 1.9}{1.5} = \underline{65.4 \text{ A.}}$$

$$I_c = \frac{\beta}{\beta + 1} (I_1 + I_L) = \frac{16}{16 + 1} (4.88 + 65.4)$$

$$I_c = 66.14 \text{ A}$$

(7b) $V_s = 200V$; $R = 10\Omega$; $f_s = 3\text{ KHz}$

$\frac{dv}{dt} = 100\text{ V}/\mu\text{s}$; $I_{TD} = 100\text{ A}$; $L = L_s = 0$.

- (i) R_s & $C_s = ?$ (ii) Snubber loss (iii) power rating of snubber circuit.

(i) To Find R_s .

$$R_s = \frac{V_s}{I_{TD}} = \frac{200}{100} = \underline{\underline{2\Omega}}$$

To Find C_s

$$\frac{dv}{dt} = \frac{0.632 R V_s}{C_s (R_s + R)^2}$$

$$\frac{100}{10^{-6}} = \frac{0.632 \times 10 \times 200}{C_s (2 + 10)^2}$$

$$C_s = \frac{0.632 \times 10 \times 200 \times 10^{-6}}{(2+10)^2 \times 100} = 0.088 \times 10^{-6}$$

$C_s = 0.088\ \mu\text{F}$


(ii) Snubber loss $P_s = 0.5 C_s V_s^2 f_s$
 $= 0.5 \times 0.088 \times 10^{-6} \times 200^2 \times 3 \times 10^3$
 $= \underline{\underline{5.28\text{ W}}}$

(iii) Power rating of snubber circuit = 5.28 W

8a

$$I_L = 200 \text{ mA}$$

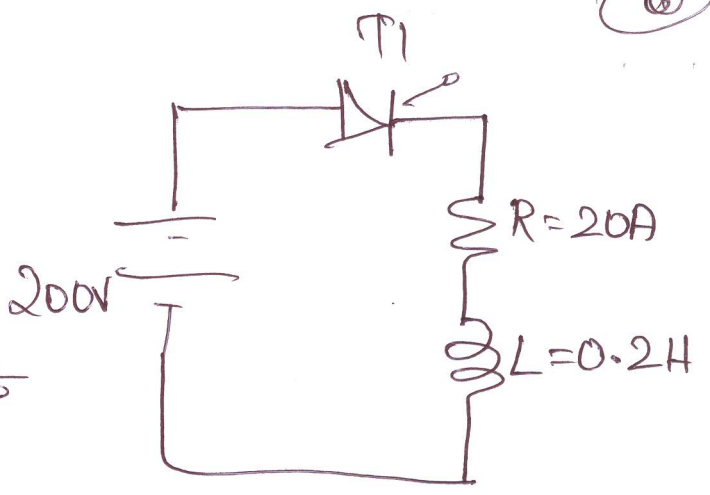Minimum width of gate pulse required to turn on the SCR.



$$V = 200 \text{ V}; R = 20 \Omega; L = 0.2 \text{ H}$$

When the circuit is ON, it will act as a RL circuit

RL Circuit

$$i(t) = \frac{V}{R} (1 - e^{-R/L t})$$

$$200 \times 10^{-3} = \frac{200}{20} (1 - e^{-\frac{20}{0.2} t})$$

$$0.02 = (1 - e^{-\frac{20}{0.2} t})$$

$$e^{-\frac{20}{0.2} t} = 1 - 0.02 = 0.98$$

$$-\frac{20}{0.2} t = \ln 0.98 = -0.02$$

$$t = 202 \mu\text{s}$$

$$(8b) \quad V_s = 200V; \quad t = 40 \mu s$$

(7)

$$I_L = 36 \text{ mA}, \quad R = 60 \Omega; \quad L = 2 \text{ H}.$$

(i) Will the thyristor get triggered?

To turn on the SCR $I(t) > I_L$.

$$i(t) = \frac{V}{R} (1 - e^{-R/Lt})$$

$$= \frac{200}{60} \left(1 - e^{-\frac{60}{2} \times 40 \times 10^{-6}} \right)$$

$$i(t) = 3.99 \times 10^{-3} \text{ A} = 3.99 \text{ mA}.$$

$i(t) < I_L$; $t = 40 \mu s$ is not the pulse width to turn on the device.

(ii) Pulse width for successful triggering.

$$i(t) = \frac{V}{R} (1 - e^{-R/Lt})$$

$$36 \times 10^{-3} = \frac{200}{60} \left(1 - e^{-\frac{60}{2} t} \right)$$

$$0.9892 = e^{-\frac{60}{2} t}$$

$$\ln 0.9892 = -\frac{60}{2} t$$

$$t = 0.3619 \text{ ms}$$

$$\boxed{t = 361.9 \mu s}$$