

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EE53

Fifth Semester B.E. Degree Examination, Feb./Mar. 2022 Power Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. With neat circuit diagram, input and output waveform, explain the different types of Power Electronics Converters. (10 Marks)
- b. With block diagram, explain the peripheral effects of power electronic equipment. (06 Marks)
- c. Compare the advantages and disadvantages of full wave bridge rectifier and full wave centre tapped transformer rectifier. (04 Marks)


OR

- 2 a. Briefly explain the different types of Power diodes and its applications. (08 Marks)
- b. List the applications of Power Electronics. (04 Marks)
- c. With circuit diagram and waveform, explain the working of single phase full wave uncontrolled rectifier with R load. (08 Marks)

Module-2

- 3 a. Explain Switching characteristics of BJT with waveforms. (08 Marks)
- b. A power BJT is connected as a switch as in figure Q3(b) with the following data. Calculate
 - i) The value of R_B that will result in saturation with an overdrive factor of 20.
 - ii) The forced β
 - iii) Power loss in the transistor. (06 Marks)

Fig. Q3(b)

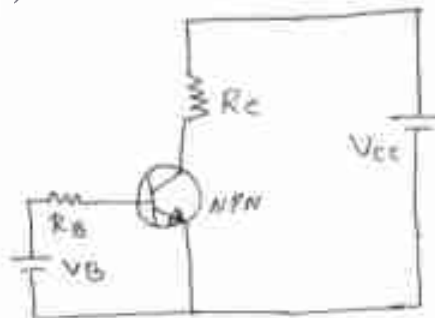

$V_{CC} = 100V$ $V_B = 8V$
 $V_{CE sat} = 2.5V$
 $V_{BE sat} = 1.75V$
 β of the transistor is varied from 10 to 60.
 $R_C = 10\Omega$


- c. Give a comparison between BJT and MOSFET. (06 Marks)

OR

- 4 a. Discuss the need of base drive control in a Power transistor. (08 Marks)
- b. A simple transistor switch is used to connect a 24V DC supply across a relay coil, which has a DC resistance of 200Ω . An input pulse of 0 to 5V amplitude is applied through a series base resistor R_B at the base so as to turn ON the transistor switch. Sketch the device current waveform with reference to the input pulse. Calculate :
 - i) $I_{C sat}$.
 - ii) Value of resistor R_B required to obtain over drive factor of 2.
 - iii) Total Power dissipation in the transistor that occurs during the saturation state. (06 Marks)

Modified

Fig. Q4(b)

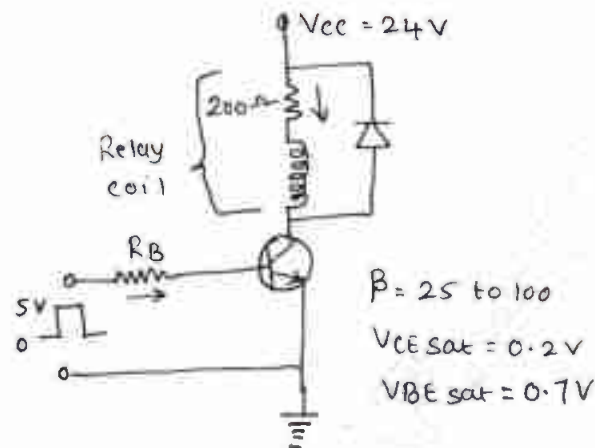

- c. Explain steady state characteristics of n channel MOSFET with necessary diagram.

(06 Marks)

Module-3

- 5 a. Explain the V.I characteristics of SCR also define :
 i) Holding current ii) Latching current. (12 Marks)
- b. Explain any four method of Turn – ON used for Thyristors. (04 Marks)
- c. The latching current of an SCR used in a phase controlled circuit. Comprising an inductive load of $R = 10\Omega$ and $L = 0.1H$ is 15mA. The input voltage is $325 \sin 314t$. Obtain the minimum gate pulse width required for reliable triggering of the SCR if gated at $\frac{\pi}{3}$ angle in every positive half cycle. (04 Marks)


OR

- 6 a. Derive an expression for anode current using two transistor model of Thyristor. (08 Marks)
- b. A UJT is connected across a 220V DC supply. The valley and peak point voltages are 1V and 15V. The period of UJT relaxation oscillator is 20MS. Find the value of charging capacitor, if a charging resistor of 100k Ω is used. (06 Marks)
- c. Explain Half wave RC firing circuit with necessary diagrams. (06 Marks)

Module-4

- 7 a. With the help of circuit diagram and waveform, explain the working of single phase full wave AC voltage controller with R load. (10 Marks)
- b. The single phase full wave AC voltage controller operates on a single phase supply voltage of 230V rms at 50Hz. If the triac is triggered at a delay angle of 45° during each half cycle of input supply. i) RMS value of output voltage ii) RMS value of current through heater iii) Average value of triac current iv) RMS value of triac current v) Input power factor. (10 Marks)

Fig. Q7(b)

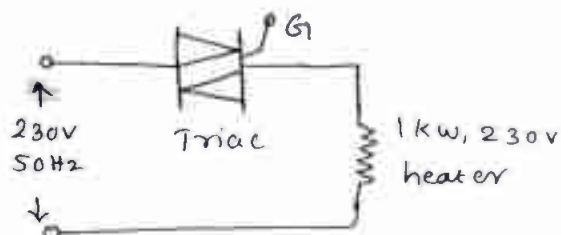

OR

- 8 a. Explain Half wave controlled rectifier with R_L load, without freewheeling diode. Draw necessary diagrams. (10 Marks)
- b. A single phase half wave converter is operated from a 120V , 50Hz supply and the load resistance $R = 10\Omega$. If the average output voltage is 25% of the maximum possible average output voltage calculate : i) Delay angle α ii) The rms and average output currents
iii) The average and rms thyristor currents iv) The input power factor. (10 Marks)

Module-5

- 9 a. A Chopper circuit drives an Inductive load from 200V DC supply. Given the load resistance as 4Ω , the average load current as 30A and operating frequency is 400Hz. Compute the ON period and OFF period of the Chopper. Also determine the duty cycle of the Chopper. (06 Marks)
- b. With the help of circuit and waveforms, explain the operation of step up Chopper. (08 Marks)
- c. Explain Performance Parameters of Chopper. (06 Marks)

OR


- 10 a. Explain Single Phase full bridge Inverter operation with R load. Draw necessary diagrams. (10 Marks)
- b. Draw and explain Single Phase Transistorised Current Source Inverter. (10 Marks)

* * * * *


Comments from BOE EEE, to the following Subjects Scheme & Solutions

Subject Code	Name of Subject	Comments from BOE EEE
18EE53	Power Electronics	<p>Q.No. 3(c) the tabular column should be MOSFET in the first column and BJT in the second column</p> <p>Q.No. 4 (c) it is not clearly mentioned whether it is for depletion mode or enhancement mode, the given answer is for enhancement mode but we need to consider the depletion mode answer also. (because in the question it is not mentioned whether it is depletion mode or enhancement mode) Give Marks for both mode as per the scheme steps</p>

Hence the may be considered for the further Process.


BOE Chairman 3/03/2022
EEE Composite Board
Dr. H L Suresh

Sir MVIT, Bangalore

" APPROVED "

Registrar (Evaluation)
JESVARAYA Technological University
RELAGAVI - 590018



Visvesvaraya Technological University
Belagavi, Karnataka - 590 018.


Scheme & Solutions



Signature of Scrutinizer



Subject Title : POWER ELECTRONICS

Subject Code : 18EE53

Question Number	Solution	Marks Allocated
11 a)	<p>a) Ac to Dc Converter (Rectifier)</p> <p>i) uncontrolled Rectifier ii) controlled Rectifier.</p> <p>b) Dc to Ac converter (Inverter)</p> <p>c) Dc to Dc Converter (Chopper)</p> <p>d) Ac to Ac Converter (Ac Voltage Controller)</p> <p>a) Ac to Dc Converter (Rectifier)</p> <p>i) uncontrolled Rectifier (using diode)</p> <div style="display: flex; justify-content: space-around;"> <div data-bbox="287 1568 813 1825"> <p>Step down Tfr</p> <p>$V_s < V_p$ V_s = secondary Voltage . V_p = Primary Voltage</p> </div> <div data-bbox="861 1545 1276 1926"> </div> </div> <p>V_i = Input Voltage V_o = output voltage</p>	<p style="text-align: center;">APPROVED</p> <p style="text-align: center;">Registrar (Evaluation) Visvesvaraya Technological University BELAGAVI - 590018</p> <p style="text-align: right; font-size: 2em;">01m</p>

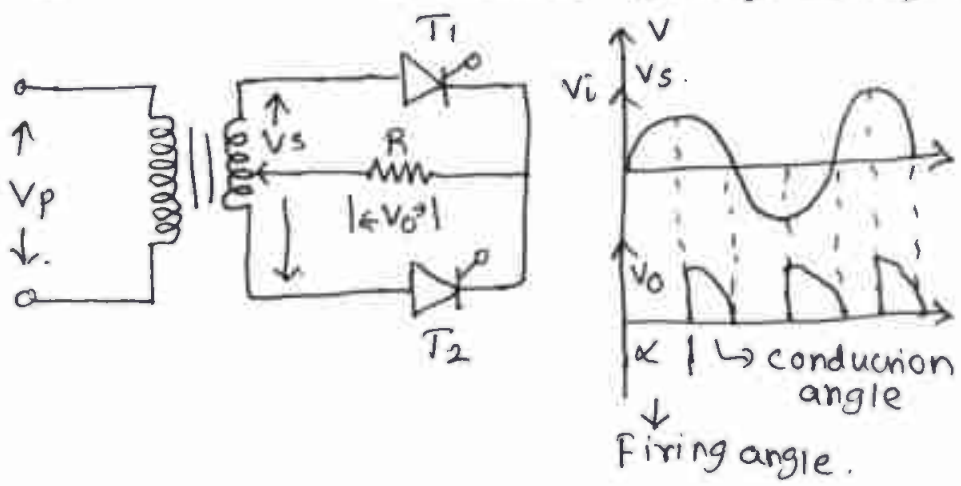
Question Number	Solution	Marks Allocated
	<p>The converter circuit which converts AC to DC is called a Rectifier.</p> <p>The Rectifier circuit using diode only are called uncontrolled Rectifier circuit.</p> <p>ii) controlled Rectifier (using SCR's)</p>  <p>The Rectifier circuit using SCRS are called controlled Rectifier circuit. output Phase angle will be controlled by SCR's.</p> <p>(b) DC to AC Converter (Inverter)</p> <p>A DC to AC Converter is also known as an Inverter. The Input to the Inverter is fixed DC voltage usually obtained from battery. The output of the Inverter is the fixed or variable frequency AC voltage.</p>	<p>01M</p> <p>01M</p> <p>01M</p>

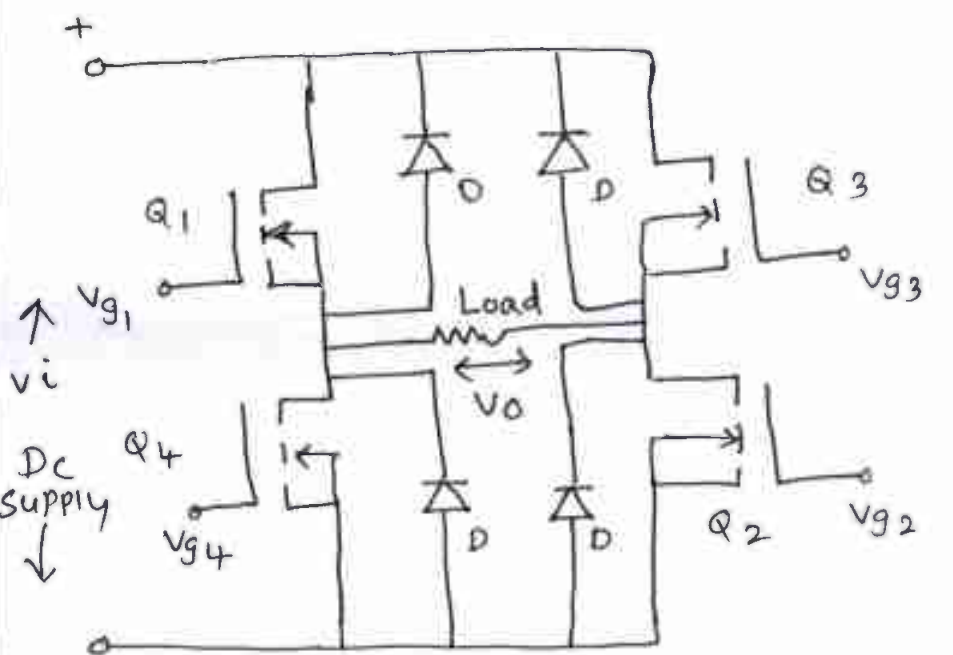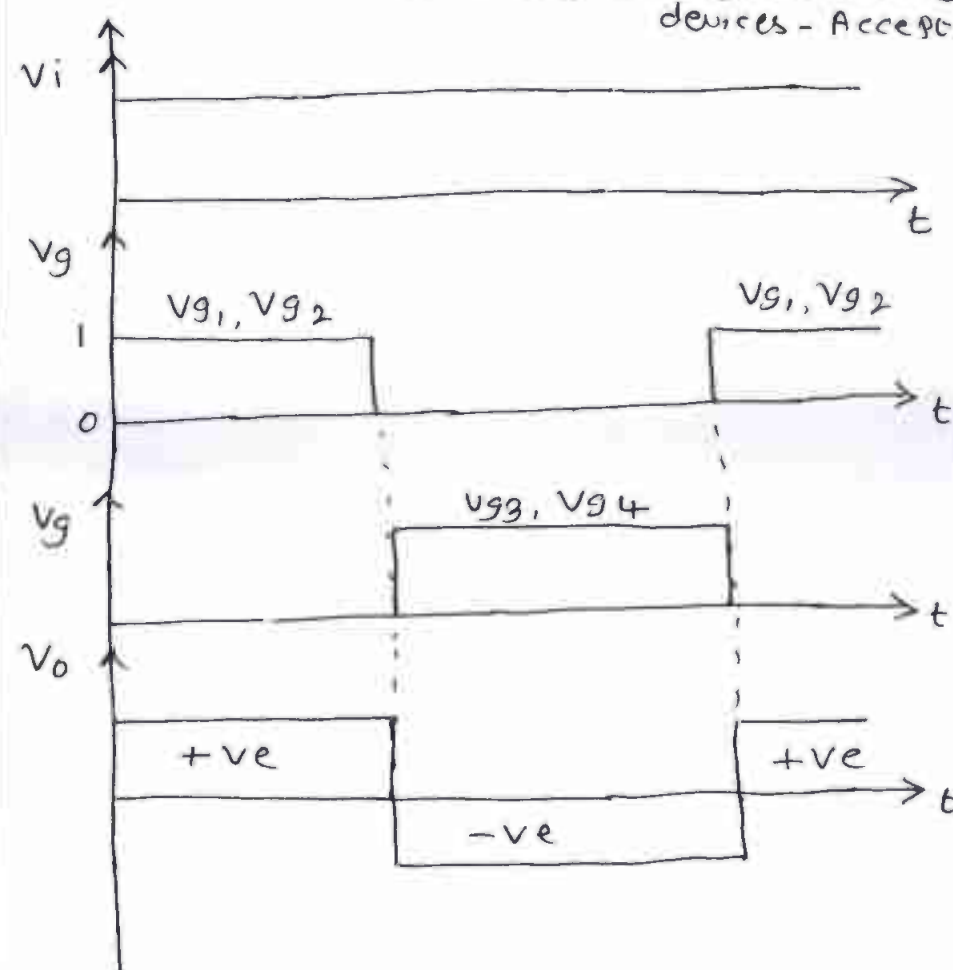Question Number	Solution	Marks Allocated
	 <p>$Q_1, Q_2, Q_3, Q_4 \rightarrow$ Any Switching devices - Accepted</p>  <p>01m</p> <p>01m</p>	

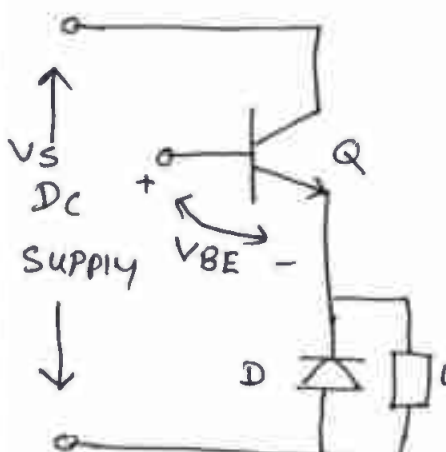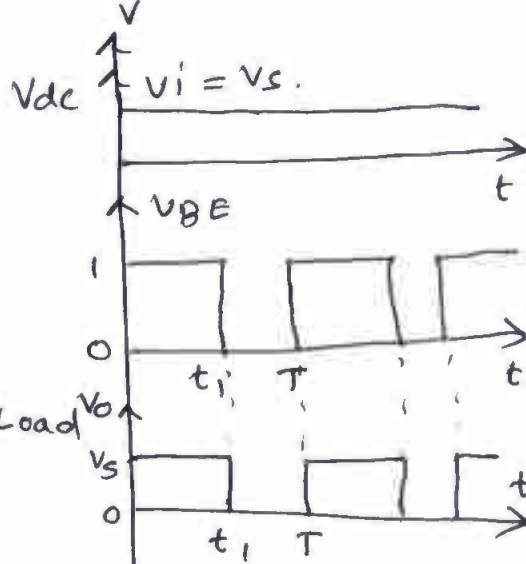Question Number	Solution	Marks Allocated
	<p>(c) DC to DC Converter (Chopper)</p> <p>A chopper is a static device that converts fixed DC input voltage to a variable DC output voltage. It is basically a high speed on/off semiconductor switch.</p>   <p>When switch is ON $V_o = V_s$ When switch is OFF $V_o = 0$.</p>	<p>01m</p> <p>01m</p>
	<p>(d) AC to AC converter (Voltage controller)</p> <p>A single phase AC voltage controller is a device which converts fixed single phase alternating voltage directly to a variable alternating voltage without a change in frequency.</p>	<p>01m</p>



Question Number	Solution	Marks Allocated
		<p>01m</p> <hr/> <p>10m</p>
<p>①</p> <p>②</p>	<p><u>Peripheral effects:-</u></p> <p>Explanation about each --- block</p>	<p>02m</p> <hr/> <p>04m</p> <hr/> <p>06m</p>
<p>①</p> <p>③</p>	<p><u>centre tapped transformer:-</u></p> <ol style="list-style-type: none"> 1. center tapped rectifier as the name suggest is requires a center tapped transformer. 2. The Peak Inverse Voltage (PIV) of diode in center tapped full wave rectifier is twice the transformer Secondary terminal voltage. 	



Question Number	Solution	Marks Allocated
	<p>3. center tapped Rectifier uses only two diodes in its circuit.</p> <p>4. The transformer utilization factor (TUF) is equal to 0.672.</p> <p><u>Bridge Rectifier</u></p> <p>1. No center tapped transformer required in bridge Rectifier.</p> <p>2. Peak inverse voltage PIV of diode is equal to the transformer secondary voltage. Thus this type of rectifier can be used for high voltage applications.</p> <p>3. Bridge Rectifier uses four diodes in its circuit. This result to increment in the circuit complexity in case of the bridge Rectifier.</p> <p>4. The transformer Utilization factor (TUF) is equal to 0.810 for bridge Rectifier.</p> <p>(or)</p> <p>Any four Points for each Rectifier 1 X 4</p>	<p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>4 m</p> <hr/> <p>04 m</p>

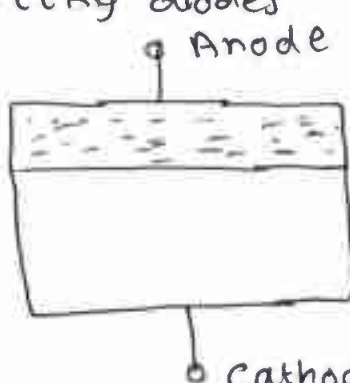Question Number	Solution	Marks Allocated
<p>②</p> <p>①</p>	<p><u>Types of diodes:</u></p> <ol style="list-style-type: none"> 1. General Purpose diodes Explanation - - - - - 2. Fast recovery diodes Explanation - - - - - 3. Schottky diodes <div style="text-align: center;">  <p style="margin-left: 100px;">← metal</p> <p style="margin-left: 100px;">← Junction</p> <p style="margin-left: 100px;">← semiconductor</p> </div> <p style="text-align: center;">Explanation - - - - -</p> <p><u>Applications:</u></p> <ol style="list-style-type: none"> 1. Power diodes are used in uncontrolled Rectifier. 2. Feedback and Free wheeling operations in choppers, Inverters and controlled converters use Power diodes. 3. Almost all the Commutating Circuits for SCR's use Power diodes. 4. Half controlled converters and half bridge Inverters use Power diodes. 1x4 	<p>1m</p> <p>1m</p> <p>1m</p> <p>1m</p> <p>4m</p> <p>08m</p>

Subject Title :

Subject Code :

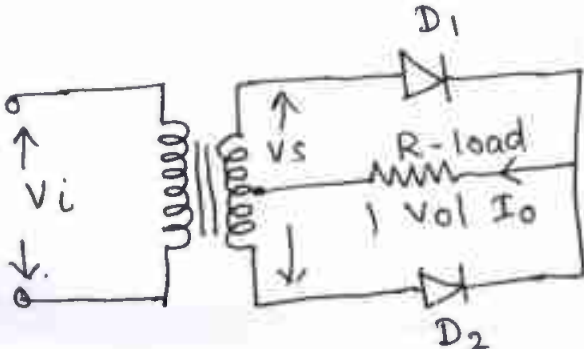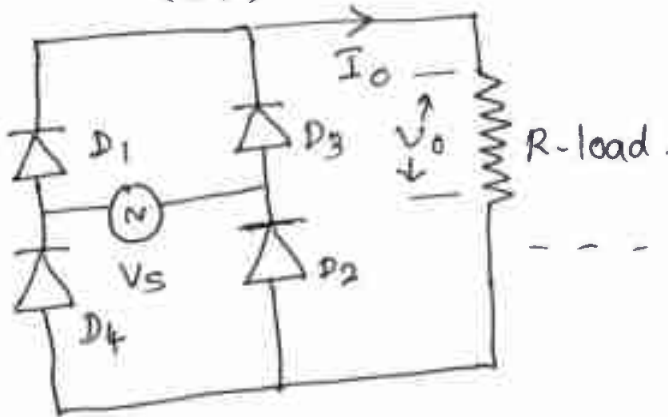Question Number	Solution	Marks Allocated
<p>2) b)</p>	<p>1. UPS and Stand by Power supplies for critical loads such as computers, medical equipments etc.</p> <p>2. Power control in resistance welding, induction heating, electrolysis Process etc.</p> <p>3. Power conversion for HVDC and HVAC transmission system.</p> <p>4. Speed control of motors which are used in traction drives, textile mills, rolling mills, cranes, lifts, compressor, pumps etc.</p> <p>(or)</p> <p>Any four points 1x4</p>	<p>4m</p> <hr/> <p>4m</p>
<p>2) c)</p>	<div style="text-align: center;">  <p>(or)</p>  </div>	<p>02m</p>

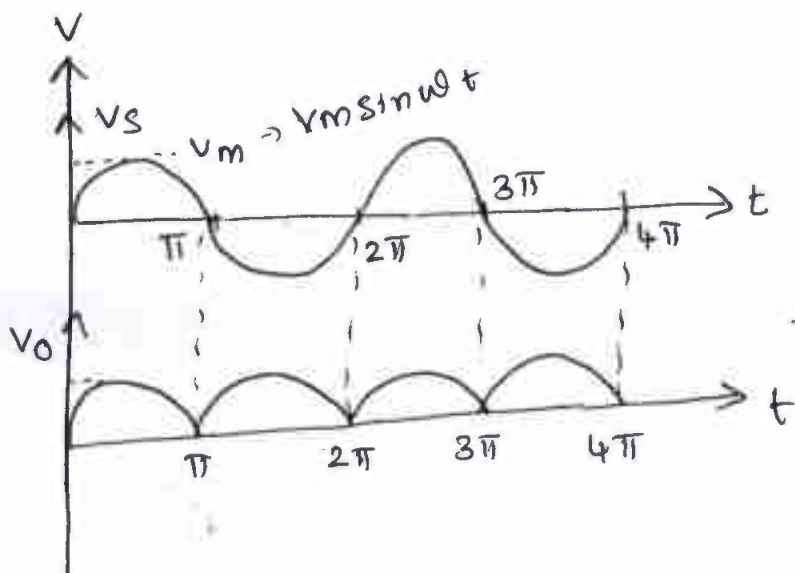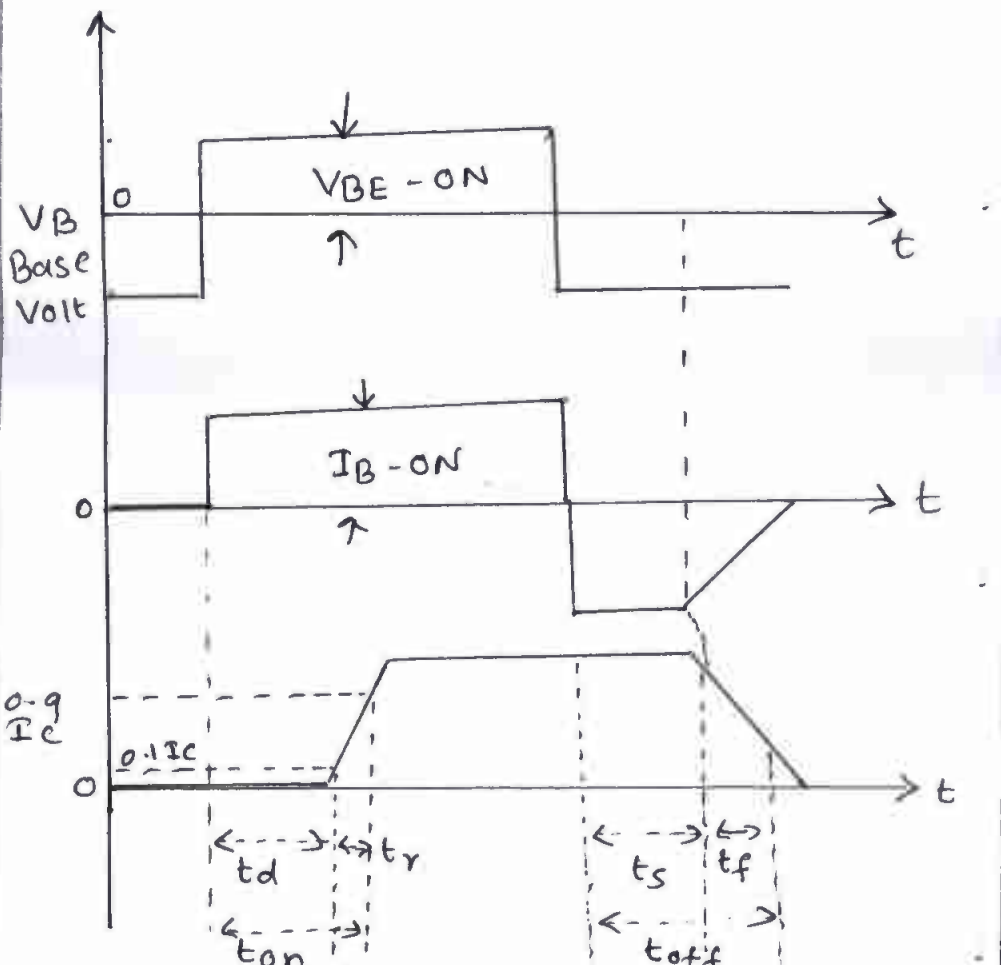Question Number	Solution	Marks Allocated
	 <p style="text-align: right;">Explanation ----- 04 m</p>	<p style="text-align: center;">02 m</p>
<p>3)</p>		<p style="text-align: center;">08 m</p>
<p>a)</p>		<p style="text-align: center;">03 m</p>

Question Number	Solution	Marks Allocated
	Explanation - - - - -	03m
	$t_{on} = t_d + t_r$ - - - - -	02m
	$t_{off} = t_s + t_f$ - - - - -	02m
		<hr/> 08m <hr/>
③	<u>Solution</u>	
⑥	i) To obtain value of R_B From collector emitter loop	
	$I_{c\text{ sat}} = \frac{V_{cc} - V_{ce\text{ sat}}}{R_c} = \frac{100 - 2.5}{10}$	01m
	$I_{e\text{ sat}} = 9.75 \text{ A}$	
	$I_{B\text{ sat}} = \frac{I_{c\text{ sat}}}{\beta_{\text{min}}} = \frac{9.75}{10} = 0.975 \text{ A}$	01m
	$\text{ODF} = \frac{I_B}{I_{B\text{ sat}}} \Rightarrow 20 = \frac{I_B}{0.975} \quad I_B = 19.5 \text{ A}$	01m
	From base emitter loop	
	$V_B = I_B R_B + V_{BE}$	
	$8 = 19.5 \times R_B + 1.75 \Rightarrow R_B = 0.32 \Omega$	01m

Subject Title :

Subject Code :

Question Number	Solution	Marks Allocated																
	<p>ii) To obtain forced β_f</p> $\beta_{\text{forced}} = \frac{I_{c \text{ sat}}}{I_B} = \frac{9.75}{19.5} = 0.5$ <p>iii) To obtain Power loss in transistor</p> $P_T = V_{BE} I_B + V_{CE} I_C$ $= 1.75 \times 19.5 + 2.5 \times 9.75 = 58.5 \text{ W}$ <p>$P_T = 58.5 \text{ Watts}$</p>	<p>1</p> <p>01m</p> <p>01m</p> <hr/> <p>06m</p>																
<p>3)</p> <p>c)</p>	<p><u>Compare BJT and MOSFET</u></p> <table border="0" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 50%; text-align: center; border-right: 1px solid black;"><u>BJT</u> BJT</td> <td style="width: 50%; text-align: center;"><u>MOSFET</u> BJT</td> </tr> <tr> <td style="border-right: 1px solid black;">1. N channel and P channel</td> <td>1. NPN and PNP</td> </tr> <tr> <td style="border-right: 1px solid black;">2. Output current is controlled by input gate voltage.</td> <td>2. Output current is controlled by input base current</td> </tr> <tr> <td style="border-right: 1px solid black;">3. more expensive</td> <td>3. less expensive</td> </tr> <tr> <td style="border-right: 1px solid black;">4. very high current gain</td> <td>4. Lower current gain</td> </tr> <tr> <td style="border-right: 1px solid black;">5. High input resistance 10^7 ohms.</td> <td>5. very low.</td> </tr> <tr> <td style="border-right: 1px solid black;">6. Input current Pico amps</td> <td>6. micro amps or milli amps.</td> </tr> <tr> <td style="border-right: 1px solid black;"></td> <td style="text-align: center;">Any six points. 6x1</td> </tr> </table>	<u>BJT</u> BJT	<u>MOSFET</u> BJT	1. N channel and P channel	1. NPN and PNP	2. Output current is controlled by input gate voltage.	2. Output current is controlled by input base current	3. more expensive	3. less expensive	4. very high current gain	4. Lower current gain	5. High input resistance 10^7 ohms.	5. very low.	6. Input current Pico amps	6. micro amps or milli amps.		Any six points. 6x1	<hr/> <p>06m</p> <hr/> <p>06m</p>
<u>BJT</u> BJT	<u>MOSFET</u> BJT																	
1. N channel and P channel	1. NPN and PNP																	
2. Output current is controlled by input gate voltage.	2. Output current is controlled by input base current																	
3. more expensive	3. less expensive																	
4. very high current gain	4. Lower current gain																	
5. High input resistance 10^7 ohms.	5. very low.																	
6. Input current Pico amps	6. micro amps or milli amps.																	
	Any six points. 6x1																	

Question Number	Solution	Marks Allocated
<p>④</p> <p>①</p>	<p><u>Requirement of base drive:</u> -</p> <ol style="list-style-type: none"> 1. A fast rising ($< 1\mu s$) current to turn on the device. 2. A hard drive of adequate magnitude (I_B) to reduce Turn on loss. 3. A steady base current of adequate (I_B) to keep the device in saturation during the on period of the switch. 4. A fast falling ($< 1\mu s$) current of adequate magnitude (I_B) during the storage time (typically 5 to 10s) of the turn on period of the switch. 5. A base voltage of adequate negative magnitude typically 5V during the OFF period of the device. 6. The drive circuit must be such that the switching performance is insensitive 7. Electrical isolation between the control input and the switch may be desired. This will be necessary very often when the system has several switches located at different electrical potentials. 8. The drive circuit must have over riding protection to switch of the device under fault. 	<p>11</p> <p>11</p> <p>11</p> <p>11</p> <p>11</p> <p>11</p> <p>11</p> <p>8m</p> <p>8m.</p>

1X 8m


Subject Title :


Subject Code :

Question Number	Solution	Marks Allocated
<p>4</p> <p>b</p>	<p><u>Solution:</u></p> <p>i) To obtain $I_{c sat}$ From collector emitter loop</p> $I_{c sat} = \frac{V_{cc} - V_{ce sat}}{R_c}$ $= \frac{24 - 0.2}{200} = 0.12 A$ <p>$I_{c sat} = 0.12 A$</p> <p>ii) To obtain R_B for $ODF = 2$</p> $I_{B sat} = \frac{I_{c sat}}{\beta_{min}} = \frac{0.12}{25}$ <p>$I_{B sat} = 4.8 mA$</p> $ODF = \frac{I_B}{I_{B sat}}$ $2 = \frac{I_B}{4.8 \times 10^{-3}}$ <p>$I_B = 9.6 mA$</p> <p>From emitter base loop we get</p> $V_B = I_B R_B + V_{BE}$ $R_B = \frac{V_B - V_{BE}}{I_B} = \frac{5 - 0.7}{9.6 \times 10^{-3}}$ <p>$R_B = 448 \Omega$</p>	<p>1</p> <p>1</p> <p>01m</p> <p>1</p> <p>01m</p> <p>1</p> <p>01m</p> <p>1</p> <p>01m</p> <p>1</p> <p>01m</p> <p>1</p> <p>01m</p> <p>1</p> <p>01m</p> <p>1</p> <p>01m</p>

Question Number	Solution	Marks Allocated
	<p>iii) To obtain Power dissipation</p> $P_T = V_{BE} I_B + V_{CE} I_C$ $= 0.7 \times 9.6 \times 10^{-3} + 0.2 \times 0.12$ <p>$P_T = 0.0307 \text{ watts}$</p>	<p>1</p> <hr/> <p>01m</p>
<p>4)</p>		<p>06m</p>
<p>c)</p>	<p>$V_{GS5} > V_{GS4} > V_{GS3} > V_{GS2} > V_{GS1}$</p>	<p>02m</p>
	<p>Explanation</p>	<p>04m</p>
		<p>06m</p>



Question Number	Solution	Marks Allocated
<p>(5) (a)</p>		<p>2 m</p>
	<p>1. Reverse blocking mode</p>	
	<p>Explanation - - - - -</p>	<p>2 m</p>
	<p>2. Forward blocking mode</p>	
	<p>Explanation - - - - -</p>	<p>2 m</p>
	<p>3. Forward conduction mode</p>	
	<p>Explanation - - - - -</p>	<p>2 m</p>
	<p>4. Latching current</p>	
	<p>Explanation - - - - -</p>	<p>2 m</p>
	<p>5. Holding current Explanation - - - - -</p>	<p>2 m</p>
		<p>12 m</p>

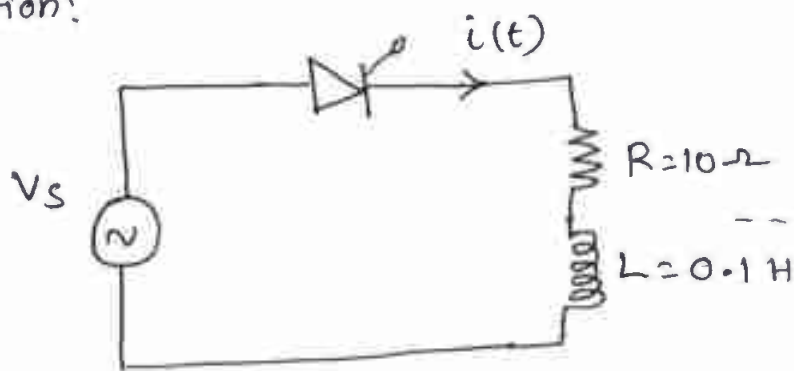Question Number	Solution	Marks Allocated
<p>(5) (b)</p>	<p>1. Gate drive - Explanation 2. High forward Voltage - Explanation 3. $\frac{dv}{dt}$ - Explanation 4. Light - Explanation 5. High temperature - Explanation.</p> <p>Any four methods. 4x1</p>	<p>4m 4m</p>
<p>(5) (c)</p>	<p>Solution:</p>  <p>$V_s = 325 \sin 314 t$</p> <p>The SCR is triggered at $\frac{\pi}{3}$. Hence applied voltage at this angle will be</p> $V_s = 325 \sin \frac{\pi}{3}$ $= 281.458 \text{ volts}$ <p>The current through load is</p> $i(t) = \frac{V_s}{R} \left(1 - e^{-t \frac{R}{L}} \right)$	<p>01m 01m 01m</p>

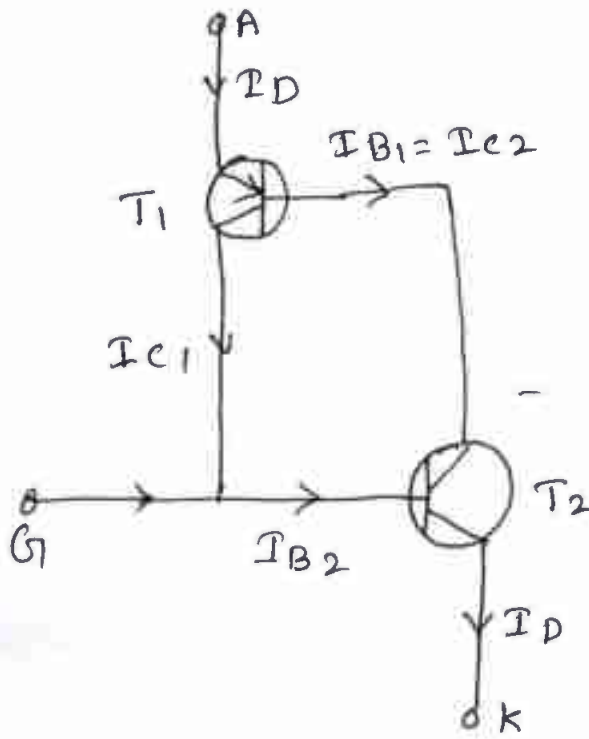Question Number	Solution	Marks Allocated
	<p>When $i(t) = I_L = 15 \text{ mA}$</p> $15 \times 10^{-3} = \frac{281.458}{10} \left(1 - e^{-t \frac{10}{0.1}} \right)$ <p>by above equation</p> $t = 5.33 \mu \text{ seconds}$	<p>01m</p> <hr/> <p>04m</p>
<p>(b)</p> <p>(a)</p>	 <p>$I_{C1} = \alpha_1 I_{E1} + I_{C01}$</p> <p>$I_{E1} = I_D$ and I_{C01} is leakage current of T_1. Similarly for T_2</p> <p>$I_{C2} = \alpha_2 I_{E2} + I_{C02}$</p>	<p>02m</p> <p>01m</p> <p>01m</p>



Question Number	Solution	Marks Allocated
	$I_{E2} = I_D \text{ and } I_{CO2} \text{ is leakage current of } T_2$ $I_{C1} = \alpha_1 I_D + I_{CO1}$ $I_{C2} = \alpha_2 I_D + I_{CO2}$ \vdots $I_D = \frac{I_{CO1} + I_{CO2}}{1 - (\alpha_1 + \alpha_2)}$ $I_D = \frac{I_{CO}}{1 - (\alpha_1 + \alpha_2)}$	<p>1</p> <p>01m</p> <p>02m</p> <p>01m</p> <hr/> <p>08m</p>
<p>(b)</p> <p>(b)</p>	<p><u>Solution:</u></p> <p>$V_{BB} = 220V \quad V_r = 1 \quad V_p = 15V \quad T = 20 \times 10^{-3} s$</p> <p>$R_c = 100 k\Omega$</p> <p>The Peak voltage of the uST is given as</p> $V_p = \eta V_{BB} + V_D$ $V_D = 0.8$ $15 = \eta \times 220 + 0.8$ $\eta = 0.71$ $T = R_c C \ln \left(\frac{1}{1 - \eta} \right)$	<p>1</p> <p>03m</p>

Question Number	Solution	Marks Allocated
<p>(b)</p> <p>(c)</p>	<p> $20 \times 10^{-3} = 10 \times 10^3 \times C \ln \left(\frac{1}{1-0.71} \right)$ $C = 0.162 \mu F$ </p> <p> </p> <p>Explanation - - -</p>	<p>03m</p> <hr/> <p>06m</p> <hr/> <p>01m</p> <hr/> <p>02m</p> <hr/> <p>03m</p> <hr/> <p>06m</p> <hr/>

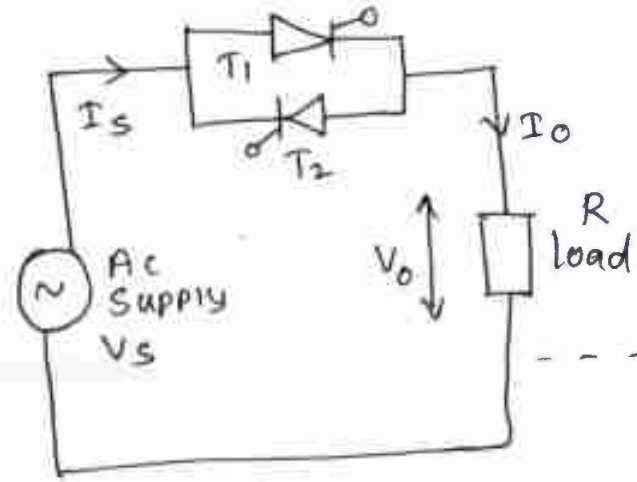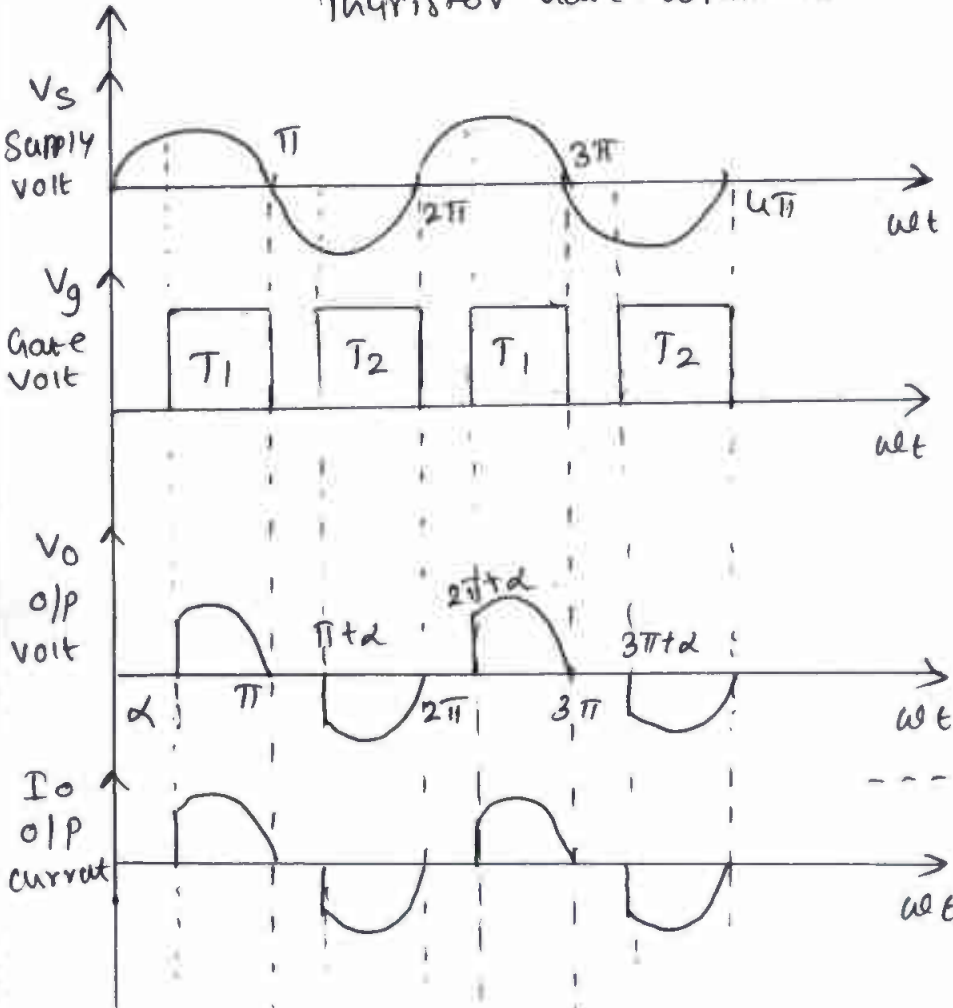Question Number	Solution	Marks Allocated
<p>a) 7</p>	 <p>$V_g \rightarrow$ Gate Voltage applied to Thyristor Gate terminals</p>  <p>Explanation</p>	<p>02m</p> <p>03m</p> <p>05m</p> <p>10m</p>

Question Number	Solution	Marks Allocated
<p>(7)</p> <p>(b)</p>	<p><u>Solution:</u></p> <p>i) To obtain V_{rms}.</p> $V_{rms} = V_m \sqrt{\frac{\pi - \alpha + \frac{\sin 2\alpha}{2}}{2\pi}}$ $V_{rms} = 230 \times \sqrt{2} \sqrt{\frac{\pi - \frac{\pi}{4} + \frac{\sin(2 \cdot \frac{\pi}{4})}{2}}{2\pi}}$ $V_{rms} = 219.3V \text{ --- --- --- --- --- } 01m$ <p>ii) To obtain Rms value of output current.</p> <p>The resistance of the heater will be</p> $R_L = \frac{(230)^2}{1000} = 53 \Omega \text{ --- --- --- --- --- } 01m$ <p>Rms current through the heater</p> $I_{orms} = \frac{V_{rms}}{R_L} = \frac{219.3}{53}$ $I_{orms} = 4.137A \text{ --- --- --- --- --- } 01m$	

Question Number	Solution	Marks Allocated
	<p>iii) Average value of triac current</p> <p>The average value of triac current = 0 = zero</p>	01m
	<p>iv) Rms value of triac current</p> <p>The triac current is same as O/P current</p> <p>$I_{T \text{ rms}} = I_{\text{orms}} = 4.137 \text{ A}$</p>	01m
	<p>v) To obtain input Power factor</p> <p>Active load Power = $I_{\text{O rms}}^2 \times R_L$</p> <p>$= (4.137)^2 \times 53$</p> <p>$= 907 \text{ watts}$</p> <p>Total Rms input Power = $V_{\text{orms}} \times I_{\text{srms}}$</p> <p>$= 230 \times 4.137$</p> <p>$= 951.5 \text{ VA}$</p>	01m
	<p>Then input Power factor will be</p> <p>$\text{PF} = \frac{\text{O/P Power}}{\text{I/P Power}} = \frac{907}{951.5}$</p> <p>Power factor = 0.953</p>	01m 02m <hr/> 10m

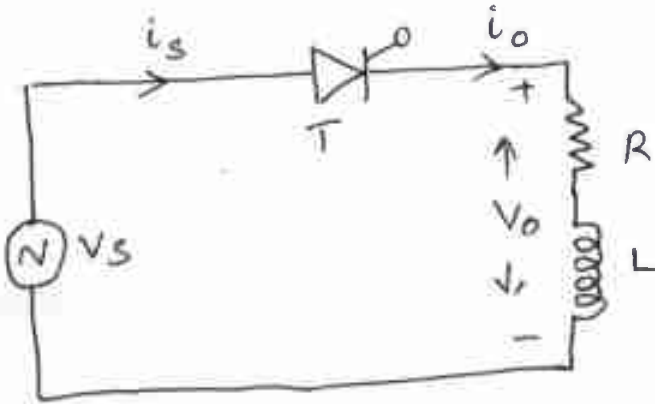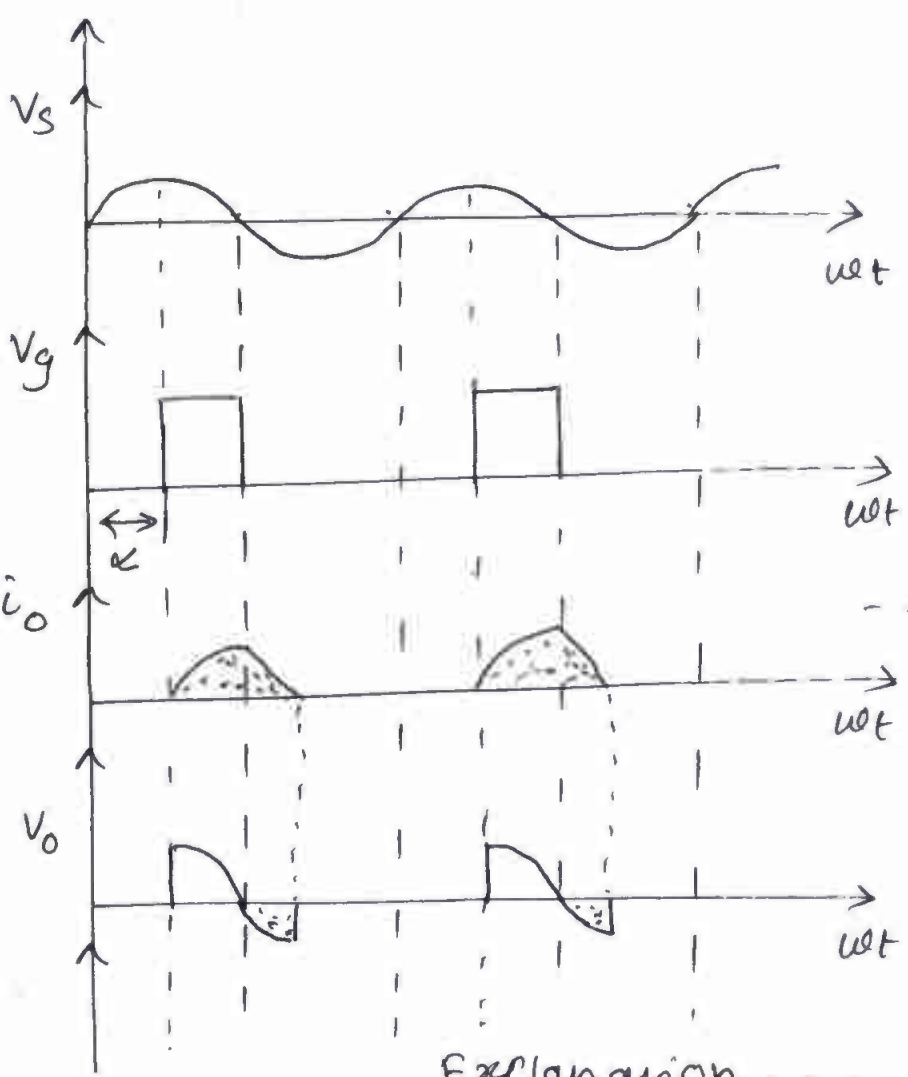Question Number	Solution	Marks Allocated
<p>(a) 8</p>	  <p>Explanation</p>	<p>02m</p> <p>03m</p> <p>05m</p> <hr/> <p>10m</p>



Question Number	Solution	Marks Allocated
<p>8</p> <p>b</p>	<p><u>Solution:</u></p> <p>i) To obtain delay angle α</p> <p>The average output voltage of half wave-converter is given</p> $V_{o\ av} = \frac{V_m}{2\pi} (1 + \cos \alpha)$ $\therefore V_m = V_s \sqrt{2}$ $V_m = 120 \times \sqrt{2}$ $V_m = 169.7\text{V}$ <p>$V_{o\ av}$ is maximum at $\alpha = 0$</p> $V_{o\ av\ max} = \frac{V_m}{2\pi} (1 + \cos \alpha)$ $= \frac{V_m}{2\pi} (1 + \cos 0)$ $= \frac{V_m}{\pi} = \frac{169.7}{\pi}$ $V_{o\ av\ max} = 54\text{V}$ <p>Average output voltage is 25% of its maximum value.</p> $V_{o\ av} = 25\% \text{ of } V_{o\ av\ max}$ $= 0.25 \times 54 = 13.5\text{V}$ $V_{o\ av} = \frac{V_m}{2\pi} (1 + \cos \alpha)$ $13.5 = \frac{169.7}{2\pi} (1 + \cos \alpha)$ $\alpha = 2.09 \text{ radian}$ $\alpha = 120^\circ$	<p>01M</p> <p>01M</p> <p>01M</p> <p>01M</p> <p>01M</p> <p>01M</p> <p>01M</p> <p>01M</p>


Subject Title: POWER ELECTRONICS

Subject Code: 18EE53

Question Number	Solution	Marks Allocated
	<p>ii) To obtain rms and average output currents.</p> $I_{Oav} = \frac{V_{Oav}}{R}$ $= \frac{13.5}{10} = 1.35A$ $I_{Oav} = 1.35A$ <p>The rms output voltage</p> $V_{Orms} = \frac{V_m}{2} \left[1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi} \right]^{1/2}$ $= \frac{169.7}{2} \left[1 - \frac{2.09}{\pi} + \frac{\sin(2 \times 2.09)}{2\pi} \right]^{1/2}$ $V_{Orms} = 37.718V$ <p>Hence rms current will be</p> $I_{Orms} = \frac{V_{Orms}}{R} = \frac{37.718}{10}$ $I_{Orms} = 3.77A$ <p>iii) Rms and average thyristor currents</p> $I_{Tav} = I_{Oav} = 1.35A$ $I_{Trms} = I_{Orms} = 3.77A$ <p>iv) Input Power factor = 0.04 lagging..</p>	<p>01m</p> <p>01m</p> <p>01m</p> <p>01m</p> <p>01m</p> <p>10m</p>

Question Number	Solution	Marks Allocated
<p>9)</p> <p>a)</p>	<p>i) To obtain V_{oav}</p> $V_{oav} = R \times I_{oav}$ $= 4 \times 30$ $V_{oav} = 120V$ <p>ii) To obtain δ</p> $V_{oav} = \delta V_s$ $\delta = \frac{V_{oav}}{V_s} = \frac{120}{200} = 0.6$ <p>iii) To obtain T_{on} and T_{off}</p> $\delta = \frac{T_{on}}{T} = T_{on} \times f$ $T_{on} = \frac{\delta}{f} = \frac{0.6}{400} = 1.5 \text{ msec.}$ $T = T_{on} + T_{off}$ $T_{off} = T - T_{on} = \frac{1}{f} - T_{on}$ $T_{off} = \frac{1}{400} - 1.5 \times 10^{-3}$ $T_{off} = 1 \text{ msec.}$	<p>2m</p> <p>2m</p> <p>2m</p> <hr/> <p>06m</p>

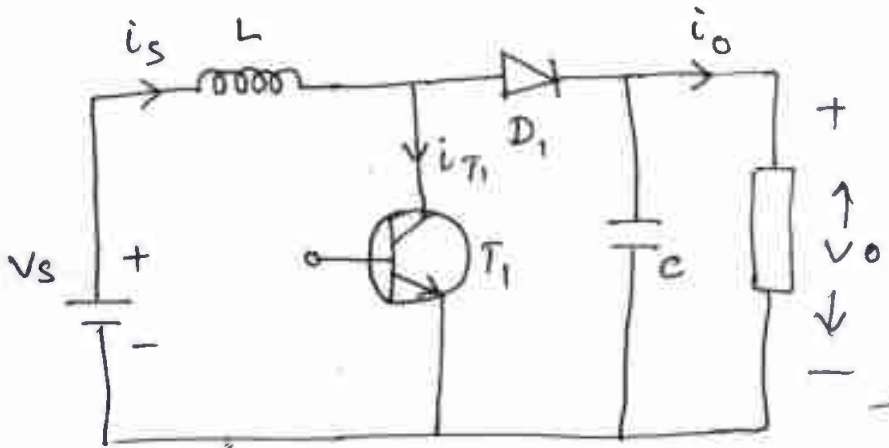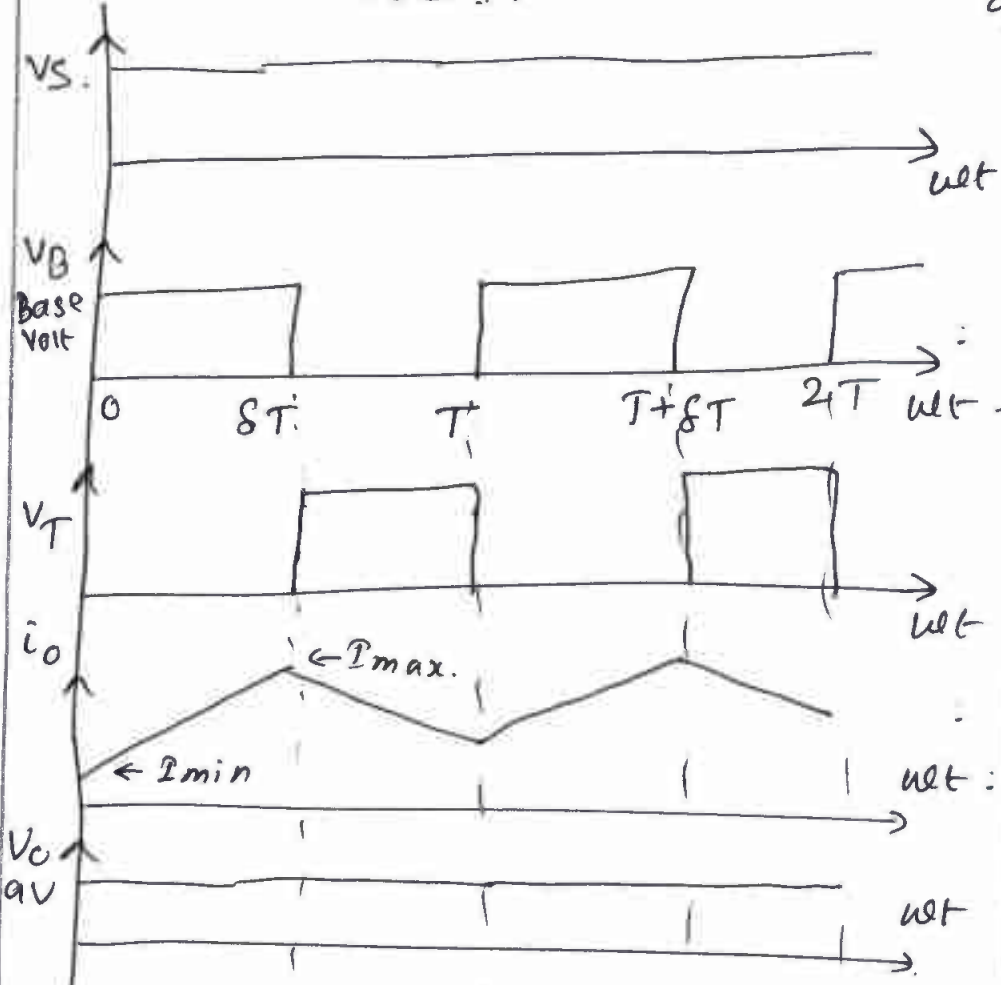Question Number	Solution	Marks Allocated
<p>9</p> <p>b)</p>	 <p>With capacitor or without capacitor both are accepted. The waveform will change.</p>  <p>Explanation ---</p>	<p>02m</p> <p>03m</p> <p>03m</p> <p>08m</p>

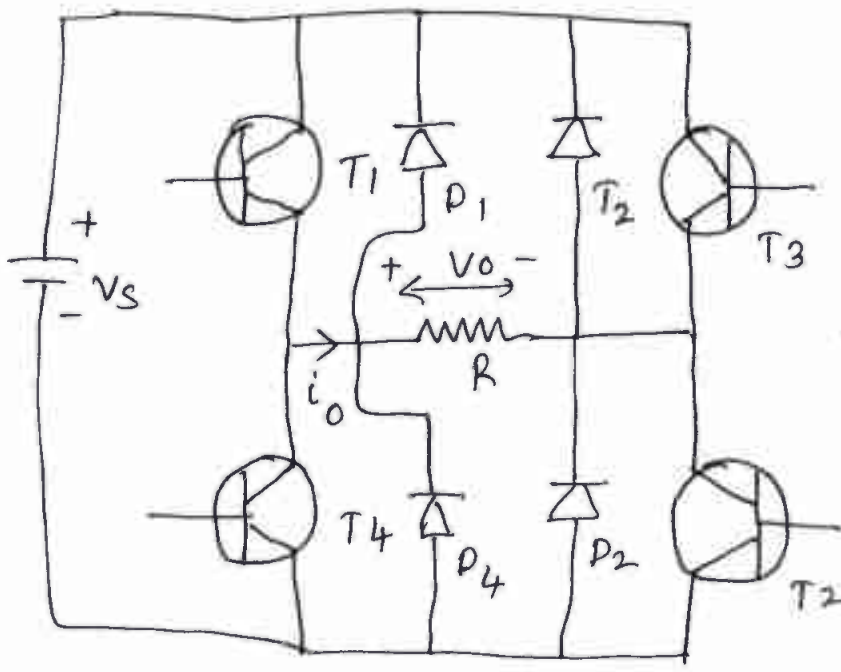Question Number	Solution	Marks Allocated
9 c	<p><u>Performance Parameters:-</u></p> <ol style="list-style-type: none"> Duty cycle - δ with explanation - - - - - operating speed of switch (devices) with explanation - - - - - frequency of the chopper (f). with explanation - - - - - 	<p>02m 02m 02m <u>06m</u></p>
10 a		<p>03m</p>

Question Number	Solution	Marks Allocated
-----------------	----------	-----------------

Wavetforms - - -

03m


Explanation - - -

04m

10m

(10)

(b)

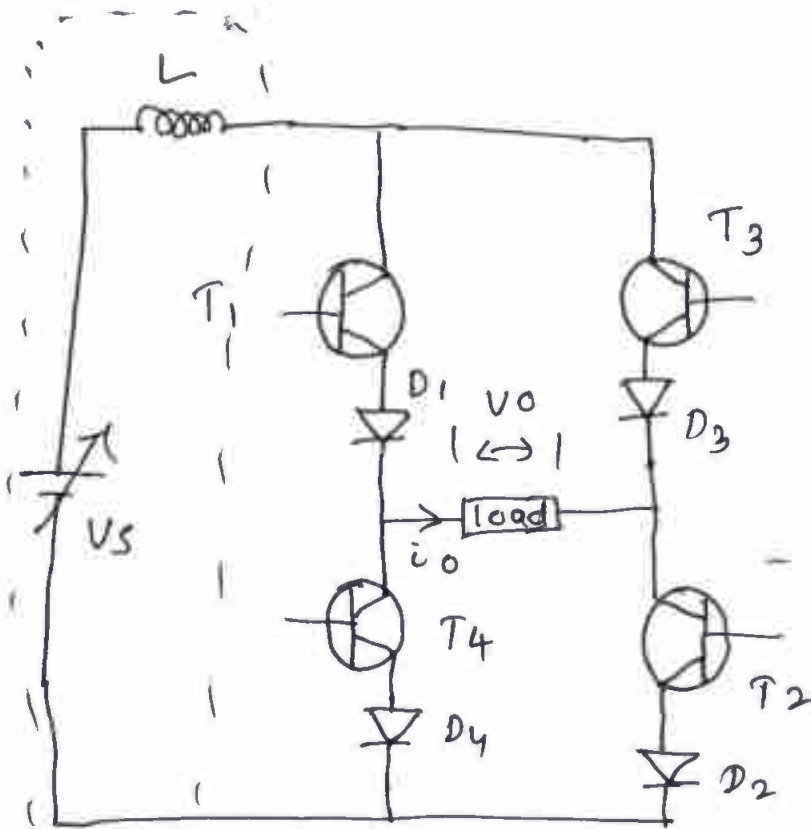

03m

Constant current source

Wavetw m - - -

03m

$$i_{on} = \sum_{n=1,3,5}^{\infty} \frac{4I}{n\pi} \sin \frac{n\theta}{2} \sin n\omega t$$

01m

Explanation

03m

10m

APPROVED

Registrar (Evaluation)

Visvesvaraya Technological University
BELAGAVI - 590018