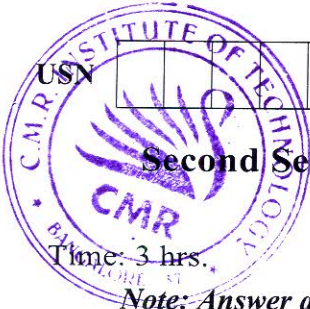


# CBCS SCHEME



20EVE241

Second Semester M.Tech. Degree Examination, Feb./Mar. 2022

## Advances in VLSI Design

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Explain standard cell based design techniques. (10 Marks)  
b. Explain semi-custom design flow. (10 Marks)

OR

- 2 a. Explain Pre-diffused (or mask-programmable) arrays. (10 Marks)  
b. With a neat diagram, Explain switch-box based programmable interconnect. (10 Marks)

### Module-2

- 3 a. Explain briefly interwire capacitance and cross-talk. (08 Marks)  
b. Explain about resistance and reliability ohmic voltage drop in resistive parasities. (08 Marks)  
c. Explain briefly Electromigration. (04 Marks)

OR

- 4 a. Briefly discuss about the design techniques available to the designer to address the  $L \left( \frac{di}{dt} \right)$  problem (12 Marks)  
b. Explain current mode transmission techniques. (08 Marks)

### Module-3

- 5 a. With neat diagrams, differentiate between synchronous and mesochronous interconnect methodologies. (10 Marks)  
b. Explain clock skew and clock filter in detail. (10 Marks)

OR

- 6 a. Explain in detail various clock distribution techniques. (10 Marks)  
b. With a neat diagram, explain the concept of synchronizer. (10 Marks)

### Module-4

- 7 a. Explain general memory architecture and building blocks. (10 Marks)  
b. Explain in detail the operation of SRAM cell. (10 Marks)

OR

- 8 a. What is an address decoder? Explain a NAND decoder using 2-input pre-decoder. (10 Marks)  
b. Explain the concept of voltage down converters. (10 Marks)

### Module-5

- 9 a. Write short notes on: i) Signal to noise ratio ii) Memory yield. (10 Marks)  
b. How is retention current reduced in SRAMS? (10 Marks)

OR

- 10 a. What are the sources of power dissipation in memories? (10 Marks)  
b. Explain folded bit-line architecture of IT-DRAM. (10 Marks)

CMRIT LIBRARY  
BANGALORE - 560 037

\*\*\*\*\*

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.