

# CBCS SCHEME



--	--	--	--	--	--	--	--	--	--

20EVE14

First Semester M.Tech. Degree Examination, Feb./Mar. 2022

## VLSI Testing

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- Differentiate between fault and failure with an example. Explain the major fault models used in modern VLSI testing. (10 Marks)
  - What is a temporary fault? Explain how temporary faults can be modeled for testing VLSI circuits. (10 Marks)

OR

- Explain with examples the types of logic simulation used in VLSI testing (10 Marks)
  - What are the delay models used in VLSI testing? Explain with an example for each. (07 Marks)
  - Explain stuck-at-faults for a 2-input NAND gate. (03 Marks)

### Module-2

- List the rules for finding Boolean difference. (04 Marks)
  - Explain how Boolean difference can be used in VLSI testing. (06 Marks)
  - Find the Boolean difference with respect to  $x_1$  and  $x_2$  in the logic circuit shown in Fig.Q3(c), and give the test patterns for testing for :  
i)  $x_1$  s-a-1 and ii)  $x_2$  s-a-0.

 


Fig.Q3(c)

(10 Marks)

OR

- Explain the process of automatic synthesis of testable logic with reference to VLSI circuit design. Elaborate the following with reference to automatic synthesis of testable logic.
    - Translation and optimization phases
    - Minimization and Restructuring
    - Cube and Support
    - Algebraic and Boolean product.(10 Marks)
  - Explain Reed-Muller expansion technique with the help of an example. (10 Marks)

**Module-3**

- 5 a. Explain with the help of examples the concept of redundancy in the synthesis of random pattern testable combinational circuits. (10 Marks)
- b. Explain the three kinds of faults that can normally occur in PLAs. Explain the easily testable PLA design proposed by Fujiwara. (10 Marks)

**OR**

- 6 a. Explain the testing of sequential circuits as iterative combinational circuits. (10 Marks)
- b. The state table of a sequential machine is given in Fig.Q6(b). Find :  
 i) Response of the machine for the sequence 010  
 ii) Homing tree.

Present state	Input	
	x = 0	x = 1
A	B, 1	C, 0
B	A, 0	D, 1
C	B, 0	A, 0
D	C, 1	A, 1

Fig.Q6(b)

- c. Explain briefly the three phases of a checking experiment. (07 Marks) (03 Marks)

**Module-4**

- 7 a. Explain how testability can be improved by using Ad Hoc design rules. (10 Marks)
- b. Explain the concepts of controllability and observability in the design of testable sequential circuits. (10 Marks)

**OR**

- 8 a. Explain Level-Sensitive Scan Design (LSSD) with the help of suitable diagrams. (10 Marks)
- b. Explain Random Access Scan technique with the help of suitable diagrams. (10 Marks)

**Module-5**

- 9 a. Explain Pseudo-Random Pattern generator for BIST with a suitable example. (10 Marks)
- b. Explain BILBO and STUMPS with reference to built-in-self-test (BIST). (10 Marks)

**OR**

- 10 a. Explain RAM fault models with the help of a schematic block diagram. (10 Marks)
- b. Explain any four test algorithms for RAMs. (10 Marks)

\* \* \* \* \*

CMRIT LIBRARY  
 BANGALORE - 560 037