

Modified

CBCS SCHEME

USN

--	--	--	--	--	--	--	--

18EC32

Third Semester B.E. Degree Examination, Feb./Mar. 2022 Network Theory

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Determine current through 12Ω resistor shown in Fig.Q1(a), using source transformation.

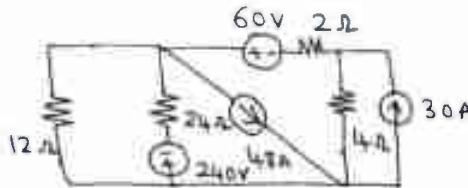


Fig.Q1(a)

- b. Find the equivalent resistance of the circuit shown in Fig.Q1(b), using star delta transformation. (08 Marks)

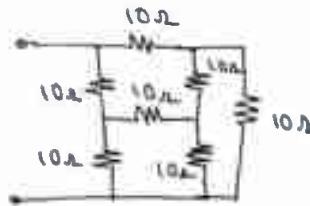


Fig.Q1(b)

- c. Discuss the dependent sources. (08 Marks)
(04 Marks)

OR

- 2 a. Using loop analysis, find the current through 10Ω resistor for the circuit shown in Fig.Q2(a).

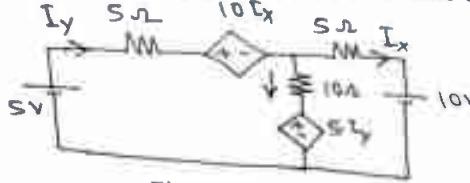


Fig.Q2(a)

- b. For the network shown in Fig.Q2(b), determine node voltages V_1, V_2, V_3 and V_4 using nodal analysis. (08 Marks)

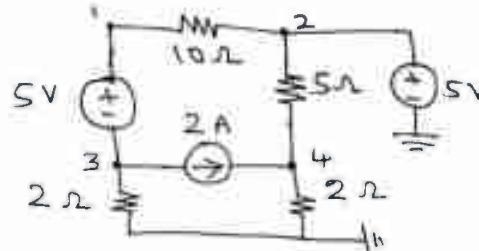


Fig.Q2(b)

- c. Explain the super Mesh with example. (08 Marks)
(04 Marks)

Module-2

- 3 a. Using super position theorem, find the current through 20Ω resistor shown in Fig.Q3(a).



Fig.Q3(a)

- b. Using Millman's theorem, determine the current through $(2 + j2)\Omega$ impedance for the network shown in Fig.Q3(b). (08 Marks)

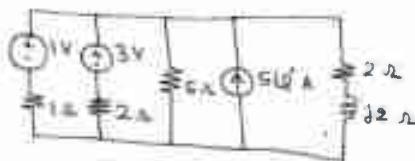


Fig.Q3(b)

- c. State the Norton's theorem and also write the procedure to be followed for solving the problem. (08 Marks)
(04 Marks)

OR

- 4 a. What should be the value of R such that maximum power transfer can takes place from the rest of the network to R. Obtain the amount of this power for circuit shown in Fig.Q4(a). (08 Marks)

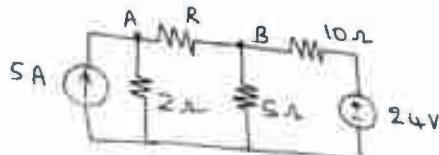


Fig.Q4(a)

- b. Obtain the Thevinin's equivalent circuit cross AB for the circuit shown in Fig.Q4(b). (08 Marks)

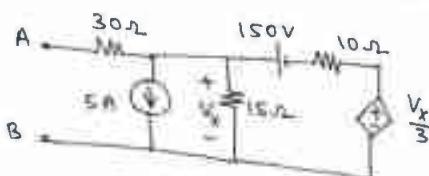


Fig.Q4(b)

- c. State the maximum power transfer theorem and also write equation of P_{max} for both DC and AC circuits. (08 Marks)
(04 Marks)

Module-3

- 5 a. Explain the transient behavior of the resistance, inductance and capacitor. Also write the procedure for evaluating transient behavior.
b. In the network shown in Fig.Q5(b), a steady state is reached with the switch 'K' open. At $t = 0$ the switch is closed. Determine the value of $V_a(0^+)$ and $V_a(0^-)$. (10 Marks)

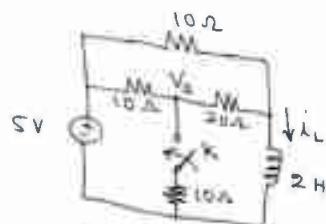


Fig.Q5(b)

OR

- 6 a. For the network shown in Fig.Q6(a) $V_1(t) = e^{-t}$ for $t \geq 0$ and is zero for all $t < 0$. If the capacitor is initially uncharged determine the value of $\frac{d^2V_2}{dt^2}$ and $\frac{d^3V_2}{dt^3}$ at $t = 0^+$.

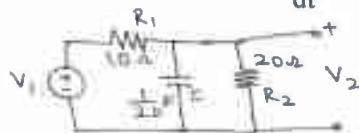


Fig.Q6(a)

- b. The switch 'S' is changed from position 1 to position 2 at $t = 0$. Steady state conditions have been reached in position 1. Find the value of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$ for the circuit shown in Fig.Q6(b).

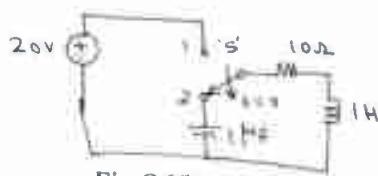


Fig.Q6(b)

(10 Marks)

Module-4

- 7 a. Find the Laplace transform of $f(t)$ shown in Fig.Q7(a).

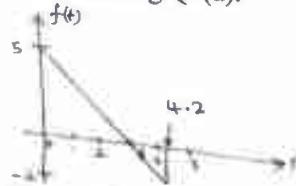


Fig.Q7(a)

- b. Find the Laplace transform of the pulse shown in Fig.Q7(b).

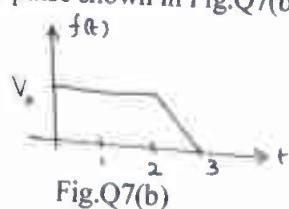


Fig.Q7(b)

(10 Marks)

OR

- 8 a. Find $i(t)$ for the circuit shown in Fig.Q8(a).

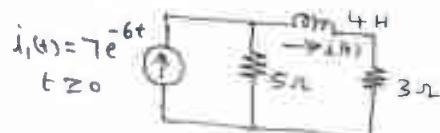


Fig.Q8(a)

- b. A voltage pulse of 10V and 5μsec duration is applied to the RC network shown in Fig.Q8(b). Find the current $i(t)$.

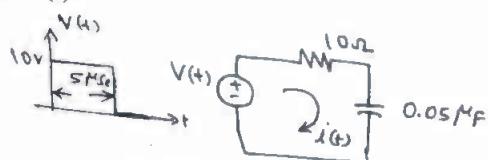


Fig.Q8 (b)

3 of 4

(10 Marks)

Module-5

- 9 a. Obtain y-parameters in terms of z-parameters and h-parameters.
 b. For the network shown in Fig.Q9(b), find the T-parameters. (10 Marks)

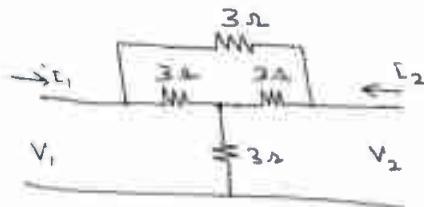


Fig.Q9(b)

(10 Marks)

- 10 a. Derive the expression of bandwidth, half power frequencies and selectivity of a series resonance circuit.
 b. For the parallel resonant circuit shown in Fig.Q10(b), find I_0 , I_L , I_C , f_0 and dynamic resistance. (10 Marks)

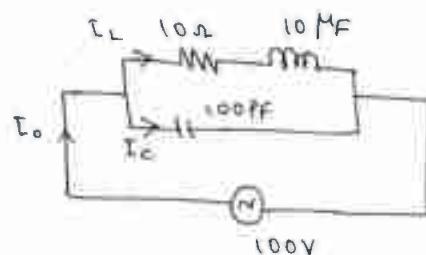


Fig.Q10(b)

(10 Marks)

* * * * *



201218EC3228334

Visvesvaraya Technological University
Belagavi, Karnataka - 590 018.

Signature of Scrutinizer

Subject Title : Network Theory

Subject Code : 18 EC 32

Scheme & Solutions

Question Number




Solution P-1/g

6-2

Marks Allocated


1 a)			80V
			2 M
			18 A } 3 M
			2 M
1 b)			1 M
	$\therefore I_{12\Omega} = \frac{28 \times 4.8}{12 + 4.8} = 8 \text{ A}$		8 M
1 b)			$R = 10 + 10 + \frac{10 \times 10}{10} = 30 \Omega$
			2 M
		$R_1 = \frac{10 \times 10}{50} = 2 \Omega$	
		$R_2 = R_3 = \frac{10 \times 30}{50} = 6 \Omega$	
1 b)		$R'_1 = R'_2 = \frac{10 \times 30}{50} = 6 \Omega$	3 M
		$R'_3 = \frac{10 \times 10}{50} = 2 \Omega$	
			1 M

Question Number	Solution	Marks Allocated
	<p>$\frac{2}{2} \parallel \frac{12}{2+2} = 19.5\Omega$</p> <p>$\frac{2}{2} \parallel 12 \parallel 19.5 \Rightarrow \frac{12}{11.4+2} = 11.4\Omega$</p>	8M
c)	<p>① VCVS ② VCCS ③ CCVS ④ CCCS</p> <p>$V = KV_1$, $E = KV_1$, $V = KI_1$, $I = KI_1$</p>	4M
2 a)	<p>Loop ①</p> $5 - 5I_y - 10I_x - 10(I_y - I_x) - 5I_y = 0$ $\therefore I_y = 0.25A$ <p>Loop ②</p> $-5I_x - 10 + 5I_y + (I_y - I_x) 10 = 0$ $\therefore I_x = -0.4166 A$ $I_{10\Omega} = I_y - I_x = 0.666 A$	3M + 3M + 2M = 8M
b)	<p>$V_2 = 5V$</p> <p>KCL at Super node</p> $\frac{V_1 - V_2}{10} + \frac{V_3 - V_2}{2} + 2 = 0$ $\frac{V_1 - 5}{10} + \frac{V_3 - 5}{2} + 2 = 0$ $\therefore V_1 = 1.66V$ <p>$V_1 - 5 - V_3 = 0$</p> $V_3 = V_1 - 5$ $\therefore V_3 = 1.66 - 5 = -3.33V$ <p>KCL at ④</p> $\frac{V_4 - V_2}{5} + \frac{V_4 - V_3}{2} - 2 = 0$ $\frac{V_4 - 5}{5} + \frac{V_4 - (-3.33)}{2} - 2 = 0$ $V_4 = 4.28V$	1M + 1M + 3M = 5M
3 a)	<p>Supermesh \rightarrow Depolarization with Example - 4M</p> <p>$f_1, f_2 \rightarrow$ redundant, hence neglected</p>	8M
		1M
	<p>$R_1, R_2 \rightarrow$ Redundant</p>	

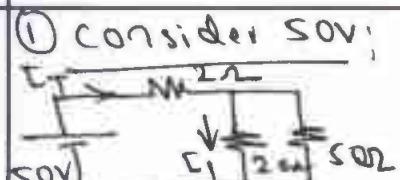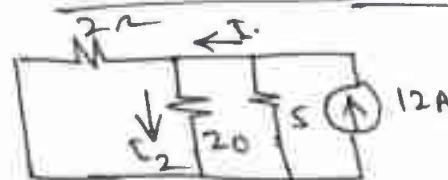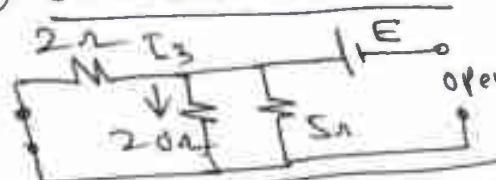Question Number	Solution	Marks Allocated
	P-3 9	
① Consider SOV:	$R_T = 20 \parallel 5 + 2 = 6 \Omega$  $I_T = \frac{V}{R_T} = \frac{50V}{6} = 8.33 A$ $I_1 = \frac{I_T \times s}{20+s} = 1.66 A$	3 M
② Consider 12 A Source	 $I_1 = \frac{12 \times s}{s + (2 \parallel 20)} = 8.8 A$ $I_2 = \frac{I \times 2}{2 + 20} = 0.8 A$	3 M
③ Consider E source	 $I_3 = 0$ $\therefore I_{20\Omega} = I_1 + I_2 + I_3 = 2.46 A$	1 M
5)	$V_o = \frac{V_1 y_1 + V_2 y_2 + V_3 y_3}{y_1 + y_2 + y_3}$ $= \frac{\frac{1}{1} + \frac{3}{2} + \frac{25}{5}}{1 + \frac{1}{2} + \frac{1}{5}}$ $V_o = 4.41 V$	8 M
	$Z = \frac{1}{Y} = \frac{1}{y_1 + y_2 + y_3} = 0.588 \Omega$	2 M
	 $I(2+j2) = \frac{4.41}{2.588+j2}$ $I(2+j2) = 1.35 - j37.69 A$	8 M
C)	Statement + Procedure	4 M
4 a)	 $I = \frac{V}{R} = \frac{24}{15} = 1.6 A$ $V_B = I \times s = 8 V$ $but V_A = 10 V$	4 M
	$V_{oc} = V_{AB} = V_A - V_B = 2 V$ $\Rightarrow R_{th} = 10 \parallel 5 + 2 = 5.33 \Omega$	3 M

Question Number	Solution	Marks Allocated
	$I = 4/8$	
4 b)	<p>$\therefore R_{TH} = 5.33 \Omega$</p> $P_{max} = \frac{V_{TH}^2}{4R_L} = \frac{2^2}{4 \times 5.33} = 0.1875 \text{ W}$ <p>(i) find V_{TH} or V_{OC}</p> $V_{TH} = 75 \text{ V}$ <p>(ii) find R_{TH}:</p> $V_x = V_1$ <p>KCL at node 0:</p> $\frac{V_1}{30} + s + \frac{V_1}{15} + \frac{V_1 - 150 - \frac{V_1}{3}}{10} = 0$ $\therefore V_1 = 60 \text{ V}$ $\therefore I_{sc} = \frac{V_1}{30} = 2 \text{ A}$ $R_{TH} = \frac{V_{TH}}{I_{sc}} = \frac{75}{2} = 37.5 \Omega$	2 M 8 M 2 M 2 M 2 M 8 M
c)	<p>Statement</p> $P_{max} = \frac{V_{TH}^2}{4R_L}$ → DC $P_{max} = \frac{(V_{TH})^2}{8R_{TH}}$ → AC	2 M 2 M 4 M
5 a)	<p>Analysis of Transient behaviour of R, L & C procedure</p>	7 M 3 M 10 M
b)	<p>At $t = 0^- \Rightarrow$ open \Rightarrow steady state</p> <p>$t = 0^+ \Rightarrow$ closed</p> <p>At $t = 0^-$</p> $i_L(0^-) = \frac{5}{30//10} = 0.666 \text{ A}$ $\therefore i_L(0^-) = i_L(0^+)$ $V_o(0^-) = \frac{5 \times 2.5}{5+2.5} = 3.33 \text{ V}$	1 M 4 M

Question Number	Solution	Marks Allocated
	$t = 0^+$	
	<p>KCL at $\textcircled{2} \leftarrow \textcircled{3}$</p> $\frac{V_a - 5}{10} + \frac{V_a}{10} + \frac{V_a - V_b}{20} = 0$ $0.25V_a - 0.05V_b = 0.5 \quad \textcircled{1}$ $0.66 + \frac{V_b - 5}{20} + \frac{V_b - V_a}{20} = 0$ $-0.05V_a + 0.15V_b = -0.16 \quad \textcircled{2}$ $V_a(0^+) = 1.91V \quad V_b(0^+) = -0.42V$	5M
6 a)	<p>$V_2(0^-) = V_2(0^+) = 0$</p> <p>KCL at A</p> $\frac{V_2(t) - V_1(t)}{10} + \frac{1}{20F} \frac{dV_2(t)}{dt} + \frac{V_2(t)}{20} = 0$ $0.15V_2(t) + 0.05 \frac{dV_2(t)}{dt} = 0.1e^{-t} \quad \textcircled{1}$	-1M
	(i) $t = 0^+$	3M
	$\frac{dV_2(0^+)}{dt} = 2V/\text{sec}$	2M
	Q.7th Eqn ①, we get	
	$0.15 \frac{dV_2(t)}{dt} + 0.05 \frac{d^2V_2(t)}{dt^2} = -0.1e^{-t} \quad \textcircled{2}$	
	(ii) $t = 0^+$	2M
	$\frac{d^2V_2(0^+)}{dt^2} = -8V/\text{sec}^2$	
	Q.8th Eqn ②, we get	
	$0.15 \frac{d^2V_2(t)}{dt^2} + 0.05 \frac{d^3V_2(t)}{dt^3} = 0.1e^{-t}$	
	(iii) $t = 0^+$	2M
	$\frac{d^3V_2(t)}{dt^3} = 26V/\text{sec}^3$	10M
b)	$t = 0^- \Rightarrow$ position 1 \Rightarrow steady state	
	$i(0^-) = \frac{20}{10} = 2A$ $V_L(0^-) = V_L(0^+) = 0V$	2M

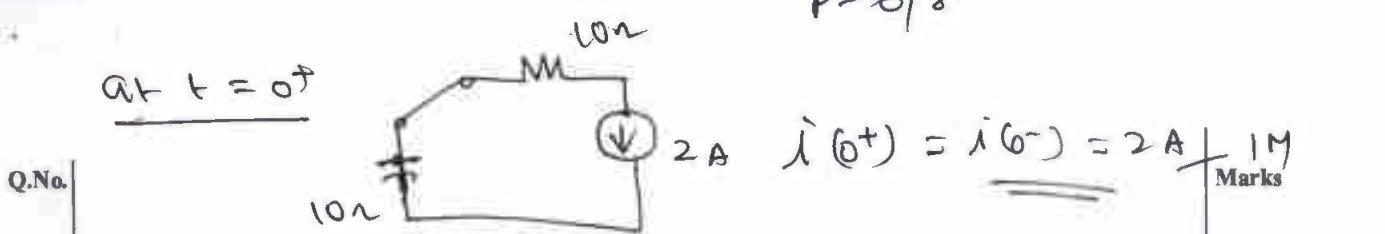

C = 1MF

$$\begin{aligned} R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt &= 0 \quad \boxed{\text{Eqn 1}} \\ R i(t) + L \frac{di(t)}{dt} + V_C(t) &= 0 \end{aligned} \quad \boxed{\text{Eqn 2}} - 3 \text{ M}$$

(ii) at $t = 0^+$: $\frac{di(0^+)}{dt} = -20 \text{ A/sec}$

0 from Eqn 1

$$R \frac{di(t)}{dt} + L \frac{d^2 i(t)}{dt^2} + \frac{i(t)}{C} = 0 \Rightarrow \frac{d^2 i(0^+)}{dt^2} = -1.99 \times 10^6 \text{ A/sec}^2$$

7 a)

$$f(t) = x(t) g(t)$$

$$= \left[-\frac{5}{3}t + 5 \right] [u(t) - u(t-4.2)]$$

After simplification

$$f(t) = -\frac{5}{3}t u(t) + \frac{5}{3}(t-4.2) u(t-4.2) + 2 u(t-4.2) + 5 u(t)$$

$$\therefore F(s) = \mathcal{L}\{f(t)\} = \frac{-5}{3s^2} + \frac{5}{3s^2} e^{-4.2s} + \frac{2}{s} e^{-4.2s} + \frac{5}{s}$$

$$F(s) = \frac{-5 + 5e^{-4.2s} + 6.5e^{-4.2s} + 15s}{3s^2}$$

5M
10M

5)

$$f(t) = \begin{cases} V_0, & 0 < t < 2 \\ -V_0 t + 3V_0, & 2 < t < 3 \end{cases}$$

2M

$$= -V_0 [u(t) - u(t-2)] + [-V_0 t + 3V_0] [u(t-2) - u(t-3)]$$

$$f(t) = V_0 u(t) - V_0 u(t-2) - V_0 t u(t-2) + V_0 + u(t-3) + 3V_0 u(t-2) - 3V_0 u(t-3)$$


3M

$$f(t) = V_0 u(t) - V_0 u(t-2) + V_0 u(t-3)$$

5M
10M

$$F(s) = \mathcal{L}\{f(t)\} = \frac{V_0}{s} - \frac{V_0}{s^2} e^{-2s} + \frac{V_0}{s^2} e^{-3s}$$

8

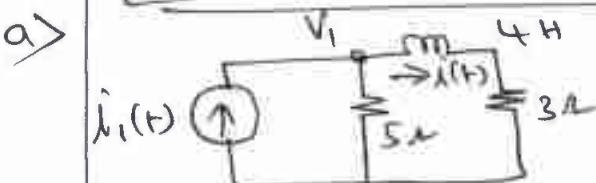

KCL at V_1

$$\frac{V_1}{5} + i = 7e^{-6t}$$

$$\text{Also } V_1 = 3i + 4 \frac{di}{dt}$$

$$\text{Here } \frac{1}{5} [3i + 4 \frac{di}{dt}] + i = 7e^{-6t}$$

$$\Rightarrow di/dt + 2i = \frac{35}{4} e^{-6t}$$

Taking LT

$$[s I(s) - i(0)] + 2 I(s) = \frac{35}{4} \frac{1}{s+6}$$

$$I(s) = \frac{35}{4} \frac{1}{(s+2)(s+6)}$$

using PFE

$$I(s) = \frac{K_1}{s+2} + \frac{K_2}{s+6}$$

$$= \frac{35}{16} \left[\frac{1}{s+2} - \frac{35}{16} \frac{1}{s+6} \right]$$

$$i(t) = \frac{35}{16} [e^{-2t} - e^{-6t}] u(t)$$

6M

Network Theory

Subject Title :

Subject Code : 18EC32

Question Number	Solution	Marks Allocated
8 b)	$V(t) = V_1(+) - V_2(-) = 10 \text{ u}(t) - 10 \text{ u}(t-t_0)$ $V(s) = L\{V(t)\} = \frac{10}{s}(1 - e^{-t_0 s})$ $\therefore I(s) = \frac{V_s}{R + \frac{1}{C}s} = \frac{10}{R} \left[\frac{1}{s + \frac{1}{RC}} - \frac{1}{s + \frac{1}{RC}} e^{-t_0 s} \right]$	1M 1M 3M
	Taking L^{-1} $I(t) = \frac{10}{R} e^{-\frac{t}{RC}} u(t) - \frac{10}{R} e^{-\frac{t}{RC}} u(t-t_0) \Big _{t \rightarrow t-t_0}$ $I(t) = \frac{-t}{0.5 \times 10^{-6}} u(t) - e^{-\frac{(t-5 \times 10^{-6})}{0.5 \times 10^{-6}}} u(t-5 \times 10^{-6})$	5M 5M 10M
9 a)	Obtaining (Starting from basic equation) $[Y] = \frac{1}{\Delta Z} \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix}$	5M
b)	$[Y] = \frac{1}{h_{11}} \begin{bmatrix} 1 & -h_{12} \\ h_{21} & h_{22}h_{11}-h_{12}h_{21} \end{bmatrix}$ $R_1 = R_2 = R_3 = \frac{9}{9} = 1 \Omega$ (1) When $E_2 = 0$ $\Rightarrow \frac{E_1}{N1-N2} = \frac{E_1}{4\Omega} = V_1$ $V_2 = 4E_1$ $\frac{E_1}{V_2} = C = \frac{1}{4}$ $V_1 = 5E_1$ $V_1 = 5 \frac{1}{4} V_2$ $\frac{V_1}{V_2} = A = \frac{5}{4}$	5M 1M 1M 2M 2M 2M
	(2) When $V_2 = 0$ $E_2 = -\frac{E_1}{5} = -\frac{9}{5} = -1.8 \text{ V}$ $\frac{E_1}{V_1} = D = \frac{5}{4}$ $V_1 = 5E_1 + 4E_2$ $= 5(-\frac{9}{4}) + 4E_2$ $\frac{V_1}{E_2} = B = \frac{9}{4} = 2.25 \Omega$ $[T] = \begin{bmatrix} 5/4 & 9/4 \\ 1/4 & 5/4 \end{bmatrix}$	10M 2M 2M

Q.
No

Solution

P-8/8

E

10a) Starting from basic equation to get

$$(WL - \frac{1}{WC}) = \pm R \quad \text{--- (1)}$$

$$WL - \frac{1}{WC} = -R$$

$$W_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \quad \text{--- (2)}$$

$$\text{Hence } \left(W_2 L - \frac{1}{W_2 C}\right) = R$$

$$W_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \quad \text{--- (3)}$$

$$W_2 - W_1 = \frac{R}{L} \Rightarrow f_2 - f_1 = \frac{R}{2\pi L} \Rightarrow 8W$$

$$Q = \frac{W_0}{W_2 - W_0} = \frac{2\pi f_0}{R/L} = \frac{2\pi f_0 L}{R} = \boxed{\frac{W_0 L}{R}} \Rightarrow \text{Selecting } 10M$$

b)

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = 5.03 \text{ MHz}$$


$$Z_0 = \frac{L}{C R_L} = 10 \text{ k}\Omega$$

$$I_0 = \frac{V}{Z_0} = \frac{100}{10k} = 0.01 \text{ A}$$

$$I_L = \frac{V}{R_L + jX_L} = \frac{100}{10 + j2\pi f_0 L} = \frac{100}{10 + j316.04} = 0.316 \angle -88.18^\circ \text{ A}$$

$$I_C = \frac{V}{-jX_C} = 100 \angle 90^\circ = 100 (\angle 90^\circ)$$
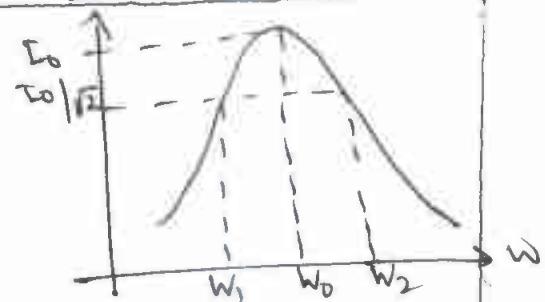
$$I_C = 0.316 \angle 90^\circ \text{ A}$$



\Rightarrow Half power frequencies

5M

3M

2M

2M

2M

2M

2M

10M

"APPROVED"

Registrar (Evaluation)
Visvesvaraya Technological University
BELAGAVI - 590018

D.

BE

M