



USN

--	--	--	--	--	--	--	--	--	--

14ELN15/25

First/Second Semester B.E. Degree Examination, July/August 2022

Basic Electronics

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- Define load line for a diode and explain the DC load line for circuit consisting of supply voltage in series with resistance and diode. (06 Marks)
 - Draw the bridge rectifies circuit and explain its working with waveform. (06 Marks)
 - In a full wave rectifier consists of two diode each having internal resistance of 600Ω . The circuit feeds a pure resistive load of 1800Ω . The secondary voltage with reference to the centre tap is $250V$. Calculate DC load current, DC output power and PIV across each diode. (04 Marks)
 - Draw a sketch to show the various currents and voltages of a transistor and hence obtain relationship between β_{dc} and α_{dc} . (04 Marks)

OR

- What do you mean by a noise clipper? Explain series and shunt noise clipper circuits with circuit diagram. (06 Marks)
 - Draw the input and output characteristics of a transistor in common – base configuration indicate various region of operation and explain the shapes of the curves. (10 Marks)
 - Calculate I_C and I_E for a transistor that has $\alpha_{dc} = 0.98$ and $I_B = 100\mu A$. determine the value of $\beta_{dc} =$ for the transistor. (04 Marks)

Module-2

- Define biasing of transistor. Explain with a neat diagram the operation of voltage divider bias circuit. (08 Marks)
 - Define the following in case of practical op-Amp.
i) CMRR ii) Slew rate iii) Offset voltage iv) PSRR. (04 Marks)
 - For the base bias circuit using NPN transistor find I_C , I_B and V_{CB} if $R_C = 2.2K\Omega$, $R_B = 470K\Omega$, $V_{CC} = 18V$ and transistor has $h_{FE} = 100$. Assume $V_{BE} = 0.7V$. Draw the DC load line and indicate the Q point. (08 Marks)

OR

- Explain how an op-Amp can be used for the following applications with circuit diagram and derive expression for output voltage.
i) Inverting amplifier
ii) Differentiator
iii) Voltage follower. (10 Marks)
 - Design an adder circuit using op-amp to given the output $V_0 = -(8V_1 + 6V_2 + 5V_3)$. (06 Marks)
 - Explain why closed loop configuration of op-Amp is used in all practical amplifier circuit and bring out the advantages of closed loop operation with negative feedback. (04 Marks)

Module-3

- 5 a. Explain the construction of NOT gate using transistor along with truth table. (04 Marks)
 b. State and prove the following :
 i) De Morgan's theorem
 ii) Distributive property. (06 Marks)
 c. Convert :
 i) $(95.0625)_{10} = (\quad)_2$
 ii) $(243.65)_8 = (\quad)_{10}$
 iii) $(10101.10100110)_2 = (\quad)_8 = (\quad)_{16}$ (06 Marks)
 d. Subtract $(1010)_2$ from $(11000)_2$ using is and 2's complement method. (04 Marks)

OR

- 6 a. Design a full adder circuit and show the implementation using suitable gates. (06 Marks)
 b. Explain the basic logic gates with symbol, truth table, Boolean expression and switch logic. (06 Marks)
 c. Show the implementation of 2 input Ex-OR gate using only NAND gates. (04 Marks)
 d. Simplify and implement using NAND gates $y = A(B + CA(\overline{AB + AC}))$. (04 Marks)

Module-4

- 7 a. Explain the operation of clocked RS flip-flop using NAND gate. (06 Marks)
 b. What is thermistor? Explain its advantages and limitations. (06 Marks)
 c. Explain the architecture of 8085 micro-processor with neat block diagram. (08 Marks)

OR

- 8 a. Explain the pin diagram and architecture of 8051 micro controller with neat figures. (10 Marks)
 b. Explain the working of LVDT. (05 Marks)
 c. What is a transducer? Distinguish between active and passive transducers. (05 Marks)

Module-5

CMRIT LIBRARY
 BANGALORE - 560 037

- 9 a. Explain with block diagram the elements of communication systems. (06 Marks)
 b. Define modulation index in AM. Derive an expression for total power in an AM signal. (06 Marks)
 c. Explain the principle of OFC With neat block diagram. (08 Marks)

OR

- 10 a. Compare the performance of AM and FM communication system. (04 Marks)
 b. Explain the AM detection With neat circuit diagram. (06 Marks)
 c. Explain principle operations of cellular mobile phone. (05 Marks)
 d. What is ISDN? Explain with block diagram. (05 Marks)
