

# CBCS SCHEME

15EE32

Third Semester B.E. Degree Examination, July/August 2022

## Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. In the network shown in Fig.Q1(a), find the current in  $R_L$  using the concept of source transformation.

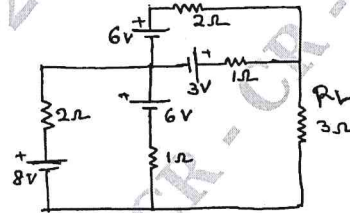


Fig.Q1(a)

(05 Marks)

- b. Find the equivalent resistance of the circuit between a - b as shown in Fig.Q1(b).

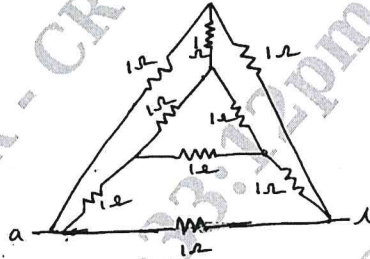


Fig.Q1(b)

(06 Marks)

- c. Using mesh analysis, find the magnitude of the current dependent voltage source in the network shown in Fig.Q1(c).

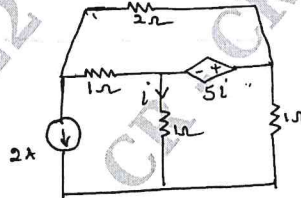


Fig.Q1(c)

(05 Marks)

### OR

- 2 a. Find the node voltages  $V_1$ ,  $V_2$  and  $V_3$  in the circuit diagram shown in Fig.Q2(a), using Nodal Analysis.

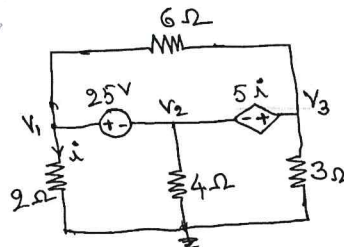


Fig.Q2(a)

(06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- b. Obtain the dual of the network in Fig.Q2(b).

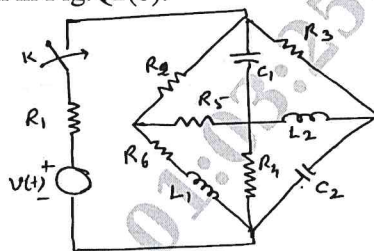


Fig.Q2(b)

(04 Marks)

- c. A variable frequency constant voltage signal generator supplies a RLC circuit at sinusoidal mode. Find the frequency at which maximum voltage across the inductor would appear.

(06 Marks)

**Module-2**

- 3 a. Find the power loss in  $5 \Omega$  resistor by superposition theorem in Fig.Q3(a).

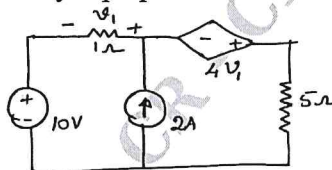


Fig.Q3(a)

(06 Marks)

- b. State and verify Reciprocity theorem.  
 c. For the circuit shown in Fig.Q3(c), find the value of  $R_L$  that will receive maximum power. Determine this power.

(04 Marks)

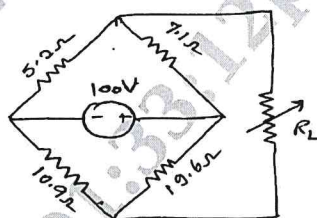


Fig.Q3(c)

(06 Marks)

CMRIT LIBRARY  
BANGALORE - 560 037

OR

- 4 a. State and prove Millman's theorem.  
 b. In the circuit shown in Fig.Q4(b), find the Thevenin's equivalent circuit across the terminals A and B.

(05 Marks)

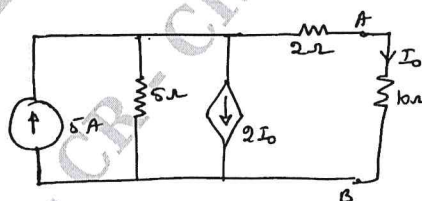


Fig.Q4(b)

(06 Marks)

- c. Obtain Norton's equivalent for the circuit shown in Fig.Q4(c).

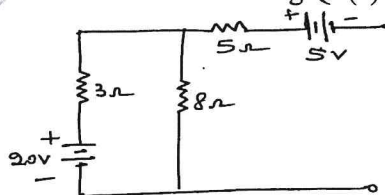


Fig.Q4(c)

(05 Marks)

**Module-3**

- 5 a. A D.C. voltage of 100V is applied in the circuit of Fig.Q5(a) and switch K is open. The switch K is closed at  $t = 0$ . Find the complete expression for the current.

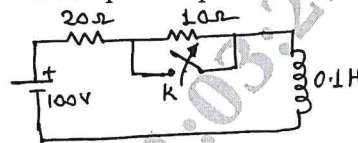


Fig.Q5(a)

(08 Marks)

- b. In the network shown in Fig.Q5(b) has two independent node pairs. The switch K is opened at  $t = 0$ . Find the  $V_1$ ,  $V_2$ ,  $\frac{d}{dt} V_1$  and  $\frac{d}{dt} V_2$  at  $t = 0_+$ .

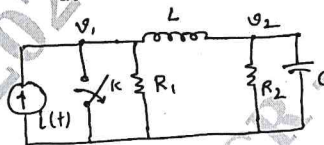


Fig.Q5(b)

(08 Marks)

**OR**

- 6 a. In the network shown in Fig.Q6(a), switch K is changed from position a to b at  $t = 0$ . Solve for  $i$ ,  $\frac{d}{dt} i$  and  $\frac{d^2}{dt^2} i$  at  $t = 0_+$ .

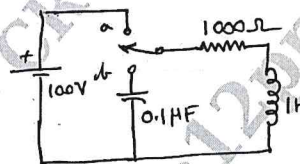


Fig.Q6(a)

(06 Marks)

- b. Steady state is reached in the circuit shown in Fig.Q6(b) when the switch is at 1. At  $t = 0$ , the switch is moved to 2. Find the drop across the capacitor as well as across the capacitor. Also find the energy stored in the capacitor at  $t = 0.1$  msec.

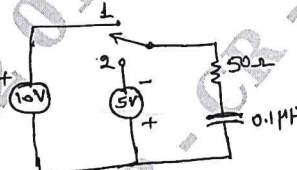


Fig.Q6(b)

(10 Marks)

CMRIT LIBRARY  
BANGALORE - 560 037

**Module-4**

- 7 a. State and prove initial and final value theorem. (06 Marks)  
 b. Represent the function shown in Fig.Q7(b) using step and ramp function. Hence determine its Laplace transform.

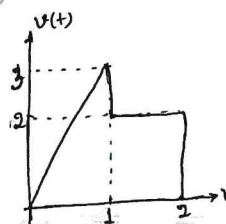


Fig.Q7(b)

(05 Marks)

- c. Find the initial and final values of  $i(t)$  using initial and final value theorems

$$I(s) = \frac{(s+1)}{(s^2 + 2s)}$$

(05 Marks)



OR

- 8 a. In the network shown in Fig.Q8(a), the switch K is closed at  $t = 0$ . Find  $i_2(t)$  using Laplace transformation technique.

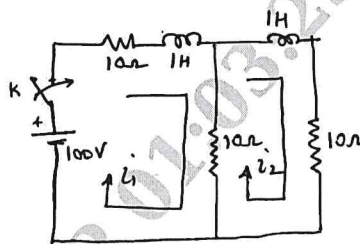


Fig.Q8(a)

(08 Marks)

- b. In a series L-C circuit, the supply voltage being  $V = V_m \cos(t)$ , find  $i(t)$  at  $t = 0_+$  following switching at  $t = 0$  with zero initial conditions. [Refer Fig.Q8(b)]

(08 Marks)

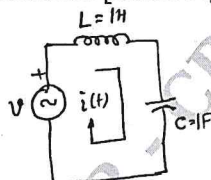


Fig.Q8(b)

**Module-5**

- 9 a. In a star connected unbalanced system of impedances of  $20 \Omega$ ,  $16+j12 \Omega$  and  $6 - j12 \Omega$  in the phases a, b, and c is being supplied by a 400 V balanced, 3 phase generator with phase sequence abc. Determine the line currents and the power supplied to the load, when the neutrals are connected. (05 Marks)
- b. Define ABCD parameters. (04 Marks)
- c. Find Y-parameters of the network shown in Fig.Q9(c), from Z-parameters.

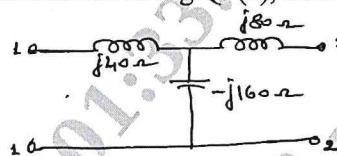


Fig.Q9(c)

(07 Marks)

OR

- 10 a. Obtain transmission parameters of the network shown in Fig.Q10(a).

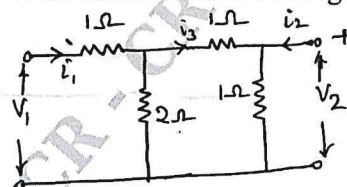


Fig.Q10(a)

(08 Marks)

- b. Find the expression of voltage transfer ratio for the network shown in Fig.Q10(b).

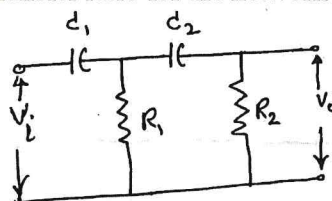


Fig.Q10(b)

(08 Marks)

\*\*\*\*\*

CMRIT LIBRARY  
BANGALORE - 560 037