



USN

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, July/August 2022
Linear ICs and Applications

Time: 3 hrs

Max. Marks:100

- Note:** 1. Answer FIVE full questions, selecting at least TWO questions from each part.
 2. Use of standard resistance and capacitance values table is permitted.

PART – A

- 1
 - a. With a neat circuit diagram, explain the working of a basic op-amp circuits. (07 Marks)
 - b. Sketch an op-amp difference amplifier circuit. Explain the operation of the circuit and derive an equation for the output voltage. (07 Marks)
 - c. Two signals each ranging from 0.1V to 1V are to be summed and amplified by a factor of 5. Using 741 op-amp design a suitable inverting summing amplifier circuit. (06 Marks)

- 2
 - a. Draw neat circuit diagram of a capacitor coupled voltage follower and give its design steps. (07 Marks)
 - b. With neat circuit diagram, explain the high input impedance capacitor coupled non-inverting amplifier. (07 Marks)
 - c. Using a LF353BIFET op-Amp design a high Z_{in} capacitor coupled non-inverting amplifier to have a low cut off frequency of 200 Hz. The input and output voltages are to be 15 mV and 3V respectively and the minimum load resistance is 12 K Ω . (06 Marks)

- 3
 - a. How upper cutoff frequency of IC741 is determined? (07 Marks)
 - b. For a voltage follower circuit using a 741 opamp, calculate the following. Assume slew rate = 0.5 V/ μ sec.
 - (i) Slew rate limited cutoff frequency if the peak of the sine wave output is 5 V.
 - (ii) Maximum value of the sinusoidal output voltage that will allow the circuit to operate at the 800 kHz unity-gain cutoff frequency.
 - (iii) Cutoff frequency limited rise time at 800 kHz unity gain cut off frequency and slew rate limited rise time if the output amplitude is 5V. (06 Marks)
 - c. Design an inverting amplifier to have a gain of 100. Input signal amplitude is 50 mV. Calculate the capacitance and resistance values to be added using Z_{in} mod compensation method to reduce the gain to 60 dB. Assume $I_{B(max)} = 200$ nA , new cutoff frequency = 2 MHz. (07 Marks)

- 4
 - a. Draw the circuit of an instrumentation amplifier and explain its working and show how voltage gain can be varied. (08 Marks)
 - b. Explain the working of precision full wave rectifier using bipolar op-amp. (06 Marks)
 - c. Sketch the circuit of a current amplifier with floating load. Explain circuit operation and derive an equation for current gain. (06 Marks)

PART – B

- 5
 - a. Draw the op-Amp sample and hold circuit and explain its operation. (08 Marks)
 - b. Explain the working of phase shift oscillator using op-Amp. (06 Marks)
 - c. With a neat circuit diagram, explain the Wein-Bridge oscillator using op-amp. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 6 a. Using a bipolar opamp with $\pm 18\text{V}$ supply, design an inverting Schmitt trigger circuit to have $UTP = 1.5\text{ V}$ and $LTP = -3\text{ V}$. Assume diode current = $500\ \mu\text{A}$, $V_F = 0.7\text{ V}$. (10 Marks)
- b. Build a circuit to have one stable output stage using opamp and write the necessary equations to design the circuit. (10 Marks)
- 7 a. What is an voltage regulator? With a neat sketch, explain the working of series op-amp regulator. (06 Marks)
- b. Design a voltage regulator using IC 723 to get an output voltage of 5V . (06 Marks)
- c. Explain the basic principle of operation of switching regulator. Discuss its advantages and limitations. (08 Marks)
- 8 a. Draw the internal schematic diagram of 555 IC configuring it for monostable operation. Explain its working. (08 Marks)
- b. With the help of basic block diagram, explain PLL. (06 Marks)
- c. Explain the working of D to A converter using R-2R network. (06 Marks)
