

# CBCS SCHEME

18EC32



## Third Semester B.E. Degree Examination, July/August 2022 Network Theory

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Briefly explain the classification of electrical networks. (10 Marks)
- b. Three resistance are connected in delta obtain the star equivalent of the network. (05 Marks)
- c. Find the equivalent resistance between any 2 corners. (Ref. Fig Q1(c))

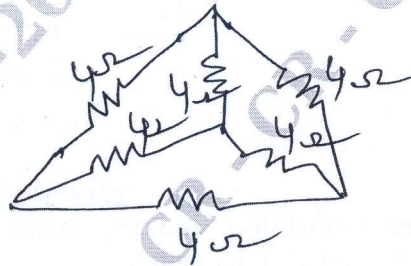


Fig Q1(c)

(05 Marks)

OR

- 2 a. Using Mesh current analysis, find the currents in various branches in the circuit. (Ref. Fig Q2(a))

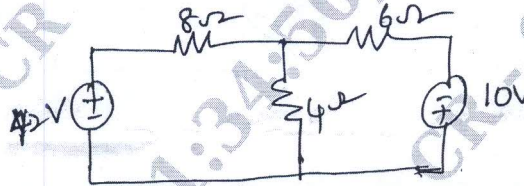


Fig Q2(a)

(10 Marks)

- b. Find the current through the branches using Nodal analysis. (Ref. Fig Q2(b)).

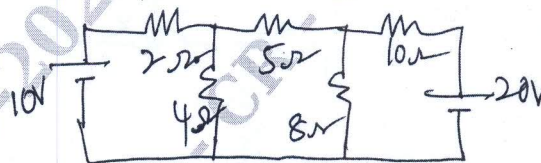


Fig Q2(b)

(10 Marks)

### Module-2

- 3 a. State and explain Thevenin's theorem. (10 Marks)
- b. Find the Norton's equivalent for the given Fig Q3(b).

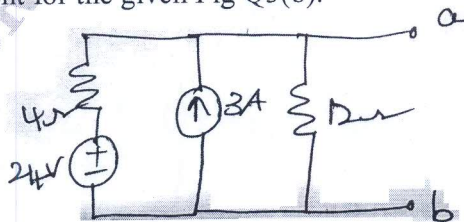


Fig Q3(b)

1 of 3

(10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 4 a. State and explain maximum power transfer when load impedance consisting of variable resistance and variable reactant. (10 Marks)
- b. Using Millman's theorem, find the current flowing through  $(4+j3) \Omega$  of the circuit as in Fig Q4(a).

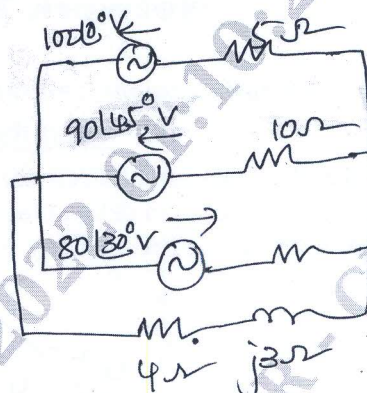


Fig Q4(a)

(10 Marks)

**Module-3**

- 5 a. Discuss the initials and final conditions in inductor, capacitor and resistor. (10 Marks)
- b. Find  $V_c(0^+)$ . Assume that the switch was in closed state for a long time. (Ref. Fig Q5(b))

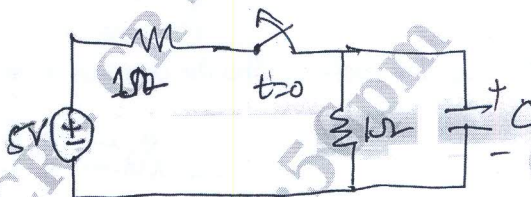


Fig Q5(b)

(10 Marks)

OR

- 6 a. In the given network, K is closed at  $t = 0$  with zero current in the inductor. Find the values of  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ , if  $R = 8\Omega$  and  $L = 0.2H$ . (Ref. Fig Q6(a))

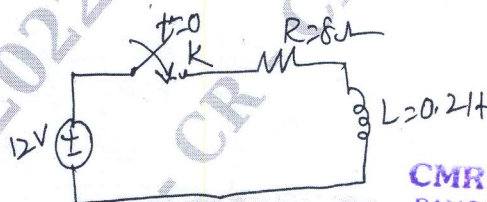
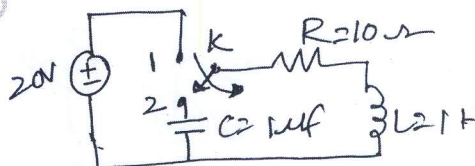


Fig Q6(a)

CMRIT LIBRARY  
BANGALORE - 560 037

(10 Marks)

- b. In circuit shown in Fig Q6(b). The switch K is changed from position 1 to position 2 at  $t = 0$ . Steady state condition having been reached at position. Find the values of  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ .

Fig Q6(b)  
2 of 3

(10 Marks)



**Module-4**

- 7 a. Obtain the Laplace transform of  
 i) Unit step function    ii) Unit Ramp function    iii) Unit impulse function.    (10 Marks)  
 b. Find the Laplace transform of following :  
 (i)  $x(t) = 2t u(t) - \frac{4d}{dt} \delta(t)$     ii)  $x(t) = 5u(t/3)$     iii)  $x(t) = 5e^{-t/2}u(t)$     (10 Marks)

OR

- 8 a. Find the Laplace transform for the given Figure Q8(a).

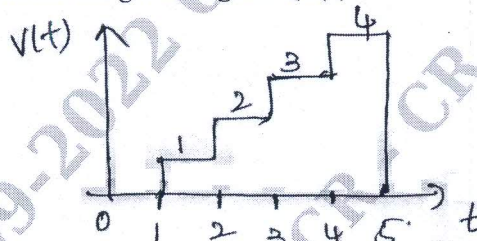


Fig Q8(a)

(10 Marks)

- b. Find the Laplace transform for the Fig Q8(b)

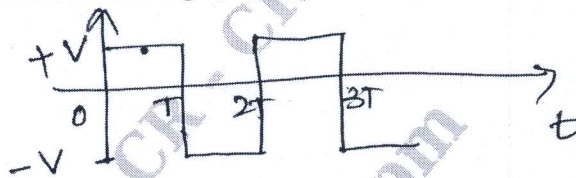


Fig Q8(b)

(10 Marks)

**Module-5**

- 9 a. What is resonance? Derive an expression for half power frequencies in series RLC circuit. Define Q-factor, selectivity and Bandwidth.    (10 Marks)  
 b. Find the value of  $R_L$  for which, circuit shown below in Fig Q9(b), is resonant.

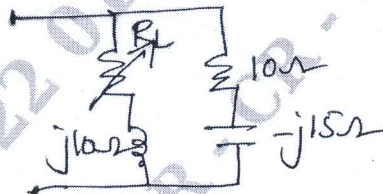


Fig Q9(b)

**CMRIT LIBRARY**  
 BANGALORE - 560 037

(10 Marks)

OR

- 10 a. Find Y and Z parameters for the network (Ref. Fig Q10(a)).

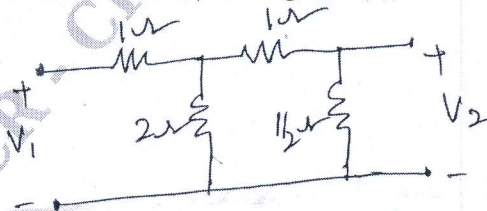


Fig Q10(a)

(10 Marks)

- b. Derive Y parameters in terms of ABCD parameters.    (10 Marks)