

CBCS SCHEME

USN

--	--	--	--	--	--	--

15EC33

Third Semester B.E. Degree Examination, July/August 2022

Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

1. a. Place the following expression into proper canonical form:
 i) $P = f(a, b, c) = a\bar{b} + a\bar{c} + bc$ ii) $T = f(a, b, c) = (a + \bar{b})(\bar{b} + \bar{c})$ (06 Marks)
- b. Simplify the following using Quine-McCluskey method. Obtain the prime implicants and essential prime implicants: $P = f(a, b, c, d) = \sum m(4, 5, 6, 8, 9) + \sum d(0, 7, 15)$ verify using K-map. (10 Marks)

OR

2. a. Simplify the Boolean expression using 5-variable K-map.
 $T = f(a, b, c, d, e) = \sum(0, 2, 8, 10, 16, 18, 24, 26)$. (08 Marks)
- b. Design a 4-bit combinational circuit that generates a high output when only any of the two inputs are high. Obtain the Boolean expression. (08 Marks)

Module-2

3. a. Implement the full adder using 2-input NAND gates, with truth table and Boolean equations. (08 Marks)
- b. Implement
 $f(a, b, c, d) = \sum m(0, 1, 5, 6, 7, 9, 10, 15)$ using 8:1 and 4:1 multipliers. (08 Marks)

OR

4. a. Explain simple 4:2 encoder, with truth table. (04 Marks)
- b. Implement $f(a, b, c) = \sum m(0, 1, 2, 5)$ using active low output dual 2:4 decoder IC74139. (04 Marks)
- c. Explain the working principle of 4-bit parallel fast look ahead carry adder. (08 Marks)

Module-3

5. a. Define the following terms, and explain using a timing diagram.
 i) Propagation delay ii) t_{PLH} and t_{PHL} . (06 Marks)
- b. Explain the working of master slave J-K flipflop with logic diagram, function table, logical symbol and timing diagram. (10 Marks)

OR

6. a. Obtain the characteristic equations for T, D, SR and JK flipflops. (08 Marks)
- b. With the timing diagram, explain the working of switch de bouncer, using SR latch. (08 Marks)

Module-4

7. a. Design a serial In serial Out unidirectional shift register and explain. (06 Marks)
- b. Design a synchronous Mod-6 counter for the sequence (0, 2, 3, 6, 5, 1) using JK-flipflops. (10 Marks)

OR

- 8 a. Design a twisted ring counter using D flip flops, illustrate with truth table. (06 Marks)
 b. With the help of neat block diagram, explain parallel in, serial out unidirectional shift register. (10 Marks)

Module-5

- 9 a. With a suitable example, explain Mealy and Moore model in a sequential circuit analysis. (06 Marks)
 b. Construct the transition table, state table and state diagram in Fig.Q.9(b) for Moore Model. (10 Marks)

 


Fig.Q.9(b)

CMRIT LIBRARY
BANGALORE - 560 037

OR

- 10 a. A sequential circuit has one input and one output. Design a circuit using DFF for the state diagram shown in Fig.Q.10(a). (08 Marks)

 


Fig.Q.10(a)

- b. Construct the excitation table, transition table state table and state diagram for the sequential circuit given below in Fig.Q.10(b). (08 Marks)

 


Fig.Q.10(b)
