



CBCS SCHEME

15EC34

Third Semester B.E. Degree Examination, July/August 2022

Network Analysis

USN

* Time: 3 hrs.

Note: Answer any FIVE full questions, choosing ONE full question from each module.


Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. $42+8=50$, will be treated as malpractice.

Module-1

1. a. Find the current 'I' in 5Ω using Mesh analysis for Fig. Q1(a).

(08 Marks)


Fig. Q1(a)

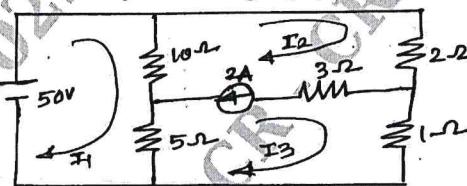

- b. Find the voltage V_x using Node Analysis for Fig. Q1(b).

(08 Marks)

Fig. Q1(b)

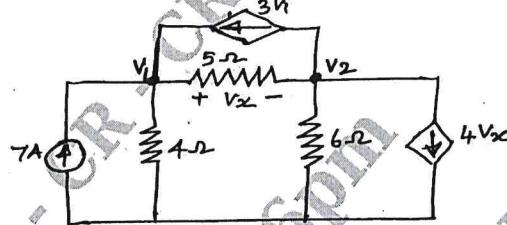


OR

2. a. Determine the resistance between A and B using Δ to Y conversion for Fig. Q2(a).

(04 Marks)


Fig. Q2(a)

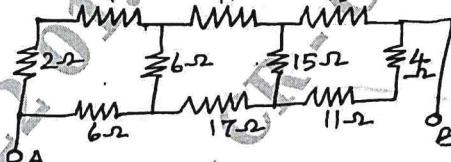

- b. Find the current I_1 , I_2 using Mesh Analysis for Fig. Q2(b).

(06 Marks)


Fig. Q2(b)

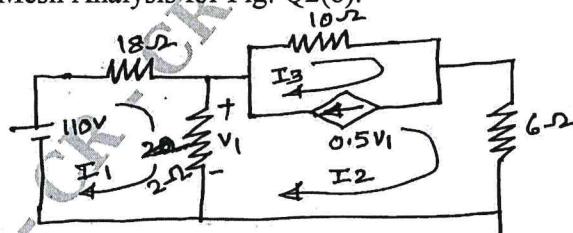

- c. Calculate I_1 , I_2 , I_3 , V_a , V_b using Node analysis for Fig. Q2(c).

(06 Marks)

Fig. Q2(c)

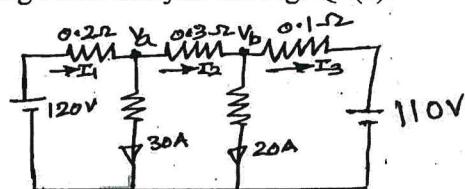

Module-2

- 3 a. State and prove Thevenin's theorem.
b. Find I_x using Super position theorem for Fig. Q3(b).

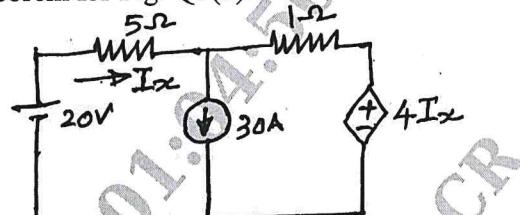
(05 Marks)
(05 Marks)

Fig. Q3 (b)

- c. Verify the Reciprocity theorem for the circuit in Fig. Q3(c).

(06 Marks)

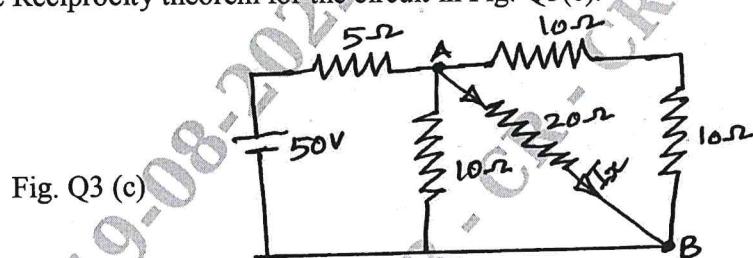


Fig. Q3 (c)

OR

- 4 a. State and prove Millman's theorem.
b. Determine I through 8Ω using Norton's theorem for Fig. Q4(b).

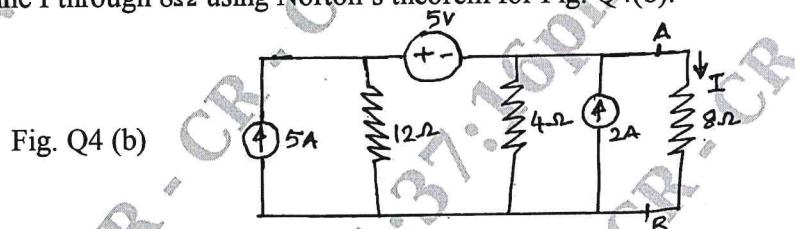
(05 Marks)
(05 Marks)

Fig. Q4 (b)

- c. Find the value of R_L and Maxi Power delivered to R_L using Maxi Power theorem for Fig. Q4(c).

(06 Marks)

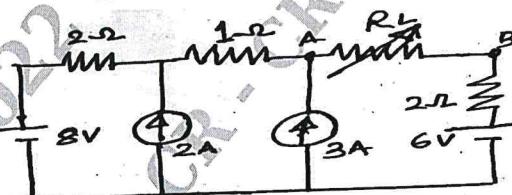


Fig. Q4 (c)


Module-3CMRIT LIBRARY
BANGALORE - 560 037

- 5 a. S – opened at $t = 0$ for the circuit Fig. Q5(a). Calculate $V(0^+)$

$$\frac{dv(0^+)}{dt}, \frac{d^2v(0^+)}{dt^2}$$

(05 Marks)

Fig. Q5(a)

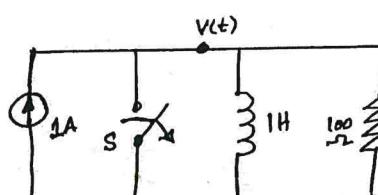

- b. S – is moved from 1 to 2 at $t = 0$ find $I(0^+)$, $\frac{dI(0^+)}{dt}$, $\frac{d^2I(0^+)}{dt^2}$ for the circuit in Fig. Q5(b).

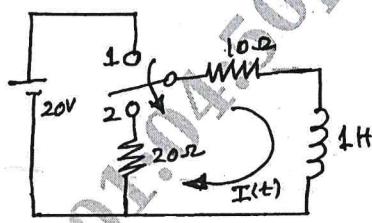



Fig. Q5 (b)

(05 Marks)

- c. S – is moved from 1 to 2 at $t = 0$. Determine $I(t)$ using Laplace Transformation for $t > 0$ in the circuit Fig. Q5(c).

(06 Marks)


Fig. Q5 (c)

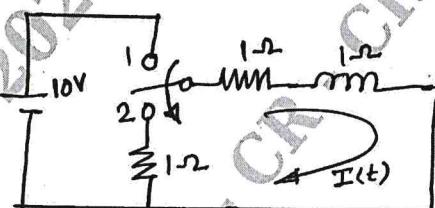

OR

- 6 a. Find Inverse Laplace Transform of $\frac{1}{s(s+1)}$. (04 Marks)
- b. S – is changed from 1 to 2 at $t = 0$, find $I(t)$ for $t > 0$ in the circuit Fig. Q6(b). (06 Marks)

Fig. Q6 (b)

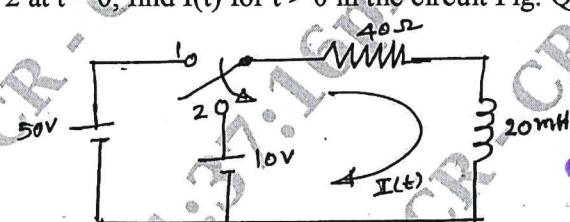CMRIT LIBRARY
BANGALORE - 560 037

- c. A series R, L circuit with initial current I_0 in inductor is connected to a D.C voltage V at $t = 0$. Derive an expression for $I(t)$ through the inductor for $t > 0$. (06 Marks)

Module-4

- 7 a. Show the resonance frequency $f_0 = \sqrt{f_1 f_2}$ for series resonance circuit. (05 Marks)
- b. Derive an expression for resonance frequency f_0 in case of parallel resonance circuit when inductor L resistance R_L is considered. (05 Marks)
- c. A series resonance circuit $C = 1\mu F$ and its inductor L resistance is 16Ω . If the Bandwidth is 500rad/sec. Determine f_0 , Q, L. (06 Marks)


OR

- 8 a. Define Q – factor, Bandwidth, selectivity of series resonance circuit. (06 Marks)
- b. Determine the frequency w_c , when the voltage across the capacitor is maximum incase of series resonance circuit. (05 Marks)

- c. The inductor value $L = 0.1\text{H}$ for the circuit Fig. Q8(c) and its Q value is 5. The resonance frequency of the circuit is 500rad/sec . Determine the values of capacitance C and R.

(05 Marks)


Fig. Q8 (c)

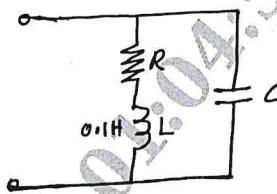**Module-5**

- 9 a. Determine Z – parameters for the circuit Fig. Q9(a). Using interrelationship between parameters, find Y parameters.

(08 Marks)


Fig. Q9 (a)

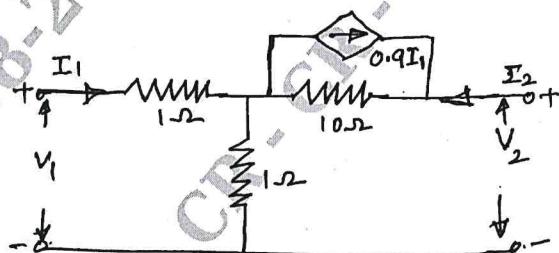

- b. Determine the h – parameters for the circuit Fig. Q9(b).

(08 Marks)

Fig. Q9 (b)

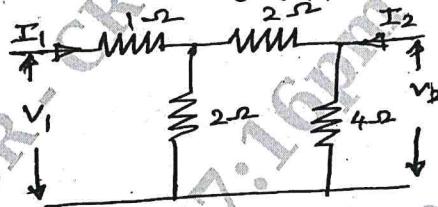CMRIT LIBRARY
BANGALORE - 560 037

OR

- 10 a. Define Z – parameters and obtain the condition for symmetry.

(08 Marks)

- b. Determine Z – parameters, using Interrelationship between parameters, determine h parameters for the circuit Fig. Q10(b).

(08 Marks)

Fig. Q10 (b)

