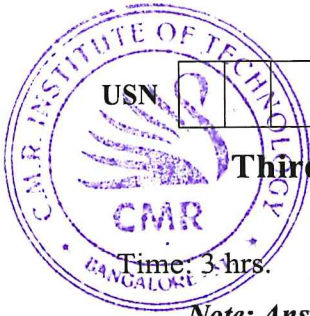


CBCS SCHEME



15EC35

Third Semester B.E. Degree Examination, July/August 2022 Electronic Instrumentation

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- a. Define the following terms as applied to an electronic instruments:
(i) Accuracy (ii) Precision (iii) Error (iv) Sensitivity (v) Resolution (10 Marks)
b. Calculate multiplier resistance for a voltage range of (0-10)V. If a full-scale deflection current is 40 μ A and internal resistance of the meter is 500 Ω . (06 Marks)

OR

- a. Explain the various types of thermocouples used in RF ammeter with a sketch. (08 Marks)
b. Explain the operation of True RMS voltmeter with a diagram. (08 Marks)

Module-2

- a. Explain the working principle of successive approximation DVM with a help of block diagram. (10 Marks)
b. Draw a neat block diagram and explain Digital pH meter. (06 Marks)

OR

- a. Describe the working of V-F conversion integrating type DVM. (08 Marks)
b. Explain the operation of Digital frequency meter with a block diagram. (08 Marks)

Module-3

- a. Explain the operation of vertical amplifier used in CRO with a block diagram. (08 Marks)
b. With a neat block, explain the operation of function generator. (08 Marks)

OR

- a. Explain Digital Storage Oscilloscope with a block diagram. (10 Marks)
b. Explain AF sine and square wave generator with a block diagram. (06 Marks)

Module-4

- a. Explain the measurement of phase using phase meter with a neat sketch. (06 Marks)
b. Describe the operation of Wien's bridge with a neat circuit diagram and derive the expression for the frequency. (10 Marks)

OR

- a. The self-inductance of a coil is to be measured by Q-meter. The first measurement results are $f_1 = 8$ MHz and $C_1 = 550$ pF. The second measurement result is 3 times f_1 with a tuning capacitance of 50 pF. Find the stray capacitance and the inductance. (08 Marks)
b. State and derive the expression for Wheatstone bridge at balance condition. (08 Marks)

Module-5

- a. Explain the Resistance Thermometer with a neat sketch. (06 Marks)
b. Explain the construction and working of LVDT with a necessary diagram. (10 Marks)

OR

- a. Define gauge factor. Derive the expression for gauge factor and prove that $K = (1 + 2\mu)$. (10 Marks)
b. Explain the working of piezo-electric transducer with a neat sketch. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

CMRIT LIBRARY
BANGALORE - 560 037