

CBCS SCHEME

17EC34



Third Semester B.E. Degree Examination, July/August 2022 Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- Construct a truth table and write the Boolean equations when a output variable 'z' is true when input variable a and b are true and when input variables a and c are true but b is false. (04 Marks)
 - Find the prime implicants and the essential prime implicants of the following Boolean function using K-Map.
 - $f(a, b, c, d) = \sum m(1, 3, 5, 7, 8, 10, 12, 13, 14) + \sum d(4, 6, 15)$
 - $f(a, b, c, d) = \pi(0, 1, 4, 5, 8, 9, 11) + \pi d(2, 10)$ (06 Marks)
 - Find the minimal sum for the following Boolean function using Quine McCluskey method. $f(a, b, c, d) = \sum(2, 3, 4, 5, 13, 15,) + \sum d(8, 9, 10, 11).$ (10 Marks)

OR

- Convert the following into proper canonical form
 - $P = (\bar{w} + x)(y + \bar{z})$
 - $x = \bar{a}b + bc$ (04 Marks)
 - Find the minimal sum and minimal product for the following function using K-map $f(a, b, c, d) = \sum(6, 7, 9, 10, 13) + \sum d(1, 4, 5, 11, 15).$ (08 Marks)
 - Find the prime implicants of the function using Quine McCluskey method. $f(w, x, y, z) = \sum(1, 3, 4, 5, 6, 9, 11, 12, 13, 14)$ (08 Marks)

Module-2

- Explain 4 bit look ahead carry adder with necessary diagram and relevant expression. (10 Marks)
 - Implement full subtractor using 74138 decoder. (04 Marks)
 - Implement $f(a, b, c, d) = \sum(0, 4, 8, 10, 14, 15)$ using
 - 8:1 MUX with a, b, c as select line
 - 4:1 MUX with a, b as select lines. (06 Marks)

OR

- Design 4 lines to 2 line priority encoder which gives MSB the highest priority and LSB least priority. (06 Marks)
 - Design a two bit magnitude comparator. (08 Marks)
 - Design a binary full subtractor using only NAND gates. (06 Marks)

Module-3

- Explain the operation of switch debouncer using SR latch with the help of circuit and waveforms. (06 Marks)
 - What is the significance of edge triggering? Explain the working of positive edge triggered D flip-flop with their function table. (08 Marks)
 - Derive the characteristics equation for JK and T flip flop. (06 Marks)

OR

- Explain the working of master slave JK flip-flop with the help of circuit diagram and waveform. (10 Marks)
 - Explain race around condition and how it is overcome. (05 Marks)
 - Explain with timing diagram (i) SR flip-flop (ii) D flip-flop. (05 Marks)

Module-4

- 7 a. Design a register using positive edge triggered D flip-flop and multiplexes to operate as indicated below.

S ₁	S ₂	Register operation
0	0	Hold
0	1	Synchronous clear
1	0	Complement – contents
1	1	Circular shift left

(10 Marks)

- b. Design a Mod 6 synchronous counter using D flip-flop to generate of sequence 0, 2, 3, 6, 5, 1, 0. (10 Marks)

OR

- 8 a. Design a 3 bit binary synchronous counter using the JK flip-flop. Write excitation table, transition table and logic diagram. (12 Marks)
- b. With a neat diagram, explain the operation of universal shift register. (08 Marks)

Module-5

- 9 a. Explain the Mealy and Moore model of clocked synchronous sequential network. (10 Marks)
- b. Analyse by given sequential circuit shown in Fig Q9(b), by writing input and output equations, state table and state diagram. (10 Marks)

 


Fig Q9(b)

(10 Marks)

OR

- 10 a. Design a Mealy type sequence detector to detect a serial input sequence of 101. (10 Marks)
- b. Design a sequential circuit for a state diagram shown in Fig Q10(b) using JK flip-flop. (10 Marks)

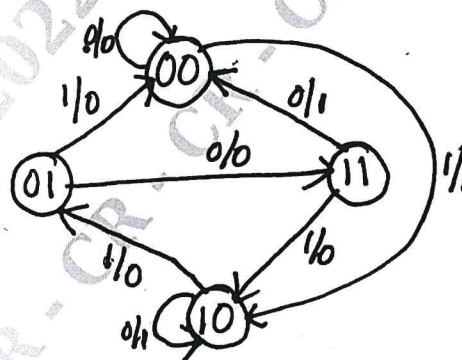


Fig Q10(b)

(10 Marks)
