

| | | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|



Internal Assesment Test - I

| | | | | | | | | | | | | | | |
|--------------------------------|---|-----------|---------|------------|----|------|-----|---------|-----|--|-------|--------|-----|--|
| Sub: | Operational Amplifiers and linear Ics | | | | | | | | | | Code: | 18EE46 | | |
| Date: | 12/07/2022 | Duration: | 90 mins | Max Marks: | 50 | Sem: | 4th | Branch: | EEE | | | | | |
| Answer Any FIVE FULL Questions | | | | | | | | | | | | | | |
| | | | | | | | | | | | Marks | OBE | | |
| | | | | | | | | | | | | CO | RBT | |
| 1 | Sketch the circuit of 3 input non inverting summing amplifier and derive the expression of output voltage and illustrate how the same can be used as averaging amplifier. | | | | | | | | | | 10 | CO1 | L2 | |
| 2 | Define the following a. Input bias current b. Input offset current c. Slew rate d. CMRR e. Offset Voltage | | | | | | | | | | 10 | CO1 | L1 | |
| 3 | Explain the Instrumentation amplifier circuit and obtain expression for output voltage of a transducer bridge Instrumentation amplifier with a neat circuit diagram. | | | | | | | | | | 10 | CO1 | L2 | |
| 4 | Why are active filters are preferred over passive filters? Derive the expression of gain for first order LPF | | | | | | | | | | 10 | CO2 | L2 | |

P.T.O


| | | | | | | | | | | | | | |
|---|---|--|--|--|--|--|--|--|--|--|----|-----|----|
| 5 | Design a Butterworth second order high pass filter circuit to have a cut-off frequency of 6Khz calculate the actual cut-off frequency for the circuit using the selected component values | | | | | | | | | | 10 | CO2 | L3 |
| 6 | Explain in detail about the all pass filter and derive the magnitude and phase of the same. | | | | | | | | | | 10 | CO2 | L2 |

Handwritten signature
CCI

Handwritten signature
CCI

Handwritten signature
HOD

1.

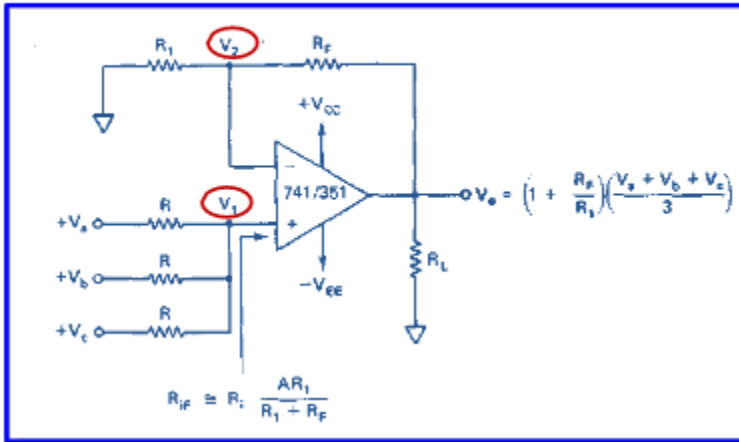

Non-inverting Summing Amplifier

Therefore, using the superposition theorem, the voltage $V_2 = V_1$
 V_b & $V_c = 0$. Net resistance
 $= R + R/2$

$$V_1 = \frac{R/2}{R + R/2} V_a + \frac{R/2}{R + R/2} V_b + \frac{R/2}{R + R/2} V_c$$

$$V_1 = \frac{R/2}{3R/2} V_a + \frac{R/2}{3R/2} V_b + \frac{R/2}{3R/2} V_c$$

$$V_1 = \frac{V_a}{3} + \frac{V_b}{3} + \frac{V_c}{3} = \frac{V_a + V_b + V_c}{3}$$

If $R_f = 2R_1$, $1 + R_f/R_1 = 3$
 $V_o = V_a + V_b + V_c$

2.

Input bias current: The dc current required by the inputs of the amplifier to properly operate the first stage. It is the average of both input currents.

Input Offset Current It is the difference of input bias currents.


Slew Rate It is the maximum rate of change of the output voltage in response to a step input voltage.

COMMON-MODE REJECTION RATIO (CMRR) The ability of amplifier to reject the common-mode signals (unwanted signals) while amplifying the differential signal (desired signal).

The input offset voltage is defined as the voltage that must be applied between the two input terminals of the op amp to obtain zero volts at the output. Ideally the output of the op amp should be at zero volts when the inputs are grounded. In reality the input terminals are at slightly different dc potentials.

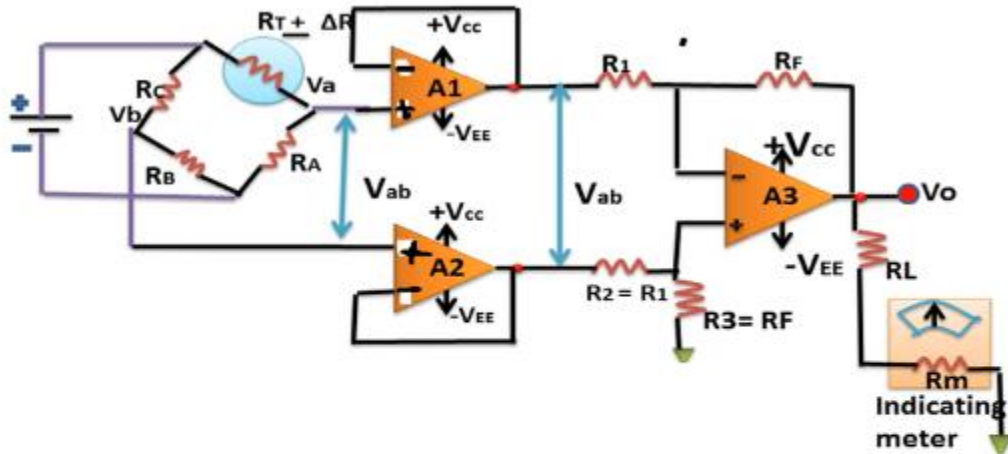3.

INSTRUMENTATION AMPLIFIER USING TRANSDUCER BRIDGE



According to voltage divider rule

$$V_a = \frac{R_A(V_{dc})}{R_A + (R_T + \Delta R)} \quad V_b = \frac{R_B(V_{dc})}{R_B + R_C}$$

Voltage V_{ab} across the output terminal

$$V_{ab} = V_a - V_b$$

$$= \frac{R_A(V_{dc})}{R_A + (R_T + \Delta R)} - \frac{R_B(V_{dc})}{R_B + R_C}$$

If $R_A = R_B = R_C = R_T = R$ THEN

$$V_{ab} = - \frac{\Delta R(V_{dc})}{2(2R + \Delta R)}$$

- Sign show $V_a < V_b$ because R_T increase

Output voltage V_{ab} of the bridge is applied to differential instrumentation amplifier composed to three op amp .

Gain of the basic amplifier is $(-R_F/R_1)$, then V_o is

Voltage V_{ab} across the output terminal

ΔR is small and $2R + \Delta R = 2 R$

$$V_o = V_{ab} \cdot \frac{R_F}{R_1} = - \frac{\Delta R(V_{dc})}{2(2R + \Delta R)} \frac{R_F}{R_1}$$

$$V_o = \frac{R_F}{R_1} \frac{\Delta R}{4R} V_{dc}$$

4.

| Basis for Comparison | Active Filter | Passive Filter |
|-----------------------|--|---|
| Composed of | Active components like op-amp, transistor etc. | Passive components like resistor, inductor and capacitor etc. |
| Cost | High | Comparatively low. |
| Circuit complexity | More complex | Less complex than active filter. |
| Weight | Low | Comparatively bulkier due to presence of inductors. |
| Q factor | High | Very low in comparison to active filters. |
| External power supply | Required | Not required |

First Order Low Pass Filter

➤ The resistors R_f and R_1 decide the gain of the filter in the pass band.


The impedance of the capacitor C is $-jX_C$ where X_C is the capacitive reactance given by $X_C = 1/2\pi fC$.

$$V_A = -\frac{-jXC}{R - jXC} * VIN$$

$$V_A = -\frac{-j \frac{1}{2\pi fC}}{R - j \frac{1}{2\pi fC}} * VIN = \frac{VIN}{1 - \frac{2\pi fRC}{j}}$$

$-j = 1/j$; $j = -1/j$

$$V_A = -\frac{VIN}{1 + j2\pi fRC}$$

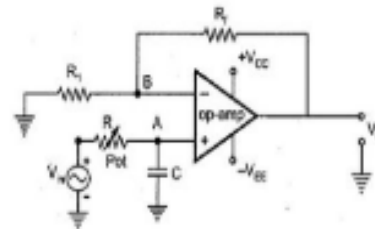

First order low pass butterworth filter

$$V_A = -\frac{VIN}{1 + j2\pi fRC}$$


the op-amp is in the non-inverting configuration,

$$V_O = \left(1 + \frac{R_f}{R_1}\right) V_A = \left(1 + \frac{R_f}{R_1}\right) \frac{VIN}{1 + j2\pi fRC}$$

$$\frac{V_O}{VIN} = \frac{A_F}{1 + j\left(\frac{f}{f_H}\right)}$$

Where, $A_F = 1 + \frac{R_f}{R_1}$

$$f_H = \frac{1}{2\pi RC}$$

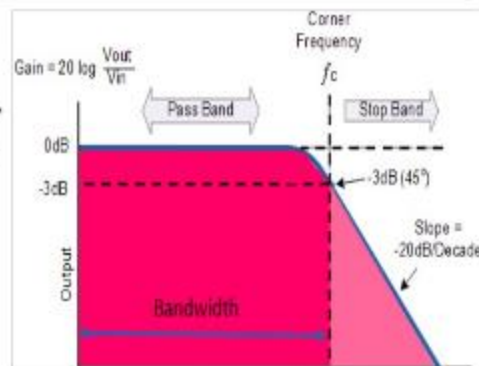

5.

VIU : Aug.-02, July-08,09, Jan.-16, Marks 6

Solution : As decay rate in the stop band is + 40 dB/decade, it is second order high pass filter.

Choose $C_2 = C_3 = C = 1000 \text{ pF}$
and $f_L = 6 \text{ kHz}$

$$\therefore f_L = \frac{1}{2\pi RC} \quad \text{i.e.} \quad 6 \times 10^3 = \frac{1}{2\pi R \times 1000 \times 10^{-12}}$$

$$\therefore R = 26.525 \text{ k}\Omega \approx 27 \text{ k}\Omega$$

$$\therefore R = R_2 = R_3 = 27 \text{ k}\Omega$$

For Butterworth response,

$$A_F = 1.586 = \frac{R_f}{R_1} + 1$$

$$\therefore R_f = 0.586 R_1$$

Choose $R_f = 10 \text{ k}\Omega$ and $R_1 = 17 \text{ k}\Omega$

Hence the designed circuit is,

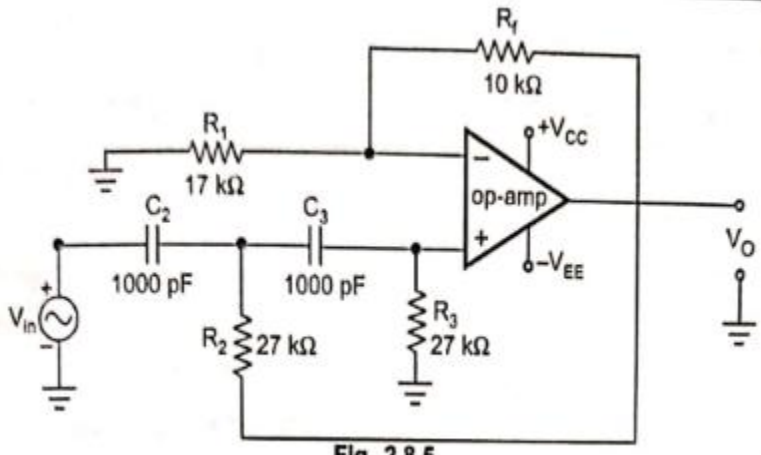


Fig. 2.8.5

6.

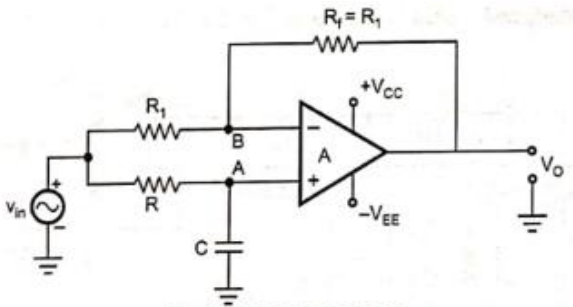


Fig. 2.12.1 All pass filter

Let us use the superposition principle to obtain the expression for the output voltage V_O .

Assume input to the non-inverting terminal zero. The circuit acts as an inverting amplifier.

$$\therefore V_{O1} = -\frac{R_f}{R_1} V_{in}$$

$$\therefore V_{O1} = -V_{in} \quad \text{as } R_f = R_1 \quad \dots (2.12.1)$$

Now, assume input to the inverting terminal zero. The circuit acts as a non-inverting amplifier.

$$\therefore V_{O2} = \left(1 + \frac{R_f}{R_1}\right) V_A$$

$$\therefore V_{O2} = 2 V_A \quad \text{as } R_f = R_1 \quad \dots (2.12.2)$$

and $V_A =$ Voltage at node A

By the potential divider rule, the voltage V_A can be obtained as

$$V_A = V_{in} \left[\frac{-jX_C}{R - jX_C} \right]$$

$$\text{where } -jX_C = -j \left(\frac{1}{2\pi fC} \right) = \left(\frac{1}{j2\pi fC} \right) \text{ as } -j = \frac{1}{j}$$

$$\therefore V_A = V_{in} \left[\frac{\frac{1}{j2\pi fC}}{R + \frac{1}{j2\pi fC}} \right] = V_{in} \left[\frac{1}{1 + j2\pi fRC} \right] \quad \dots (2.12.3)$$

Substituting in (2.12.2),

$$V_{O2} = 2 V_{in} \left[\frac{1}{1 + j2\pi fRC} \right] \quad \dots (2.12.4)$$

Hence, the total output voltage is

$$V_O = V_{O1} + V_{O2} = -V_{in} + 2 V_{in} \left[\frac{1}{1 + j2\pi fRC} \right]$$

$$\therefore V_O = V_{in} \left[-1 + \frac{2}{1 + j2\pi fRC} \right] \quad \dots (2.12.5)$$

$$\therefore \frac{V_O}{V_{in}} = \frac{1 - j2\pi fRC}{1 + j2\pi fRC} \quad \dots (2.12.6)$$

The magnitude of the transfer function is

$$\left| \frac{V_O}{V_{in}} \right| = \frac{\sqrt{1 + (2\pi fRC)^2}}{\sqrt{1 + (2\pi fRC)^2}} = 1 \quad \dots (2.12.7)$$

It is mentioned earlier that the magnitude is always 1 for all pass filter and it can pass the entire range of frequency. But the phase angle is given by

$$\phi = -2 \tan^{-1} \left(\frac{2\pi fRC}{1} \right) \quad \dots (2.12.8)$$