

Internal Assessment Test - III

Sub:	Industrial Drives and Applications						Code:	17EE82	
Date:	18/06/2022	Duration:	90mins	Max Marks:	50	Sem:	8 th	Branch:	EEE
Answer any FIVE FULL Questions.									
							Marks	OBE	
								CO	RBT
1.	A 400 V, star connected, 3- phase ,6-pole, 50 Hz induction motor has following parameters referred to the stator; $R_s=R_r'=1 \Omega$, $X_s=X_r'=2 \Omega$ For regenerative braking operation of this motor determine: (i)maximum overhauling torque it can hold and range of speed for safe operation (ii)speed at which it will hold an overhauling load with a torque of 100 N-m						10	CO4	L3
2.	Discuss the operation of self-controlled synchronous motor drive employing load commutated thyristor inverter.						10	CO5	L1
3.	Explain the behavior of 3 phase induction motor when fed from a non-sinusoidal voltage supply.						10	CO4	L1
4.	Describe with relevant diagrams the voltage source inverter (VSI) control of three phase induction motor.						10	CO4	L2
5.	Explain brushless dc motor drive for servo application.						10	CO5	L1
6.	A 2200 V, 50 Hz, 3- phase, 6 pole, Y – connected, Squirrel cage induction motor has following parameters: $R_s=0.075\Omega$, $R_r'=0.12 \Omega$, $X_s=X_r'=0.5 \Omega$ The combined inertia of motor and load is 200 kg-m ² .(i)Calculate time taken and energy dissipated in the motor during starting.(ii)Calculate time taken and energy dissipated in the motor when it is stopped by plugging. (iii)What resistance should be inserted in the rotor to stop motor by plugging in the minimum time? Also calculate stopping time and energy dissipated in the motor during braking.						10	CO5	L3

CCI

CI

HOD

Q.1

- ① A 400V, λ -connected 3 ϕ , 6-pole, 50Hz IM has following parameters referred to stator
- $$R_s = R_r' = 1\text{-}\Omega, \quad X_s = X_r' = 2\text{-}\Omega.$$

For regenerative braking, determine.

- (i) max torque (overhauling) it can hold and range of speed for safe operation.
 (ii) speed at which it can hold an overhauling load with a torque of 100N-m.

$$N_s = \frac{120 \times 50}{6} = 1000.$$

$$\omega_{ms} = \frac{2\pi \times 1000}{60}$$

$$= 104.71 \text{ rad/sec.}$$

$$N_s = \frac{120f}{P}$$

$$\frac{2\pi N_s}{60} = \omega_{ms}$$

$$S_m = - \frac{R_r'}{\sqrt{R_s^2 + (X_s + X_r')^2}} = - \frac{1}{\sqrt{1 + (2+2)^2}}$$

$$= \frac{-1}{4.123} = -0.2425$$

$$\frac{120f \times 2\pi \times N_s}{60}$$

$$N_s = \frac{60 \times \omega_{ms}}{2\pi}$$

$$= \frac{30\omega_{ms}}{\pi}$$

$$S_m = -0.2425$$

$$I_r'^2 = \frac{V^2}{(R_s + \frac{R_r'}{s})^2 + (X_s + X_r')^2} = \frac{(400/\sqrt{3})^2}{\left[1 + \frac{1}{(-0.2425)}\right]^2 + (2+2)^2}$$

$$= \frac{53333.33}{9.7575 + 16} = 2070.594 \text{ A}$$

$$I_r' = 45.5 \text{ A}$$

$$T_{\max} = \frac{3 I_r'^2 R_r'}{s \omega_{ms}} = \frac{3 \times (45.5)^2 \times 1}{(-0.2425) \times 104.71} = -244.59$$

$$T_{\max} = -244.59 \text{ Nm}$$

$$N_m \omega_{ms} = (1-s) \omega_{ms} = [1 - (-0.2425)] \times 1000$$

$$= 1.2425 (1000)$$

$$N = 1242.5 \text{ rpm}$$

$$T_{\max} = 100 \text{ Nm}$$

$$T = \frac{3 R_r'}{s \omega_{ms}} \frac{V^2}{(R_s + \frac{R_r'}{s})^2 + (X_s + X_r')^2}$$

$$100 = \frac{3 (1)}{104.71 (s)} \left[\frac{(400/\sqrt{3})^2}{\left(1 + \frac{1}{s}\right)^2 + 16} \right]$$

$$100 = \frac{0.02}{s} \left[\frac{230.9}{1 + \frac{1}{s^2} + \frac{2}{s} + 16} \right]$$

$$\frac{1066.29}{S + \frac{17}{S} + 2 + 16/S} = 100.$$

$$1066.29 = 100 \left[\frac{S^2 + 17 + 2S + 16}{S} \right]$$

$$100 \frac{(S^2 + 17 + 2S)}{S} = 1066.29$$

$$100S^2 + 1700 + 200S = 1066.29S$$

$$100S^2 + 1700 - 866.29S = 0$$

$$17S^2 + 17.33S + 1 = 0.$$

$$S = -0.957 \text{ or } S = -0.063.$$

choose $S = -0.063$.

$$N_m = (1 - S) \cdot 1000 = 1 - (-0.063) (1000)$$


$$N_m = 1063$$

Q.2

Self controlled synchronous motor fed from a load commutated thyristor inverter.

This drive employs two converters

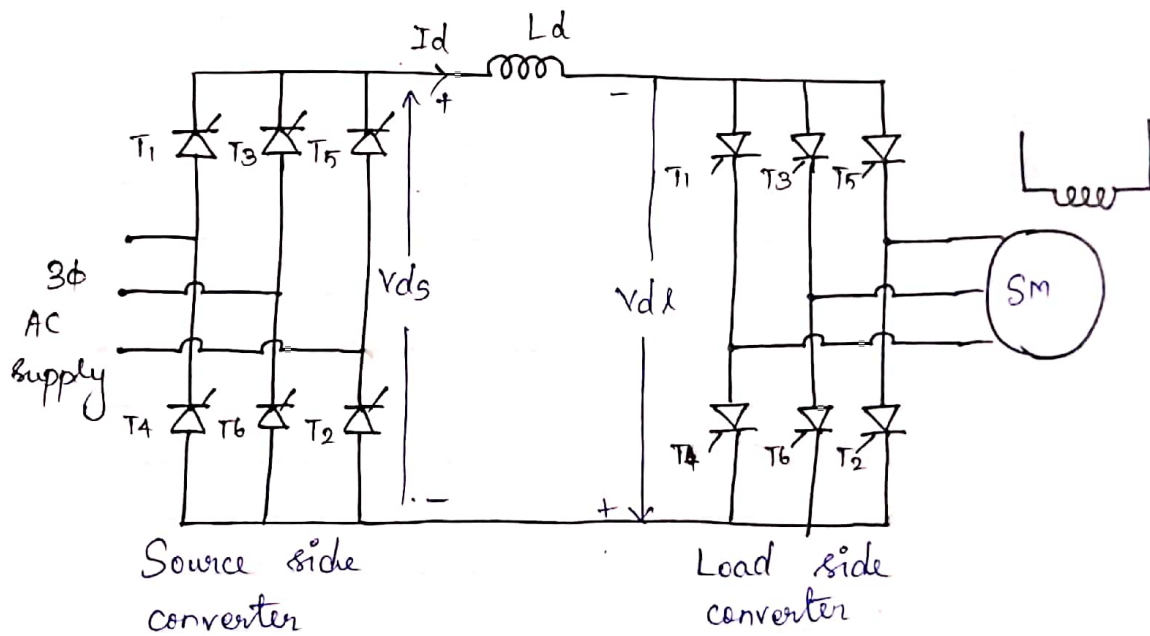- ① Source side converter
- ② Load side converter



Source side converter :-

=> acts as a line commutated controlled rectifier for $0 \leq \alpha_s \leq 90^\circ$

o/p voltage V_{ds} and o/p current I_d are +ve.

=> acts as a line commutated inverter for $90^\circ \leq \alpha_s \leq 180^\circ$.

o/p voltage V_{ds} is -ve and I_d is +ve.

Load side converter:-

\Rightarrow When SM operates at leading PF, the thyristors of the load side converter can be commutated by the motor induced voltages. This is called load commutation.

\Rightarrow This converter operates as an inverter for $90 < \alpha_2 < 180$ and delivers -ve V_{dL} and +ve I_d .

It operates as a rectifier for $0 \leq \alpha_2 < 90$ and delivers +ve V_{dL} and I_d .

\Rightarrow The SM can be operated at leading PF by adjusting the field excitation. When source side converter is operated as inverter and load side converter as rectifier then the power flows from the motor to ac source which gives regenerative braking operation.

\Rightarrow For motoring operation, source side con acts as rect and load side converter as inverter. The torque produced by the motor depends on the difference in voltages i.e $V_{dS} - V_{dL}$.

\Rightarrow The speed of the motor is changed by changing the voltage V_{dS} i.e by controlling α_1 .

\Rightarrow When both the converters are working as inverters, the firing angle should be less than 180 to avoid the short of supply. So care should be taken for commutation overlap and turn-off of thyristors.

Let β_L - commutation lead angle for load side converter.

$$\text{Then } \beta_L = 180^\circ - \alpha_L.$$

\Rightarrow If commutation overlap is neglected, then the i_p ac current will lag the i_p dc voltage by an angle α_L . As the motor current is opposite to converter i_p current, the motor current will lead the terminal voltage by β_L . Thus the motor operates at leading PF.

\Rightarrow If μ is the commutation overlap, then the duration for which reverse bias applied is given by

$$\gamma = \beta_L - \mu.$$

for successful commutation, $\gamma > \omega t_q$
where t_q - turn-off time

Commutation overlap is proportional to the dc link current I_d . Keeping $\gamma = \gamma_{\min}$, β_L will be reduced and PF will improve.

This control is called constant angle margin control.

\Rightarrow At lower speeds, forced commutation is used, since the motor voltage is less and not enough for thyristor commutation.

Analysis of IM fed from non-sinusoidal voltage supply

- * The motor terminal voltage becomes non-sinusoidal when fed from inverter or cyclo-converter.
- * voltage has half-wave symmetry:

Non-sinusoidal waveform can be resolved into fundamental and harmonic components (Fourier analysis). For half-wave symmetry only odd harmonics will be present.

+ve sequence harmonics - same phase sequence as that of fundamental.

-ve sequence harmonics - opposite phase sequence to fundamental.

zero sequence harmonics - all 3 phase voltage are in phase.

Let fundamental phase voltage be,

$$V_{AN} = V_1 \sin \omega t$$

$$V_{BN} = V_1 \sin (\omega t - 2\pi/3)$$

$$V_{CN} = V_1 \sin (\omega t - 4\pi/3)$$

with phase sequence ABC.

5th Harmonic Phase Voltage :-

$$V_{AN} = V_5 \sin 5\omega t$$

$$V_{BN} = V_5 \sin 5(\omega t - 2\pi/3)$$

$$= V_5 \sin 5\omega t - 10\pi/3 = V_5 \sin 5\omega t - 4\pi/3$$

$$V_{CN} = V_5 \sin 5\omega t - \frac{20\pi}{3} = V_5 \sin 5\omega t - 2\pi/3$$

$$\frac{10\pi}{3}$$

$$\frac{10\pi}{3}$$

$$= 4\pi/3$$

$$= 4\pi/3$$

$$= 14\pi/3$$

7th Harmonic phase voltage

$$V_{AN} = V_7 \sin 7\omega t$$

$$V_{BN} = V_7 \sin(7\omega t - 2\pi/3)$$

$$V_{CN} = V_7 \sin(7\omega t - 4\pi/3)$$

7th harmonic has phase sequence ABC

5th harmonic has phase sequence ACB -

∴ 7th, 13th, 19th - +ve seq

5th, 11th, 17th - -ve seq

3rd and its odd multiples zero seq harmonics.

$m = 6k+1$ - +ve seq

$m = 6k-1$ - -ve "

$m = 3k$ - zero "

+ve seq produces RMF ~~which~~ ^{which} moves in same dir as gen at a speed m times that of the gen field.

-ve seq opposite dir
 → zero seq donot produce rotating field.

$$\frac{10\pi}{3}$$

$$= 3\pi + \pi/3$$

$$\left(2\pi + \frac{4\pi}{3}\right) \quad \left(2\pi + \frac{2\pi}{3}\right)$$


$$\left(6\pi + \frac{2\pi}{3}\right) \quad \left(6\pi + \frac{4\pi}{3}\right)$$

$$\frac{10\pi}{3} = \frac{4\pi}{3}$$

$$\Rightarrow \frac{20\pi}{3} = \frac{2\pi}{3}$$

VSI IM Drives:-

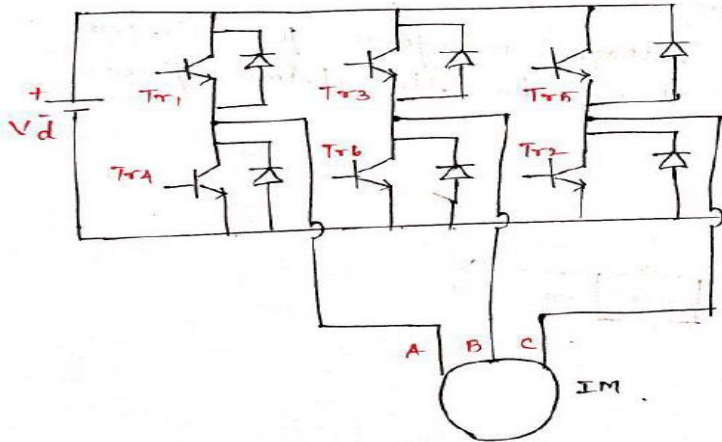⇒ VSI allows a variable freq from dc supply. Transistor inverter fed IM drive is shown in the below figure.




⇒ instead of transistors, any other self commutated devices [MOSFET (low voltage and low power), IGBT, GTO, IGCT - high power levels can be used].


⇒ VSI can be operated as stepped wave inverter or a PWM inverter.

* For a given time period T (one cycle), each device is ON for $T/2$ duration, in which all the devices are switched in the sequence of their numbers with a time difference of $T/6$.

* frequency is varied by varying T and o/p voltage is varied by varying dc i/p voltage (chopper is required).

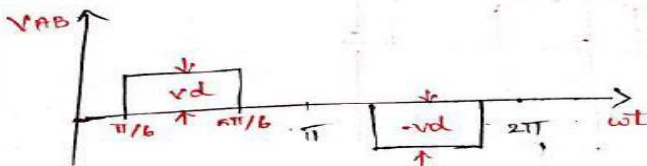The line voltage waveform for stepped wave inverter is shown in the below figure.




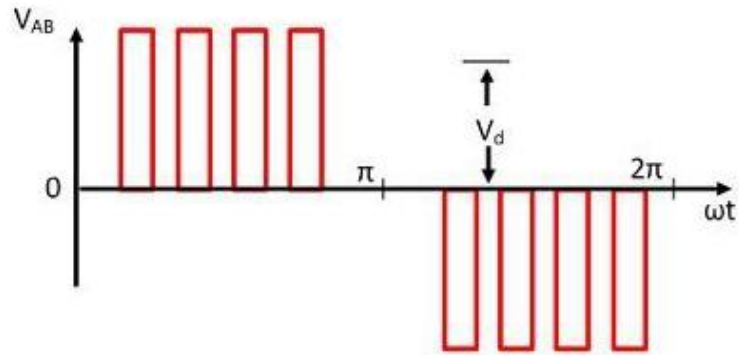

PWM Inverter Line Voltage Waveform


Circuit Globe

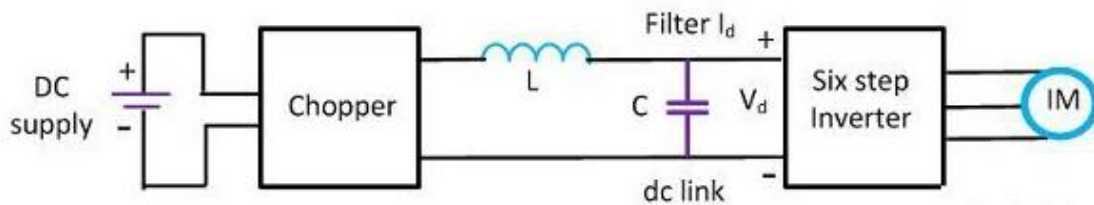When the supply is DC, then the variable DC input is obtained by connecting a chopper between DC supply and inverter.



Circuit Globe

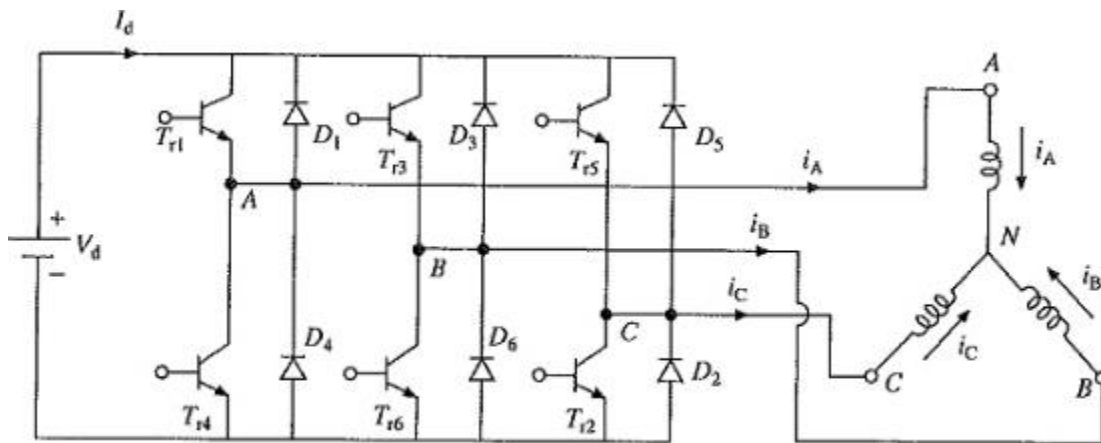Q.5 A brushless DC motor drives employing a **current regulated voltage source inverter (VSI)** and a trapezoidal PMAC motor is shown in fig




The stator winding are star connected and rotors are having rotor sensors which is not shown in

the figure

- The stator is fed with current pulses whose polarity is same as that of induced voltage
- Since air gap flux is constant , the induced voltage is prop to speed of the rotor
- i.e $E = KeWm$
- Also $P = EId + (-E * -Id) = 2EId = 2KeWmId$
- $T = P/Wm = 2Keld = KT Id$

During the period 0° to 60° , $i_a = Id$ and $i_b = -Id$. The current i_a enters through the phase A and leaves through the phase B. When transistors $Tr1$ and $Tr6$ are on, terminals A and B are respectively connected to positive and negative terminals of the dc source V_d . A current will flow through the path consisting of V_d , $Tr1$, phase A, phase B and $Tr6$ and rate of change of current i_a will be positive. When $Tr1$ and $Tr6$ are turned off this current will flow through a path consisting of phase A, phase B, diode $D3$, V_d and diode $D4$. Since the current has to flow against voltage V_d , the rate of change of i_a will be negative. Thus, by alternately turning on and off $Tr1$ and $Tr6$ phase A current can be made to follow the reference current Id within a hysteresis band as shown in fig..

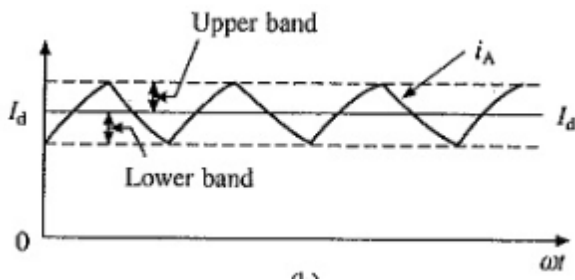By reducing the band sufficiently nearly a dc current of desired value can be produced.



Q.6

$$i) \quad t_s = T_m \left[\frac{1}{4S_m} + 1.5 S_m \right]$$

$$T_m = \frac{J \omega_{ms}}{T_{max}} ;$$

$$S_m = \frac{R_r'}{\sqrt{R_s^2 + (X_s + X_r')^2}} = \frac{0.12}{\sqrt{0.075^2 + (0.5 + 0.5)^2}}$$

$$\boxed{S_m = 0.1196}$$

$$I_r' = \frac{v^2}{(R_s + \frac{R_r'}{s})^2 + (X_s + X_r')^2} = \frac{(2200/\sqrt{3})^2}{(0.075 + \frac{0.12}{0.1196})^2 + (0.5 + 0.5)^2}$$

$$= 1/6 \text{ MA} = 745937.362 \text{ A}$$

$$I_r' = 12/6/6/6/6/6 = 863.67 \text{ A}$$

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{6} = 1000$$

$$T_{max} = \frac{3 I_r'^2 R_r'}{\omega_{ms} s} ; \quad \omega_{ms} = \frac{2\pi N_s}{60}$$

$$= 104.7 \text{ rad/sec}$$

$$= \left[3 \frac{(745.9 \times 10^3)^2}{(1.6 \times 10^6)} \times 0.12 \right] = 21443.97 \text{ Nm}$$

$$t_s = \tau_m \left[\frac{1}{4(0.1196)} + (1.5 \times 0.1196) \right]$$

$$\tau_m = \frac{J W_{ms}}{T_{max}} = \frac{100 \times 104.72}{2143.97} = 0.4884 \text{ sec}$$

$$t_s = 0.4884 \left[\frac{1}{4 \times 0.1196} + (1.5 \times 0.1196) \right]$$

$$t_s = 1.1084 \text{ sec}$$

$$E_s = \frac{1}{2} J W_{ms}^2 \left[1 + \frac{R_s}{R_r'} \right]$$

$$= \frac{1}{2} \times 100 \times (104.72)^2 \left[1 + \frac{0.075}{0.12} \right]$$

$$E_s = 891 \text{ kJ}$$

$$ii) t_b = \tau_m \left[\frac{0.75}{S_m} + 0.3465 S_m \right]$$

$$= 0.4884 \left[\frac{0.75}{0.1196} + 0.3465 (0.1196) \right]$$

$$= 3.08 \text{ sec}$$

$$E_b = \frac{3}{2} J W_{ms}^2 \left[1 + \frac{R_s}{R_r'} \right]$$

$$= \frac{3}{2} \times 100 \times (104.72)^2 \left[1 + \frac{0.075}{0.12} \right]$$

$$= 2673 \text{ kJ}$$

iii)

$$t_b(\text{min}) = 1.027 (0.4881) \\ = 0.5015$$

$$(R_r' + R_e) = 1.47 (x_s + x_r')$$

$$0.12 + R_e = 1.47 (0.5 + 0.5)$$

$$R_e' = 1.35$$

$$R_e' = R_e \Rightarrow \boxed{k=1}$$

assume,

$$E_b = \frac{3}{2} J \omega_{ms}^2 \left[1 + \frac{R_s}{R_r' + R_e} \right]$$

$$= \frac{3}{2} \times 100 \times (104.72)^2 \left[1 + \frac{0.075}{0.12 +} \right]$$

$$= 1728 \text{ kJ}$$