


Internal Assessment Test - III

Sub:	Operational Amplifiers and Linear IC's						Code:	18EE46		
Date:	27/08/2022	Duration:	90 mins	Max Marks:	50	Sem:	4th	Branch:	EEE	
Answer Any FIVE FULL Questions										
								Marks	OBE	
									CO	RBT
1	What are the major limitations of conventional rectifier? Explain the operation of precision full wave rectifier as a combination of half wave rectifier and a summing circuit.						10	CO3	L2	
2	Explain the principle of operation of R-2R ladder digital to analog converter with the neat diagram.						10	CO4	L2	
3	Explain the working of ADC using successive approximation method.						10	CO4	L2	
4	An astable multivibrator is to be designed for getting rectangular waveform for $T_{ON}=0.6ms$ , Total time period = 1ms. Assume $C=0.1\mu F$ Draw the circuit diagram.						10	CO4	L3	
5	Explain the working of linear Ramp ADC with necessary input and output waveform.						10	CO4	L2	
6	Explain working of monostable multivibrator using 555 timer and draw its input and output waveforms.						10	CO5	L2	
7	Sketch the block diagram for a basic PLL system together with the system waveforms.						10	CO5	L2	

Solution

- The major limitations of these Precision Rectifiers circuits is that they cannot rectify voltages below  $V_{D(ON)} = 0.7 V$ , the cut-in voltage of the diode. In these circuits  $V_i$  has to rise to a threshold of the order of  $V_{D(ON)}$  before any appreciable change can be seen at the output.

Half-wave Rectifier and Summing Circuit

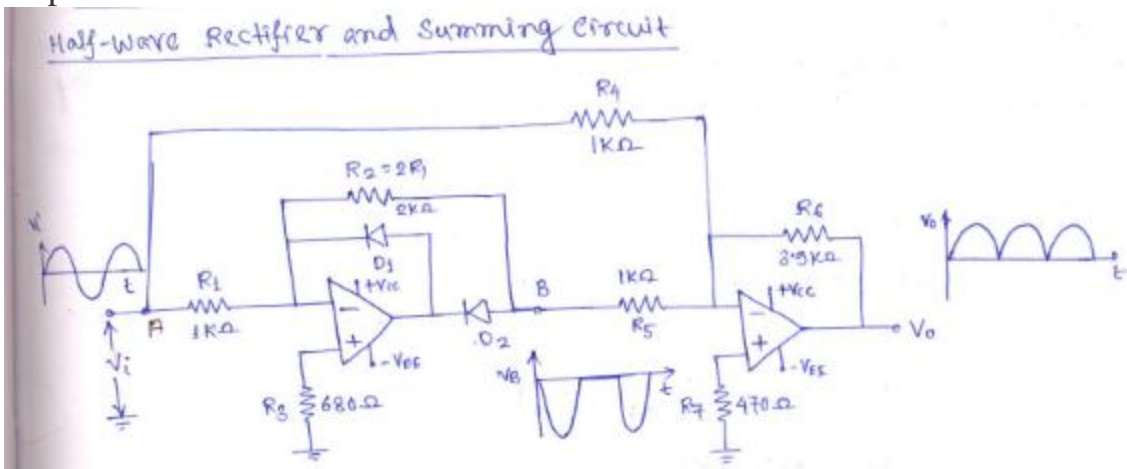

The above circuit is a combination of half-wave rectifier with gain = 2 and an inverting adder with gain = 3.9

during +ve half-cycle

voltage at terminal A =  $+V_i$   
 while that at terminal B is  $-2V_i$ .  
 [Diode  $D_1$  is off and  $D_2$  is on]

A4 College Book

~~During~~ The output of the summing circuit, with  $R_4 = R_5$

$$\begin{aligned} V_o &= -\frac{R_6}{R_4} (V_A + V_B) \\ &= -\frac{R_6}{R_4} (V_i - 2V_i) \\ &= -\frac{R_6}{R_4} (-V_i) = \frac{R_6}{R_4} V_i \end{aligned}$$

During -ve half-cycle

$$V_A = -V_i$$

$V_B = 0$  as  $D_1$  is on and  $D_2$  is off.

consequently the output is,

$$V_o = -\frac{R_6}{R_4} (V_A + V_B) = -\frac{R_6}{R_4} (-V_i + 0)$$

$$\boxed{V_o = +\frac{R_6}{R_4} V_i}$$

So, it can be seen that the output voltage is positive for both the cycle of the input voltage. If  $R_6 = R_4 = R_5$  then the gain of the circuit is 1. when  $R_6$  is greater than  $R_4$  then rectification and amplification both occurs.

2.

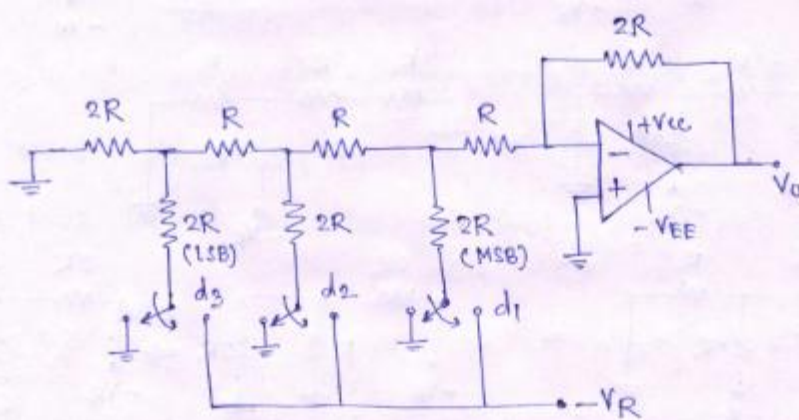


Fig- R-2R Ladder type DAC


The range for  $R$  is  $2.5 \text{ k}\Omega$  to  $10 \text{ k}\Omega$ .

For simplicity, consider a 3-bit DAC, where  $d_1, d_2, d_3$  corresponds to the binary word input to the DAC.

$-V_R$  is the reference voltage.

The feedback resistance is  $2R$ . The network consist of  $R-2R$  network connected with the op-amp.

3.)

 

Functional diagram of the successive approximation ADC

correct digital representation	successive approximation resistor output $V_d$ at different stages in conversion	comparator output
11010100	10000000	1
	11000000	1
	11100000	0
	11010000	1
	11011000	0
	11010100	1
	11010110	0
	11010101	0
	11010100	

For successive approximation type ADC, for  $n$ -bit conversion just  $n$ -clock pulses are required. An eight bit converter would require eight clock pulses to obtain a digital output. The circuit uses a successive approximation resistor (SAR) to find the required value of each bit by trial & error.

4.

Solution

$$f = \frac{1.45}{(R_A + 2R_B)C} = 1 \times 10^3$$

$$\text{or, } (R_A + 2R_B) \times 0.1 \times 10^{-6} = \frac{1.45}{1 \times 10^3} \quad \left[ \begin{array}{l} \text{Assume select,} \\ C = 0.1 \mu\text{F} \end{array} \right]$$

$$\text{or, } R_A + 2R_B = 14.5 \times 10^3 = 14.5 \text{ K}\Omega \quad \text{--- (1)}$$


$$D = \frac{R_A + R_B}{R_A + 2R_B} = 0.6$$

$$\text{or, } R_A + R_B = 0.6 (R_A + 2R_B) = 0.6 \times 14.5 \text{ K}\Omega = 8.7 \text{ K}\Omega \quad \text{--- (2)}$$


Let's Using eq (1) and (2) we get,

$$R_B = (14.5 - 8.7) \text{ K}\Omega = 5.8 \text{ K}\Omega \approx 5.6 \text{ K}\Omega$$
 
$$R_A = 8.7 - 5.6 = 3.1 \text{ K}\Omega \approx 3.3 \text{ K}\Omega$$




5.

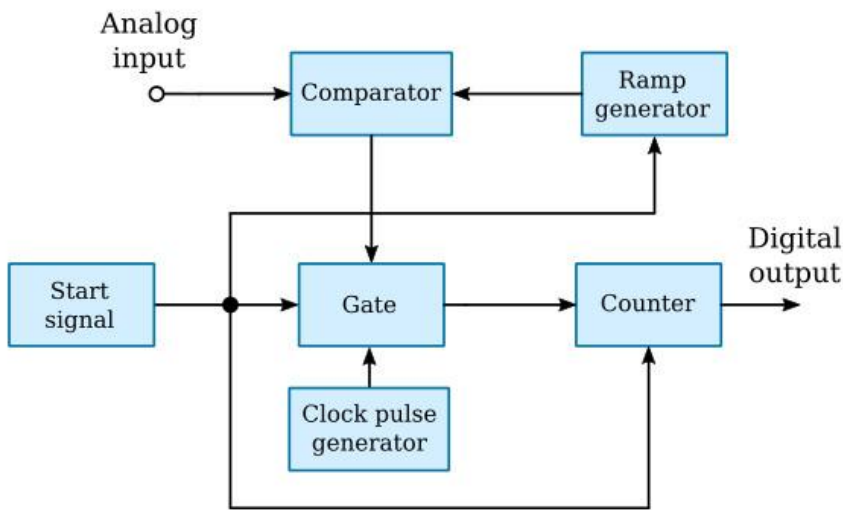

Two inputs are applied to the comparator in the figure above. These are: (1) the analog input, and (2) a linear ramp (sawtooth) voltage from the ramp generator. The generator output is initiated each time a start signal is applied. The start signal also resets the counter to zero and enables the gate circuit.

As long as the analog and ramp generator inputs to the comparator differ in magnitude, the clock pulse generator will be permitted to transmit pulses at a constant repetition rate through the gate into the counter. When the two inputs to the comparator become equal (as a result of the linearly rising sawtooth) the comparator will generate a stop signal which disables the gate circuit and ends the comparison time interval. The disabled gate circuit blocks the flow of pulses from the clock pulse generator to the counter. The number of pulses accumulated in the counter during the comparison time interval is proportional to the amplitude of the analog input voltage. The counter indication is the desired digital representation of the input signal.

6.

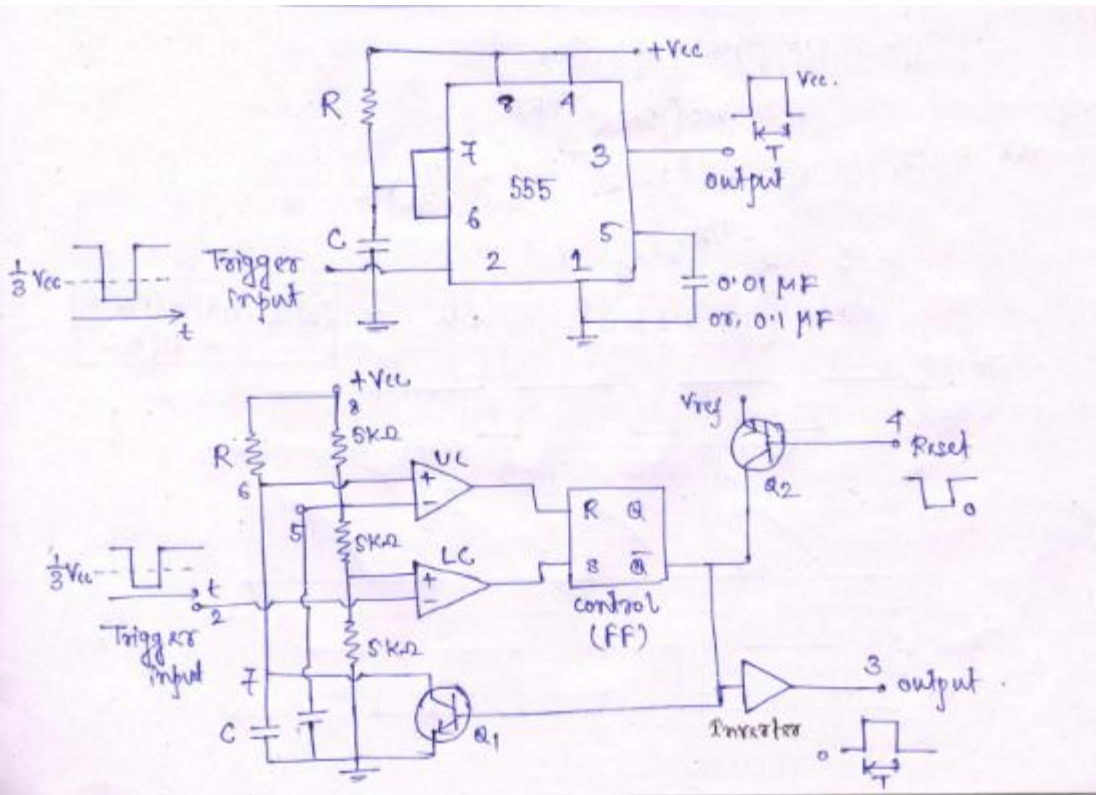

In standby mode, FF holds transistor  $Q_1$  on, thus clamping the external timing capacitor  $C$  to ground. The FF is in reset condition.  $\therefore \bar{Q} = 1$ ,  $op = \text{LOW}$ .


As the trigger passes through  $\frac{V_{cc}}{3}$ , the FF is set i.e.  $\bar{Q} = 0$ . This makes  $Q_1$  off and the short circuit across the timing capacitor is released. As  $\bar{Q}$  is LOW, output goes HIGH ( $=V_{cc}$ ). The timing cycle now begins. Since  $C$  is unclamped, voltage across it raises exponentially through  $R$  towards  $V_{cc}$  with a time constant  $RC$ .

If the voltage across the capacitor is just greater than  $\frac{2}{3}V_{cc}$  and the upper comparator resets the FF i.e.  $R=1, S=0$ . This makes  $\bar{Q} = 1$ , transistor  $Q_1$  goes on (i.e. saturates), the output returns to standby state (i.e. LOW).

7.

The basic block schematic of the PLL is shown. The feed system consists of

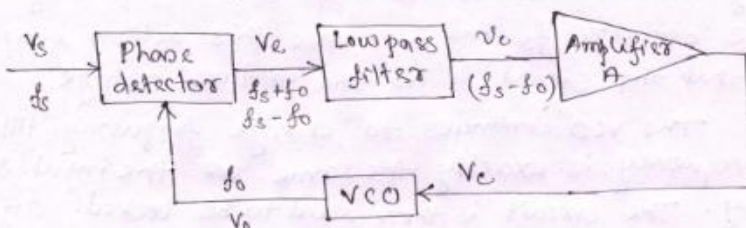- (i) Phase detector/comparator.
- (ii) A low pass filter.
- (iii) An error amplifier.
- (iv) A voltage controlled oscillator.



Block schematic of the PLL