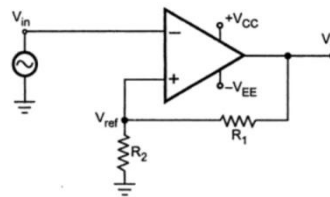


Internal Assessment Test - II


Sub:	Analog Circuits						Code:	18EC42	
Date:	03/ 08/ 2022	Duration:	90 mins	Max Marks:	50	Sem /Sec :	4 th /A,B,C, D	Branch :	ECE

Answer Any FIVE FULL Questions


		Marks	OBE	
			CO	RBT
1.	Draw and explain the complete frequency response of a common source amplifier. Derive the expression for its lower cut-off frequency.	[10]	CO2	L3
2.	With the help of neat circuit diagram and small signal equivalent model explain the working of FET based RC Phase shift Oscillator. Also explain how three RC pair can be used to in the feedback to achieve 180 degree phase shift.	[10]	CO3	L3
3.	Find the midband gain A_M , and the upper 3-dB frequency f_H of a CS amplifier fed with a signal source having an internal resistance $R_{sig} = 100 \text{ k}\Omega$. The amplifier has $R_G = 4.7 \text{ M}\Omega$, $R_D = R_L = 15 \text{ k}\Omega$, $g_m = 1 \text{ mA/V}$, $r_o = 150 \text{ k}\Omega$, $C_{gs} = 1 \text{ pF}$ and $C_{gd} = 0.4 \text{ pF}$	[10]	CO2	L3
4.	Explain the internal capacitances of a MOSFET. For the n-channel MOSFET in saturation with $t_{ox} = 10 \text{ nm}$, $L = 1 \mu\text{m}$, $W = 10 \mu\text{m}$, $L_{OV} = 0.05 \mu\text{m}$, $C_{sbo} = C_{dbo} = 10 \text{ fF}$, $V_{O} = 0.6 \text{ V}$, $V_{SB} = 1 \text{ V}$ and $V_{DS} = 2 \text{ V}$. Given dielectric used is SiO_2 . Calculate i) C_{OX} ii) C_{OV} iii) C_{gs} iv) C_{gd} v) C_{sb} vi) C_{db}	[10]	CO2	L3
5.	With relevant circuit diagrams and equations explain the following a) Colpitts Oscillator b) Crystal Oscillator.	[10]	CO2	L3
6.	Draw the circuit of noninverting amplifier and derive the expressions for a) Exact gain b) Ideal gain c) Input Resistance d) Bandwidth.	[10]	CO2	L2
7.	With a neat circuit diagram explain the opamp based non - inverting Summing amplifier, scaling amplifier and averaging circuit with relevant expressions for the output.	[10]	CO3	L3
8.	Draw the circuit and waveforms for an inverting Schmitt Trigger using opamp, with relevant expressions. For an inverting Schmitt Trigger circuit $R_2 = 1 \text{ k}\Omega$; $R_1 = 3 \text{ k}\Omega$ and $V_{in} = 10 \text{ Vp-pp}$ sine wave. The saturation voltages are $\pm 14 \text{ V}$. i) Determine the threshold voltages V_{ut} and V_{lt} .	[10]	CO2	L3
	ii) Find the value of Hysteresis voltage V_{hy} .			



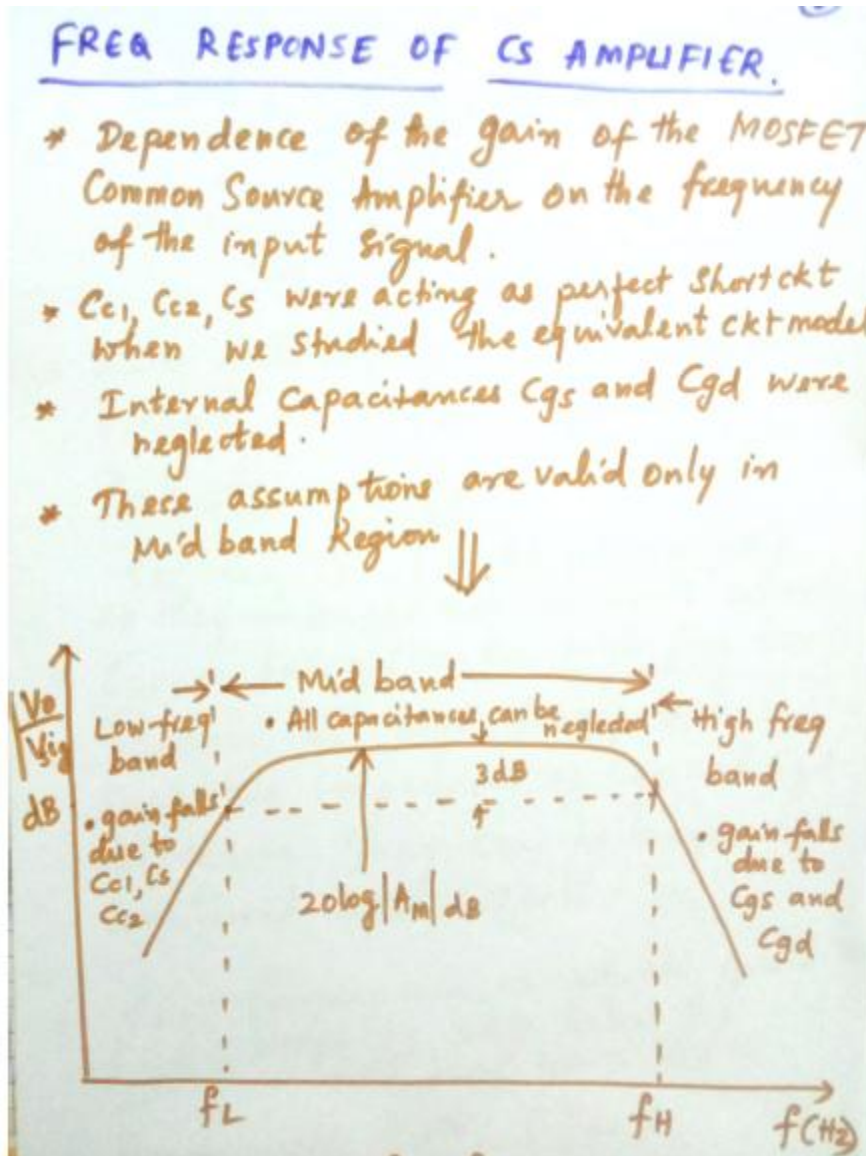Question 1 - Draw and explain the complete frequency response of a common source amplifier. Derive the expression for its lower cut-off frequency.



Low-Frequency Response (4.9.3)

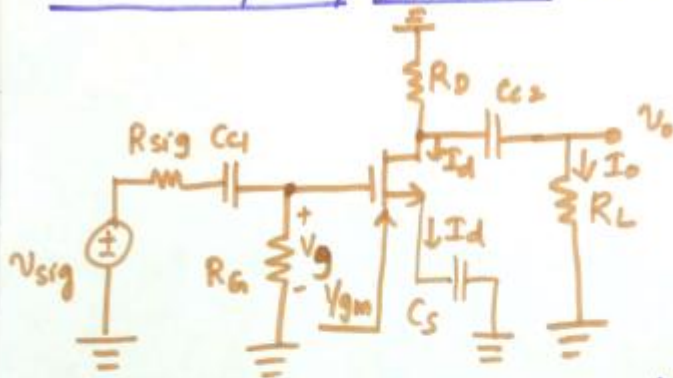

To find the low-freq Response, V_{DD} and V_{SS} voltage sources are short circuited, current source I is open circuited. The coupling capacitors and bypass capacitor is taken into consideration. For simplicity r_o is neglected (it has minor effect also)

$$V_g = V_{sig} \cdot \frac{R_G}{R_{sig} + \frac{1}{sC_{c1}} + R_G}$$

In low freq Response we need to consider the effect of 3 capacitors. All of them affect the Low frequency Response.

There will be three break frequencies represented as :-


$$\omega_{p1} = \frac{1}{C_1(R_G + R_{sig})}$$

$$\omega_{p2} = \frac{g_m}{C_S}$$

$$\omega_{p3} = \frac{1}{C_2(R_D + R_L)}$$


Overall low-frequency transfer function is given by
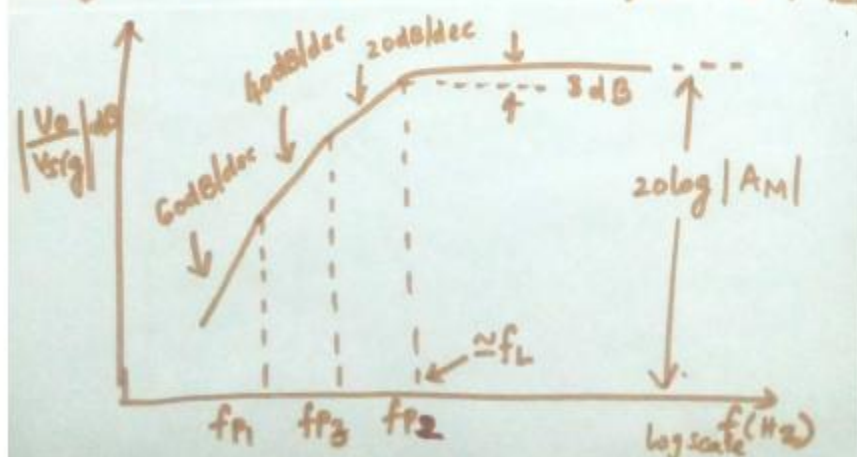
$$\frac{V_o}{V_{sig}} = - \left[\frac{R_G}{R_G + R_{sig}} \right] (g_m R_D // R_L) \left(\frac{s}{s + \omega_{p1}} \right) \left(\frac{s}{s + \omega_{p2}} \right) \left(\frac{s}{s + \omega_{p3}} \right)$$




Question 2 - With the help of neat circuit diagram and small signal equivalent model explain the working of FET based RC Phase shift Oscillator. Also explain how three RC pair can be used to in the feedback to achieve 180 degree phase shift.

FET Based RC Phase Shift Oscillator

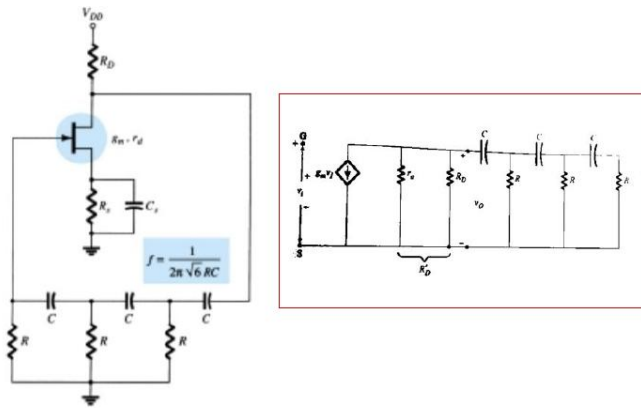

Small Signal Equivalent

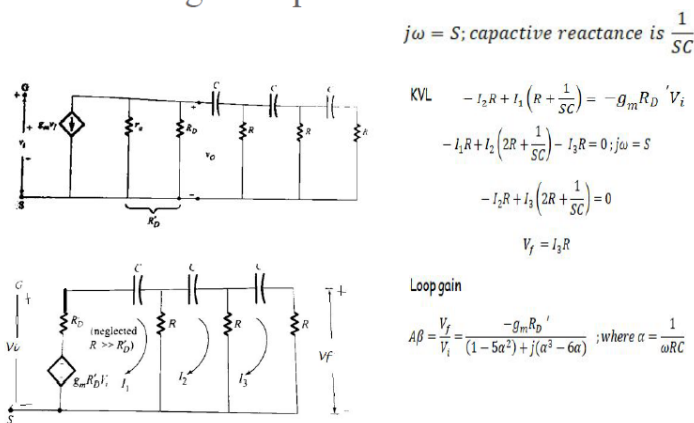

Loop gain

$$A\beta = \frac{V_f}{V_i} = \frac{-g_m R_D'}{(1 - 5\alpha^2) + j(\alpha^3 - 6\alpha)} ; \text{where } \alpha = \frac{1}{\omega RC}$$

Loop gain is real

$$\alpha^3 - 6\alpha = 0 \xrightarrow{\text{yields}} \alpha^2 = 6$$

$$\frac{1}{(\omega RC)^2} = 6$$

$$(2\pi f_o RC)^2 = \frac{1}{6}; f_o = \frac{1}{2\pi RC\sqrt{6}}$$

$$A\beta = \frac{V_f}{V_i} = \frac{-g_m R_D'}{(1 - 5\alpha^2)} = \frac{g_m R_D'}{29}$$

For sustained oscillation

$$|A\beta| > 1; |A| = g_m R_D' > 29 \text{ and } \beta = \frac{1}{29}$$

Question 3 - Find the midband gain A_M , and the upper 3-dB frequency f_H of a CS amplifier

fed with a signal source having an internal resistance $R_{sig} = 100 \text{ k}\Omega$. The amplifier has $R_G = 4.7 \text{ M}\Omega$, $R_D = R_L = 15 \text{ k}\Omega$, $g_m = 1 \text{ mA/V}$, $r_o = 150 \text{ k}\Omega$, $C_{gs} = 1 \text{ pF}$ and $C_{gd} = 0.4 \text{ pF}$

3] Given $R_{sig} = 100 \text{ k}\Omega$
 $R_G = 4.7 \text{ M}\Omega$, $R_D = R_L = 15 \text{ k}\Omega$, $g_m = 1 \text{ mA/V}$, $r_o = 150 \text{ k}\Omega$
 $C_{gs} = 1 \text{ pF}$, $C_{gd} = 0.4 \text{ pF}$

① Mid Band Gain $G_V = A_M = \frac{-R_L}{R_G + R_{sig}} \times g_m (R_D || R_L || r_o)$

$$= \frac{-4.7 \text{ M}}{4.8 \text{ M}} \times 1 \text{ mA/V} (15 \text{ k} || 15 \text{ k} || 150 \text{ k})$$

$A_M = -6.99 \text{ V/V}$

$A_M(\text{dB}) = 20 \log_{10}(|A_M|) = 16.9 \text{ dB}$

② $f_H = \frac{1}{2\pi R_{sig}' C_{in}'}$

where $R_{sig}' = R_G || R_{sig}$
 $C_{in}' = C_{gs} + C_{gd} [1 + g_m (R_D || R_L || r_o)]$

$R_{sig}' = 97.9 \text{ k}\Omega$
 $C_{in}' = 1 \text{ pF} + 0.4 \text{ pF} (1 + 7.14)$
 $= 4.256 \text{ pF}$

$f_H = 382 \text{ kHz}$

Question 4 -

Explain the internal capacitances of a MOSFET.

For the n-channel MOSFET in saturation with $t_{ox} = 10 \text{ nm}$, $L = 1 \mu\text{m}$, $W = 10 \mu\text{m}$, $L_{OV} = 0.05 \mu\text{m}$, $C_{sbo} = C_{dbo} = 10 \text{ fF}$, $V_0 = 0.6 \text{ V}$, $V_{SB} = 1 \text{ V}$ and $V_{DS} = 2 \text{ V}$. Given dielectric used is SiO_2 . Calculate i) C_{OX} ii) C_{OV} iii) C_{gs} iv) C_{gd} v) C_{sb} vi) C_{db}

MOSFET in saturation

$t_{ox} = 10 \text{ nm}$, $L = 1 \mu\text{m}$, $W = 10 \mu\text{m}$, $L_{OV} = 0.05 \mu\text{m}$
 $C_{sbo} = C_{dbo} = 10 \text{ fF}$, $V_0 = 0.6 \text{ V}$, $V_{SB} = 1 \text{ V}$, $V_{DS} = 2 \text{ V}$

$C_{ox} = \frac{\epsilon_0 \epsilon_r}{t_{ox}} = \frac{3.45 \times 10^{-17} \times 8.85 \times 10^{-12} \text{ F/m}}{10 \times 10^{-9} \text{ m}} = 3.045 \text{ fF}$

In saturation
 $C_{gs} = \frac{2}{3} W L C_{ox} + C_{ov}$
 $C_{gd} = C_{ov}$
 $C_{ov} = W L_{OV} C_{ox} = 10 \mu\text{m} \times 0.05 \mu\text{m} \times 3.045 \text{ fF} = 1.725 \text{ fF}$

$C_{gs} = \frac{2}{3} W L C_{ox} + C_{ov}$

$$= \left[\frac{2}{3} \times 10 \mu\text{m} \times 10 \mu\text{m} \times 3.045 \text{ fF} \right] + 1.725 \text{ fF}$$

$$= 23 \text{ fF} + 1.725 \text{ fF} = 24.725 \text{ fF}$$


$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{V_0}}} = \frac{10 \text{ fF}}{\sqrt{1 + \frac{1}{0.6}}} = 6.1 \text{ fF}$

$C_{db} = \frac{C_{dbo}}{\sqrt{1 + \frac{V_{DS}}{V_0}}} = \frac{10 \text{ fF}}{\sqrt{1 + \frac{2}{0.6}}} = 4.1 \text{ fF}$

Question 5- With relevant circuit diagrams and equations explain the following

a) Colpitts Oscillator b) Crystal Oscillator.

Colpitts Oscillator

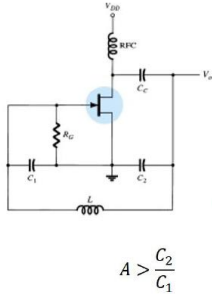

$$X_1 + X_2 = \frac{1}{\omega C_1} + \frac{1}{\omega C_2} = \omega L$$


$$\omega = 2\pi f_0$$

$$f_0 = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$


Crystal Oscillator

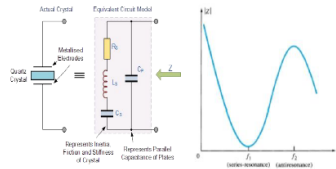- The crystal (usually quartz) has a greater stability in holding constant at whatever frequency the crystal is originally cut to operate. Crystal oscillators are used whenever great stability is required, such as in communication transmitters and receivers.



- Piezoelectric Crystal
- A quartz crystal (one of a number of crystal types) exhibits the property that when mechanical stress is applied across the faces of the crystal, a difference of potential develops across opposite faces of the crystal. This property of a crystal is called the piezoelectric effect. Similarly, a voltage applied across one set of faces of the crystal causes mechanical distortion in the crystal shape.
- When alternating voltage is applied to a crystal, mechanical vibrations are set up—these vibrations having a natural resonant frequency dependent on the crystal.

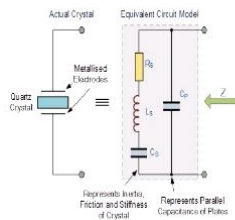Series and Parallel Resonance Frequencies



- Series Resonance**

$$X_{CS} = X_{LS} \quad \frac{1}{\omega C_s} = \omega L_s$$

$$f_s = \frac{1}{2\pi\sqrt{C_s L_s}}$$

- Parallel Resonance**

$$X_{CS} + X_{CP} = X_{LS}$$


$$\frac{1}{\omega C_s} + \frac{1}{\omega C_p} = \omega L_s \quad f_p = \frac{1}{2\pi\sqrt{C_{eq} L_s}}$$

$$\frac{C_s C_p}{C_s + C_p} = C_{eq}$$

Question 6 - Draw the circuit of noninverting amplifier and derive the expressions for

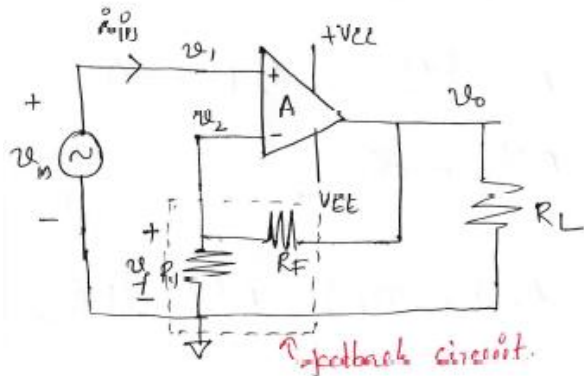a) Exact gain b) Ideal gain c) Input Resistance d) Bandwidth.

Non inverting Amplifier [Voltage Series feedback Amplifier]



A] Closed Loop Voltage Gain (AF)

Recall $A_F = \frac{v_o}{v_{in}}$

and $v_o = A(v_i - v_f) = A v_{in} \quad \text{--- (1)}$

$v_f = B v_o \quad \text{--- (2)}$


from (1) and (2)
 $v_o = A(v_{in} - v_f) = A(v_{in} - B v_o)$

On rearranging

$$(1 + AB) v_o = A v_{in}$$

$$A_F = \frac{v_o}{v_{in}} = \frac{A}{1 + AB} \quad \text{--- (3)}$$

from the ckt

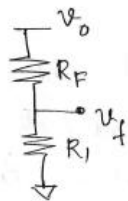

$$v_f = \frac{v_o \times R_1}{R_1 + R_F}$$

$$B = \frac{v_f}{v_o} = \frac{R_1}{R_1 + R_F}$$

substituting value of B in (3)

$$A_F = \frac{A}{1 + \frac{A R_1}{R_1 + R_F}} = \frac{A(R_1 + R_F)}{R_1 + R_F + A R_1} \quad \text{--- (4)}$$

closed loop Voltage gain A_F

Exact

$$A_F = \frac{A(R_1 + R_F)}{R_1 + R_F + AR_1}$$

Ideal

$$A_F = 1 + \frac{R_F}{R_1}$$

Note: Gain of the feedback amplifier is decided by ratio of R_F and R_1 . All components must be kept below 1M Ω so that the external circuitry won't affect op-amp internal circuit.


Note: In ideal case $A \gg \frac{R_1 + R_F}{R_1}$ thus if ideal op-amp is considered $1 + \frac{AR_1}{R_1 + R_F} \approx \frac{AR_1}{R_1 + R_F}$ OR $\frac{AR_1}{R_1 + R_F + AR_1} \approx \frac{AR_1}{AR_1}$

thus eqn (4) becomes under ideal con.

$$A_F = \frac{A(R_1 + R_F)}{AR_1} = 1 + \frac{R_F}{R_1} \quad \text{--- (5)}$$

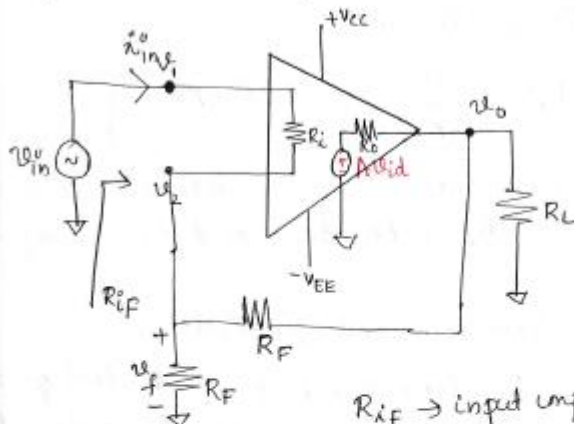B) Input Resistance

Consider the amplifier ckt with the op-amp replaced with its equivalent model



$R_{iF} \rightarrow$ input impedance with feedback

from the ckt

$$R_{iF} = \frac{v_{in}}{i_{in}} \quad \text{--- (6)}$$

$$i_{in} = \frac{v_{in} - v_f}{R_L} = \frac{v_{in} - v_o}{R_L} \quad \text{--- (7)}$$

Recall $\Rightarrow v_{in} - v_f = \frac{v_o}{A}$

and $v_o = A_F v_{in}$

$$v_{in} - v_f = \frac{A_F v_{in}}{A} = \frac{A}{1 + AB} v_{in} = \frac{v_{in}}{1 + AB}$$

substitute this in (F)

$$i_{in} = \frac{v_{in}}{R_i(1+AB)}$$

and (C) yields


$$R_{iF} = \frac{v_{in}}{i_{in}} = R_i(1+AB)$$

Note: Input impedance of op-amp with feedback is improved by $(1+AB)$ times of that of an open loop op-amp circuit.

C] Output Resistance with feedback

output impedance can be found by looking back into the feedback amplifier from the output terminal.

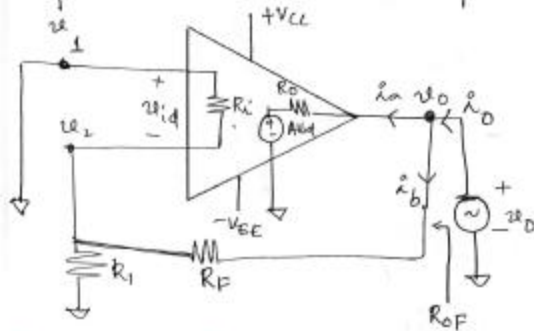- 1] Replace input side by its thevenin equivalent \Rightarrow replace v_{in} with internal impedance, ideally zero.



- 2] Apply an external voltage v_o , which forces a current i_o

Let i_a be the current through R_o , and i_b through $[R_F + (R_i || R_1)]$

Since $R_F + (R_i || R_1) \gg R_o$; $i_b \ll i_a$

$$i_o = i_a + i_b \approx i_a$$

Writing KVL

$$R_{of} = \frac{v_o}{i_o}$$

$$v_o - i_o R_o - A v_{id} = 0$$

$$v_o - i_o R_o + A v_f = 0$$

$$v_o - i_o R_o + AB v_o = 0$$

$$(1+AB)v_o = i_o R_o$$

$$R_{of} = \frac{v_o}{i_o} = \frac{R_o}{1+AB}$$

Note: Output impedance has substantially improved by a factor $\frac{1}{1+AB}$ with feedback.

Question 7 - With a neat circuit diagram explain the opamp based non-inverting Summing amplifier, scaling amplifier and averaging circuit with relevant expressions for the output.

Non-Inverting Configuration.

Refer the circuit diagram in Fig. 4.2, where the input voltages are connected at non-inverting terminals.

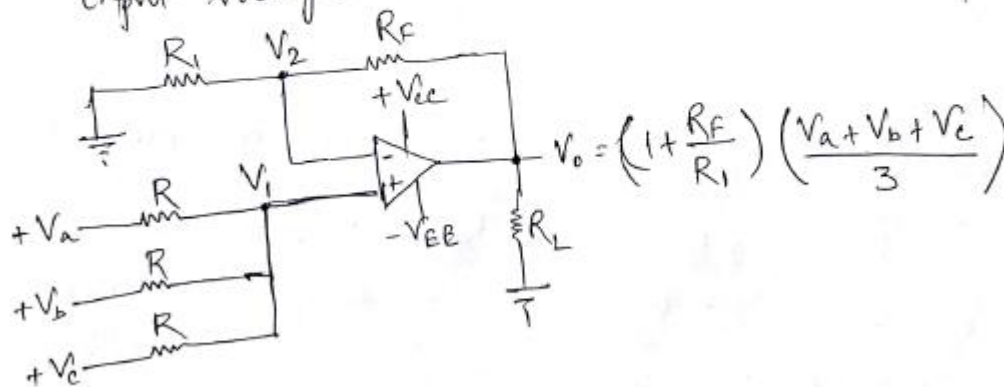


Fig 4.2: Non-inverting configuration with 3 inputs

$$\begin{aligned} \text{Voltage at } V_1 \text{ due to only } V_a &= \frac{R/2}{R+R/2} V_a. \\ \text{" " } V_1 \text{ " " " } V_b &= \frac{R/2}{R+R/2} V_b. \\ \text{" " " due " " " } V_c &= \frac{R/2}{R+R/2} V_c. \end{aligned}$$

Hence using Superposition theorem, the total voltage at ~~the~~ non V_1 at non-inverting terminal is

$$V_1 = \frac{R/2}{R+R/2} V_a + \frac{R/2}{R+R/2} V_b + \frac{R/2}{R+R/2} V_c.$$

$$\Rightarrow V_1 = \frac{V_a}{3} + \frac{V_b}{3} + \frac{V_c}{3}$$

$$\Rightarrow V_1 = \frac{V_a + V_b + V_c}{3} \quad \text{--- (8)}$$

Therefore the output voltage can be given as

$$V_o = \left(1 + \frac{R_F}{R_1}\right) V_1$$

$$V_o = \left(1 + \frac{R_F}{R_1}\right) \left(\frac{V_a + V_b + V_c}{3}\right) \quad \text{--- (9)}$$

(a) Summing Amplifier (Non-inverting configuration)

after analyzing Eq(9), one can conclude that is the gain of the circuit in Fig. 4.2 is chosen such that

$$1 + \frac{R_F}{R_1} = 3$$

Then Eqn 9, becomes -

$$V_o = 3 \left(\frac{V_A + V_B + V_C}{3} \right)$$

$$\Rightarrow \boxed{V_o = V_A + V_B + V_C} \quad \text{--- (10)}$$


The output voltage is sum of all three input voltages. Hence it is called a non-inverting summing amplifier.

(b) Averaging Amplifier (non-inverting configuration)

From Eq. 9, it is clear that output voltage is equal to all input voltages multiplied by gain of the circuit $\left(1 + \frac{R_f}{R_i}\right)$, hence the name as averaging amplifier.

Question 8 - Draw the circuit and waveforms for an inverting Schmitt Trigger using opamp, with relevant expressions. For an inverting Schmitt Trigger circuit $R_2 = 1\text{K}\Omega$; $R_1 = 3\text{K}\Omega$ and $V_{in} = 10\text{Vp-p}$ sine wave. The saturation voltages are $\pm 14\text{V}$.

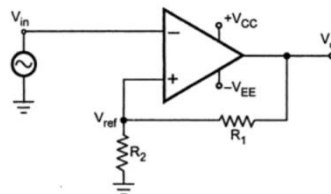i) Determine the threshold voltages V_{ut} and V_{lt} .



ii) Find the value of Hysteresis voltage V_{hy} .

SCHMITT TRIGGER

Need for Schmitt Trigger:

In some applications, the input V_{in} may be slowly changing waveform i.e. low frequency signal. Hence in the presence of noise around 0V, V_o may fluctuate quickly from one saturation voltage to another. This problem can be cured by the use of regenerative or positive feedback that causes the output V_o to change faster and eliminate any false output transitions due to noise signals at the input. This arrangement give rise to Schmitt Trigger circuit.

Schmitt Trigger.

- Fig 4.6 shows an inverting comparator with positive feedback, known as Schmitt Trigger, which converts an irregular shaped waveform to square wave or pulse.
- The input voltage V_{in} triggers the output V_o everytime it exceeds certain voltage levels called the upper threshold voltage V_{ut} and lower threshold voltage V_{lt} .

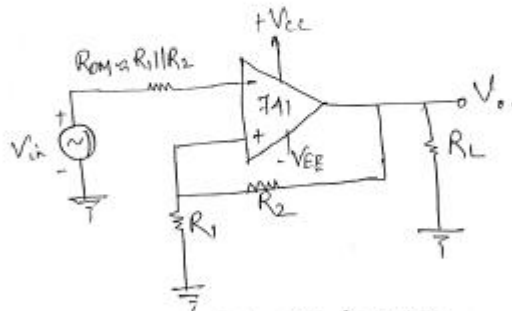


Fig 4.6.a :- Schmitt Trigger.

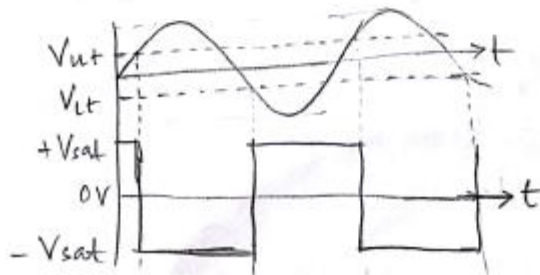


Fig 4.6. b :-
Input/Output
Waveform of
Schmitt Trigger

- From circuit diagram in Fig 4.6.a, using voltage divider rule across R_1 & R_2 , V_{ut} is given as:

$$V_{ut} = \frac{R_1}{R_1 + R_2} (+V_{sat}) \quad \text{--- 1.}$$

- Similarly when $V_o = -V_{sat}$, the V_{lt} is given as

$$V_{lt} = \frac{R_1}{R_1 + R_2} (-V_{sat}) \quad \text{--- 2}$$

- Thus if threshold voltages V_{ut} & V_{lt} are made larger than the input noise voltages, the positive feedback will eliminate the false output transitions.
- Rem: $R_1 || R_2$ is used to minimize offset problem.
- Hysteresis in Schmitt Trigger:

The comparator with positive feedback is said to exhibit hysteresis, a dead band condition. This is when the input of the comparator exceeds V_{ut} , its output switches from $+V_{sat}$ to $-V_{sat}$ and ~~over~~ again comes back to $+V_{sat}$ when the ~~input~~ input V_{in} goes below V_{lt} (Refer Fig 4.6.b)

- Therefore it is obvious, the hysteresis voltage is equal to difference of V_{ut} & V_{lt} i.e.

$$V_{hy} = V_{ut} - V_{lt}$$

$$= \frac{R_1}{R_1 + R_2} [+V_{sat} - (-V_{sat})]$$

$$V_{hy} = 2 \cdot \frac{R_1}{R_1 + R_2} \cdot V_{sat} \quad -3$$


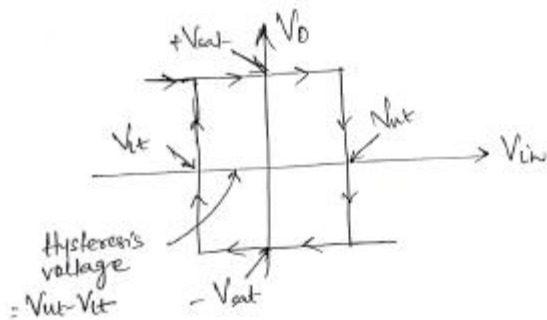


Fig 1.6.2: Hysteresis Voltage

8] Schmitt

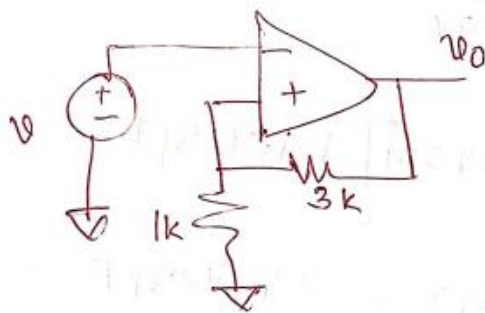

$$V_{sat} = 14V$$

$$V_{UT} = V_{sat} \times \frac{R_2}{R_1 + R_2} = 14 \times \frac{1}{4} = \underline{\underline{+3.5V}}$$

$$V_{LT} = -V_{sat} \times \frac{R_2}{R_1 + R_2} = -14 \times \frac{1}{4} = \underline{\underline{-3.5V}}$$