

--	--	--	--	--	--	--	--


Internal Assessment Test III – August 2022

Sub:	Analog Circuits				Sub Code:	18EC42	Branch :	ECE	
Date:	26-08-2022	Duration:	1.5 hour	Max Marks:	50	Sem/Sec :	4 th sem /A,B,C,D		OBE

ANSWER ANY 5 FULL QUESTIONS

		MARKS	CO	RBT
1.	With circuit diagram and waveforms, explain the working of binary weighted resistor 4 bit Digital to Analog converter.	[10]	CO4	L2
2.	Explain the working of a monostable multivibrator using 555 Timer IC. Design a circuit using 555 Timer to get a monoshot pulse of width 10ms. Choose $C = 1\mu F$	[10]	CO5	L3
3.	Explain the operation of 4-bit R-2R DAC with neat circuit. For the R-2R DAC, with $R=10k\Omega$ and $RF=20k\Omega$ and $V_{REF}=5V$, determine the output voltage when the inputs $b_0=b_1=5V$ and $b_2=b_3=0V$	[10]	CO4	L3
4.	Explain the operation of a Successive -approximation ADC with neat circuit diagram.	[10]	CO4	L2
5.	Draw the circuit and frequency response of a first order low pass filter. Design a first order low pass filter to have a cutoff frequency of 1kHz with a passband gain of 2.	[10]	CO4	L2
6.	With necessary circuit and waveforms, explain the operation of a Astable multivibrator (Symmetric and Asymmetric) using 555 timer IC.	[10]	CO5	L2
7.	With a neat block diagram explain the working of a Voltage series feedback amplifier. Derive an expression for the overall gain, input and output impedances.	[10]	CO2	L3
8.	Draw the circuit and frequency response of a first order high pass filter. Design a first order high pass filter to have a cutoff frequency of 1kHz with a passband gain of 2.	[10]	CO4	L2
9.	Give the circuit diagram, gain expression and frequency response plots of:- (a) First order Low pass filter (b) Second order Low pass filter (c) Wide band pass filter (d) Narrow band reject filter	[10]	CO4	L2
10	Explain the working of positive and negative half wave precision rectifier with necessary circuit and wave forms.	[10]	CO4	L2

Weighted resistor

 

* Since there are 4 input bits it is known as 4-bit DAC.

$$* \text{ If } R = 10 \text{ k}\Omega, \frac{R}{2} = \frac{10}{2} = 5 \text{ k}\Omega$$

$$\frac{R}{4} = \frac{10}{4} = 2.5 \text{ k}\Omega, \frac{R}{8} = \frac{10}{8} = 1.25 \text{ k}\Omega$$

- * Let us consider if the switch b_0 is closed & connected to $5V$ V_{cc} and the remaining switches are open.
i.e $\Rightarrow b_0 = 1$, $b_1 = b_2 = b_3 = 0$.
- * Then the current is given as $I = \frac{V}{R}$
 $I = \frac{5}{10} = 0.5 \text{ mA}$.
 This is the ~~over~~ current across R and for the ideal one the current across R_f is same as that of 0.5 mA .
- * Since all other switches are grounded the current through them is zero.
- * The total current through R_f is given as
 $I_f = (0.5 + 0 + 0 + 0) \text{ mA}$
 $= 0.5 \text{ mA}$.
- * Therefore the o/p voltage is given as
 $V = IR = (0.5)(10) = 5V$.
- * The maximum voltage is obtained when all the switches are closed.

$$V_o = -R_f \left[\frac{R}{\infty} + \cancel{\frac{2R}{\infty}} + \frac{S}{R} + \frac{S}{2R} + \frac{S}{R/4} + \frac{S}{R/18} \right]$$

$$= -1k \left[\frac{S}{10} + \frac{S}{5} + \frac{S}{2.5} + \frac{S}{1.25} \right]$$



The main drawback of this type DAC is that the 8 different resistance values. Which may not be available.


$$V_o = -R_f [R + 2R + 4R + 8R]$$

Due to this drawback we have arrived at R-2R ladder type.

The current calculated based on the switch position will be the current flowing through the feedback resistor R_f .

Weighted resistor DAC

3.

 


- * 4-bit R-2R DAC is used instead of binary weighted resistor because in the binary weighted resistor there is a requirement of weighted resistors which are not always available.
- * In this R to 2R ladder we use

$$R = 10\text{k}\Omega$$

$$2R = 20\text{k}\Omega$$

$$R_f = 20\text{k}\Omega$$
 Resistor which are easily available.
- * b_0 is LSB & b_3 is MSB.
- * b_0 towards the left end and b_3 towards the right are bits.
- * According to the above circuit let's consider b_3 pin to be connected to the 5V pin.

Hence,

 

On applying Thévenin's theorem, we get

$$R_{th} = \{(((2R||2R+R)||2R)+R)||2R\} + R$$

$$R_{th} = 2R \\ = R_f$$

$$I = \frac{V}{R} \\ = \frac{5}{20k} \\ = 0.25mA$$

$$V_o = -0.25mA \times 20k \\ = -5V.$$

The Output of the R-2R ladder is given by.

$$V_o = -V_{ref} R_f \left[\frac{b_0}{16R} + \frac{b_1}{8R} + \frac{b_2}{4R} + \frac{b_3}{2R} \right]$$

$$20 \times 10^3 \left[\frac{5}{2 \times 10} \right]$$

The Output of the DAC is Maximum when all the bits are high

$$V_o = -20 \times 10^3 \left[\frac{5}{16R} + \frac{5}{8R} + \frac{5}{4R} + \frac{5}{2R} \right]$$

$$= -\frac{20 \times 10^3}{10^3} \left[\frac{5}{16} + \frac{5}{8} + \frac{5}{4} + \frac{5}{2} \right]$$

$$V_o = \underline{\underline{-9.37V}}$$

for $R = 10k\Omega$

$$R_f = 20k\Omega$$

$$V_{ref} = 5V$$

when $b_0 = b_1 = 5V$ & $b_2 = b_3 = 0V$.


$$V_o = -5 \times \frac{20 \times 10^3}{10^3} \left[\frac{1}{160} + \frac{1}{80} + \frac{0}{40} + \frac{0}{20} \right]$$

$$= -5 \times 2 \left[\frac{1}{16} + \frac{1}{8} \right]$$

Successive approximation ADC

ADC - Analog to digital converter.

 The below is the successive approximation type ADC.



* In successive approximation we make use of a successive approximation register, a comparator, clock pulse etc.


* When the MSB bit Q_7 is made low to high ~~on~~ of SAR signal the Q_7 is pushed up. and there is a start of comparator cycle

- * If the comparator output is low, then the SAR is then Q_7 is made to accept.
- * If comparator output is high, then the ~~previous~~ bit Q_7 is set and not moved anywhere.
- * Then next considering Q_6 , based on the ~~comparator~~ value and DAC output values Q_6 is either set or ~~set~~ processed based on the ~~comparator~~ value.
- * Similarly all the bits from MSB to LSB $Q_7 Q_6 Q_5 Q_4$ are processed based on the ~~comparator~~ value.
- * Finally when Q_0 is tried, the SAR forces a ~~comparator~~ then the process stops.
- * Finally the output is seen through ~~the~~ ~~display~~.
- * The successive approximation ADC process it a format or one after the other format, till it finds the bit of SAR.


bits of STAR.

First order low pass butterworth filter.

 - * First order low pass filter is designed using RC circuit



Frequency response :

 

By applying voltage divider rule to the circuit, we get

$$V_i = \frac{-j\omega C}{R - j\omega C} V_{in} \quad \text{--- (1)}$$

$$\omega = \sqrt{1}, \quad -j\omega C = \frac{1}{j2\pi f_H C}$$

eqn (1) =

$$V_i = \frac{\frac{1}{j2\pi f_H C}}{R + \frac{1}{j2\pi f_H C}} V_{in}$$

$$V_i = \frac{1}{1 + j2\pi f_H R C} V_{in} \quad \text{--- (2)}$$

W.R.T

$$V_o = A_F V_i$$

$$V_o = \left(1 + \frac{R_F}{R_i} \right) \frac{V_{in}}{1 + j2\pi f_H R C}$$

$$\boxed{\frac{V_o}{V_{in}} = \frac{A_F}{1 + j2\pi f_H R C}} \quad \text{--- (2)}$$

$$\boxed{\frac{V_o}{V_{in}} = \frac{A_F}{1 + j(\frac{1}{f_H})}}$$

Magnitude $\left| \frac{V_o}{V_{in}} \right| = \frac{|A_F|}{\sqrt{1 + (\frac{1}{f_H})^2}}$

Phase angle $\boxed{\phi = \tan^{-1} \left(\frac{1}{f_H} \right)}$

Given: $f_H = 1 \text{ kHz}$

$$R = \frac{1}{2\pi f_H C}$$

$$R = \frac{1}{2(\pi)(1 \times 10^3)(0.01 \times 10^{-12})(10^{-12})} \quad \left. \begin{array}{l} \text{Considering} \\ C = \text{constant} \\ 1 \text{ nF} \end{array} \right\}$$

$$R = 0.1591 \Omega \times 1000$$

$$\boxed{R = 159.1 \Omega}$$

$$\text{Gain} = \alpha = A_F$$

$$\alpha = 1 + \frac{R_F}{R_I}$$

$\alpha \approx 1$


This is possible only when $R_F = R_I$

$$\therefore \boxed{R_F = R_I = 10k\Omega}$$

$$R_f = R_1 = 10\text{ k}\Omega$$

6.

Block diagram

 

Astable Multivibrator

The both the states are not stable in a Astable Multivibrator.

when the Astable multivibrator is power on or switched on for the first .

upper comparator is low $R=0$

lower comparator is high $S=1$

hence the flip flop is set $Q=1$ & $\bar{Q}=0$ the transistor behaves as a open circuit and the capacitor starts charging through the R_A & R_B resistors .

② when the capacitor voltage is more than $\frac{1}{3}V_{cc}$ then the

upper comparator $R=0$
is low

low comparator is low $S=0$.

when $S=0$; $R=0$ the flip flop is memory state hence it function same as $S=1$ & $R=0$ the above state where capacitor is charging

③ when the capacitor voltage is more than $\frac{2}{3}V_{cc}$ then the

upper comparator is high $R=1$

lower comparator is low $S=0$

hence the flip flop is in reset state $Q=0$ & $\bar{Q}=1$ here the transistor acts as a closed switch and the capacitor begin to discharge.


when capacitor discharges $S=0$, $R=0$ at this time the flip flop is in memory state & hence discharges

④ when the capacitor voltage goes below $\frac{1}{3}V_{cc}$ then the

upper comparator is ~~now~~ low $R=0$

lower comparator is high $S=1$

 The transistor switch acts as open switch and the process starts to repeat .



To find the T_{on} & T_{off} .

$$V_C(t) = V_{final} + (V_{initial} - V_{final}) e^{-t/R_C}$$

for T_{on}

$$V_C(t) = V_{CC} + \left(\frac{1}{3}V_{CC} - V_{CC}\right) e^{-T_{on}/R_C}$$

$$\frac{2}{3}V_{CC} = V_{CC} + \left(\frac{1}{3}V_{CC} - V_{CC}\right) e^{-T_{on}/R_C}$$

$$\frac{2}{3} - 1 = \left(\frac{1}{3} - 1\right) e^{-T_{on}/R_C}$$

$$-\frac{1}{3} = \frac{2}{3} e^{-T_{on}/R_C}$$

here, $R = R_A + R_B$.

$$-\ln\left(\frac{1}{2}\right) = -T_{on}/R_C$$

$$0.693(R_A + R_B)C = T_{on}$$

for T_{off}

$$\frac{1}{2}V_{CC} = 0 + \left(0 - \frac{1}{2}V_{CC}\right) e^{-T_{off}/R_B C}$$

$$-\frac{T_{off}}{R_B C} = \ln\left(\frac{1}{2}\right)$$

$$T_{off} = 0.693 R_B C$$

$$T = T_{on} + T_{off}$$

$$= 0.693 C (R_A + 2R_B)$$


Duty cycle

◆ Duty Cycle = $\frac{T_{on}}{T} \times 100$.


$$= \frac{0.693 (R_A + R_B) C}{0.693 (R_A + 2R_B) C} \times 100$$

$$= \frac{R_A + R_B}{\cancel{R_A + 2R_B}} \times 100$$

 ⑧ First order high pass butterworth filter



Frequency response:

 

By applying voltage divider rule to the circuit, we get

$$V_1 = \frac{R}{R - jX_C} V_{in}$$

$$V_1 = \frac{R}{R + \frac{1}{j\omega f_L C}} V_{in}$$

$$V_1 = \frac{j\omega f_L R C}{1 + j\omega f_L R C} V_{in} \quad - \textcircled{1}$$

$$V_o = A_F V_1$$

$$V_o = \left(1 + \frac{R_F}{R}\right) \frac{j\omega f_L R C}{1 + j\omega f_L R C} V_{in}$$

$$\frac{V_o}{V_{in}} = \frac{(A_F) j\omega f_L R C}{1 + j\omega f_L R C}$$

$$\boxed{\frac{V_o}{V_{in}} = \frac{A_F j(\frac{t}{f_L})}{1 + j(\frac{t}{f_L})}}$$

$$\text{Magnitude } \left| \frac{V_o}{V_{in}} \right| \geq \frac{A_F (\frac{t}{f_L})}{\sqrt{1 + (\frac{t}{f_L})^2}}$$

$$f_L = 1 \text{ kHz}, \quad C = 0.01 \mu\text{F},$$

$$R = \frac{1}{2\pi f_L C}$$

$$R = \frac{1}{2\pi \times 1 \times 10^3 \times 10^{-6} \times 1}$$

$$R = 159.1 \Omega$$

$$A_F = 2$$

$$1 + \frac{R_F}{R_1} = 2$$

$$\text{let } R_F = R_1$$

only then $A_F = 2$

$$\text{Now } R_F = R_1 = 10k\Omega$$

$$\frac{V_o}{V_{in}} = \frac{2j(\tau/10^3)}{1+j(\tau/10^3)}$$

10 -

10)



Precision Rectifier

Normally diodes required the input to be more than the ideal value. So for precision rectifier which is a combination of op-amp and diodes effective voltage is reduced by gain. The effective voltage is given as

$$V_{\text{eff}} = \frac{V_x}{A}$$

Precision Half wave Rectifier



Positive Half wave Rectifier.

  

- * The op-amp is made to work as voltage follower. The combination of op-amp and diode is used.
- * When the positive voltage is given or when the voltage is increased positive the voltage V_o' also increases which makes the diode forward biased and the Diode is ~~on~~ in 'ON' condition as shown in the graph.

- * When the voltage increases negatively then the diode is reverse biased even when V_0' is increased. This makes the diode D_1 off during the negative half cycle as shown in the diagram!
- * When V_0' increases during positive half cycle the circuit acts as a voltage follower and the output follows the input.

Negative half cycle

  

- * During the negative half cycle
The negative half cycle design is same as that of positive half cycle only change is that the diode direction is reversed.
- * When the voltage is increased positively the

diode D_1 is reverse biased even when the V_o' is increased therefore the output voltage is zero , as shown in the graph .

- * When the negative voltage is applied or
When the ~~the~~ voltage is increased negatively
the diode D_1 is forward biased with the
voltage V_o' increased . The output voltage
follows the input voltage during the
negative half cycle as shown in the graph .